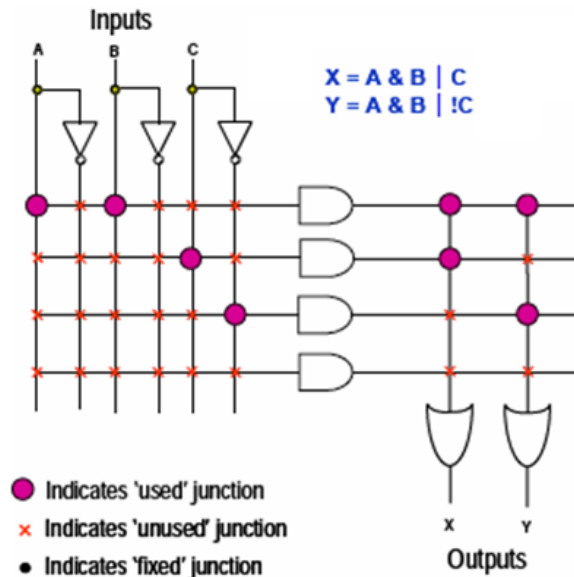


ANSWER THE FOLLOWING QUESTIONS:

1. Briefly discuss pros and cons of simple PAL

Solution:

- Any combination of ANDs/ORs
- High Input-to-output delay (or propagation delay)
- Wafer geometries of $10\mu\text{m}$ technology



2. Consider the next VHDL code:
 - (a) Check and correct syntax errors.
 - (b) Synthesize the next code, and Draw the circuit.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_6411.all;
3
4  ENTITY freq IS
5      PORT ( IN1; IN2; IN3; AND : IN STD LOGIC;
6            Data : out STD LOGIC Vector(7 downto 0));
7  END freq;
8
9  ARCHITECTURE example OF freq IS
10     SIGNAL count1 : STD LOGIC Vector(7 downto 0);
11     BEGIN
12         count1(7) <= not count1(6);

```

[Total Marks is 5]

```

13 count1(6)<= not count1(5);
14 count1(5)<= not count1(3);
15 count1(4)<= not IN1;
16 count1(3)<= in3 or AND;
17 count1(2)<= in3 and in2;
18 count1(1)<=count1(2);
19 count1(1)<=count1(0);
20 Data <= count1;
21 END Freq;
22

```

Solution:


```

1  LIBRARY ieee;
2  USE ieee.std_logic_6411.all;
3  -----
4  ENTITY freq IS
5      PORT ( IN1; IN2; IN3; AND : IN STD LOGIC;
6            Data : out STD LOGIC Vector(7 downto 0));
7  END freq;
8  -----
9  ARCHITECTURE example OF freq IS
10     SIGNAL count1 : STD LOGIC Vector(7 downto 0);
11     BEGIN
12         count1(7)<= not count1(6);
13         count1(6)<= not count1(5);
14         count1(5)<= not count1(3);
15         count1(4)<= not IN1;
16         count1(3)<= in3 or AND;
17         count1(2)<= in3 and in2;
18         count1(1)<=count1(2);
19         count1(1)<=count1(0);
20         Data <= count1;
21     END Freq;

```

▲ VHDl Use Clause error at Vhd11.vhd(2): design library "ieee" does not contain primary unit "std_logic_6411"
 VHDl syntax error at Vhd11.vhd(5) near text ";"; expecting ":", or ",",
 VHDl syntax error at Vhd11.vhd(5) near text "AND"; expecting an identifier
 VHDl error at Vhd11.vhd(5): object "LOGIC" is used but not declared
 VHDl syntax error at Vhd11.vhd(6) near text "Vector"; expecting ";", or ")"
 VHDl syntax error at Vhd11.vhd(10) near text "Vector"; expecting ";", or ":", or "bus", or "register"
 Can't resolve multiple constant drivers for net "count1[1]" at Vhd11.vhd(19)
 VHDl syntax error at Vhd11.vhd(21): name used in construct must match previously specified name "example"

 3. Write a VHDL entity code that realizes the shown circuit.



Solution:

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3

```

4
5
6
7
8
9
10
11
12
13
14
15
16
17

```
ENTITY vhd11 IS
PORT ( a,b,c : IN STD_LOGIC;
y : out STD_logic);
END vhd11;

-----

ARCHITECTURE example OF vhd11 IS
SIGNAL and_out , or_out : STD_logic;
BEGIN
and_out<= a and b;
or_out<= and_out or not c;
y<= not or_out;

END example;

-----
```