 


ANSWER THE FOLLOWING QUESTIONS:

1. Write a VHDL code to implement a minute-to-seconds converter, that accepts two digits and results in the binary equivalent value.

Solution:



```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.numeric_STD.ALL;
4
5  entity div_binary is
6  Port (ina, inb : in std_logic_vector (15 downto 0));
7    result: out std_logic_vector (30 downto 0);
8  end div_binary;
9
10 architecture Behavioral of div_binary is
11 begin
12 process (ina, inb)
13 variable acc: std_logic_vector (30 downto 0):=(others
14 =>'0');
15 variable temp: std_logic_vector (30 downto 0):=(others
16 =>'0');
17 begin
18 acc := (others => '0');
19 temp := "0000" & ina ;
20 for j in 0 to 3 loop
21 if (inb(j)='1') then
22 c(0):='0';
23 for i in 0 to 7 loop
24 sum(i) <= acc(i) xor temp(i) xor c(i);
25 c(i+1):=(acc(i)and temp(i))or(acc(i)and c(i))or(c(i)and
26 temp(i));
27 end loop;
28 acc :=sum;
29 end if;
30 temp:= temp(6 downto 0) & '0';
31 end loop;
32 result <= acc;

```


[Total Marks is 5]

```

30     end process ;
31     end Behavioral ;

```

 2. Write a VHDL entity code that realizes the shown circuit.



Solution:

```

1      LIBRARY ieee ;
2      USE ieee.std_logic_1164.all ;
3
4      ENTITY vhd11 IS
5      PORT ( a,b,c,ab  : IN STD_LOGIC;
6            y : out STD_logic);
7      END vhd11 ;
8
9      ARCHITECTURE example OF vhd11 IS
10     SIGNAL or_out ,mux_out : STD_logic ;
11     BEGIN
12     mux_out<= (a nand b) when bc='0' else not c ;
13     or_out<= (a and b) or not c ;
14
15     y<= 'z' when ab='1' else (mux_out and or_out) ;
16
17     END example ;

```