 


ANSWER THE FOLLOWING QUESTIONS:

1. Write a VHDL code to implement a minute-to-hours converter, that accepts two digits and results in the binary equivalent value.

Solution:




```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.numeric_STD.ALL;
4
5 entity div_binary is
6     Port (ina, inb : in std_logic_vector (15 downto 0);
7         quot, rest: out std_logic_vector (15 downto 0);
8 end div_binary;
9
10 architecture Behavioral of div_binary is
11 begin
12     process (ina, inb)
13         variable temp1: std_logic_vector (30 downto 0):=(others
14             =>'0');
15         variable temp2: std_logic_vector (30 downto 0):=(others
16             =>'0');
17     begin
18         temp1(15 downto 0):=ina;
19         temp2(30 downto 15) :=inb;
20         for i in 15 downto 0 loop
21             if (temp1>temp2 ) then
22                 quot(i):= '1';
23                 temp1:=std_logic_vector (unsigned (
24                     temp1)-unsigned(temp2));
25             else quot(i):= '0';
26             end if;
27             temp2:='0'&temp2(30 downto 1);
28         end loop;
29         rest <= temp1;
30     end process;
31 end Behavioral;

```

[Total Marks is 5]

 2. Write a VHDL entity code that realizes the shown circuit.



Solution:

```

1      LIBRARY ieee;
2      USE ieee.std_logic_1164.all;
3
4      ENTITY vhd11 IS
5      PORT ( a,b,c,ab : IN STD_LOGIC;
6            y : out STD_logic);
7      END vhd11;
8
9      ARCHITECTURE example OF vhd11 IS
10     SIGNAL and_out ,or_out : STD_logic;
11     BEGIN
12     and_out<= (a nand b) and not c;
13     or_out<= (a and b) or not c;
14     y_temp<='z' when ab='1' else and_out;
15     y_temp2<='z' when ab='0' else or_out;
16     -- Multiple driver
17     y<= y_temp or y_temp2;
18
19     END example;
20

```