

# Selected Topics in Electronics

## ECE569/EET21E

Dr. Ashraf Eltholth

ECE  
Misr International University

Spring 2017

# Outline

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

**1 Chapter 5**

2 Chapter 6

3 Chapter 7

4 Chapter 8

# Sequential Circuits

## Outlines


Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

 

# Sequential Circuits

## Outlines


Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

 

## Latches & Flip Flops

- D Latches & D Flip Flops
- Preset & Clear
- JK. FF & T.FF

# Sequential Circuits

## Outlines


Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

 

## Latches & Flip Flops

- D Latches & D Flip Flops
- Preset & Clear
- JK. FF & T.FF

## Registers

- n-bit Registers with controls
- Shift Registers
- Register Applications

# Sequential Circuits

## Outlines


Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

 

## Latches & Flip Flops

- D Latches & D Flip Flops
- Preset & Clear
- JK. FF & T.FF

## Registers


- n-bit Registers with controls
- Shift Registers
- Register Applications

## Counters

- Behavioral Counters
- Structural Counters



# Latches vs. Flip Flops

## Remember

 

# Latches vs. Flip Flops

## Remember

  

Chapter 5

Sequential Circuits

Chapter 6



Chapter 7

Chapter 8



# Latches vs. Flip Flops

## Remember

  

entity Latch is

```
end entity;
Architecture bhv of Latch is
begin
```

```
end Architecture;
```



entity DFF is

```
end entity;
Architecture beh of DFF is
begin
```

```
end Architecture;
```

# Latches vs. Flip Flops

## Remember

  

```
entity Latch is
port (D,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture bhv of Latch is
begin
```



```
end Architecture;
```

```
entity DFF is
port (D,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture beh of DFF is
begin
```

```
end Architecture;
```

# Latches vs. Flip Flops

## Remember

  

```
entity Latch is
port (D,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture bhv of Latch is
begin
```

```
    if (CLK = '1') then
        Q <= D ;
    end if;
```



```
end Architecture;
```

```
entity DFF is
port (D,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture beh of DFF is
begin
```

```
end Architecture;
```

# Latches vs. Flip Flops

## Remember

  

```
entity Latch is
port (D,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture bhv of Latch is
begin
```

```
    if (CLK = '1') then
        Q <= D ;
    end if;
```

```
end Architecture;
```



```
entity DFF is
port (D,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture beh of DFF is
begin
```

```
    if rising_edge(CLK) then
-   if falling_edge(CLK) then
        Q <= D ;
    end if;
```

```
end Architecture;
```

# Latches vs. Flip Flops

## Remember

  

```
entity Latch is
port (D,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture bhv of Latch is
begin
  Process(CLK, D)
  begin
    if (CLK = '1') then
      Q <= D ;
    end if;
  end Process;
end Architecture;
```

```
entity DFF is
port (D,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture beh of DFF is
begin
  Process(CLK)
  begin
    if rising_edge(CLK) then
- if falling_edge(CLK) then
      Q <= D ;
    end if;
  end Process;
end Architecture;
```

# Synchronous vs. Async. Controls

## Preset & Clear



Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

# Synchronous vs. Async. Controls



## Preset & Clear

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity syn is
port (D,CLK : in std_logic;
      preset : in std_logic;
      clear  : in std_logic;
      Q     : out std_logic);
end entity;
Architecture beh of syn is
begin
```

```
end Architecture;
```

```
entity asyn is
port (D,CLK : in std_logic;
      preset : in std_logic;
      clear  : in std_logic;
      Q     : out std_logic);
end entity;
Architecture beh of asyn is
begin
```

```
end Architecture;
```

# Synchronous vs. Async. Controls



## Preset & Clear

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity syn is
port (D,CLK : in std_logic;
      preset : in std_logic;
      clear  : in std_logic;
      Q      : out std_logic);
end entity;
```

```
Architecture beh of syn is
begin
```

```
    Process(CLK)
```

```
    begin
```

```
        end Process;
```

```
end Architecture;
```

```
entity asyn is
port (D,CLK : in std_logic;
      preset : in std_logic;
      clear  : in std_logic;
      Q      : out std_logic);
end entity;
```

```
Architecture beh of asyn is
begin
```

```
    Process(CLK,preset,clear)
```

```
    begin
```

```
        end Process;
```

```
end Architecture;
```



# Synchronous vs. Async. Controls



## Preset & Clear

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity syn is
port (D,CLK : in std_logic;
      preset : in std_logic;
      clear  : in std_logic;
      Q      : out std_logic);
end entity;
Architecture beh of syn is
begin
  Process(CLK)
  begin
    if rising_edge(CLK) then
      if preset = '1' then
        Q <= '1' ;
      elsif clear = '1' then
        Q <= '0' ;
      else
        Q <= D ;
      end if;
    end if;
  end if;
end Process;
end Architecture;
```

```
entity asyn is
port (D,CLK : in std_logic;
      preset : in std_logic;
      clear  : in std_logic;
      Q      : out std_logic);
end entity;
Architecture beh of asyn is
begin
  Process(CLK,preset,clear)
  begin
    end Process;
end Architecture;
```

# Synchronous vs. Async. Controls



## Preset & Clear

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity syn is
port (D,CLK : in std_logic;
      preset : in std_logic;
      clear  : in std_logic;
      Q      : out std_logic);
end entity;
Architecture beh of syn is
begin
  Process(CLK)
  begin
    if rising_edge(CLK) then
      if preset = '1' then
        Q <= '1' ;
      elsif clear = '1' then
        Q <= '0' ;
      else
        Q <= D ;
      end if;
    end if;
  end Process;
end Architecture;
```


```
entity asyn is
port (D,CLK : in std_logic;
      preset : in std_logic;
      clear  : in std_logic;
      Q      : out std_logic);
end entity;
Architecture beh of asyn is
begin
  Process(CLK,preset,clear)
  begin
    if preset = '1' then
      Q <= '1' ;

    elsif clear = '1' then
      Q <= '0' ;

    elsif rising_edge(CLK)
      then Q <= D ;
    end if;
  end Process;
end Architecture;
```

# Latches vs. Flip Flops

## Example

 

```
entity example is
```

```
end entity;
```


```
Architecture behav of example is
```

```
begin
```

```
end Architecture;
```

# Latches vs. Flip Flops

## Example

 


```
entity example is
port (A,B,C,CLK : in std_logic;
      Y : out std_logic);
end entity;
Architecture behav of example is

begin
```

```
end Architecture;
```

# Latches vs. Flip Flops

## Example

 


```
entity example is
port (A,B,C,CLK : in std_logic;
      Y : out std_logic);
end entity;
Architecture behav of example is
signal x1, x2, x3 : std_logic := '0';
begin
```

```
end Architecture;
```

# Latches vs. Flip Flops

## Example

 


```
entity example is
port (A,B,C,CLK : in std_logic;
      Y : out std_logic);
end entity;
Architecture behav of example is
signal x1, x2, x3 : std_logic := '0';
begin
  x1 <= A nand B ;
  x3 <= x2 nor C ;
```

```
end Architecture;
```

# Latches vs. Flip Flops

## Example

 


```

entity example is
port (A,B,C,CLK : in std_logic;
      Y : out std_logic);
end entity;
Architecture behav of example is
signal x1, x2, x3 : std_logic := '0';
begin
  x1 <= A nand B ;
  x2 <= x2 nor C ;
  Process(CLK, x1, x3)
  begin
    end Process;
end Architecture;

```

# Latches vs. Flip Flops

## Example

 

```


entity example is
port (A,B,C,CLK : in std_logic;
      Y : out std_logic);
end entity;
Architecture behav of example is
signal x1, x2, x3 : std_logic := '0';
begin
  x1 <= A nand B ;
  x3 <= x2 nor C ;
  Process(CLK, x1, x3)
  begin
    if (CLK = '1') then
      x2 <= x1 ;
      Y <= x3 ;
    end if;
  end Process;
end Architecture;

```



# Latches vs. Flip Flops

## Example

 


```

entity example is
port (A,B,C,CLK : in std_logic;
      Y : out std_logic);
end entity;
Architecture behav of example is
signal x1, x2, x3 : std_logic := '0';
begin
  x1 <= A nand B ;
  x3 <= x2 nor C ;
  Process(CLK)
  begin
    if rising_edge(CLK) then
      x2 <= x1 ;
      Y <= x3 ;
    end if;
  end Process;
end Architecture;

```

# Latches vs. Flip Flops

## Example

 

```

entity example is
port (A,B,C,CLK : in std_logic;
      Y : out std_logic);
end entity;
Architecture behav of example is
signal x1, x2, x3 : std_logic := '0';
begin
  x1 <= A nand B ;
  x3 <= x2 nor C ;
  Process(CLK)
  begin
    if falling_edge(CLK) then
      x2 <= x1 ;
      Y <= x3 ;
    end if;
  end Process;
end Architecture;

```

# JK Flip Flops

## Remember

```
entity JK_FF is
```

```
end entity;
```

```
Architecture behav of JK_FF is
```

```
begin
```

```
end Architecture;
```

# JK Flip Flops

## Remember

```
entity JK_FF is
port (J,K,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture behav of JK_FF is
```

```
begin
```

```
end Architecture;
```

# JK Flip Flops

## Remember

```
entity JK_FF is
port (J,K,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture behav of JK_FF is
signal Q_temp : std_logic := '0';
signal jk : std_logic_vector(1 downto 0);
begin
```

```
end Architecture;
```

# JK Flip Flops

## Remember

```
entity JK_FF is
port (J,K,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture behav of JK_FF is
signal Q_temp : std_logic := '0';
signal jk : std_logic_vector(1 downto 0);
begin
    jk <= J & K ;
```

```
end Architecture;
```

# JK Flip Flops

## Remember

```
entity JK_FF is
port (J,K,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture behav of JK_FF is
signal Q_temp : std_logic := '0';
signal jk : std_logic_vector(1 downto 0);
begin
    jk <= J & K ;
    Process(CLK)
    begin

end Process;

end Architecture;
```

# JK Flip Flops

## Remember

```
entity JK_FF is
port (J,K,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture behav of JK_FF is
signal Q_temp : std_logic := '0';
signal jk : std_logic_vector(1 downto 0);
begin
    jk <= J & K ;
    Process(CLK)
    begin
        if rising_edge(CLK) then

            end if;
        end Process;
    end Architecture;
```



# JK Flip Flops

## Remember

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity JK_FF is
port (J,K,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture behav of JK_FF is
signal Q_temp : std_logic := '0';
signal jk : std_logic_vector(1 downto 0);
begin
    jk <= J & K ;
    Process(CLK)
    begin
        if rising_edge(CLK) then
            if (jk="10") then
                Q_temp <= '1';
            elsif (jk="01") then
                Q_temp <= '0';
            if (jk="11") then
                Q_temp <= not(Q_temp);
            end if;
        end if;
    end Process;
end Architecture;
```

# JK Flip Flops

## Remember

```
entity JK_FF is
port (J,K,CLK : in std_logic;
      Q : out std_logic);
end entity;
Architecture behav of JK_FF is
signal Q_temp : std_logic := '0';
signal jk : std_logic_vector(1 downto 0);
begin
    jk <= J & K ;
    Process(CLK)
    begin
        if rising_edge(CLK) then
            if (jk="10") then
                Q_temp <= '1';
            elsif (jk="01") then
                Q_temp <= '0';
            if (jk="11") then
                Q_temp <= not(Q_temp);
            end if;
        end if;
    end Process;
    Q <= Q_temp;
end Architecture;
```

# Flip Flops

## Check Your Understanding


Chapter 5

Sequential Circuits

Chapter 6


Chapter 7

Chapter 8

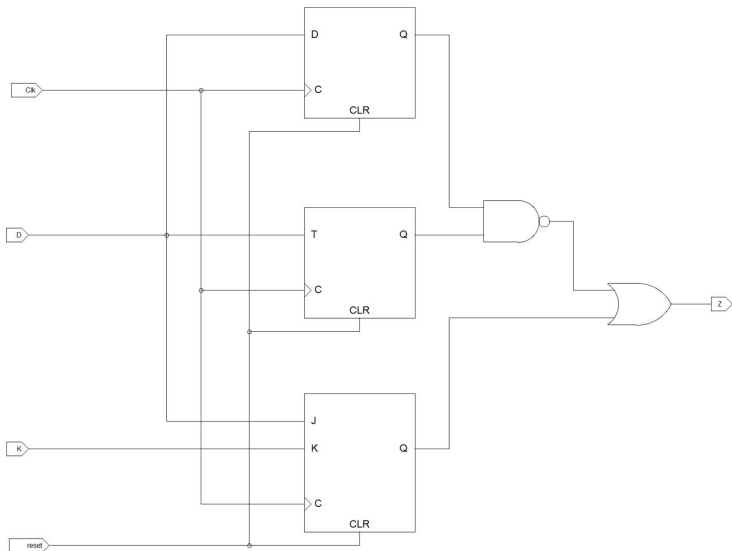

# Registers

## General

 

```
entity REG is
```


```
end entity;
```

```
Architecture beh of REG is
```

```
begin
```

# Registers

## General

 

entity REG is

```
port (CLK, clk_en, reset, set : in std_logic;
      D: in std_logic_vector(7 downto 0);
      Q : out std_logic_vector(7 downto 0));
```

end entity;

Architecture beh of REG is

begin


```
    Process(CLK, reset, set)
```

```
    begin
```

```
end Process;
```

# Registers

## General

 


```
entity REG is
port (CLK, clk_en, reset, set : in std_logic;
      D: in std_logic_vector(7 downto 0);
      Q : out std_logic_vector(7 downto 0));
end entity;
Architecture beh of REG is
begin
  Process(CLK, reset, set)
    begin
```

```
      if rising_edge(CLK) then
        Q <= D ;
      end if;
```

```
end Process;
```

# Registers

## General

 

```

entity REG is
port (CLK, clk_en, reset, set : in std_logic;
      D: in std_logic_vector(7 downto 0);
      Q : out std_logic_vector(7 downto 0));
end entity;
Architecture beh of REG is
begin
  Process(CLK, reset, set)
  begin
    if reset = '1' then Q <= (others => '0') ;
    elsif set = '1' then Q <= (others => '1') ;
    elsif clk_en = '1' then
      if rising_edge(CLK) then
        Q <= D ;
      end if;
    end if;
  end Process;

```

# Shift Registers



## Key Component

Chapter 5  
Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

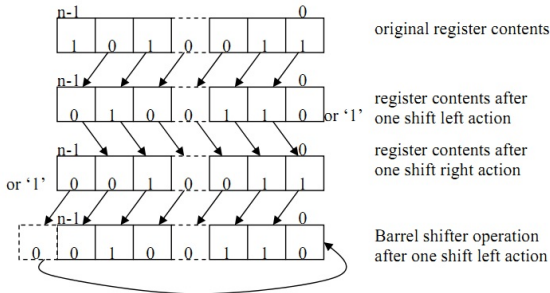 



# Shift Registers

## Key Component

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity SREG is
```

```
end entity;  
Architecture beh of SREG is
```

```
begin
```

```
end Architecture;
```

# Shift Registers

## Key Component

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity SREG is
port (clk, rst, shift_right, shift_left: in std_logic;
      reg_in: in std_logic_vector(7 downto 0);
      reg_in : out std_logic_vector(7 downto 0));
end entity;
Architecture beh of SREG is
    signal shift_control: std_logic_vector(1 downto 0);
    signal reg_temp: std_logic_vector(7 downto 0);
begin
    shift_control <= shift_left & shift_right;
    Process(rst, clk)
    begin
        end Process;
    end Architecture;
```

# Shift Registers

## Key Component

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity SREG is
port (clk, rst, shift_right, shift_left: in std_logic;
      reg_in: in std_logic_vector(7 downto 0);
      reg_in : out std_logic_vector(7 downto 0));
end entity;

Architecture beh of SREG is
  signal shift_control: std_logic_vector(1 downto 0);
  signal reg_temp: std_logic_vector(7 downto 0);
begin
  shift_control <= shift_left & shift_right;
  Process(rst, clk)
  begin
    if rst = '1' then reg_temp <= (others => '0') ;
    elsif rising_edge(CLK) then

    end if;
  end Process;
end Architecture;
```

# Shift Registers

## Key Component

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity SREG is
port (clk, rst, shift_right, shift_left: in std_logic;
      reg_in: in std_logic_vector(7 downto 0);
      reg_in : out std_logic_vector(7 downto 0));
end entity;

Architecture beh of SREG is
  signal shift_control: std_logic_vector(1 downto 0);
  signal reg_temp: std_logic_vector(7 downto 0);
begin
  shift_control <= shift_left & shift_right;
  Process(rst, clk)
  begin
    if rst = '1' then reg_temp <= (others => '0') ;
    elsif rising_edge(CLK) then
      case shift_control is

          end case;
        end if;
      end Process;
    end Architecture;
```

# Shift Registers

## Key Component

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity SREG is
port (clk, rst, shift_right, shift_left: in std_logic;
      reg_in: in std_logic_vector(7 downto 0);
      reg_out : out std_logic_vector(7 downto 0));
end entity;

Architecture beh of SREG is
    signal shift_control: std_logic_vector(1 downto 0);
    signal reg_temp: std_logic_vector(7 downto 0);
begin
    shift_control <= shift_left & shift_right;
    Process(rst, clk)
    begin
        if rst = '1' then reg_temp <= (others => '0') ;
        elsif rising_edge(CLK) then
            case shift_control is
                when "00" => reg_temp <= reg_in;
                when "01" => reg_temp <= '0' & reg_temp(7 downto 1);
                when "10" => reg_temp <= reg_temp(6 downto 0) & '0';
                when others => reg_temp <= reg_temp;
            end case;
        end if;
    end Process;
end Architecture;
```

# Shift Registers

## Serial to Parallel & Parallel to Serial Conversion

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity s2p is
port (clk, rst: in std_logic;
      reg_in: in std_logic;
      reg_out : out std_logic_vector(7 downto 0);
      out_ready : out std_logic);
end entity;
```

# Shift Registers

## Serial to Parallel & Parallel to Serial Conversion

Chapter 5

Sequential Circuits

Chapter 6


Chapter 7

Chapter 8

```

entity s2p is
port (clk, rst: in std_logic;
      reg_in: in std_logic;
      reg_out : out std_logic_vector(7 downto 0);
      out_ready : out std_logic);
end entity;

```

 

# Shift Registers

## Serial to Parallel & Parallel to Serial Conversion

Chapter 5

Sequential Circuits

Chapter 6


Chapter 7

Chapter 8

```

entity s2p is
port (clk, rst: in std_logic;
      reg_in: in std_logic;
      reg_out : out std_logic_vector(7 downto 0);
      out_ready : out std_logic);
end entity;

```

 

### Check Your Understanding

Write the corresponding VHDL codes?



# Shift Registers

## Serial to Parallel & Parallel to Serial Conversion

Chapter 5

**Sequential Circuits**

Chapter 6

Chapter 7

Chapter 8

# Shift Registers

## Serial to Parallel & Parallel to Serial Conversion



Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity p2s is
port (clk, rst: in std_logic;
      reg_in: in std_logic_vector(7 downto 0);
      reg_out : out std_logic);
end entity;
```

# Shift Registers

## Serial to Parallel & Parallel to Serial Conversion

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
entity p2s is
port (clk, rst: in std_logic;
      reg_in: in std_logic_vector(7 downto 0);
      reg_out : out std_logic);
end entity;
```

### Check Your Understanding

Write the corresponding VHDL codes?

# Shift Registers

## Linear Feedback Shift Register


Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

 


entity lfsr is

```
port (clk, rst, enable: in std_logic;  
      reg_out : out std_logic_vector(7 downto 0));  
end entity;
```

# Shift Registers


## Linear Feedback Shift Register

 

```
entity lfsr is
  generic(reg:std_logic_vector(7 downto 0):="00111010");
  port (clk, rst, enable: in std_logic;
        reg_out : out std_logic_vector(7 downto 0));
end entity;
```

# Shift Registers

## Linear Feedback Shift Register

 

```
entity lfsr is
generic(reg:std_logic_vector(7 downto 0):="00111010");
port (clk, rst, enable: in std_logic;
      reg_out : out std_logic_vector(7 downto 0));
end entity;
```

### Check Your Understanding

Consider the case when it is required to repeat the first 512 output symbols only, write the corresponding VHDL code.

# Counters

## Behavioral

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
entity COUNT8 is
  port(
    DIN      : in    std_logic_vector(7 downto 0);
    CLK      : in    std_logic;
    LOAD     : in    std_logic;
    DOUT     : out   std_logic_vector(7 downto 0));
end COUNT8;

architecture behavior of COUNT8 is
begin
  -- notice the process statement and the variable COUNT
  clk_proc:process(CLK)
  variable COUNT:unsigned(7 downto 0) := "00000000";
  begin
    if (CLK'EVENT AND CLK = '1') then
      if LOAD = '1' then
        COUNT := DIN;
      else COUNT := COUNT + 1;
      end if;
    end if;
    DOUT <= COUNT after 50 ns;
  end process clk_proc;
end behavior;
```

# Counters

## Behavioral

Chapter 5

Sequential Circuits

Chapter 6

Chapter 7

Chapter 8

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Counter2_VHDL is
    port( Clock,Reset,Clock_enable_B: in std_logic;
          Output: out std_logic_vector(0 to 3));
end Counter2_VHDL;
architecture Behavioral of Counter2_VHDL is
    signal temp: std_logic_vector(0 to 3);
begin process(Clock,Reset)
    begin
        if Reset='1' then
            temp <= "0000";
        elsif(Clock'event and Clock='1') then
            if Clock_enable_B='0' then
                if temp="1001" then
                    temp<="0000";
                else
                    temp <= temp + 1;
                end if;
            end if;
        end if;
    end process;
    Output <= temp;
end Behavioral;
```



Chapter 5

**Sequential Circuits**

Chapter 6

Chapter 7

Chapter 8



Chapter 5

**Chapter 6**

Finite State Machines

Chapter 7

Chapter 8

# Outline

1 Chapter 5

**2 Chapter 6**

3 Chapter 7

4 Chapter 8

# Finite State Machines

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

- Finite State Machine is a tool to model the desired behavior of a sequential system.

# Finite State Machines

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

- Finite State Machine is a tool to model the desired behavior of a sequential system.
- A FSM consists of several states, Inputs into the machine are combined with the current state of the machine to determine the new state or next state of the machine.

# Finite State Machines

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

- Finite State Machine is a tool to model the desired behavior of a sequential system.
- A FSM consists of several states, Inputs into the machine are combined with the current state of the machine to determine the new state or next state of the machine.
- Depending on the state of the machine, outputs are generated based on either the state or the state and inputs of the machine.

# Finite State Machines

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

- Finite State Machine is a tool to model the desired behavior of a sequential system.
- A FSM consists of several states, Inputs into the machine are combined with the current state of the machine to determine the new state or next state of the machine.
- Depending on the state of the machine, outputs are generated based on either the state or the state and inputs of the machine.
- The designer has to develop a finite state model of the system behavior and then designs a circuit that implements this model.

# Finite State Machines

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

- Finite State Machine is a tool to model the desired behavior of a sequential system.
- A FSM consists of several states, Inputs into the machine are combined with the current state of the machine to determine the new state or next state of the machine.
- Depending on the state of the machine, outputs are generated based on either the state or the state and inputs of the machine.
- The designer has to develop a finite state model of the system behavior and then designs a circuit that implements this model.
  - Design the State Diagram for the required Functionality.

# Finite State Machines

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

- Finite State Machine is a tool to model the desired behavior of a sequential system.
- A FSM consists of several states, Inputs into the machine are combined with the current state of the machine to determine the new state or next state of the machine.
- Depending on the state of the machine, outputs are generated based on either the state or the state and inputs of the machine.
- The designer has to develop a finite state model of the system behavior and then designs a circuit that implements this model.
  - Design the State Diagram for the required Functionality.
  - Implement that FSM design using "Flip Flops" (and **Visa Versa**)



# Finite State Machines

Chapter 5

Chapter 6

Finite State Machines

Chapter 7


Chapter 8

- Finite State Machine is a tool to model the desired behavior of a sequential system.
- A FSM consists of several states, Inputs into the machine are combined with the current state of the machine to determine the new state or next state of the machine.
- Depending on the state of the machine, outputs are generated based on either the state or the state and inputs of the machine.
- The designer has to develop a finite state model of the system behavior and then designs a circuit that implements this model.
  - Design the State Diagram for the required Functionality.
  - Implement that FSM design using "Flip Flops" (and Visa Versa)
  - Represent vthat FSM using VHDL code (and Visa Versa)

# Finite State Machine
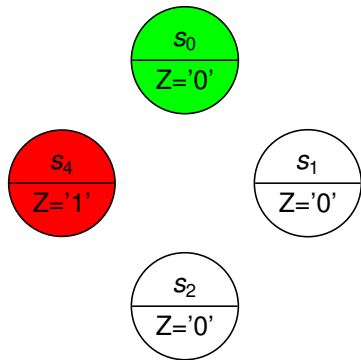
## State Diagram

The FSM diagram consists of **State Bubbles** and **conditions** controlling transitions among states.




# Finite State Machine
 
## State Diagram

The FSM diagram consists of **State Bubbles** and **conditions** controlling transitions among states.

- the lines connecting state bubbles starts from the current state and ends at the next state
- The conditions related to  $s_0$  state that if  $X=1$  then the system will change its state to  $s_1$  otherwise it will remain  $s_0$ . and the output will remain  $Z=0$ .




# Finite State Machine
 
## State Diagram


The FSM diagram consists of **State Bubbles** and **conditions** controlling transitions among states.

- the lines connecting state bubbles starts from the current state and ends at the next state
- The conditions related to  $s_0$  state that if  $X=1$  then the system will change its state to  $s_1$  otherwise it will remain  $s_0$ . and the output will remain  $Z=0$ .



# Moore vs. Mealy FSM

## Moore

 

Present state	Next state		Output (Z)
	X=0	X=1	X=0
S0	S0	S2	0
S1	S0	S2	1
S2	S2	S3	1
S3	S3	S1	0

# Moore vs. Mealy FSM

Chapter 5


Chapter 6

Finite State Machines

Chapter 7


Chapter 8

## Moore

 

Present state	Next state		Output (Z)
	X=0	X=1	X=0
S0	S0	S2	0
S1	S0	S2	1
S2	S2	S3	1
S3	S3	S1	0


## Mealy

 

Present state	Next state		Output (Z)
	X=0	X=1	X=0 X=1
S0	S0	S2	0 1
S1	S0	S2	0 0
S2	S2	S3	1 0
S3	S3	S1	0 1

 
# FSM Example

Design a module with O/P  
 $Z = '1'$  when the previous  
values of  $W$  are "110" or  
"101" otherwise  $Z = '0'$


 
# FSM Example


Design a module with O/P  
 $Z = '1'$  when the previous  
values of  $W$  are "110" or  
"101" otherwise  $Z = '0'$





 
# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$



 
# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$



 
# FSM Example

Design a module with O/P  
 $Z = '1'$  when the previous  
values of  $W$  are "110" or  
"101" otherwise  $Z = '0'$


 
# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$




# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0

 




# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0
011	0	100	0

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0
011	0	100	0
011	1	011	0

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0
011	0	100	0
011	1	011	0
100	0	000	1

 


# FSM Example

Design a module with O/P  $Z = '1'$  when the previous values of  $W$  are "110" or "101" otherwise  $Z = '0'$

We have **5 States** so, it is required to have **3 Flip Flops** to store the states for the next time slot.

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0
011	0	100	0
011	1	011	0
100	0	000	1
100	1	001	1

 

# FSM Example

Chapter 5

Chapter 6

Finite State Machines


Chapter 7

Chapter 8

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0
011	0	100	0
011	1	011	0
100	0	000	1
100	1	001	1

Boolean Equations
 
$$Z = Q_1 \cdot \overline{Q_2} \cdot \overline{Q_3}$$





# FSM Example

Chapter 5

Chapter 6

Finite State Machines

Chapter 7


Chapter 8

Current	input	next	output
$Q_1 Q_2 Q_3$	W	$D_1 D_2 D_3$	Z
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0
011	0	100	0
011	1	011	0
100	0	000	1
100	1	001	1

Boolean Equations

$$Z = Q_1 \cdot \overline{Q_2} \cdot \overline{Q_3}$$
 
$$D_1 = \overline{Q_1} \cdot Q_2 \cdot \overline{Q_3} + \overline{Q_1} \cdot Q_2 \cdot Q_3$$



# FSM Example

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8


Current	input	next	output
$Q_1 Q_2 Q_3$	W	$D_1 D_2 D_3$	Z
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0
011	0	100	0
011	1	011	0
100	0	000	1
100	1	001	1

### Boolean Equations

$$Z = \overline{Q_1} \cdot \overline{Q_2} \cdot \overline{Q_3}$$

$$D_1 = \overline{Q_1} \cdot \overline{Q_2} \cdot \overline{Q_3} + \overline{Q_1} \cdot \overline{Q_2} \cdot Q_3$$

$$D_2 = \dots + \dots + \dots$$

 

# FSM Example

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

Current	input	next	output
$Q_1 Q_2 Q_3$	$W$	$D_1 D_2 D_3$	$Z$
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	000	0
010	1	100	0
011	0	100	0
011	1	011	0
100	0	000	1
100	1	001	1


## Boolean Equations

$$Z = \overline{Q_1} \cdot \overline{Q_2} \cdot \overline{Q_3}$$

$$D_1 = \overline{Q_1} \cdot \overline{Q_2} \cdot \overline{Q_3} + \overline{Q_1} \cdot \overline{Q_2} \cdot Q_3$$

$$D_2 = \dots + \dots + \dots$$

$$D_3 = \dots + \dots + \dots + \dots$$

 

# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
```

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
    Type State is (s0,s1,s2,s3,s4);
    Signal C_state, N_state : state;
Begin
```

```
End behav;
```

# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
    Type State is (s0,s1,s2,s3,s4);
    Signal C_state, N_state : state;
Begin
    Process(CLK, RST)
    Begin
        if (RST='1') then C_state <= s0;
        elsif (rising_edge(CLK)) then C_state <= N_state;
        end if;
    End Process;
```

```
End behav;
```

# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
    Type State is (s0,s1,s2,s3,s4);
    Signal C_state, N_state : state;
Begin
    Process(CLK, RST)
    Begin
        if (RST='1') then C_state <= s0;
        elsif (rising_edge(CLK)) then C_state <= N_state;
        end if;
    End Process;
    Process(W, C_state)
    Begin
        Case C_state is

End case;
End Process;

End behav;
```

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
    Type State is (s0,s1,s2,s3,s4);
    Signal C_state, N_state : state;
Begin
    Process(CLK, RST)
    Begin
        if (RST='1') then C_state <= s0;
        elsif (rising_edge(CLK)) then C_state <= N_state;
        end if;
    End Process;
    Process(W, C_state)
    Begin
        Case C_state is
        when s0 => if (W='1') then N_state <= s1; end if;

        End case;
    End Process;

End behav;
```

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8



# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
    Type State is (s0,s1,s2,s3,s4);
    Signal C_state, N_state : state;
    Begin
    Process(CLK, RST)
    Begin
    if (RST='1') then C_state <= s0;
    elsif (rising_edge(CLK)) then C_state <= N_state;
    end if;
    End Process;
    Process(W, C_state)
    Begin
    Case C_state is
    when s0 => if (W='1') then N_state <= s1; end if;
    when s1 =>
        if (W='0') then N_state <= s2; else N_state <= s3; end if;

    End case;
    End Process;

    End behav;
```

# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
    Type State is (s0,s1,s2,s3,s4);
    Signal C_state, N_state : state;
    Begin
    Process(CLK, RST)
    Begin
    if (RST='1') then C_state <= s0;
    elsif (rising_edge(CLK)) then C_state <= N_state;
    end if;
    End Process;
    Process(W, C_state)
    Begin
    Case C_state is
    when s0 => if (W='1') then N_state <= s1; end if;
    when s1 =>
        if (W='0') then N_state <= s2; else N_state <= s3; end if;
    when s3 =>
        if (W='0') then N_state <= s4; end if;
    End case;
    End Process;

    End behav;
```

# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
    Type State is (s0,s1,s2,s3,s4);
    Signal C_state, N_state : state;
    Begin
    Process(CLK, RST)
    Begin
    if (RST='1') then C_state <= s0;
    elsif (rising_edge(CLK)) then C_state <= N_state;
    end if;
    End Process;
    Process(W, C_state)
    Begin
    Case C_state is
    when s0 => if (W='1') then N_state <= s1; end if;
    when s1 =>
        if (W='0') then N_state <= s2; else N_state <= s3; end if;
    when s3 =>
        if (W='0') then N_state <= s4; end if;
    when s2 =>
        if (W='0') then N_state <= s0; else N_state <= s4; end if;
    End case;
    End Process;

    End behav;
```

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

# Finite State Machine

## Example

```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
Type State is (s0,s1,s2,s3,s4);
Signal C_state, N_state : state;
Begin
Process(CLK, RST)
Begin
if (RST='1') then C_state <= s0;
elsif (rising_edge(CLK)) then C_state <= N_state;
end if;
End Process;
Process(W, C_state)
Begin
Case C_state is
when s0 => if (W='1') then N_state <= s1; end if;
when s1 =>
    if (W='0') then N_state <= s2; else N_state <= s3; end if;
when s3 =>
    if (W='0') then N_state <= s4; end if;
when s2 =>
    if (W='0') then N_state <= s0; else N_state <= s4; end if;
when s4 =>
    if (W='0') then N_state <= s0; else N_state <= s1; end if;
End case;
End Process;

End behav;
```

# Finite State Machine

## Example


```
entity TOP_MODULE is
    port (CLK, RST, W : IN STD_LOGIC; Z : OUT STD_LOGIC);
end TOP_MODULE;
Architecture behav of TOP_MODULE is
Type State is (s0,s1,s2,s3,s4);
Signal C_state, N_state : state;
Begin
Process(CLK, RST)
Begin
if (RST='1') then C_state <= s0;
elsif (rising_edge(CLK)) then C_state <= N_state;
end if;
End Process;
Process(W, C_state)
Begin
Case C_state is
when s0 => if (W='1') then N_state <= s1; end if;
when s1 =>
    if (W='0') then N_state <= s2; else N_state <= s3; end if;
when s3 =>
    if (W='0') then N_state <= s4; end if;
when s2 =>
    if (W='0') then N_state <= s0; else N_state <= s4; end if;
when s4 =>
    if (W='0') then N_state <= s0; else N_state <= s1; end if;
End case;
End Process;
Z<='1' when (C_state = s4) else '0';
End behav;
```

# Example

## state table

Draw the state diagram for the **FSM** represented by the following **State Table**

State Current	Next		Output	
	in 0	in 1	in 0	in 1
$s_0$	$s_0$	$s_1$	0	1
$s_1$	$s_3$	$s_2$	1	1
$s_2$	$s_1$	$s_0$	1	0
$s_3$	$s_0$	$s_1$	0	0

 

Note that this is **Mealy FSM**


Can you implement the equivalent circuit with different types of Flip Flops?

# Example

## state table

Draw the state diagram for the **FSM** represented by the following **State Table**

State Current	Next		Output	
	in 0	in 1	in 0	in 1
$s_0$	$s_0$	$s_1$	0	1
$s_1$	$s_3$	$s_2$	1	1
$s_2$	$s_1$	$s_0$	1	0
$s_3$	$s_0$	$s_1$	0	0

 

Note that this is **Mealy FSM**


Can you implement the equivalent circuit with different types of Flip Flops?

# Example

## state table

Draw the state diagram for the **FSM** represented by the following **State Table**

State	Next		Output	
	in 0	in 1	in 0	in 1
$s_0$	$s_0$	$s_1$	0	1
$s_1$	$s_3$	$s_2$	1	1
$s_2$	$s_1$	$s_0$	1	0
$s_3$	$s_0$	$s_1$	0	0

 

Note that this is **Mealy FSM**

Can you implement the equivalent circuit with different types of Flip Flops?




# Example

## state table

Draw the state diagram for the **FSM** represented by the following **State Table**

State	Next				Output	
	in	in	in	in	in	in
Current	0	1	0	1	0	1
$s_0$	$s_0$	$s_1$	0	1	0	1
$s_1$	$s_3$	$s_2$	1	1	1	1
$s_2$	$s_1$	$s_0$	1	0	1	0
$s_3$	$s_0$	$s_1$	0	0	0	0

 

Note that this is **Mealy FSM**


Can you implement the equivalent circuit with different types of Flip Flops?

# Example

## state table

Draw the state diagram for the **FSM** represented by the following **State Table**

State	Next				Output	
	in	in	in	in	in	in
Current	0	1	0	1	0	1
$s_0$	$s_0$	$s_1$	0	1	0	1
$s_1$	$s_3$	$s_2$	1	1	1	1
$s_2$	$s_1$	$s_0$	1	0	1	0
$s_3$	$s_0$	$s_1$	0	0	0	0

 

Note that this is **Mealy FSM**

Can you implement the equivalent circuit with different types of Flip Flops?

# Example

## state table

Draw the state diagram for the **FSM** represented by the following **State Table**


State	Next				
Current	00	01	11	10	output
Init	$A_0$	$A_0$	$A_1$	$A_1$	0
$A_0$	$OK_0$	$OK_0$	$A_1$	$A_1$	0
$A_1$	$A_0$	$A_0$	$OK_1$	$OK_1$	0
$OK_0$	$OK_0$	$OK_0$	$OK_1$	$A_1$	1
$OK_1$	$A_0$	$OK_0$	$OK_1$	$OK_1$	1

Note that this is **Moore FSM** Why?

Can you implement the equivalent circuit with different types of Flip Flops?

# Logic Circuit Example

Consider the Circuit Shown:

 

Chapter 5

Chapter 6


Finite State Machines

Chapter 7

Chapter 8

# Logic Circuit Example

Consider the Circuit Shown:

 

$$J_A = B, \quad K_A = B \cdot \bar{X}$$

$$J_B = \bar{X}, \quad K_B = \bar{A} \cdot X + A \cdot \bar{X} = A \oplus X$$


Excitation Table for the JK Flip-flop

$Q$	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**Can you extract the FSM?**

# Logic Circuit Example

Consider the Circuit Shown:

 

$$J_A = B \quad , \quad K_A = B \cdot \bar{x}$$

$$J_B = \bar{x} \quad , \quad K_B = \bar{A} \cdot x + A \cdot \bar{x} = A \oplus x$$

Excitation Table for the JK Flip-flop


$Q$	$Q^+$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

**Can you extract the FSM?**

A	B	x	$J_A$	$K_A$	$J_B$	$K_B$	$A^+$	$B^+$
0	0	0						

# Logic Circuit Example

Consider the Circuit Shown:

 

$$J_A = B \quad , \quad K_A = B \cdot \bar{x}$$

$$J_B = \bar{x} \quad , \quad K_B = \bar{A} \cdot x + A \cdot \bar{x} = A \oplus x$$

Excitation Table for the JK Flip-flop


$Q$	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**Can you extract the FSM?**

A	B	x	$J_A$	$K_A$	$J_B$	$K_B$	$A^+$	$B^+$
0	0	0	0	0	1	0		

# Logic Circuit Example

Consider the Circuit Shown:

 

$$J_A = B \quad , \quad K_A = B \cdot \bar{x}$$

$$J_B = \bar{x} \quad , \quad K_B = \bar{A} \cdot x + A \cdot \bar{x} = A \oplus x$$

Excitation Table for the JK Flip-flop

$Q$	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


**Can you extract the FSM?**

A	B	x	$J_A$	$K_A$	$J_B$	$K_B$	$A^+$	$B^+$
0	0	0	0	0	1	0	0	1
0	0	1						



# Logic Circuit Example

Consider the Circuit Shown:

 

$$J_A = B \quad , \quad K_A = B \cdot \bar{x}$$

$$J_B = \bar{x} \quad , \quad K_B = \bar{A} \cdot x + A \cdot \bar{x} = A \oplus x$$

Excitation Table for the JK Flip-flop


$Q$	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**Can you extract the FSM?**

A	B	x	$J_A$	$K_A$	$J_B$	$K_B$	$A^+$	$B^+$
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1		

# Logic Circuit Example

Consider the Circuit Shown:

 

$$J_A = B \quad , \quad K_A = B \cdot \bar{x}$$

$$J_B = \bar{x} \quad , \quad K_B = \bar{A} \cdot x + A \cdot \bar{x} = A \oplus x$$

Excitation Table for the JK Flip-flop


$Q$	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**Can you extract the FSM?**

A	B	x	$J_A$	$K_A$	$J_B$	$K_B$	$A^+$	$B^+$
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0

# Logic Circuit Example

Consider the Circuit Shown:

 

$$J_A = B \quad , \quad K_A = B \cdot \bar{x}$$

$$J_B = \bar{x} \quad , \quad K_B = \bar{A} \cdot x + A \cdot \bar{x} = A \oplus x$$

Excitation Table for the JK Flip-flop


$Q$	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**Can you extract the FSM?**

A	B	x	$J_A$	$K_A$	$J_B$	$K_B$	$A^+$	$B^+$
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1

# Logic Circuit Example

Consider the Circuit Shown:

 

$$J_A = B \quad , \quad K_A = \bar{B}$$


$$J_B = \bar{x} \quad , \quad K_B = \bar{A} \cdot x + A \cdot \bar{x} = A \oplus x$$

Excitation Table for the JK Flip-flop

$Q$	$Q^+$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


Can you extract the FSM?

A	B	x	$J_A$	$K_A$	$J_B$	$K_B$	$A^+$	$B^+$
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1

 

# Logic Circuit Example

Consider the Circuit Shown:

 

## Input Functions


$$DA = A \cdot X + B \cdot X$$

$$DB = \bar{A} \cdot X$$

$$y = (A + B) \cdot \bar{X}$$

# Logic Circuit Example

Consider the Circuit Shown:

 

**Input Functions**

$$DA = A \cdot X + B \cdot X$$


$$DB = \bar{A} \cdot X$$

$$Y = (A + B) \cdot \bar{X}$$

Note that this is **Mealy FSM**  
Why?

# Logic Circuit Example

Consider the Circuit Shown:

 

State Transition Table

		Input		Output	
A	B	X	A <sup>+</sup>	B <sup>+</sup>	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Input Functions

$$DA = A \cdot X + B \cdot X$$


$$DB = \bar{A} \cdot X$$

$$Y = (A + B) \cdot \bar{X}$$

Note that this is **Mealy FSM**  
Why?

# Logic Circuit Example

Consider the Circuit Shown:

 

Input Functions

$$DA = A \cdot X + B \cdot X$$


$$DB = \bar{A} \cdot X$$

$$Y = (A + B) \cdot \bar{X}$$

State Transition Table

		Input	DA	DB	Output
A	B	X	A <sup>+</sup>	B <sup>+</sup>	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State Transition Diagram

 


Note that this is **Mealy FSM**  
Why?


 
# Logic Circuit Example

The sequential circuit below has one D flip-flop, two inputs (X and Y), and one output (S). The circuit consists of a full adder circuit whose carry output is connected to a D flip-flop.



1. Derive the truth table for the above circuit.
2. Draw the state diagram for this circuit (be sure to show the output S in the diagram).
3. Is the finite state machine of the Moore type or the Mealy type? Explain.

# Logic Circuit Example

Chapter 5


Chapter 6

Finite State Machines

Chapter 7

Chapter 8

x	y	z	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Mealy. S depends on the state and the inputs.

# Counter Example

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

Design a 3 bit counter which counts in the sequence:

001, 011, 010, 110, 111, 101, 001, ...

- (a) Use clocked D flip-flops
- (b) Use clocked T flip-flop
- (c) Use J-K flip-flop

Reminder: The following table summarizes state changes for D, T, and J-K flip-flops

$Q \rightarrow Q_+$	D flip-flop D	Toggle Flip-flop T	J-K Flip-flop			
			J	K	J	K
$0 \rightarrow 0$	0	0	0	1	0	x
$0 \rightarrow 1$	1	1	1	0	1	x
$1 \rightarrow 0$	0	1	0	1	x	1
$1 \rightarrow 1$	1	0	0	0	x	0

# Counter Example

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

Step1. Determine the number of flip-flop stages required. In this case it is 3.

Step2. Flip-flop outputs  $Q_2Q_1Q_0$  are determined by the specifications. Present state and next state tables are constructed. The present state-next state table (quick and full) is shown below. Make sure that the counter counts in the following order:

→ 001 → 011 → 010 → 110 → 111 → 101 →

Quick table:

Present-state			Next-state		
$Q_2$	$Q_1$	$Q_0$	$Q_{2+}$	$Q_{1+}$	$Q_{0+}$
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	0	0	1

Full table:

Present-state			Next-state		
$Q_2$	$Q_1$	$Q_0$	$Q_{2+}$	$Q_{1+}$	$Q_{0+}$
0	0	0	x	x	x
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	x	x	x
1	0	1	0	0	1
1	1	0	1	1	1
1	1	1	1	0	1

On Karnaugh map, put x for the states that does not exist in this table

# Counter Example

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

Step 3. Find state transition relationships for each pair of present-state-next-state columns, using the state change table for the chosen flip-flop.

Step 4. Use the complete present state as input to truth tables whose outputs are state transition values corresponding to each flip-flop input.

Step 5. With map or Boolean algebra methods find expressions (excitation equations) for each flip-flop input from the truth tables of step 4.

Step 6. Form system outputs from combinations of the flip-flop outputs.

Step 7. Realize the excitation expressions as combinational logic drives for the flip-flop inputs.

Step 8. You can check your design by constructing a timing diagram.

# Counter Example

- (a) Implementation using D flip-flop. (Since the quick table is used, do not forget to put x to the respective boxes in the Karnaugh map for missing states in the table)

Present-state			Next-state			Flip-flop input		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2+</sub>	Q <sub>1+</sub>	Q <sub>0+</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	1	0	1	1	0	1	1
0	1	1	0	1	0	0	1	0
0	1	0	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	1	0	1	1	0	1
1	0	1	0	0	1	0	0	1

Q <sub>1</sub> Q <sub>0</sub> \ Q <sub>2</sub>	00	01	11	10	00	01	11	10	00	01	11	10
0	x	0	0	1	x	1	1	1	x	1	0	0
1	x	0	1	1	x	0	0	1	x	1	1	1

$$D_2 = Q_0' + Q_2Q_1$$

$$D_1 = Q_2' + Q_0'$$

$$D_0 = Q_1' + Q_2$$

# Counter Example

Chapter 5

Chapter 6

Finite State Machines


Chapter 7

Chapter 8

$$D_2 = Q_0' + Q_2Q_1$$

$$D_1 = Q_2' + Q_0'$$

$$D_0 = Q_1' + Q_2$$

 

# Counter Example

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

(b) Implementation using T flip-flop. The following table gives the states of the flip-flop inputs. (use the reminder if you don't remember the state changes).

Present-state			Next-state			Flip-flop input		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2+</sub>	Q <sub>1+</sub>	Q <sub>0+</sub>	T <sub>2</sub>	T <sub>1</sub>	T <sub>0</sub>
0	0	1	0	1	1	0	1	0
0	1	1	0	1	0	0	0	1
0	1	0	1	1	0	1	0	0
1	1	0	1	1	1	0	0	1
1	1	1	1	0	1	0	1	0
1	0	1	0	0	1	1	0	0



# Counter Example

Chapter 5

Chapter 6

Finite State Machines

Chapter 7


Chapter 8

	$T_2$				$T_1$				$T_0$			
$Q_1Q_0$	00	01	11	10	00	01	11	10	00	01	11	10
$Q_2$												
0	x	0	0	1	x	1	0	0	x	0	1	0
1	x	1	0	0	x	0	1	0	x	0	0	1

$$T_2 = Q_2'Q_0' + Q_2Q_1'$$

$$T_1 = Q_2'Q_1' + Q_2Q_1Q_0$$

$$T_0 = Q_2Q_0' + Q_2'Q_1Q_0$$

 

# State Reduction

Chapter 5

Chapter 6

Finite State Machines


Chapter 7

Chapter 8

The state diagram of a sequential circuit is given as below.

- Tabulate the related state table.
- Reduce the state table to a minimum number of states using row matching.
- Draw the reduced state diagram.

Draw the reduced state diagram.

 

# State Reduction

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

Present state	<u>Next state</u>		<u>Output</u>	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

# State Reduction

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

Present state	<u>Next state</u>		<u>Output</u>	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$a$	$a$	$b$	0	0
$b$	$c$	$d$	0	0
$c$	$a$	$d$	0	0
$d$	$e$	$f$	0	1
$e$	$a$	$f$	0	1
$f$	$e$	$f$	0	1

# State Reduction

Chapter 5

Chapter 6

Finite State Machines

Chapter 7

Chapter 8

Present state	<u>Next state</u>		<u>Output</u>	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

Chapter 5

Chapter 6

**Finite State Machines**

Chapter 7

Chapter 8



Chapter 5

Chapter 6

**Chapter 7**

VHDL to Silicon Design Flow

Chapter 8

# Outline

1 Chapter 5

2 Chapter 6

**3 Chapter 7**

4 Chapter 8


# Testing of Logic Circuits

Chapter 11


Ref.1



# VLSI Development Flow

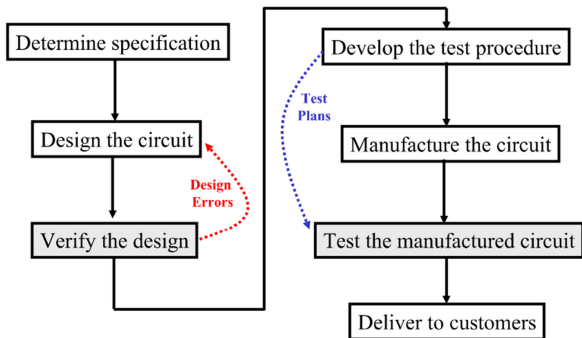

## Key Issues in Testing

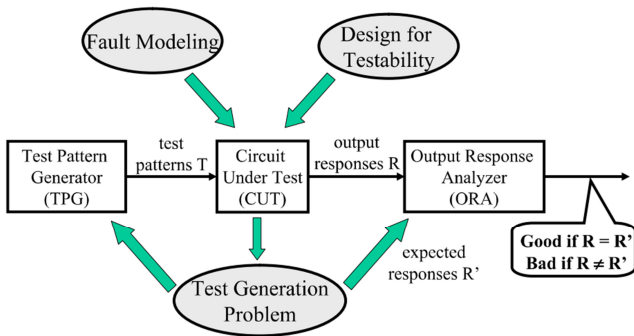

# Fault Models


- Stuck-at faults
- Bridging faults
- PLA faults
- Transistor stuck-on/open faults
- Delay faults
- Functional faults
- State transition faults
- Memory faults

## Complexity of a test

- Testing is done via applying a test patterns and comparing the O/P with the good O/P.
- A circuit with  $k$  inputs requires  $2^k$  test patterns, which is a huge task for large values of  $k$ .
- Fortunately, not all the  $2^k$  patterns must be used to cover an acceptable percentage of the probable faults in the circuit.
 
## Test Pattern Generation Combinational Circuits testing

- Fault Simulation
  - Determine the behavior of faulty circuit for all stuck-at fault wires.
  - Choose test patterns that cover faults



- Path sensitizing
  - deal with several wires that form a path as an entity that can be tested for several faults using a single test























 
## Fault Simulation

- There is only one pattern to detect b/1 .."001"



Test $w_1 w_2 w_3$	Fault detected									
	a/0	a/1	b/0	b/1	c/0	c/1	d/0	d/1	f/0	f/1
000		✓		↓				✓		✓
001		✓		↓				✓		✓
010		✓		↓		✓		✓		✓
011			✓	↓	✓		✓		✓	
100	✓			↓					✓	
101	✓			↓					✓	
110	✓			↓					✓	
111				↓					✓	















 
# Fault Simulation

- There is only one pattern to detect b/1 .."001"




Test $w_1 w_2 w_3$	Fault detected						
	$a/0$		$b/0$	$b/1$	$c/1$		
000							
001				↓	↓		
010			↓		↓		
011	↓		↓				
100	✓						
101	✓						
110	✓						
111							






## Path Sensitizing

 


- The circuit contains 4 paths :  $abcg$ ,  $dbcg$ ,  $ecg$ ,  $fg$
- The path is activated by ensuring that other paths in the circuit do not determine the value of the output  $g$ .
- To sensitize a path through an input of an AND or NAND gate, all other inputs must be set to 1. To sensitize a path through an input of an OR or NOR gate, all other inputs must be 0.

## Path Sensitizing

 

Path abcg			
w1	g	Faulty result will indicate	l/p
0	1	a/1, b/1, c/0, g/0	0101
1	0	a/0, b/0, c/1, g/1	1101


## Path Sensitizing

 

Path abcg			
w1	g	Faulty result will indicate	l/p
0	1	a/1, b/1, c/0, g/0	0101
1	0	a/0, b/0, c/1, g/1	1101

Path dbcg			
w2	g	Faulty result will indicate	l/p
0	1	d/1, b/1, c/0, g/0	1001
1	0	d/0, b/0, c/1, g/1	1101

# Path Sensitizing

 


Path abcg			
w1	g	Faulty result will indicate	l/p
0	1	a/1, b/1, c/0, g/0	0101
1	0	a/0, b/0, c/1, g/1	1101

Path dbcg			
w2	g	Faulty result will indicate	l/p
0	1	d/1, b/1, c/0, g/0	1001
1	0	d/0, b/0, c/1, g/1	1101

Path ecg			
w3	g	Faulty result will indicate	l/p
0	1	e/1, c/0, g/0	0101
1	0	e/0, c/1, g/1	0111

# Path Sensitizing

 


Path abcg			
w1	g	Faulty result will indicate	l/p
0	1	a/1, b/1, c/0, g/0	0101
1	0	a/0, b/0, c/1, g/1	1101

Path dbcg			
w2	g	Faulty result will indicate	l/p
0	1	d/1, b/1, c/0, g/0	1001
1	0	d/0, b/0, c/1, g/1	1101

Path ecg			
w3	g	Faulty result will indicate	l/p
0	1	e/1, c/0, g/0	0101
1	0	e/0, c/1, g/1	0111

Path fg			
w4	g	Faulty result will indicate	l/p
0	0	f/1, g/1	0100
1	1	f/0, g/0	0101

# Path Sensitizing

 


Path abcg			
w1	g	Faulty result will indicate	l/p
0	1	a/1, b/1, c/0, g/0	0101
1	0	a/0, b/0, c/1, g/1	1101

Path dbcg			
w2	g	Faulty result will indicate	l/p
0	1	d/1, b/1, c/0, g/0	1001
1	0	d/0, b/0, c/1, g/1	1101

Path ecg			
w3	g	Faulty result will indicate	l/p
0	1	e/1, c/0, g/0	0101
1	0	e/0, c/1, g/1	0111

Path fg			
w4	g	Faulty result will indicate	l/p
0	0	f/1, g/1	0100
1	1	f/0, g/0	0101

# Path Sensitizing

 

Test Pattern
0100
0101
0111
1001
1101

Path abcg			
w1	g	Faulty result will indicate	l/p
0	1	a/1, b/1, c/0, g/0	0101
1	0	a/0, b/0, c/1, g/1	1101


Path dbcg			
w2	g	Faulty result will indicate	l/p
0	1	d/1, b/1, c/0, g/0	1001
1	0	d/0, b/0, c/1, g/1	1101

Path ecg			
w3	g	Faulty result will indicate	l/p
0	1	e/1, c/0, g/0	0101
1	0	e/0, c/1, g/1	0111

Path fg			
w4	g	Faulty result will indicate	l/p
0	0	f/1, g/1	0100
1	1	f/0, g/0	0101
 
## Testing of Sequential Circuits

- A combinational circuit can be tested by comparing its behavior with the functionality specified in the **truth table**. An equivalent attempt would be to test a sequential circuit by comparing its behavior with the functionality specified in the **state table**.
- Represent the circuit by a state diagram.
- Verify each transition by first taking the machine to a specific state, applying the input to perform the transition and verify the output and the final state.






# Design for Testability
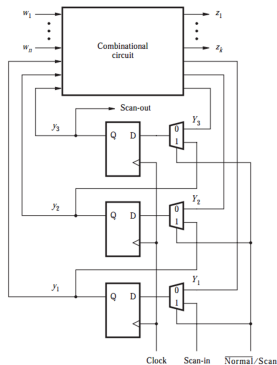
## Scan-Path Technique


- The operation of the flip-flops is tested by scanning into them a pattern of 0s and 1s, for example, 01011001, in consecutive clock cycles, and observing whether the same pattern is scanned out.

- The combinational circuit is tested by applying test vectors on  $w_1w_2 \cdots w_ny_1y_2y_3$  and observing the values generated on  $z_1z_2 \cdots z_mY_1Y_2Y_3$ .



# Design for Testability


## Scan-Path Technique

 

- The  $y_1 y_2 y_3$  portion of the test vector is scanned into the flip-flops during three clock cycles, using  $\overline{Normal}/Scan = 1$ .
- The  $w_1 w_2 \dots w_n$  portion of the test vector is applied as usual and the normal operation of the sequential circuit is performed for one clock cycle, by setting  $\overline{Normal}/Scan = 0$ . The outputs  $z_1 z_2 \dots z_m$  are observed. The generated values of  $Y_1 Y_2 Y_3$  are loaded into the flip-flops at this time.
- The select input is changed to  $\overline{Normal}/Scan = 1$ , and the contents of the flip-flops are scanned out during the next three clock cycles, which makes the


# Testing of Sequential Circuits

## Random Testing

 


# Testing of Sequential Circuits

## Random Testing

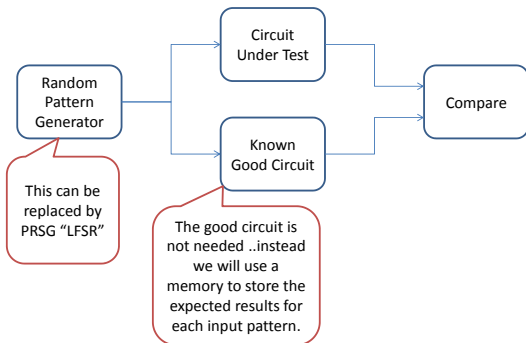


# Testing of Sequential Circuits

## Random Testing

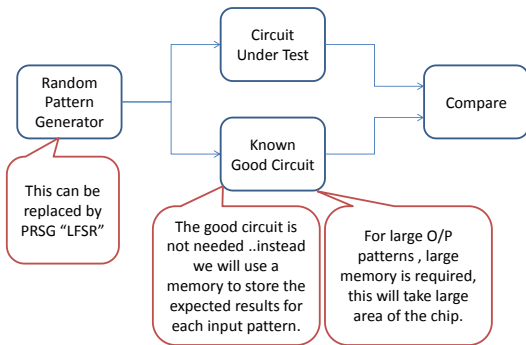


# Testing of Sequential Circuits

## Random Testing

 

# Testing of Sequential Circuits

## Random Testing

 

### Transition count testing

- Count the number of transitions (between 0,1) of the o/p pattern for each i/p pattern
- store the number of transitions only
- For example “0010011101110” contains 6 transitions which can be stored as “110”
- This will save a lot of memory

Chapter 5

Chapter 6

Chapter 7

**VHDL to Silicon Design Flow**

Chapter 8

