

# Memory Interface

Dr. M. Shiple


Microprocessor Architecture, 2019

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

فِي الْحَقِّ وَالْبَاطِلِ



# Introduction to decoders
 
## 1-OF-8 Decoder/Demultiplexer (74ls138)





Inputs						Output							
Enable			Select			0	1	2	3	4	5		
G2A	G2B	G1	C	B	A	0	1	2	3	4	5		
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0

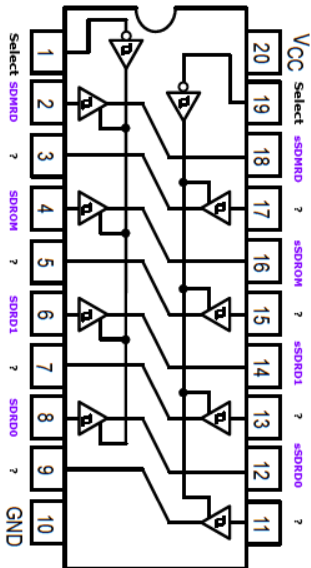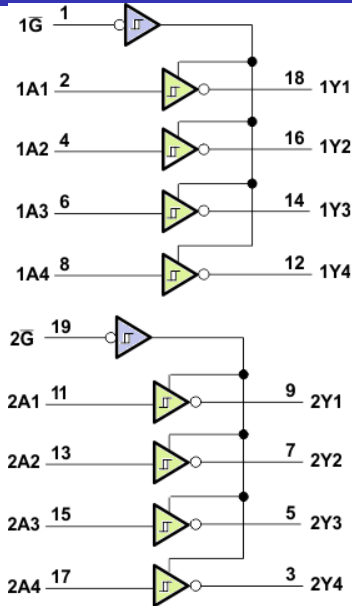
## Octal 3-STATE Buffer/Line Driver/Line Receiver (74ls244)


 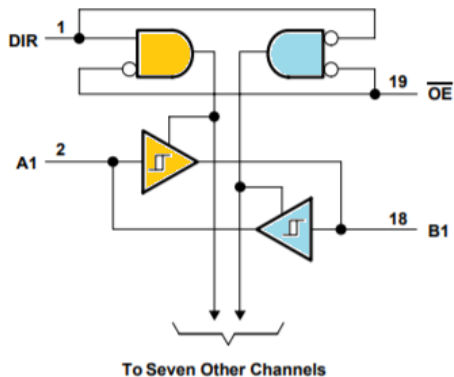
## 3-STATE Octal Bus Transceiver (74ls245)





# General 8085 Scheme

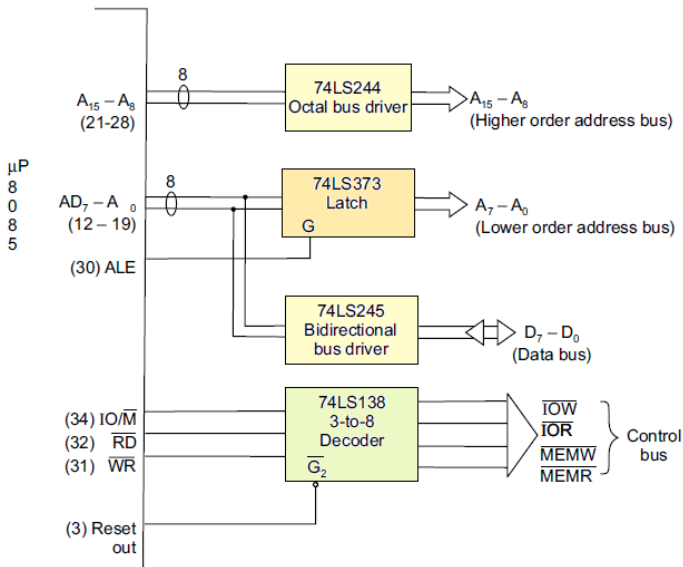
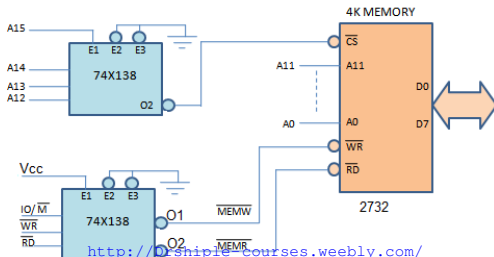 
## Memory interface

- 2K RAM : 11 address bus : A0 to A10
- 4K ROM : 12 address bus : A0 to A11







# ROM/RAM Chips

CMOS Static RAM (2K x 8-Bit)  
 NMOS 32K (4K x 8) UV EPROM

## Pin Configurations

 

## Pin Configurations

 

## Pin Description

Name	Description
A0 - A10	Address Inputs
I/O0 - I/O7	Data Input/Output
CS	Chip Select
WE	Write Enable
OE	Output Enable
Vcc	Power
GND	Ground

## Pin Description

A0 - A11	Address Inputs
Q0 - Q7	Data Outputs
E	Chip Enable
GVpp	Output Enable / Program Supply
Vcc	Supply Voltage
Vss	Ground


# ROM/RAM Chips

## RAM Memory

#	Chip No.	Size
1	2114	1k × 4bits
2	6116	2k × 8bits
3	6264	8k × 8bits

## ROM Memory


#	Chip No.	Size
1	2708	1k × 8bits
2	2716	2k × 8bits
3	2732	4k × 8bits
4	2764	8k × 8bits
5	27128	16k × 8bits
6	27256	32k × 8bits

 

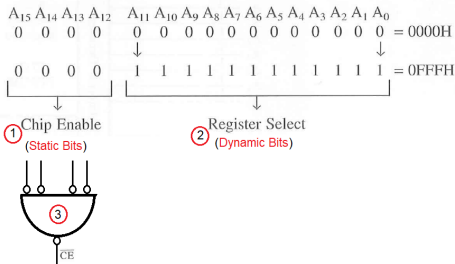
## Exercise 1

Design the decoder circuit for ROM memory its address range is 0000 to FFFF?

- 1 Determine static bits Most significant 4 bits.
- 2 Determine dynamic bits: exclude.
- 3 Design according to static bits.




## Exercise 1: 138 decoder solution

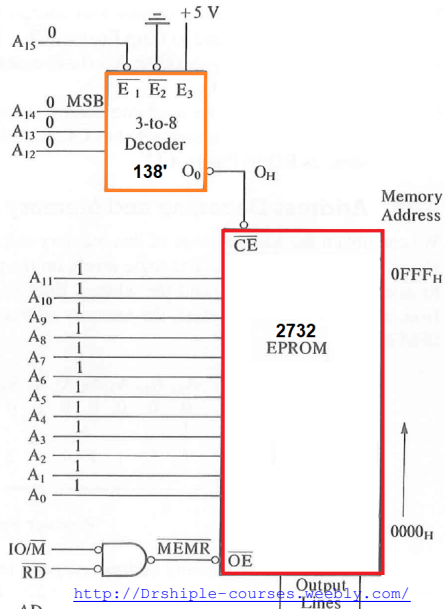

 
## Exercise 2

Design the decoder circuit for ROM memory its address range is 8800 to 8FFF?

- 1 Determine static bits Most significant 4 bits.
- 2 Determine dynamic bits: exclude.
- 3 Design according to static bits.



## Exercise 2: 138 decoder solution

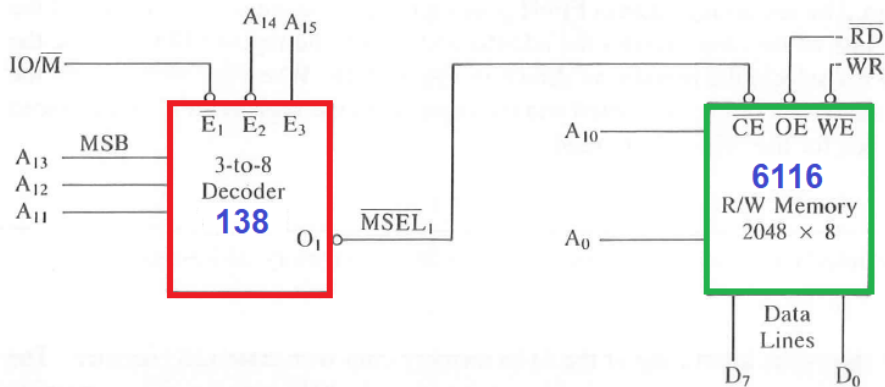


## Exercise 2

Design the decoder circuit for ROM memory its address range is 8800 to 8FFF? Solution:

- 1 Subtract range to find memory size=7FF
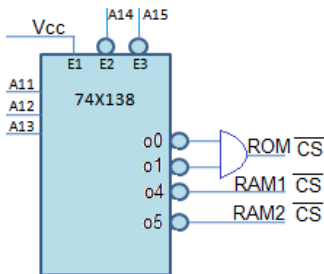
## Exercise 2


- 1 Determine static bits:  
ROM vs. RAM  $\Rightarrow$  Most significant 4 bits.  
bit no: 13 discriminate
- 2 Determine static bits:  
RAM vs. RAM  $\Rightarrow$  Most significant 5 bits.  
bit no: 11 discriminate



```
0000 0000 0000 0000
0000 1111 1111 1111
```

```
0010 0000 0000 0000
0010 0111 1111 1111
```
 
```
0010 1000 0000 0000
0010 1111 1111 1111
```





## Exercise 3

Design an interfacing circuit for memory to meet the following specifications:

- 1 2764 (8k x 8bit): EPROM address range starts from 0000h and additional 4K memory should be available for future use.
- 2 6116 (2k x 8bit): CMOS R/W memory.

## Exercise 3

2764 (4k x 8bit):

- 1 Size = 8K = 111 1111 1111 11 = FFF

- 2 End address = 1FFF + 0000 = 1FFF

2732 (4k x 8bit)  
reserved:

- 1 Size = 4K = 11 1111 1111 11 = FFF

- 2 Start address = 1FFF + 1 = 2000

- 3 End address = FFF + 2000 = 2FFF .


6116 (2k x 8bit)

- 1 Size = 4K = 1 1111 1111 11 = 7FF

- 2 Start address = 2FFF + 1 = 3000

- 3 End address = 7FF + 3000 = 37FF .


## Exercise 3

 

it is safe to discriminate according to A<sub>15</sub> , A<sub>14</sub> , A<sub>13</sub>

So EPROM=000      RAM= 001


## Exercise 3

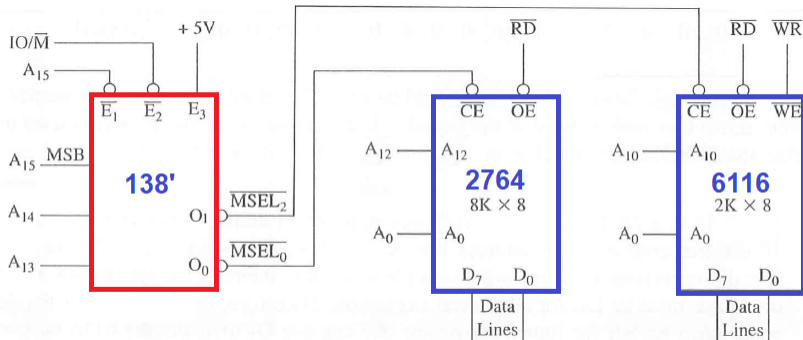

it is safe to discriminate according to  $A_{15}$ ,  $A_{14}$ ,  $A_{13}$   
 So EPROM=000      RAM= 001

 
## Exercise 4

Design the decoder circuit for shown memory structure?


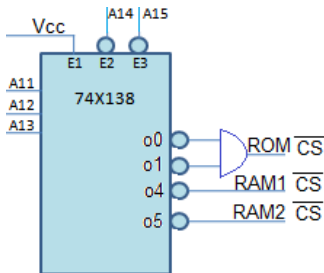
## Exercise 4


- 1 Determine static bits:  
ROM vs. RAM  $\Rightarrow$  Most significant 4 bits.  
bit no: 13 discriminate
- 2 Determine static bits:  
RAM vs. RAM  $\Rightarrow$  Most significant 5 bits.  
bit no: 11 discriminate



```
0000 0000 0000 0000
0000 1111 1111 1111
```

```
0010 0000 0000 0000
0010 0111 1111 1111
```
 
```
0010 1000 0000 0000
0010 1111 1111 1111
```



## Exercise 4

Draw the memory map of next system

