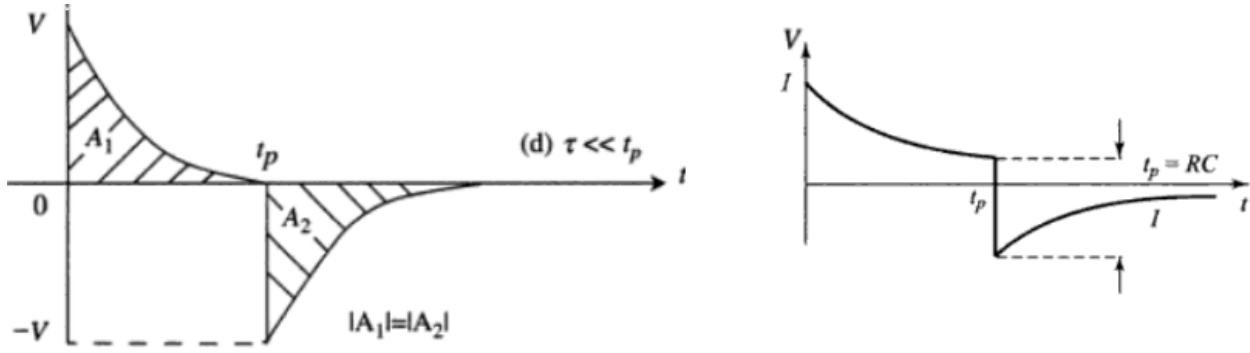




ANSWER THE FOLLOWING QUESTIONS:

1. Prove the DC level pulse response of v_o of the RC HPF is zero. In other words, the area above the reference (A1) equals the area under the reference (A2) as shown in the next figure [10 marks] [D_c]



Solution: For area A1:

$$v_o = V e^{-\frac{t}{\tau}} \Rightarrow A1 = \int_0^{t_p} V e^{-\frac{t}{\tau}} dt = V \int_0^{t_p} e^{-\frac{t}{\tau}} dt$$

$$\text{assume } : u = -\frac{t}{\tau} \Rightarrow du = -\frac{1}{\tau} dt \Rightarrow dt = -\tau du$$


$$A1 = -V\tau \int_0^{t_p} e^u du = -V\tau e^u \Big|_0^{t_p} = -V\tau e^{-\frac{t}{\tau}} \Big|_0^{t_p} = -V\tau \left[e^{-\frac{t_p}{\tau}} - 1 \right]$$

$$A2 = V \left(e^{-\frac{t_p}{\tau}} - 1 \right) \int_{t_p}^{\infty} e^{-\frac{t-t_p}{\tau}} = V \left(e^{-\frac{t_p}{\tau}} - 1 \right) \left[-\tau e^{-\frac{\infty-t_p}{\tau}} + \tau e^{-\frac{t_p-t_p}{\tau}} \right]$$

$$= V\tau \left(e^{-\frac{t_p}{\tau}} - 1 \right)$$

$$\therefore |A1| = |A2|$$

2. The input to a high-pass RC circuit in next figure is periodic and trapezoidal as indicated in next figure. Given that $T_1 = 1ms$ and $T_2 = 1.5ms$ and $\tau = 10ms$, find and sketch the steady-state output..

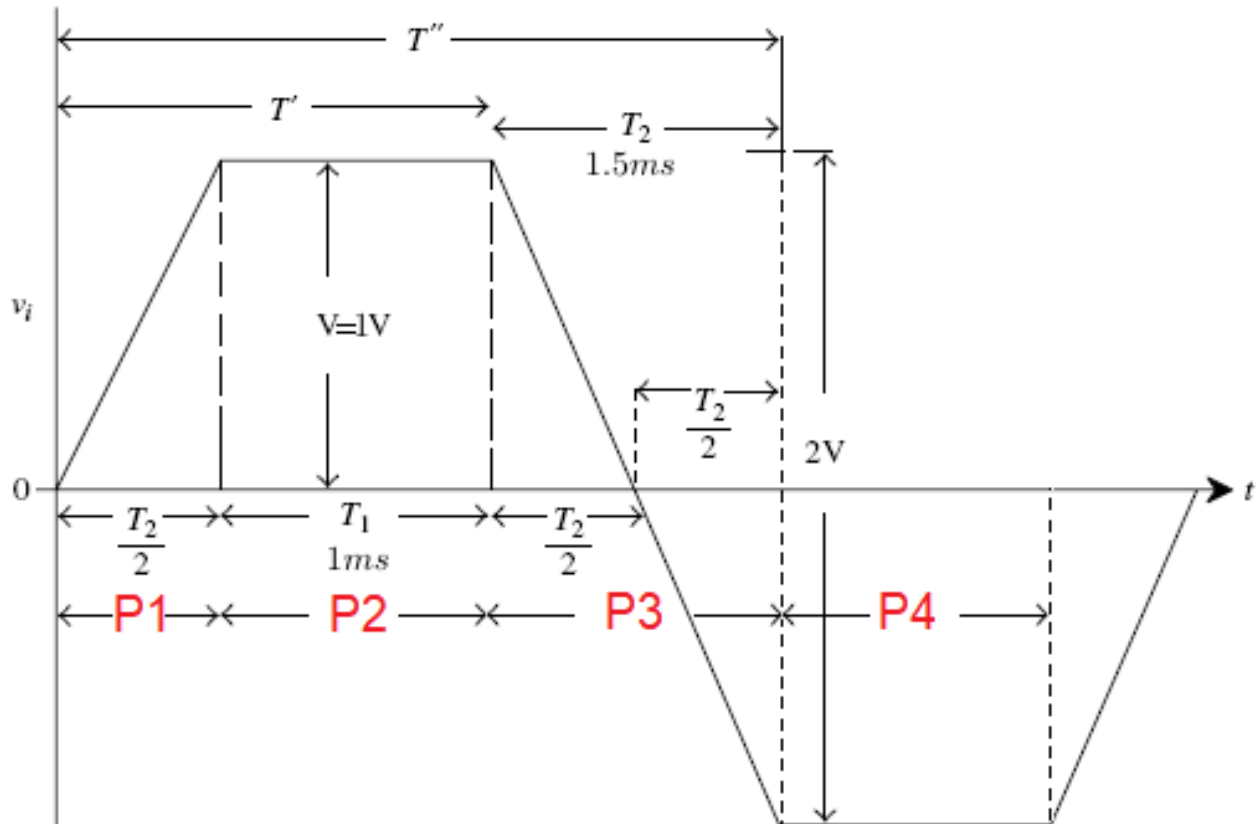[10 marks] [D_c]**Solution:**

The expected output is shown in the next figure:-

=====


For period (P1):- (ramp section)

$$\tau = 10ms > 0.75m \quad \therefore RC \gg T \Rightarrow v_o(t) = \alpha t \left(1 - \frac{t}{2(RC)}\right)$$

$$v_o(t) = \alpha \tau \left(1 - \frac{t}{2(RC)}\right) = \frac{2V}{T_2} t \left(1 - \frac{t}{20m}\right)$$

output follows input

$$v_o(t)|_{T=\frac{T_2}{2}} = \frac{2V}{T_2} \frac{T_2}{2} \left(1 - \frac{T_2}{40}\right) \approx 1 = V_1$$

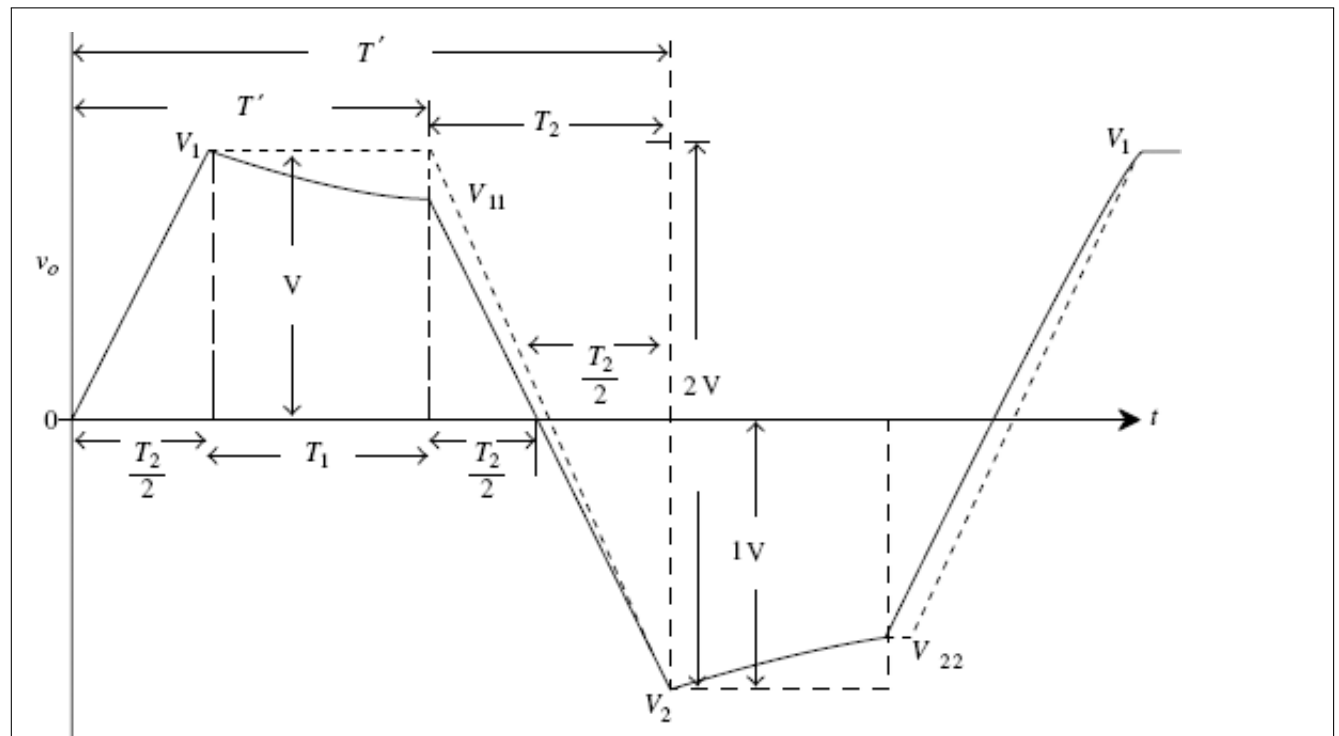

=====
 For period (P2):- (Constant section)

$$v_o(t) = Ve^{-\frac{t}{\tau}} = V_1e^{-100t}$$

$$V_{11} = v_o(t)|_{t=T_1} = V_1e^{-100 \times 1m} = 0.905V$$

=====
 For period (P3):- (Inverse Ramp section)

$$\tau = 10ms > 1.5m \quad \therefore RC \gg T \Rightarrow v_o(t) = at(1 - \frac{t}{2(RC)})$$

$$v_o(t) = V_{11} - \left[at(1 - \frac{t}{2(RC)}) \right] = V_{11} - \left[\frac{-2V}{T_2} T_2 (1 - \frac{T_2}{20m}) \right] = 0.905 - 1.85V \quad \text{output follows input}$$


$$V_2 = -0.945V$$

=====
 For period (P2):- (Constant section)

$$v_o(t) = Ve^{-\frac{t}{\tau}} = V_2e^{-100t}$$

$$V_{22} = v_o(t)|_{t=T_1} = V_2e^{-100 \times 1m} = -0.855V$$

3. The input signal shown in next figure is applied to a RC high-pass circuit, whose time constant is 0.4 ms. Draw the output waveform and mark all voltages, assuming that the capacitor is initially uncharged. [10 marks] [D_c]

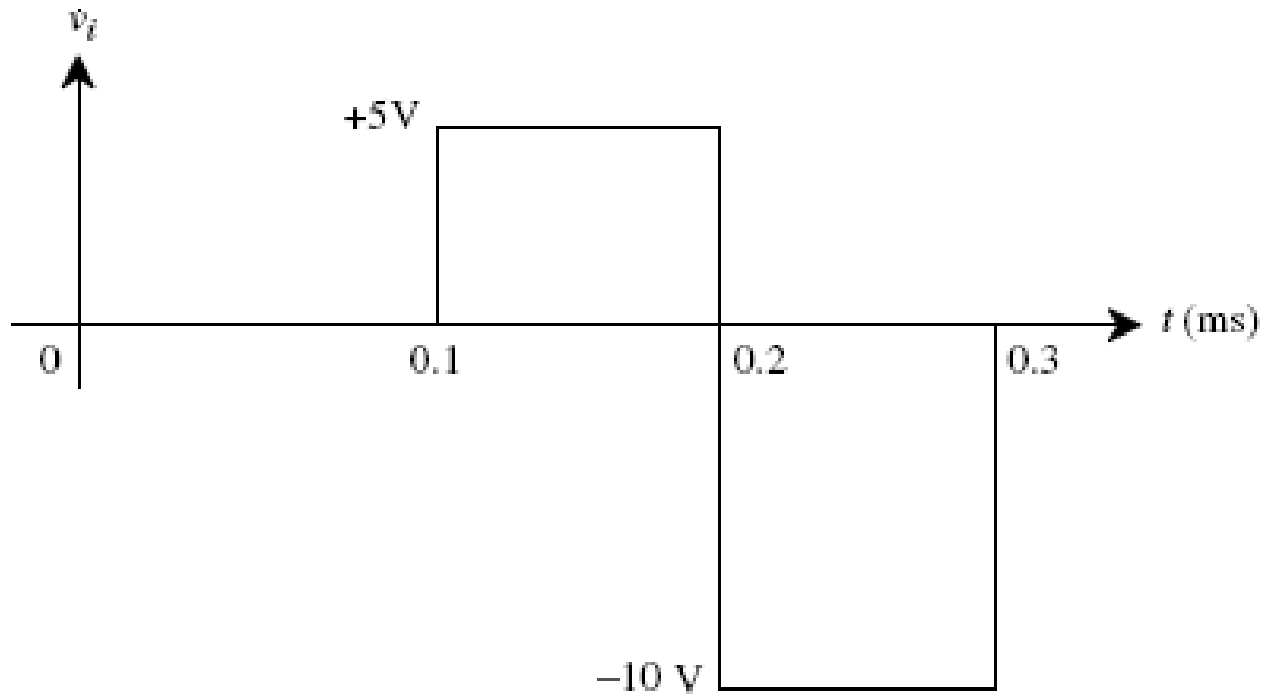
**Solution:**

The expected output is shown in the next figure:-





=====
 For period (P1):- (0.1 to 0.2 ms)


$$v_o(t) = V e^{\frac{-t}{RC}} = 5e^{\frac{-t}{0.4m}}$$

$$v_o(t)|_{T=0.2} = 5e^{\frac{-0.1m}{0.4m}} = 3.89V$$

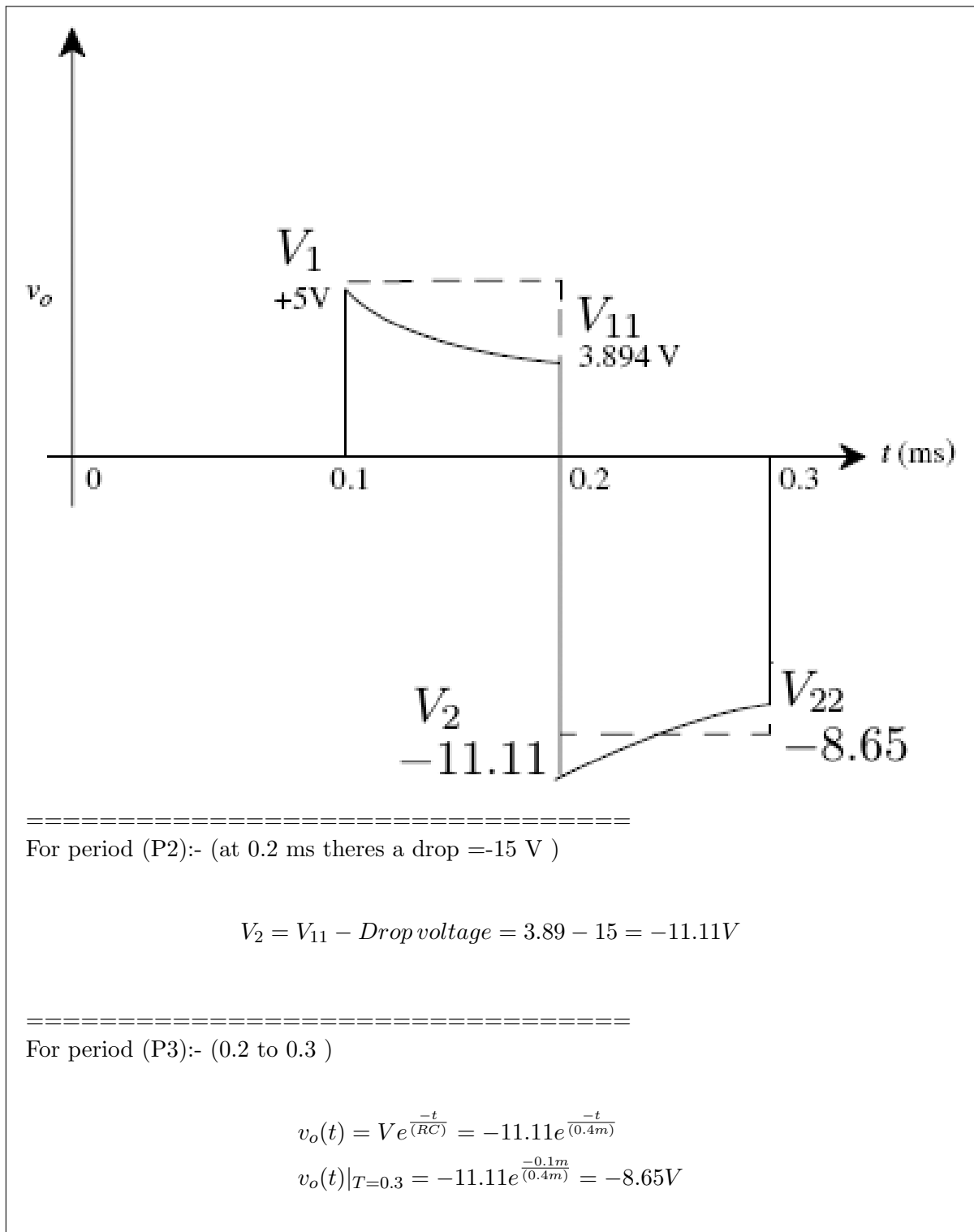

Response of RC High Pass Filter

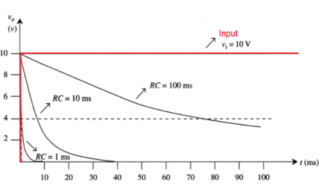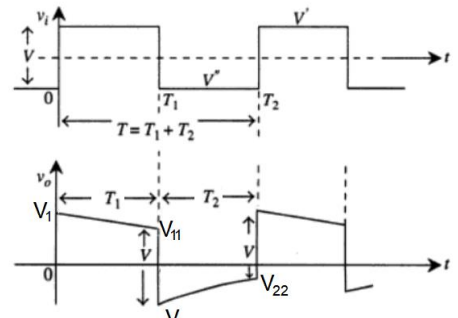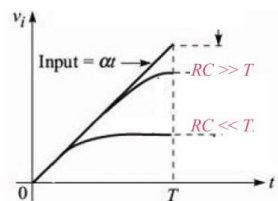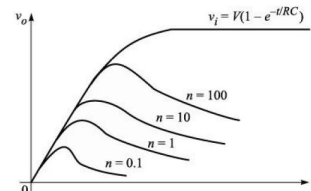	Step	Pulse	Square	Ramp	Exponential
Output signal					
V_o	$V e^{-\frac{t}{\tau}}$	$V_o = \begin{cases} V e^{-\frac{t}{\tau}} & 0 < t < t_p \\ V \left(e^{-\frac{t_p}{\tau}} - 1 \right) e^{-\frac{t-t_p}{\tau}} & t > t_p \end{cases}$ $V_2 = V_{11} - V$		$T_1 = T_2$ $V_1 = -V_2$ $V_{11} = -V_{22}$ $V_1 = \frac{V}{(1 + e^{-\frac{T}{2\tau}})}$	$\begin{cases} RC \approx T & \alpha RC (1 - e^{-\frac{t}{RC}}) \\ RC \ll T & \alpha RC \\ RC \gg T & \alpha t (1 - \frac{t}{2RC}) \end{cases}$ $\begin{cases} \tau \neq \tau_e, & \frac{V}{(\frac{\tau_e}{\tau} - 1)} \left[e^{-\frac{t}{\tau_e}} - e^{-\frac{t}{\tau}} \right] \\ \tau \gg \tau_e, & \frac{-V}{(\frac{\tau_e}{\tau} - 1)} \left[e^{-\frac{t}{\tau}} \right] \\ \tau = \tau_e, & \frac{V/\tau_e}{(s + \frac{1}{\tau_e})^2} = \frac{V}{\tau_e} t e^{-\frac{t}{\tau_e}} \end{cases}$

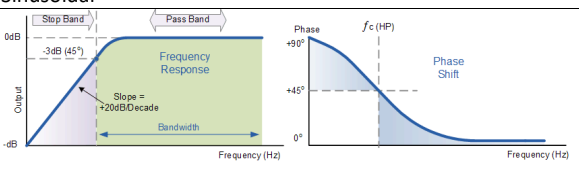	Sinusoidal
Output signal	
V_o	$ T(S) = \frac{\omega}{\omega_c} \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$ $\theta(\omega) = 90 - \tan^{-1}\left(\frac{\omega}{\omega_c}\right)$