

# **Linear Wave Shaping (High Pass Filter)**

Dr. M. Shipley

Wave Shaping Circuits (EET 232), 2020

# Outline

- 1 Sinusoidal wave
- 2 Step Signal
- 3 Pulse Signal
- 4 Square Signal
- 5 Ramp Signal
- 6 Exponential Input
- 7 Differentiator

## Section 1

# **Sinusoidal wave**

## High Pass filter

By using voltage divider:


$$V_o = V_i \frac{R}{R + \frac{1}{SC}} \times SC$$

$$\frac{V_o}{V_i} = \frac{SRc}{1 + SRc} = \frac{j\omega R c}{1 + j\omega R c}$$

To find cut off frequency, the input signal loses half power or  $\frac{1}{\sqrt{2}}$  voltages

$$|T(S)| = \frac{\omega R c}{\sqrt{(1)^2 + (\omega R c)^2}} = \frac{1}{\sqrt{2}}$$


$$\omega_c = \frac{1}{R c}$$

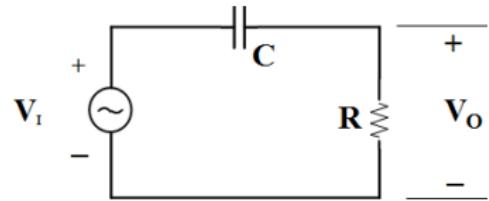


$$|T(S)| = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$$

To find the phase of TF:


$$\begin{aligned} \theta(\omega) &= \tan^{-1}\left(\frac{\omega R c}{0}\right) - \tan^{-1}\left(\frac{\omega R c}{1}\right) \\ &= 90 - \tan^{-1}\left(\frac{\omega}{\omega_c}\right) \end{aligned}$$

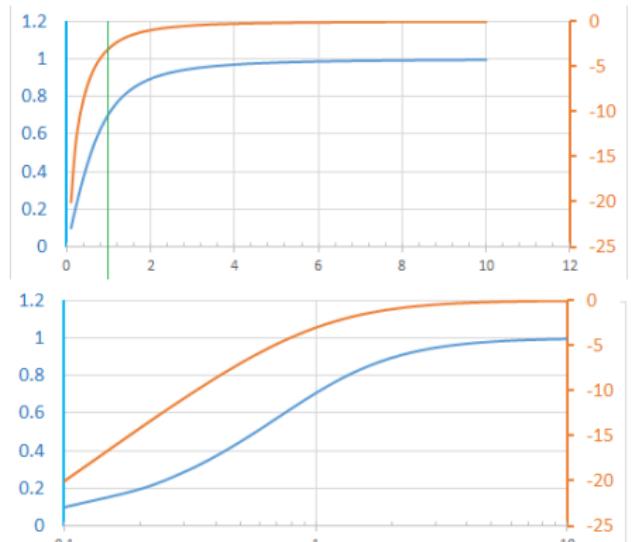$< \theta(\omega)$ 

## Phase

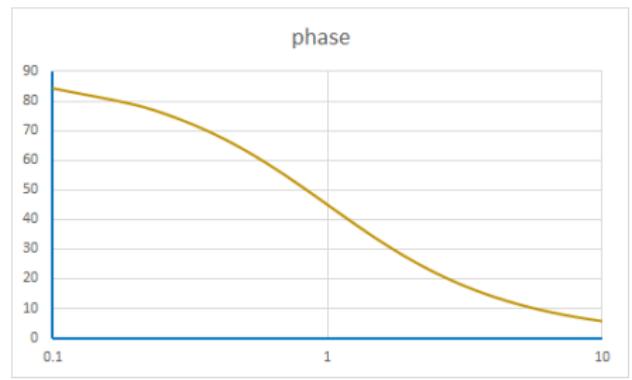

# Bode Plot

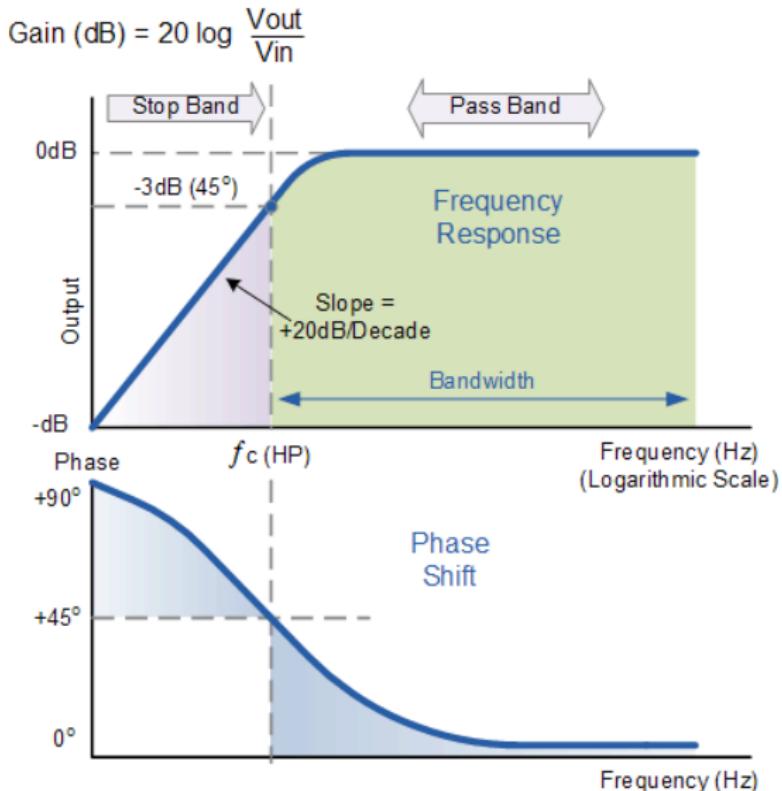

## Section 2

### **Step Signal**

## Back to basic concepts


$$\begin{aligned} v_i &= \frac{1}{C} \int idt + v_o \\ &= \frac{1}{C} \int \frac{v_o}{R} dt + v_o = \frac{1}{RC} \int v_o dt + v_o \end{aligned}$$

Laplace transform : (input = unit step)

$$\frac{V}{s} = \frac{1}{RC} \frac{v_o(s)}{s} + v_o(s)$$


$$v_o(s) = V \left( \frac{1}{s(\frac{1}{RCs} + 1)} \right) = V \left( \frac{1}{\frac{1}{RC} + s} \right)$$

$$v_o(t) = Ve^{-\frac{t}{\tau}}$$

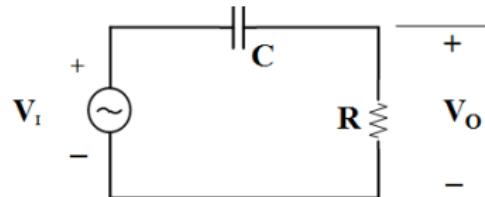

	$f(t)$	$F(s)$
1.	Unit impulse $\delta(t)$	1
2.	Unit step $1(t)$	$\frac{1}{s}$
3.	$t$	$\frac{1}{s^2}$
4.	$e^{-at}$	$\frac{1}{s+a}$
5.	$te^{-at}$	$\frac{1}{(s+a)^2}$

## Step response

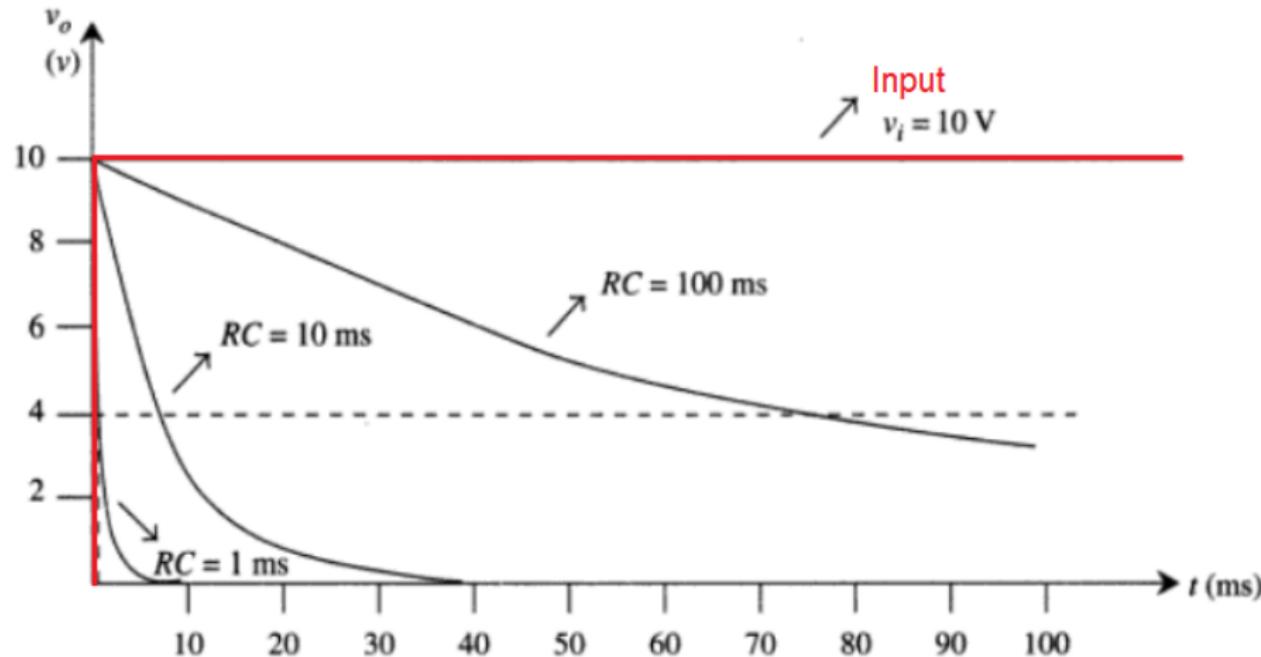


Step response for different  $\tau = RC$

## Section 3



# Pulse Signal

# Pulse response

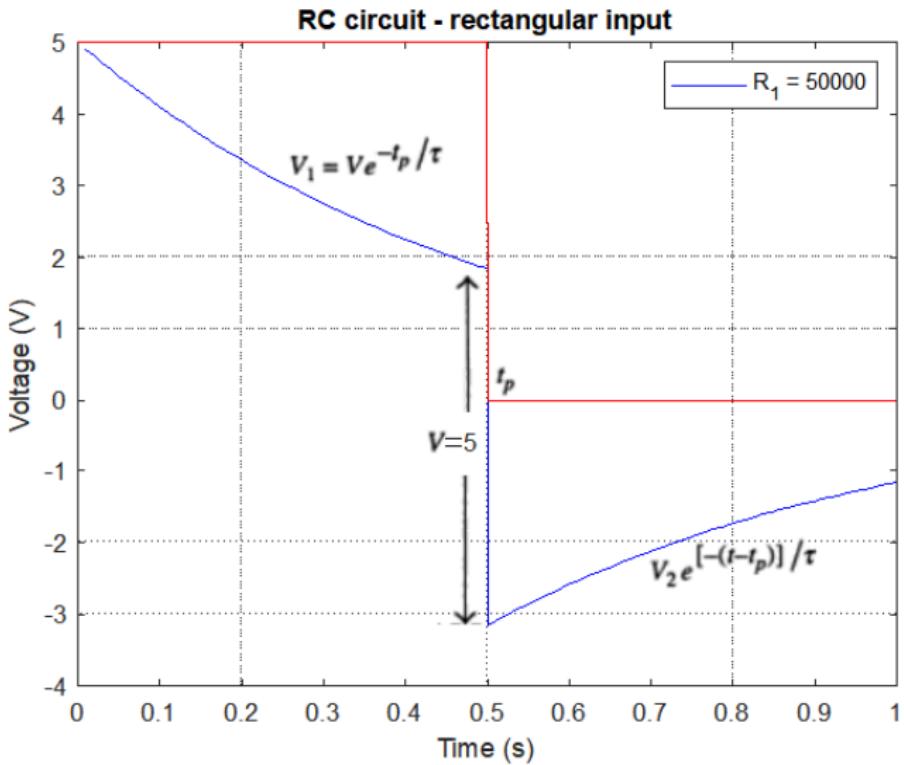
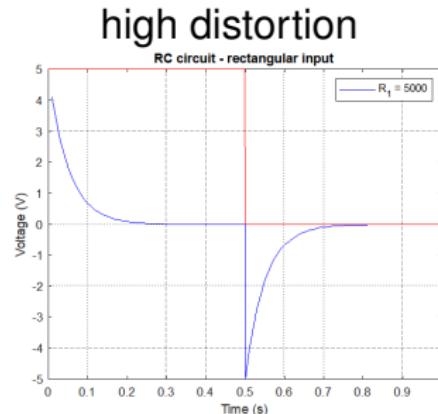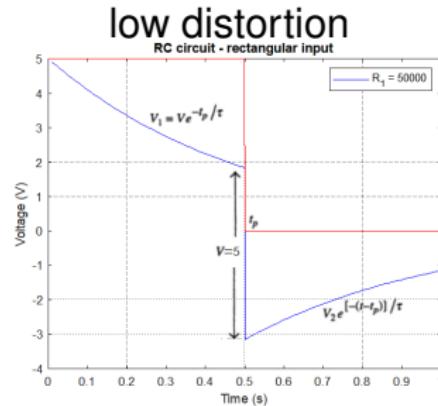
## Pulse response features

- Distortion ratio  $\alpha^{-1}$  time constant  $\tau$ .
- The output comprises a positive spike at beginning of the input pulse and negative at the end.
- $v_o = \begin{cases} Ve^{-\frac{t}{\tau}} & 0 < t < t_p \\ V \left( e^{-\frac{t_p}{\tau}} - 1 \right) e^{-\frac{t-t_p}{\tau}} & t > t_p \end{cases}$




## Pulse response: Example 1

A Pulse of 10V and duration  $10\mu S$  is applied to HPF. Sketch the output for  $RC = 0.5t_p$ .

$$v_o(t) = V e^{-\frac{t}{0.5t_p}} = 10e^{-2} = 1.35V = V_1$$

$$V_2 = V_1 - V = 1.35 - 10 = -8.65V$$


$$v_o = -8.65e^{-\frac{t}{0.5t_p}}$$

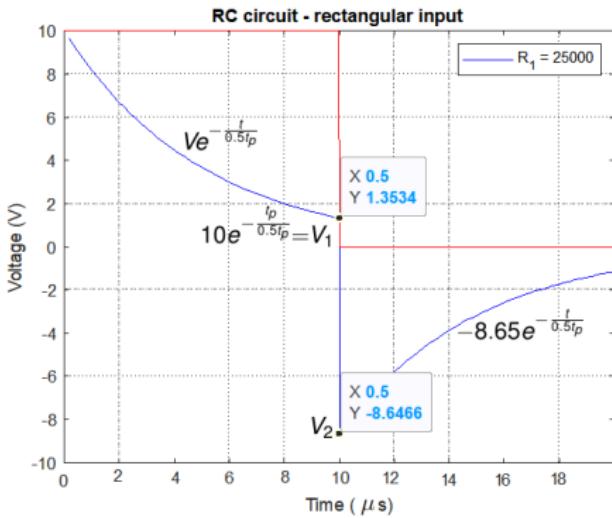

## Section 4

# **Square Signal**

## Square Response

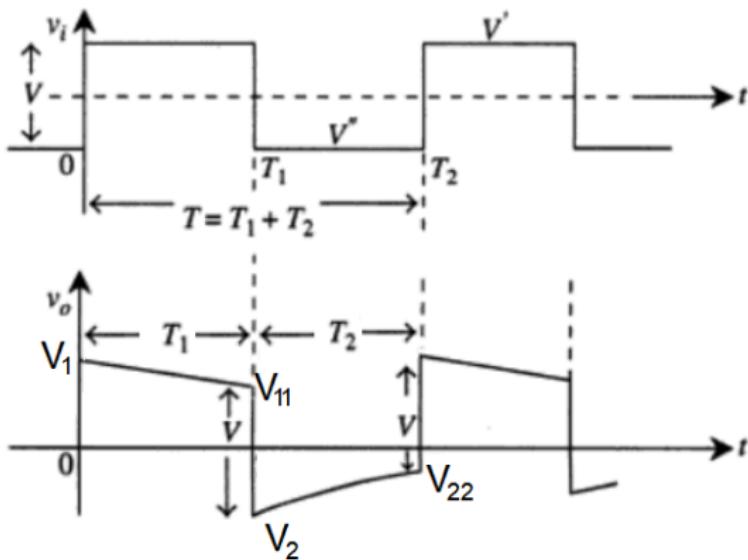

- 1 Symmetric square,  $T_1 = T_2$  .
- 2 As the capacitor blocks the DC, the DC component in the output is zero.

## Square Response

For any square wave:

$$V_{11} = V_1 e^{-\frac{T_1}{\tau}}$$

$$V_2 = V_{11} - V \quad V_{22} = V_2 e^{-\frac{T_2}{\tau}}$$


For symmetric square wave:

- $T_1 = T_2$ .
- $V_1 = -V_2$
- $V_{11} = -V_{22}$

$$V_2 = V_{11} - V \Rightarrow V_2 = V_1 e^{-\frac{T_1}{\tau}} - V$$

$$\therefore V_1 = -V_2 \Rightarrow V_1 = -V_1 e^{-\frac{T_1}{\tau}} + V$$
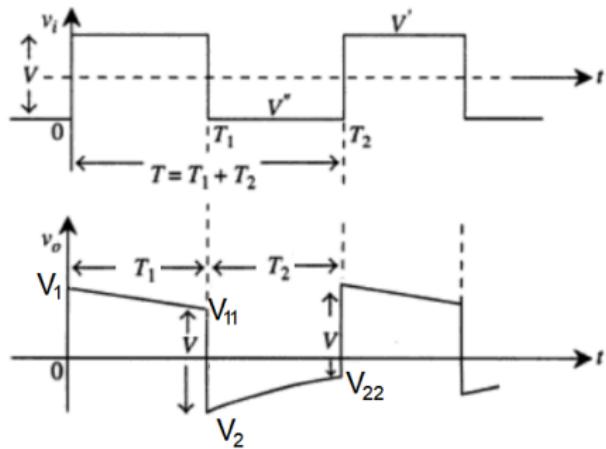
$$V_1 = \frac{V}{(1 + e^{-\frac{T_1}{\tau}})} = \frac{V}{(1 + e^{-\frac{T}{2\tau}})}$$




# Square Response

$$V_{11} = V_1 e^{-\frac{T_1}{\tau}}$$

$$V_2 = V_{11} - V \quad V_{22} = V_2 e^{-\frac{T_2}{\tau}}$$
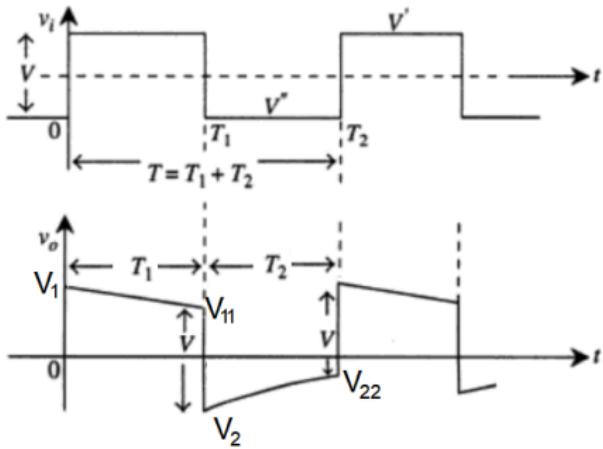
$$V_1 = \frac{V}{(1 + e^{-\frac{T}{2\tau}})}$$



## Square Response: Example 1

A 10 Hz square wave whose peak-to-peak amplitude is 2 V is fed to an amplifier. Calculate and plot the output waveform if the lower 3-dB frequency is 0.3 Hz.

**Solution:**


$$T = \frac{1}{f} = \frac{1}{10} = 0.1\text{s}$$

$$\omega_o = \frac{1}{RC} \Rightarrow RC = \frac{1}{\omega_o} = \frac{1}{2\pi 0.3}$$

$$\tau = RC = 0.53\text{s}$$

$$V_1 = \frac{V}{(1 + e^{-\frac{T}{2\tau}})} = 1.046V$$
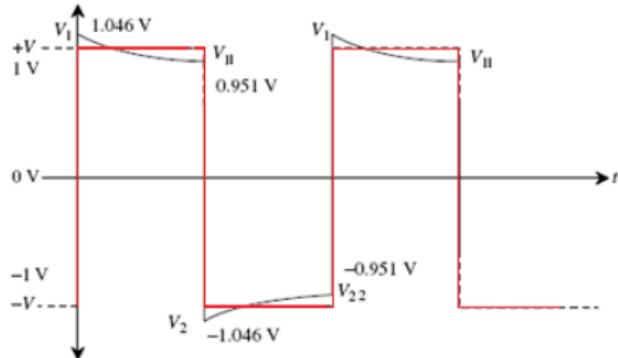
$$V_{11} = V_1 e^{-\frac{T}{2\tau}} = 1.046 e^{-\frac{0.1}{2 \times 0.53}} = 0.951V$$



$$V_2 = -V_1 = -1.046V$$

$$V_{22} = -V_{11} - 0.951V$$

## Square Response: Example 2

Given :  $T_1 = 0.2\text{s}$ ,  $T_2 = \tau = 0.4\text{s}$   
 calculate minimum and maximum values of the output waveform?

**Solution:**

$$V_{11} = V_1 e^{-\frac{T}{\tau}} = V_1 e^{-\frac{0.2}{0.4}} = 0.606 V_1$$

$$V_{22} = V_2 e^{-\frac{T}{\tau}} = V_2 e^{-\frac{0.4}{0.4}} = 0.367 V_2$$

$$\therefore V_{11} - V_2 = 2 \quad , \quad V_1 - V_{22} = 2$$

$$0.606 V_1 - V_2 = 2 \quad (1)$$


$$V_1 - 0.367 V_2 = 2 \quad (2)$$

By solving (1) and (2)

$$V_1 = 1.628 V, V_2 = -1.016 V$$

and

$$V_{11} = 0.986 V, V_{22} = -0.372 V$$

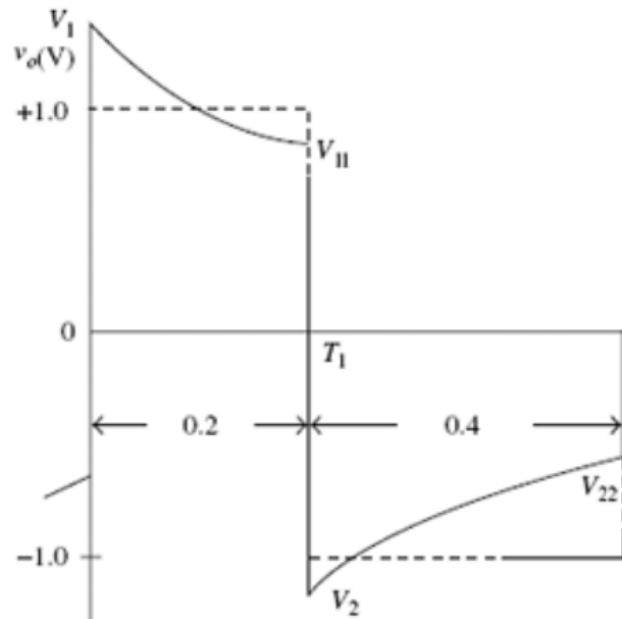

## Section 5

# **Ramp Signal**

## Back to basic concepts

$$v_i = \alpha t = \frac{\alpha}{S^2}$$

$$V_o = v_i \frac{SRC}{1 + SRC} = \frac{\alpha}{S} \frac{RC}{(1 + SRC)}$$


$$= \frac{? \alpha RC}{S} + \frac{?}{(1 + SRC)}$$

$$= \frac{\alpha RC}{S} + \frac{-\alpha(RC)^2}{(1 + SRC)}$$

last argument should be formed as table

$$= \left[ \frac{\alpha RC}{S} - \frac{\alpha(RC)}{\left(\frac{1}{RC} + S\right)} \right]$$
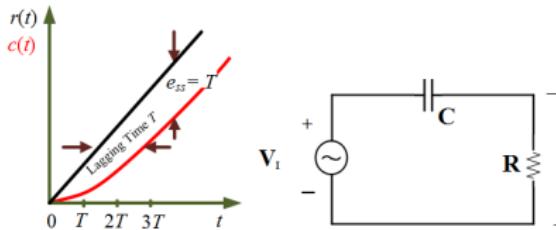
$$= \alpha RC - \alpha(RC)e^{-\frac{t}{RC}}$$



	$f(t)$	$F(s)$
1.	Unit impulse $\delta(t)$	1
2.	Unit step $1(t)$	$\frac{1}{s}$
3.	$t$	$\frac{1}{s^2}$
4.	$e^{-at}$	$\frac{1}{s+a}$
5.	$te^{-at}$	$\frac{1}{(s+a)^2}$

## Back to basic concepts

$$V_o = \alpha RC - \alpha(RC)e^{-\frac{t}{RC}} = \alpha RC(1 - e^{-\frac{t}{RC}})$$

$RC \ll T$ :

$$\begin{aligned} &= \alpha RC - \alpha(RC)e^{-\frac{t}{RC}} \\ &= \alpha RC \end{aligned}$$

$(T/RC) \approx 0$



Recall:  $e^x = 1 + \frac{x}{1!} + \frac{x^2}{2!} + \dots$

$$\begin{aligned} &= \alpha RC - \alpha(RC)e^{-\frac{t}{RC}} \\ &= \alpha RC - \alpha(RC)[1 - \frac{t}{RC} + \frac{t^2}{(RC)^2}] \\ &= \alpha RC - \alpha(RC) + t\alpha - \alpha \frac{t^2}{2(RC)} \\ &= \alpha t \left(1 - \frac{t}{2(RC)}\right) \end{aligned}$$

## Transmission error

$$e_t = \frac{v_i - v_o}{v_i} = \frac{\alpha t - \alpha t \left(1 - \frac{t}{2RC}\right)}{\alpha t} \Bigg|_{t=T} = \pi f_c T$$

where

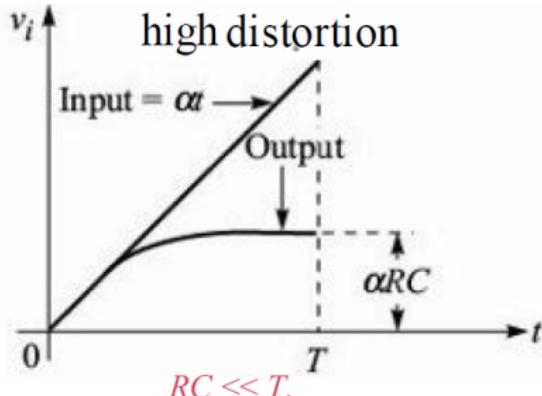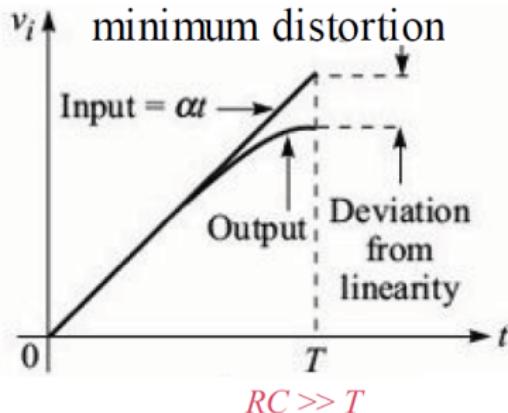

## Ramp Response Summary

$$V_o(t) = \begin{cases} \alpha RC(1 - e^{-\frac{t}{RC}}) & RC \ll T \\ \alpha RC & (T/RC) \approx 0 \\ \alpha t(1 - \frac{t}{2(RC)}) & \end{cases}$$

## Ramp Response: Example 1

A ramp is applied to an RC differentiator, as shown . Draw to scale the output waveform for the following cases: (i)  $T = RC$ , (ii)  $T = 0.5RC$ , (iii)  $T = 10RC$ .

$$(i) RC = T \quad \alpha RC(1 - e^{-\frac{t}{RC}}):$$

$$V_o(t) = \frac{V}{T} RC(1 - e^{-\frac{t}{RC}}) =$$

$$V(1 - e^{-1}) = 0.632V$$


---

$$(ii) RC \ll T \quad \alpha RC$$


$$V_o(t) = 2V$$


---

$$(iii) RC \gg T \quad \alpha RC(1 - e^{-\frac{t}{RC}})$$

$$V(0.1)(1 - e^{-10})$$




$$@ t=T \Rightarrow v(t) = 0.1V$$

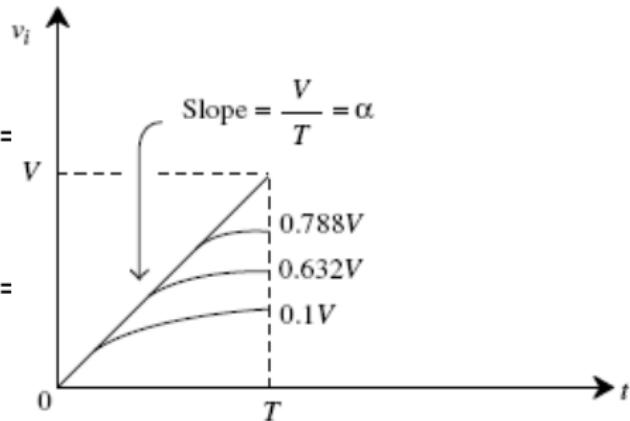

## Section 6

# **Exponential Input**

# Exponential Response

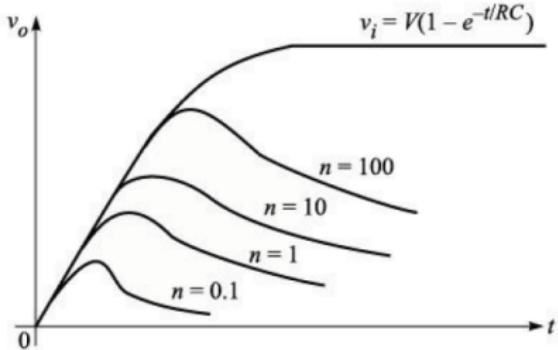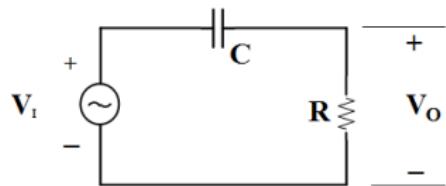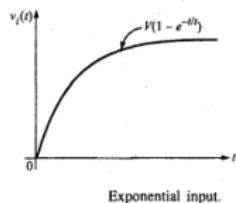

$$v_{in}(t) = \frac{q}{C} + V_o$$

$$i = \frac{dq}{dt} \quad V_R = iR$$

$$\frac{dv_{in}(t)}{dt} = \frac{dq}{Cdt} + \frac{dV_o}{dt} = \frac{i}{C} + \frac{dV_o}{dt}$$

$$\frac{dv_{in}(t)}{dt} = \frac{V_o}{C} + \frac{dV_o}{dt}$$

# Exponential Response

$$\therefore v_{in} = V(1 - e^{\frac{-t}{\tau_e}}) \quad \therefore \frac{dv_{in}(t)}{dt} = \frac{V}{\tau_e} e^{\frac{-t}{\tau_e}}$$


$$\frac{dv_{in}(t)}{dt} = \frac{V_o}{\tau} + \frac{dV_o}{dt}$$

$$\frac{V}{\tau_e} e^{\frac{-t}{\tau_e}} = \frac{V_o}{\tau} + \frac{dV_o}{dt}$$

$$\frac{V}{\tau_e} \frac{1}{S + \frac{1}{\tau_e}} = \frac{V_o(S)}{\tau} + S V_o(S)$$

$$\frac{V}{\tau_e} \frac{1}{S + \frac{1}{\tau_e}} = V_o(S) \left( \frac{1}{\tau} + S \right)$$
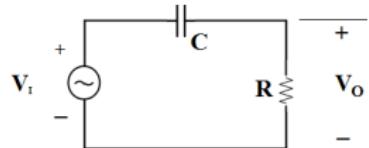
$$V_o(S) = \frac{V/\tau_e}{\left( S + \frac{1}{\tau_e} \right) \left( S + \frac{1}{\tau} \right)}$$



	$f(t)$	$F(s)$
1.	Unit impulse $\delta(t)$	1
2.	Unit step $1(t)$	$\frac{1}{s}$
3.	$t$	$\frac{1}{s^2}$
4.	$e^{-at}$	$\frac{1}{s+a}$
5.	$t e^{-at}$	$\frac{1}{(s+a)^2}$

## Exponential Response

$$V_o(S) = \frac{V/\tau_e}{(S + \frac{1}{\tau_e})(S + \frac{1}{\tau})}$$

$$\frac{A}{(S + \frac{1}{\tau_e})} + \frac{B}{(S + \frac{1}{\tau})} = \frac{V/\tau_e}{(S + \frac{1}{\tau_e})(S + \frac{1}{\tau})}$$

$$V/\tau_e = A \left( S + \frac{1}{\tau} \right) + B \left( S + \frac{1}{\tau_e} \right)$$

Cancel parameter B  $\Rightarrow S = -\frac{1}{\tau_e}$

$$\therefore A = \frac{V/\tau_e}{\left( \frac{1}{\tau_e} - \frac{1}{\tau} \right)} = \frac{V}{\left( \frac{\tau_e}{\tau} - 1 \right)}$$

## Exponential Response

In the same way Cancel parameter A  $\Rightarrow S = -\frac{1}{\tau}$

$$\therefore B = \frac{V/\tau_e}{\left(\frac{1}{\tau} - \frac{1}{\tau_e}\right)} = \frac{-V}{\left(\frac{\tau_e}{\tau} - 1\right)}$$

$$V_o(S) = \frac{V}{\left(\frac{\tau_e}{\tau} - 1\right)} \left( S + \frac{1}{\tau_e} \right) + \frac{-V}{\left(\frac{\tau_e}{\tau} - 1\right)} \left( S + \frac{1}{\tau} \right)$$

$$V_o(t) = \frac{V}{\left(\frac{\tau_e}{\tau} - 1\right)} \left[ e^{\frac{-t}{\tau_e}} - e^{\frac{-t}{\tau}} \right]$$

$$= \begin{cases} \tau \gg \tau_e, & \frac{-V}{\left(\frac{\tau_e}{\tau} - 1\right)} \left[ e^{\frac{-t}{\tau}} \right] \\ \tau = \tau_e, & \frac{V/\tau_e}{\left(S + \frac{1}{\tau_e}\right)^2} = \frac{V}{\tau_e} t e^{\frac{-t}{\tau_e}} \end{cases}$$

# Exponential Response

$$V_o(t) = \begin{cases} \tau \neq \tau_e, & \frac{V}{\left(\frac{\tau_e}{\tau} - 1\right)} \left[ e^{\frac{-t}{\tau_e}} - e^{\frac{-t}{\tau}} \right] \\ \tau \gg \tau_e, & \frac{-V}{\left(\frac{\tau_e}{\tau} - 1\right)} \left[ e^{\frac{-t}{\tau}} \right] \\ \tau = \tau_e, & \frac{V/\tau_e}{\left(S + \frac{1}{\tau_e}\right)^2} = \frac{V}{\tau_e} t e^{\frac{-t}{\tau_e}} \end{cases}$$

## Exponential Response: Example 1


An exponential input of  $10(1 - e^{-\frac{t}{10 \times 10^{-3}}})$  is applied to a high-pass RC circuit. Plot the response when (i)  $RC = 20$  ms and (ii)  $RC = 10$  ms.

$\tau \neq \tau_e$ :

$$\frac{V}{(\frac{\tau_e}{\tau} - 1)} \left[ e^{\frac{-t}{\tau_e}} - e^{\frac{-t}{\tau}} \right] = -20 \left[ e^{\frac{-t}{10m}} - e^{\frac{-t}{20m}} \right]$$

$\tau = \tau_e$ :
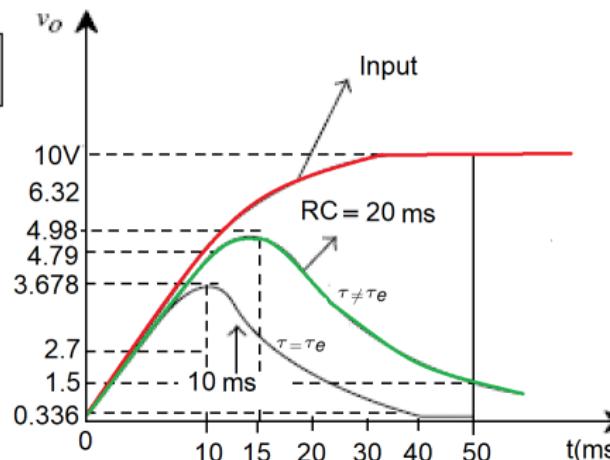
$$\frac{V}{\tau_e} t e^{\frac{-t}{\tau_e}} = 10^3 t e^{\frac{-t}{10m}}$$



## Section 7

# **Differentiator**


## Differentiator

$$v_i = \frac{1}{C} \int idt + V_o \quad V_o = iR$$






$$v_i = \frac{1}{RC} \int V_o dt + V_o$$

assume  $V_o$  is very small
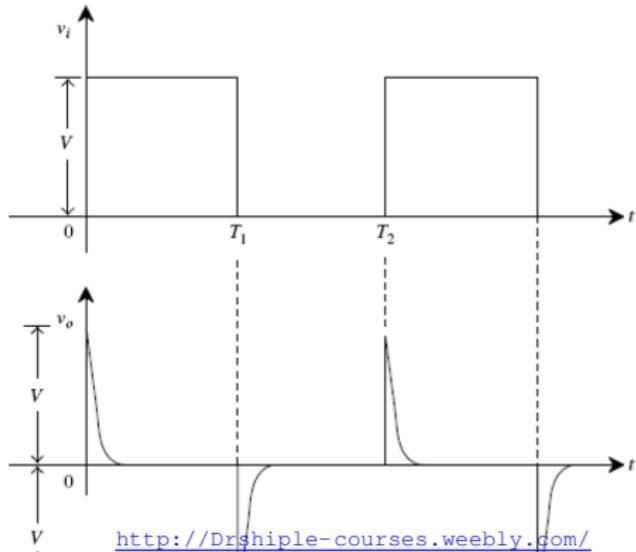
$$v_i = \frac{1}{RC} \int V_o dt \Rightarrow V_o = \tau \frac{dV_i}{dt}$$



# Positive Spikes Vs. Negative Spikes

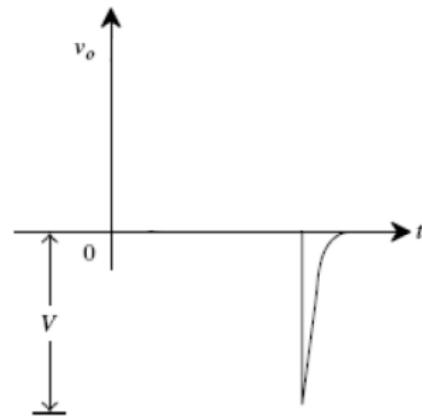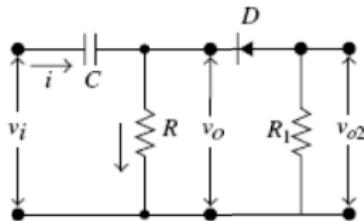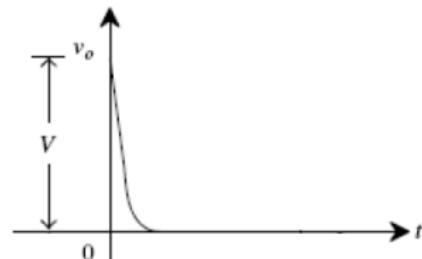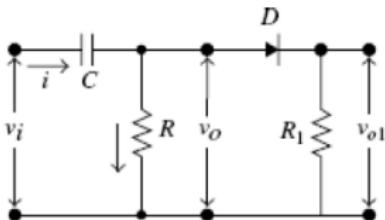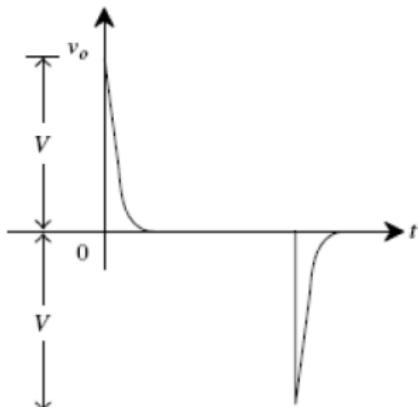

## Limitation of RC Differentiator

$$\theta = \tan^{-1} \frac{X_c}{R} = \frac{1}{\omega RC} = \frac{\omega_c}{\omega}$$

- When  $\theta = 90^\circ$ , the sine function at the input becomes a cosine function at the output, as is required in a differentiator.
- When  $\omega_c/\omega = 100$ ,  $\theta = 89.4^\circ$  which is nearly equal to  $90^\circ$ .
- A high-pass circuit behaves as a good differentiator only when  $RC \ll T$ .

## Differentiator Vs. Integrator

Integrators are almost preferred over differentiators in analog computer applications for the following reasons:

- ① It is easier to stabilize an integrator than a differentiator because the gain of an integrator decreases with frequency whereas the gain of a differentiator increases with frequency.
- ② An integrator is less sensitive to noise voltages than a differentiator because of its limited bandwidth.
- ③ The amplifier of a differentiator may overload if the input waveform changes very rapidly.
- ④ It is more convenient to introduce initial conditions in an amplifier.