

# Linear Wave Shaping (Low Pass Filter)

Dr. M. Shiple

Wave Shaping Circuits (EET 232), 2020

## Outline






- 1 Introduction
- 2 Sinusoidal wave
- 3 Step Signal
- 4 Ramp Signal
- 5 Exponential Input
- 6 Integrator

# Section 1

## **Introduction**

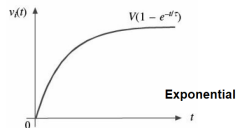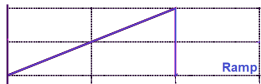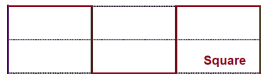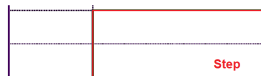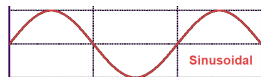
## Linear Wave Shaping

The process whereby the form of a non-sinusoidal signal is altered by transmission through a linear network is called linear wave shaping.


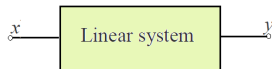
## Linear network (System): Properties

- 1 **Homogeneity:** (Multiply by constant ) for the input  $x$  to the system, the corresponding output is  $ny$  (where  $n$  is an integer).
- 2 **Additivity:** This property is called additivity. Homogeneity and additivity, taken together, comprise the principle of superposition. [ex:  $(y_1 + y_2) = x_1 + x_2$ ].
- 3 **Shift invariance:** [ex:  $(y(t - a)) = x(t - a)$ ]



## Section 2


# **Sinusoidal wave**

## Low Pass filter

By using voltage divider:

$$V_o = V_i \frac{\frac{1}{sC}}{R + \frac{1}{sC}} \quad \times SC$$
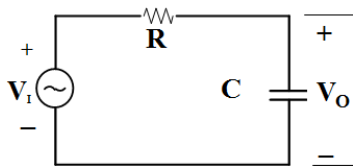
$$\frac{V_o}{V_i} = \frac{1}{1 + sRC} = \frac{1}{1 + j\omega Rc}$$



To find cut off frequency, the input signal loses half power or  $\frac{1}{\sqrt{2}}$  voltages

$$|T(S)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$|T(S)| = \frac{1}{\sqrt{(1)^2 + (\omega Rc)^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{Rc}$$

To find the phase of TF:

$$\theta(\omega) = \tan^{-1}\left(\frac{0}{1}\right) - \tan^{-1}\left(\frac{\omega Rc}{1}\right)$$


$$= 0 - \tan^{-1}\left(\frac{\omega}{\omega_c}\right) = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$

$|T(S)|$ 


$$\alpha = 20 \log_{10} |T(S)|$$

$$f_c = \frac{1}{2\pi R C} = \frac{1}{2 \times 3.14 \times 12k \times 100} = 132.6 \text{ Hz}$$


## Magnitude

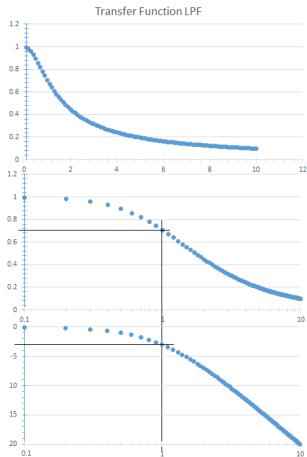

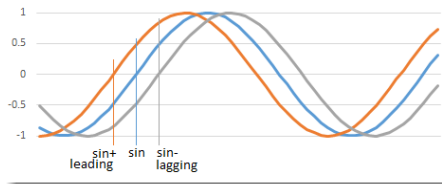


$\angle \theta(\omega)$ 

## Phase

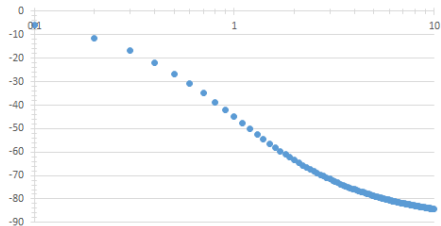


# Bode Plot

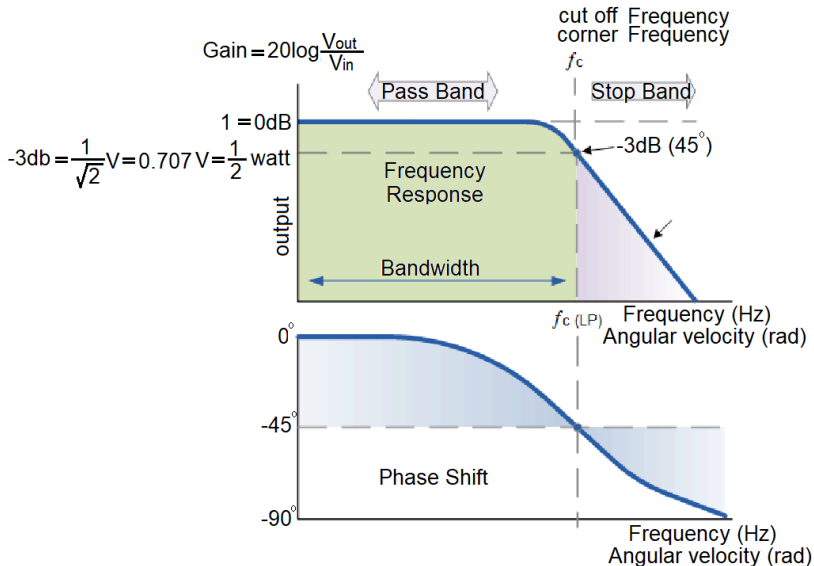

## Section 3

# Step Signal

## Step Voltage Input

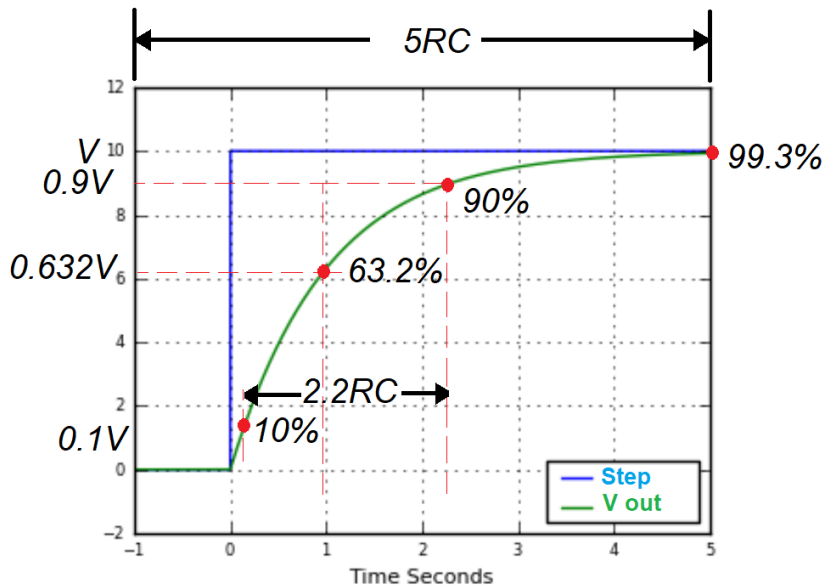

## Section 4

# Ramp Signal

## Back to basic concepts

$$v_i = \alpha t = \frac{\alpha}{S^2}$$

$$V_o = v_i \frac{1}{1 + SRC} = \frac{\alpha}{S^2} \frac{1}{(1 + SRC)}$$


$$= \frac{?}{S} + \frac{? \alpha}{S^2} + \frac{?}{(1 + SRC)}$$

$$= \frac{-\alpha RC}{S} + \frac{\alpha}{S^2} + \frac{\alpha (RC)^2}{(1 + SRC)}$$

last argument should be formed as table

$$= \left[ \frac{-\alpha RC}{S} + \frac{\alpha}{S^2} + \frac{\alpha (RC)}{\left(\frac{1}{RC} + S\right)} \right]$$
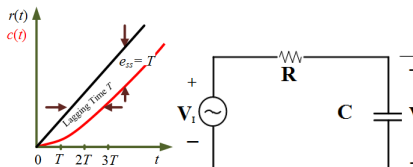
$$= -\alpha RC + \alpha t + \alpha (RC) e^{-\frac{t}{RC}}$$



	$f(t)$	$F(s)$
1.	Unit impulse $\delta(t)$	1
2.	Unit step $1(t)$	$\frac{1}{s}$
3.	$t$	$\frac{1}{s^2}$
4.	$e^{-at}$	$\frac{1}{s+a}$
5.	$te^{-at}$	$\frac{1}{(s+a)^2}$

## Back to basic concepts

$$V_o = -\alpha RC + \alpha t + \alpha(RC)e^{-\frac{t}{RC}}$$

RC very small

$$\begin{aligned} &= -\alpha RC + \alpha t + \alpha(RC)e^{-\frac{t}{RC}} \\ &= -\alpha RC + \alpha t = \alpha(t - RC) \end{aligned}$$


RC not small

Recall :  $e^x = 1 + \frac{x}{1!} + \frac{x^2}{2!} + \dots$

$$\begin{aligned} &= -\alpha RC + \alpha t + \alpha(RC)e^{-\frac{t}{RC}} \\ &= -\alpha RC + \alpha t + \alpha(RC)\left[1 - \frac{t}{RC} + \frac{t^2}{(RC)^2}\right] \\ &= -\alpha RC + \alpha t + \alpha(RC) - t\alpha + \alpha \frac{t^2}{2(RC)} \\ &= \frac{\alpha}{(RC)} \frac{t^2}{2} \end{aligned}$$

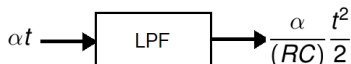
## Error Ratio

$$= \frac{\alpha}{(RC)^2} \frac{t^2}{2}$$




error between input and output at small RC values:
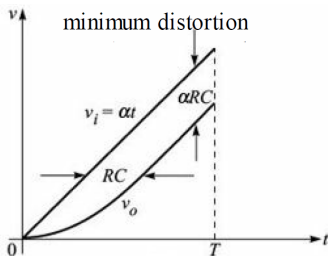
$$e_t = \frac{\alpha t - (-\alpha RC + \alpha t)}{\alpha t} = \frac{RC}{t} = \frac{1}{\omega_c T} = \frac{1}{2\pi f_c T}$$



$$RC/T \ll 1$$

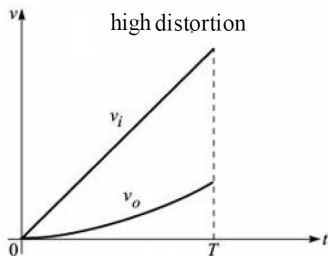

$$RC/T \gg 1$$



## Example

Consider 2 ms ramp signal input the output signal should have less than 0.1% error. Calculate the maximum yield  $f$ .

Solution:


$$e_t = \frac{1}{2\pi f_c T} \Rightarrow f_c = \frac{1}{2\pi e_t T} > 79.6 \text{ KHz}$$

$$\omega_c = \frac{1}{e_t T} = \frac{1}{RC} \Rightarrow RC < 2 \mu\text{S}$$



## Section 5

# Exponential Input

# Exponential Response

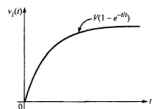




Exponential input.

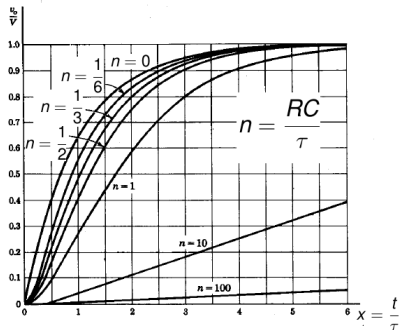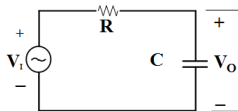

$$v_{in}(t) = V(1 - e^{-\frac{t}{\tau}})$$

$$V_{out}(t) = V \left[ 1 - \frac{e^{-\left(\frac{t}{\tau}\right)}}{1 - n} + \frac{e^{-\left(\frac{t}{RC}\right)}}{\frac{1}{n} - 1} \right]$$

## Exponential Response

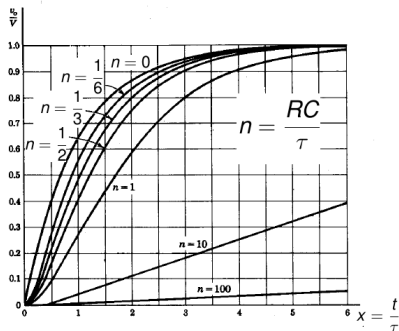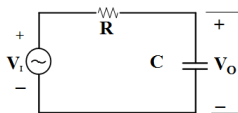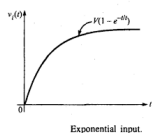


$$V_{out}(t) = \begin{cases} V \left[ 1 - \frac{e^{(-x)}}{1-n} + \frac{ne^{(-\frac{x}{n})}}{1-n} \right] & n \neq 1 \\ 1 - (1+x)e^{-x} & n = 1 \end{cases}$$

$$t_r = 1.05 \sqrt{(2.2RC)^2 + (2.2\tau)^2}$$

## Section 6

# Integrator

## Concepts

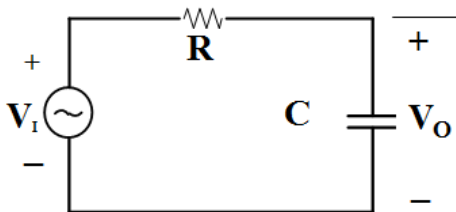

at charging if  $RC \gg T$ , where:  $T$  is the period of the input signal.

$\therefore RC \gg T$  the capacitor never charge


$\therefore V_R \gg V_C$

$$V_{in} = V_R + V_C \Rightarrow V_{in} \approx V_R$$

$$V_o = V_C = \frac{1}{C} \int i(t) dt \approx \frac{1}{C} \int \frac{V_R}{R} dt$$

$$= \frac{1}{RC} \int V_{in} dt$$

## Condition

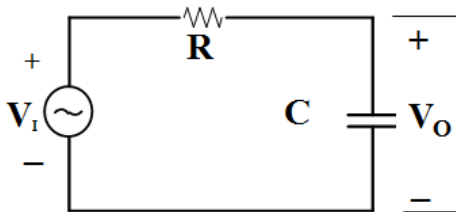

- at charging if  $RC \gg T$ , where:  $T$  is the period of the input signal.
- $RC > 15T$  sine wave will be shifted  $89^\circ \approx 90^\circ$

## Difference between LPF VS Miller

Frequency	Low pass filter: $H_s=1/(s+1)$	Pure integrator: $H_s=1/s$
for $f=1000\text{hz}$	$1/(6284+1)=1.5910899\text{e-}4$	$1/6284=1.5913431\text{e-}4$
1Hz	$1/(1+1)=1/2=0.500$	$1/(1)=1$
DC	$1/(1+0)=1$	$\infty$
step input	$f(t) = 1 - e^{(-t)}$	$t$