

---

# Active Realization

Dr. M. Shiple

Shaping Circuits (EEC 242), 2015

## Outline

### Passive realization disadvantages

### Active Realization

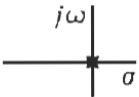
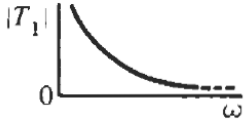
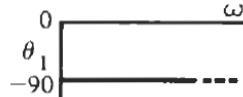

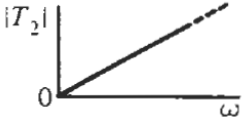
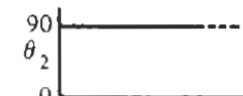
- Inverting Op Amp circuits

- Non-inverting Op Amp circuits

- Differential OpAmp


## Transfer Function

- Not all transfer functions could be realized (ex.  $\frac{K_1}{S}$ )

$T_n(S)^a$	Pole and Zero	Magnitude Response	Phase Response
$\frac{K_1}{S}$			
$K_2 S$			
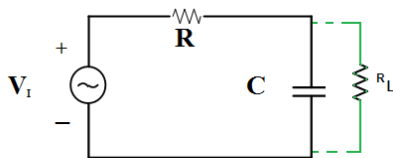
## Loading disadvantage

- ▶ Loading problems.
- ▶ The gain always  $\leq 1$ .




$$\frac{V_o}{V_i} = \frac{1}{1 + sRc} = \frac{1}{1 + j\omega Rc}$$

$$\frac{V_o}{V_i} = \frac{R_L}{R_L + R} \frac{1}{\left( s \frac{R_L Rc}{R_L + R} + 1 \right)}$$
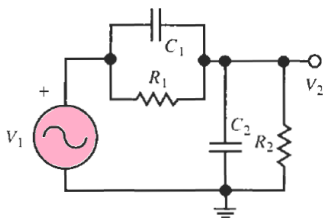
## Dependency between zeros and poles

Fixing incorrect zeros due to component tolerance through fabrication process will affect the poles of the TF.





$$|T(S)| = K \frac{s + z}{s + p}$$

$$z = \frac{-1}{R_1 C_1}$$

$$p = \frac{-1}{\left(\frac{R_1 R_2}{R_1 + R_2}\right) (C_1 + C_2)}$$



## Different topologies single Equation

$$|T(S)| = -\frac{Z_2}{Z_1} = -K \frac{S + z_1}{S + p_1}$$

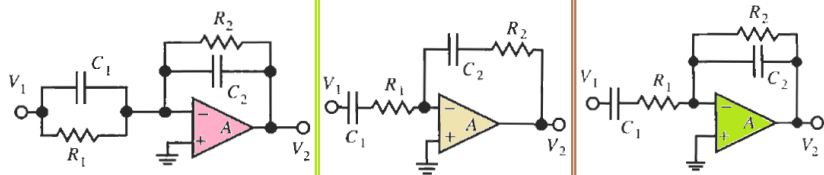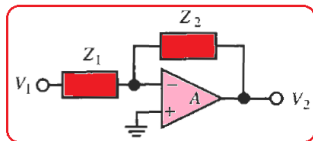


## Different topologies single Equation Solution


$$|T(S)| = -\frac{Z_2}{Z_1} = -K \frac{S + z_1}{S + p_1}$$

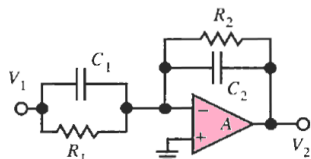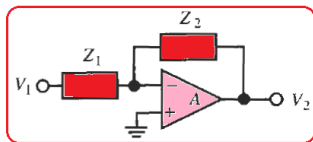

$$|T(S)| = \frac{R_2 SC_1 R_1 + 1}{R_1 SC_2 R_2 + 1}$$

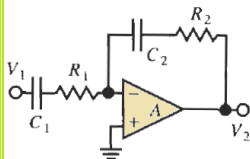


$$|T(S)| = \frac{c_1 SC_2 R_2 + 1}{c_2 SC_1 R_1 + 1}$$

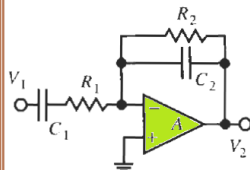

$$|T(S)| = \frac{SC_1 R_2}{(SC_1 R_1 + 1)(SC_2 R_2 + 1)}$$



## Not all topologies are valid

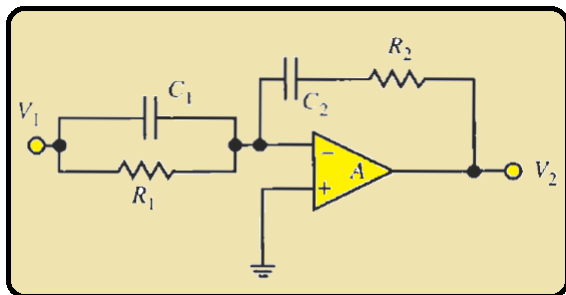


- ▶  $\omega = 0 \Rightarrow Z_c = \infty \Rightarrow$  open loop circuit.
- ▶  $\omega = \infty \Rightarrow Z_c = 0 \Rightarrow$  gain =  $\infty$



## Low pass Filter

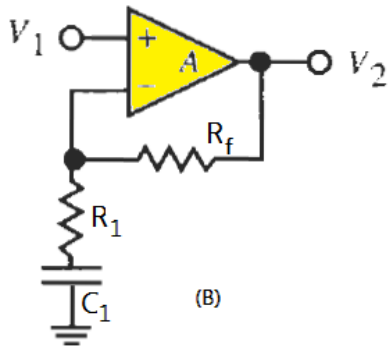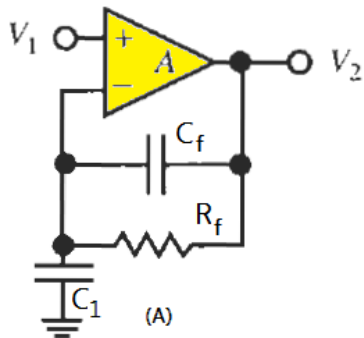


## Low pass Filter

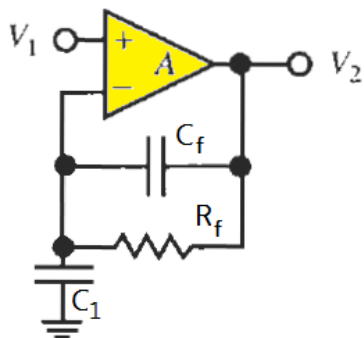

$$\frac{1 + SR_f(C_f + C_1)}{1 + SC_fR_f}$$

(A)

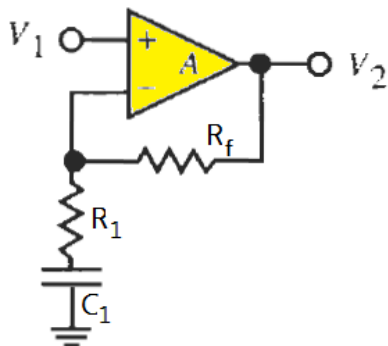



$$\frac{1 + SC_1(R_f + R_1)}{1 + SC_1R_f}$$

(B)


## Inverting vs. Non-inverting Op Amp

	Inverting op Amp	Non-inverting
<b>Gain</b>	Attenuation/Amplification	buffer / amplification
<b>Component</b>	4 passive elements	3 passive elements
<b>Implementation Technology</b>	-	adaptable (use resistors or capacitors)
<b>Input Impedance</b>	matching	$\infty$

## Allpass Filter

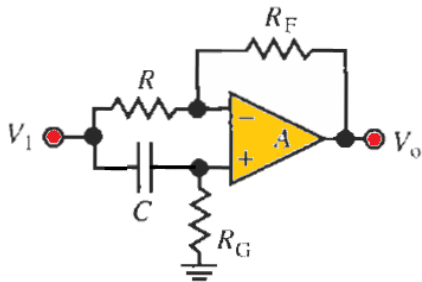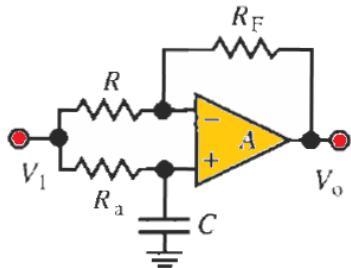

## Allpass Filter

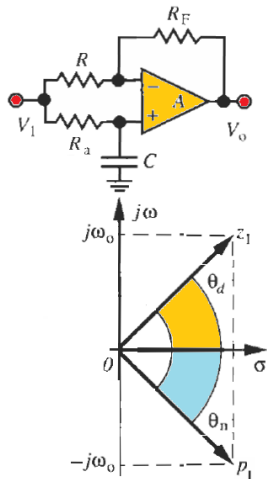

Let:  $R = R_F$

$$V^+ = V_1 \frac{\frac{1}{SC}}{R_a + \frac{1}{SC}} = V_1 \frac{1}{1 + SCR_a}$$


$$T(S) = V^+ \left(1 + \frac{R_f}{R}\right) - V^- \frac{R_f}{R}$$

$$T(S) = \frac{2}{1 + SCR_a} - 1 = \frac{1 - SCR_a}{1 + SCR_a}$$

$$|T(S)| = 1$$

$$\angle T(S) = \tan^{-1} \frac{-\omega}{1} - \tan^{-1} \frac{\omega}{1} = -2 \tan^{-1} \omega CR_a$$

## Differential OpAmp , Allpass Filter

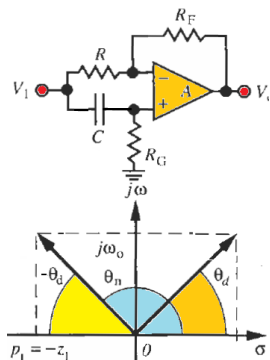

$$\text{Let: } R = R_F$$

$$V^+ = V_i \frac{R_a}{R_a + \frac{1}{SC}} = V_i \frac{SCR_a}{1 + SCR_a}$$

$$T(S) = V^+ \left(1 + \frac{R_f}{R}\right) - V^- \frac{R_f}{R}$$

$$T(S) = \frac{2SCR_a}{1 + SCR_a} - 1 = \frac{SCR_a - 1}{SCR_a + 1}$$

$$|T(S)| = 1$$

$$\begin{aligned} \angle T(S) &= \tan^{-1} \frac{\omega}{-1} - \tan^{-1} \frac{\omega}{1} \\ &= 180 - 2 \tan^{-1} \omega CR_a \end{aligned}$$