



ANSWER THE FOLLOWING QUESTIONS:

1. Design a Butterworth low-pass filter to realize the following specifications: [15 marks] [C_o, A_m]

$$\alpha_{max} = 0.5dB, \alpha_{min} = 35dB, \omega_p = 1000rad/s, \text{ and } \omega_p = 3000rad/s.$$

- Calculate the filter order, pole locations in the S-plane, and transfer function.
- Calculate denormalized frequency, gain and quality factor for each pole.
- By keeping the gain of the third pole to unity, Calculate all filter components.
- Redesign LPF to use resistors with $8.1k\Omega$.
- Redesign 5th order LPF (designed in part c) with $\omega_B = 12343.4rad/s$.

Solution:

(a)

$$n = \frac{\log\left(\frac{(10^{\frac{\alpha_{min}}{10}} - 1)}{(10^{\frac{\alpha_{max}}{10}} - 1)}\right)}{2 \log \frac{\omega_S}{\omega_P}} = \frac{\log\left(\frac{(10^{\frac{35}{10}} - 1)}{(10^{\frac{0.5}{10}} - 1)}\right)}{2 \log \frac{3000}{1000}} = 4.625 \approx 5$$

pole locations: $\psi = \frac{180}{n} = 36^\circ$

- $0 \Rightarrow (S + 1) \Rightarrow P_0 = -1$
- $\pm 36 \Rightarrow (S^2 + 2 \cos 36S + 1) = (S^2 + 0.618S + 1)$
 $\Rightarrow P_{1,2} = -\cos \psi + \pm j \sin \psi = -0.3 \pm j0.95$
- $\pm 72 \Rightarrow (S^2 + 2 \cos 72S + 1) = (S^2 + 1.618S + 1) \Rightarrow P_{3,4} = -0.8 \pm j0.58$

(b)

$$\epsilon = \sqrt{(10^{\frac{\alpha_{max}}{10}} - 1)} = 0.349$$

$$\omega_{BLPF} = \epsilon^{-\frac{1}{n}} \times \omega_P = 1234.34rad/s$$

Gain and quality factor: $S^2 + \frac{\omega_0}{Q}S + \omega_0^2$ and $k = 3 - \frac{1}{Q}$

Pole	Term	Q	K
0	$S + 1$	0.5	1
1,2	$S^2 + 1.618S + 1$	0.618	1.382
3,4	$S^2 + 0.618S + 1$	1.618	2.382

(c) Assume $C = 10nF$

$$R = \frac{1}{\omega_B C} = \frac{1}{1234.34 \times 10n} = 81k\Omega$$

$$K_{1,2} = 1 + \frac{R_A}{R_B} \Rightarrow R_B = \frac{R_A}{K_{1,2} - 1} = \frac{81K}{0.382} = 212k\Omega \quad \text{Assume } R = R_A$$


$$K_{3,4} = 1 + \frac{R_A}{R_B} \Rightarrow R_B = \frac{R_A}{K_{1,2} - 1} = \frac{81K}{1.382} = 58.6k\Omega \quad \text{Assume } R = R_A$$

Reduce the third gain to be unity = 1

$$a_{3,4} = \frac{1}{2.382} = 0.419$$

$$R_1 = \frac{R}{a} = \frac{81k}{2.382} = 193.1k\Omega$$
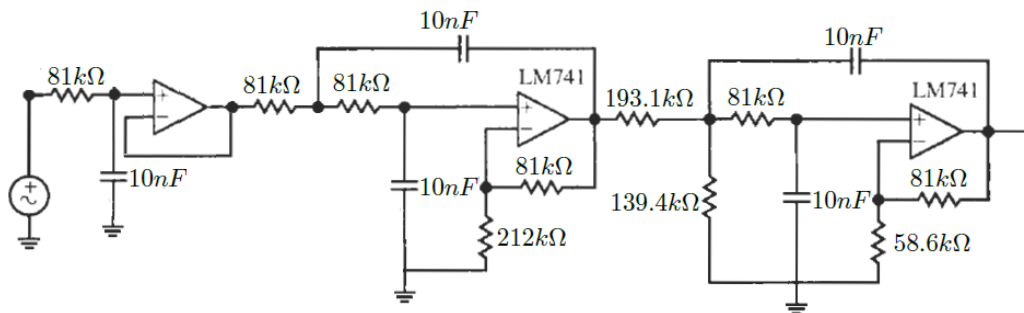
$$R_2 = \frac{R}{1 - a} = \frac{81k}{2.382} = 139.4k\Omega$$




(d)

$$\Delta K_m = \frac{\text{new value}}{\text{old value}} = \frac{8.1k}{81k} = 0.1$$

$$\forall R_{\text{new}} = 0.1 R_{\text{old}}$$
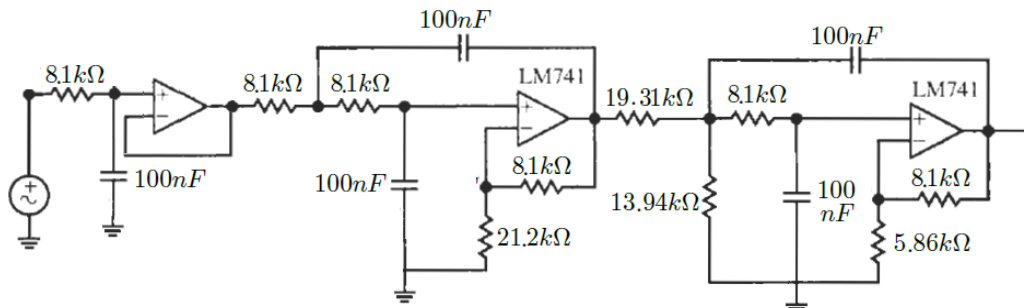
$$\forall C_{\text{new}} = \frac{C_{\text{old}}}{\Delta k_m} = \frac{10nF}{0.1} = 100nF$$




(e)

$$\Delta K_f = \frac{\text{new value}}{\text{old value}} = \frac{12343.4}{1234.34} = 10$$

$\forall R_{\text{new}} = \text{not changed}$
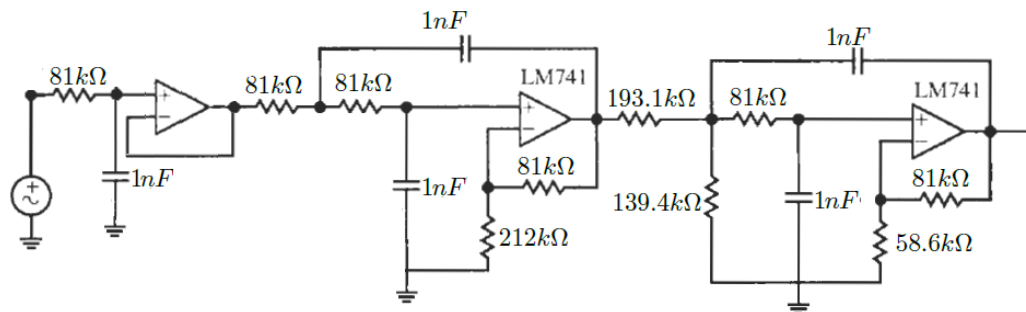
$$\forall C_{\text{new}} = \frac{C_{\text{old}}}{\Delta k_f} = \frac{10nF}{10} = 1nF$$



2. Design a Butterworth High-pass filter to realize the following specifications: [15 marks] [C_o, A_m]


$$\alpha_{\text{max}} = 1dB, \alpha_{\text{min}} = 50dB, \omega_p = 5300rad/s, \text{ and } \omega_c = 1000rad/s.$$

(a) Calculate the filter order, pole locations in the S-plane, and transfer function.

(b) Calculate denormalized frequency, gain and quality factor for each pole.

Solution:

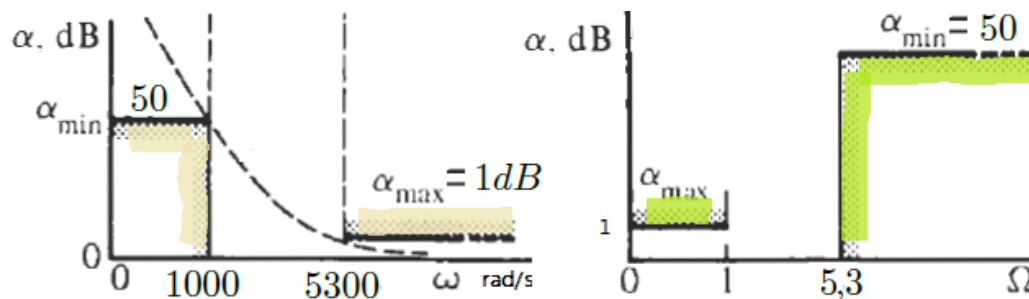(a) transform HPF \Rightarrow LPF By replace $\forall \omega_{LPF} = \frac{\omega_{HPF_{pass}}}{\omega_{HPF}}$



$$n = \frac{\log\left(\frac{(10^{\frac{\alpha_{\text{min}}}{10}} - 1)}{(10^{\frac{\alpha_{\text{max}}}{10}} - 1)}\right)}{2 \log \frac{\omega_s}{\omega_p}} = \frac{\log\left(\frac{(10^{\frac{50}{10}} - 1)}{(10^{\frac{1}{10}} - 1)}\right)}{2 \log \frac{5.3}{1}} = 3.85 \approx 4$$

pole locations: $\psi = \frac{180}{n} = 45^\circ$

- $\pm 22.5 \Rightarrow (S^2 + 2 \cos 22.5S + 1) = (S^2 + 1.847S + 1)$
 $\Rightarrow P_{1,2} = -\cos \psi \pm j \sin \psi = -0.923 \pm j0.383$
- $\pm 67.5 \Rightarrow (S^2 + 2 \cos 72S + 1) = (S^2 + .765S + 1) \Rightarrow P_{3,4} = -0.383 \pm j0.926$

(b)

$$\epsilon = \sqrt{(10^{\frac{\alpha_{max}}{10}} - 1)} = 0.509$$

$$\omega_{BLPF} = \epsilon^{-\frac{1}{n}} \times \omega_P = 1.18 \text{ rad/s}$$

Gain and quality factor: $S^2 + \frac{\omega_0}{Q}S + \omega_0^2$ and $k = 3 - \frac{1}{Q}$


Pole	Term	Q	K
1,2	$S^2 + 1.847 + 1$	0.54	1.15
3,4	$S^2 + 0.765 + 1$	1.31	2.23

Assume $C = 1F$

$$R = \frac{1}{\omega_{BLPF}C} = \frac{1}{1.18 \times 1} = 0.85\Omega$$

$$K_{1,2} = 1 + \frac{R_A}{R_B} \Rightarrow R_B = \frac{R_A}{K_{1,2} - 1} = \frac{0.85}{0.15} = 5.67\Omega \quad \text{Assume } R = R_A$$

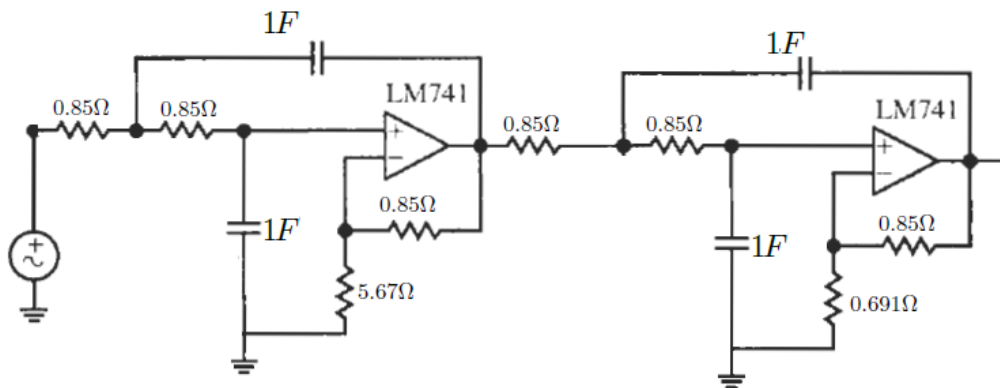
$$K_{3,4} = 1 + \frac{R_A}{R_B} \Rightarrow R_B = \frac{R_A}{K_{1,2} - 1} = \frac{0.85}{1.23} = 0.691\Omega \quad \text{Assume } R = R_A$$



Transform LPF \Rightarrow HPF :

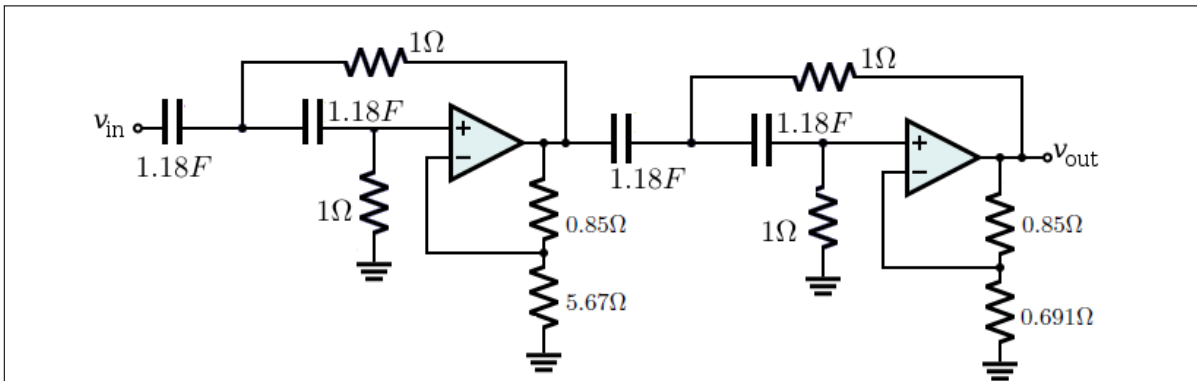(1) RC to CR transformation:

$$C_{new} = \frac{1}{R} = 1.18F \quad R_{new} = \frac{1}{C} = 1\Omega$$



(2) De-normalization:

$$\omega_{HLPF} = \frac{\omega_{HPF_{pass}}}{\omega_{LPF}} = \frac{5300}{1.18} = 4491.53 \text{ rad/s}$$

Assume $C = 10 \text{ nF}$

$$k_m = \frac{C_{old}}{c_{new} k_f} = \frac{1.18}{10 \text{ n} \times 4491.53} = 26.3 \text{ K}\Omega$$

$$R = 1 \times 26.3 \text{ k} = 26.3 \text{ K}\Omega$$

$$R_A = 0.85 \times 26.3 \text{ k} = 22.3 \text{ K}\Omega$$

$$R_{B1} = 5.67 \times 26.3 \text{ k} = 149 \text{ K}\Omega$$

$$R_{B2} = 6.91 \times 26.3 \text{ k} = 181.7 \text{ K}\Omega$$

