



Examiner : Dr. Mustafa M. Shiple
Subject: Shaping Circuits /(EEC 242)
Score: 40 Marks

Term: Feb / May 2015
Exam Time:90 min


ANSWER THE FOLLOWING QUESTIONS:

1. Draw an asymptotic of bode plot for both magnitude and phase for the following $T(S)$. [5 marks] $[A_q, A_u, B_k]$

$$T(s) = 1000 \frac{s^2}{(1 + s)(1 + 0.025s)}$$

Solution: Q1.

- $1000 \Rightarrow 20 \log 1000=60 \text{ dB}$ and $\phi = 0$.
- $S^2 \Rightarrow \text{slop} = +40$ crosses 0 dB at 1 rad and $\phi = 180$.
- $(1 + S) \Rightarrow \text{slop} = -20$ starts at 1 rad and $\phi|_{0.1} = 0, \phi|_{10} = -90$.
- $(1 + \frac{1}{40}S) \Rightarrow \text{slop} = -20$ starts at 40 rad and $\phi|_4 = 0, \phi|_{400} = -90$.
- Total.

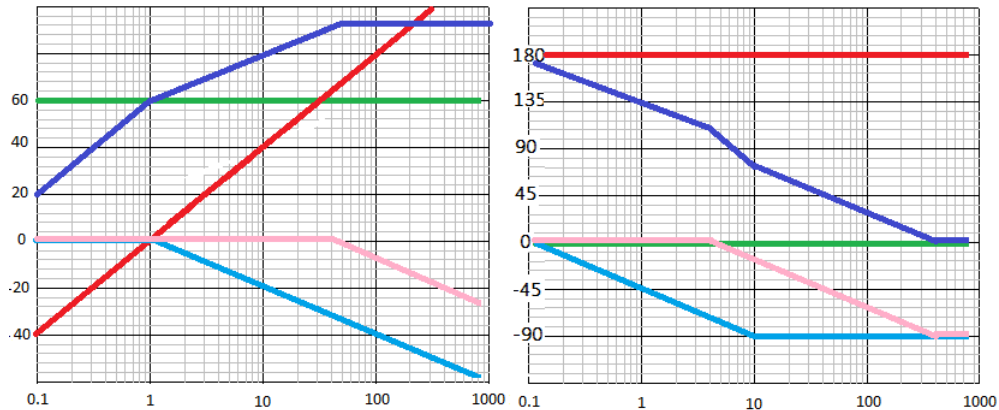

2. Draw the wiring diagram of generalized impedance converter (GIC). [10 marks] $[B_a, A_d, A_q]$

- (a) Drive an expression for transfer function of GIC.
- (b) Design a passive maximum flat high pass filter characterized by: $\alpha_{min} = 40 \text{ dB}$, $\alpha_{max} = 1 \text{ dB}$, $\omega_{stop} = 100 \text{ krad/s}$, and $\omega_{pass} = 625 \text{ krad/s}$. Use GIC in your design, The available resistors are 50Ω .

Order	R_S	C_1 a_1	L_2 a_2	C_3 a_3	L_4 a_4	C_5 a_5	L_6 a_6	C_7 a_7
1	1.0	2.0000						
2	1.0	1.4142	1.4142					
3	1.0	1.0000	2.0000	1.0000				
4	1.0	0.7654	1.8478	1.8478	0.7654			
5	1.0	0.6180	1.6180	2.0000	1.6180	0.6180		

[Total Marks is 40]

Signature of
Examiner:

Good Luck
Head of Dept.:

$$2. \omega_{BLP} = \frac{\omega_P}{(10^{\frac{\alpha_{max}}{10}} - 1)^{\frac{1}{2n}}} = \frac{1}{(10^{\frac{1}{10}} - 1)^{\frac{1}{6}}} = 1.25$$


$$3. \omega_{BHP} = \frac{625K}{\omega_{BLP}} = \frac{625K}{1.25} = 500K$$

LPF	RS	C1	L2	C3
n=3	1	1	2	1

N-HPF	RS	L1	C2	L3
n=3	1	1	0.5	1
HPF	50	0.1mH	0.2μF	0.1mH


$$Km = 50 \quad k_f = \omega_{BHP} = 500k$$
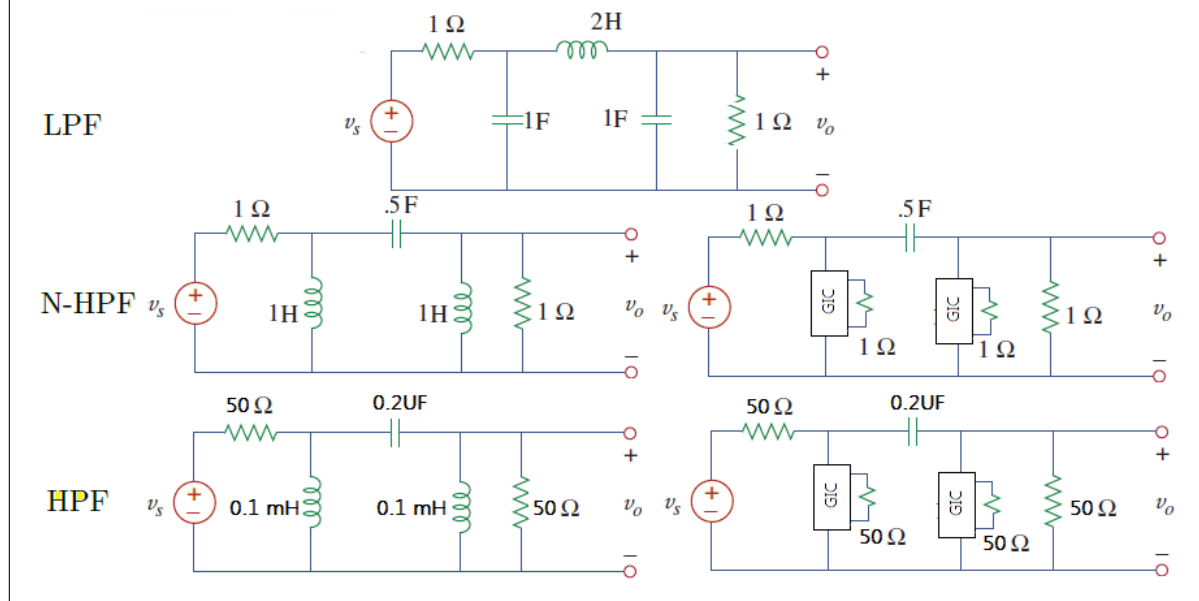
$$5. @ \text{ N-HPF } L = R_5 = 1\Omega \Rightarrow @ \text{ HPF } L = R_5 = 50\Omega$$



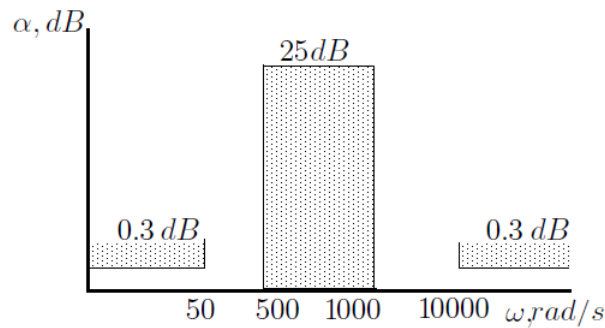3. Design an active band-rejection filter with maximum flat response to meet attenuation specification given in next Figure. (Hint: The available capacitor is $10nF$). [10 marks] [C_o, A_m]

- Adjust band-rejection gain to be 5.
- Find pole locations, ω_{PL} , ω_{PH} , and ω_o .



Solution:

(a) Low pass Filter

$$n = \frac{\log\left(\frac{(10^{\frac{\alpha_{min}}{10}} - 1)}{(10^{\frac{\alpha_{max}}{10}} - 1)}\right)}{2 \log \frac{\omega_S}{\omega_P}} = \frac{\log\left(\frac{(10^{\frac{25}{10}} - 1)}{(10^{\frac{0.3}{10}} - 1)}\right)}{2 \log \frac{500}{50}} = 1.822 \approx 2$$

$$\omega_o = \sqrt{500 * 1000} = 707.11 \text{ rad/s}$$

$$\psi = \frac{180}{2} = 90^\circ$$

$$\epsilon = \sqrt{(10^{\frac{\alpha_{max}}{10}} - 1)} = 0.2$$

$$\omega_{BLP} = \epsilon^{-\frac{1}{n}} \times \omega_P = 96.69 \text{ rad/s}$$

$$\text{assume } C = 10 \text{ nF} \Rightarrow R = \frac{1}{C \omega_{BLP}} \approx 1 \text{ K}\Omega$$

Gain and quality factor: $S^2 + \frac{\omega_0}{Q} S + \omega_0^2$ and $k = 3 - \frac{1}{Q}$

#	Degree	Location	$\frac{1}{Q}$	Q	$K = 3 - \frac{1}{Q}$	$R_F = (K - 1)R$
pole 1,2	45	$-0.71 \pm j0.71$	1.41	0.71	1.59	605Ω

(b) High pass Filter

$$\omega_{BHP} = \frac{\omega_o^2}{\omega_{BLP}} = 5171.2 \text{ rad/s} = k_f$$

$$k_m = \frac{1}{K_F C} = \frac{1}{5171.2 * 10 \text{ n}} = 19.3 \text{ K}\Omega$$

$$R_F = 22.2 \text{ K}\Omega$$

Solution:

(a)

$$\frac{v_I}{v_o} = \frac{Z_p}{Z_p + Z_s}$$


$$V_o = \left(1 + \frac{R_2}{R_1}\right)v_y$$

$$\frac{v_o}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \frac{Z_p}{Z_p + Z_s}$$

$$Z_p = \frac{R}{1 + sCR}$$

$$Z_s = \frac{1 + sCR}{sC}$$
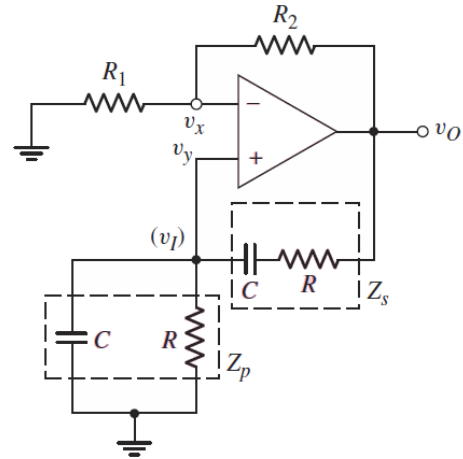
$$T(S) = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{3 + sRC + \frac{1}{sRC}}$$



Apply Barkhuasen conditions:

unity gain $A\beta = 1$

$$|T(j\omega)| = A\beta = T(S) = \left(1 + \frac{R_2}{R_1}\right) \frac{1 + j0}{3 + sRC + \frac{1}{sRC}} = 1$$

\therefore real=real & img=img

$$\therefore sRC + \frac{1}{sRC} = 0 \Rightarrow \omega_o = \frac{1}{RC}$$

$$\left(\frac{R_2}{R}\right)\left(\frac{1}{3}\right) = 1$$

let $R_1 = R$

$$R_2 = 2R$$

in Phase $\angle A\beta = 0$

by using ω_o

$$\angle T(j\omega) = \angle A\beta = \angle \left(1 + \frac{R_2}{R_1}\right) \frac{1 + j0}{3 + sRC + \frac{1}{sRC}}$$

$$= \tan^{-1}\left(\frac{0}{\frac{R_2}{R_1}}\right) - \tan^{-1}\left(\frac{0}{3}\right) = 0$$

(b)

$$f_o = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi \times 10k \times 30k} = 530pF$$

$$R_2 = 2R = 10k \times 2 = 20k\Omega$$

5. Briefly, discuss the function of phase detector. Compare between its types.

[5 marks] [C_o, A_m]

Solution: Phase Detector: This circuit produces an output voltage proportional to the phase difference between two input signals.

#	Type	θ_e	k_d
1	analog multiplier	$-\frac{\pi}{2} < \theta_e < \frac{\pi}{2}$	$\frac{k_1 k_2}{2}$
2	XOR Phase Detector	$-\frac{\pi}{2} < \theta_e < \frac{\pi}{2}$	$\frac{U_B}{\pi}$
3	JK-FF Phase Detector	$-\pi < \theta_e < \pi$	$\frac{U_B}{2\pi}$
4	PFD Phase Frequency Detector	$-2\pi < \theta_e < 2\pi$	$\frac{U_B}{4\pi}$

