

Introduction To Analog Filters

Dr. M. Shiple

Shaping Circuits (EEC 242), 2015

Outline

Introduction

Surrounding Applications

Mathematical background

Passive Filters Characteristics

Four types of filters

Realization with passive Elements

Bilinear Transfer Function

Low Pass Filter

High Pass Filter

Bandpass Filter


Band rejection Filter (BRF)

All Pass Filter

Exercises

Passive Filters

Cell phone

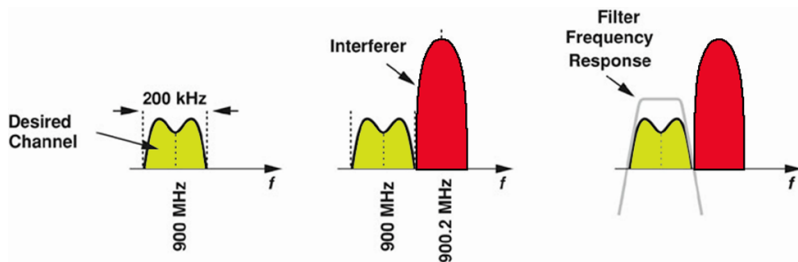

Application: Cellphone
Center frequency: 900 MHz
Bandwidth: 200 KHz


Adjacent
interference

Use a filter to remove
interference


ADSL Splitter



ADSL Frequencies

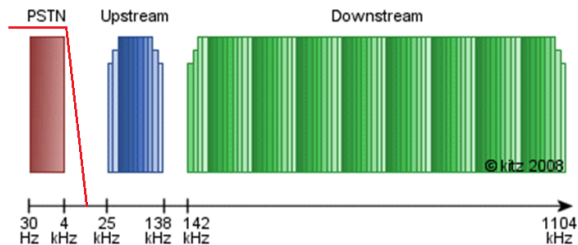

Heart Rate

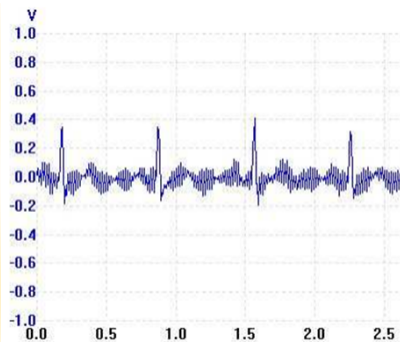

Automotive Applications

Current Sense Amplifiers


Applications:

- H-Bridge Motor Control
- Solenoid Current Sense
- PWM Control Loops
- Hydraulic Controls
- Lamp Monitoring
- Glow Plug Control
- Load Monitoring
- HEV/EV Battery Management Systems
- 12V / 24V Battery Monitoring
- High Voltage Data Acquisition



Part Number	Current Direction	Common Mode Voltage (V)	Response Time (μ s)	V_{OS} Max (μ V)	PSRR Min (dB)	Max Temperature Range	Comments
LT1787	Bidirectional	2.5 to 65	10	150	100	-40°C to 125°C	Buffered Output; Simple Input Filtering
LT1999	Bidirectional	-5 to 80	2.5	750	80	-55°C to 150°C	High Speed AC Monitor
LT6100	Unidirectional	4.1 to 48	40	300	95	-40°C to 125°C	Buffered Output with 5 Gain Settings

Fourier Series

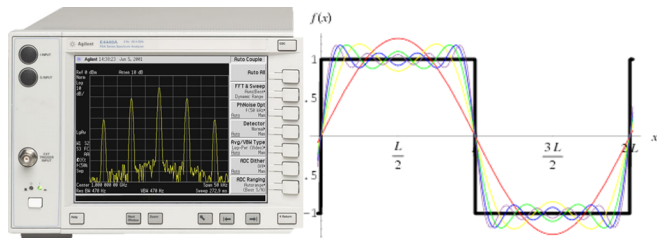


$$a_0 = \frac{2}{T} \int_a^{a+T} f(t) dt \quad (1)$$


$$a_n = \frac{2}{T} \int_a^{a+T} f(t) \cos(k\omega t) dt, \quad k \geq 1 \quad (2)$$

$$a_n = \frac{2}{T} \int_a^{a+T} f(t) \sin(k\omega t) dt, \quad k \geq 1 \quad (3)$$





Hierarchy of Filters

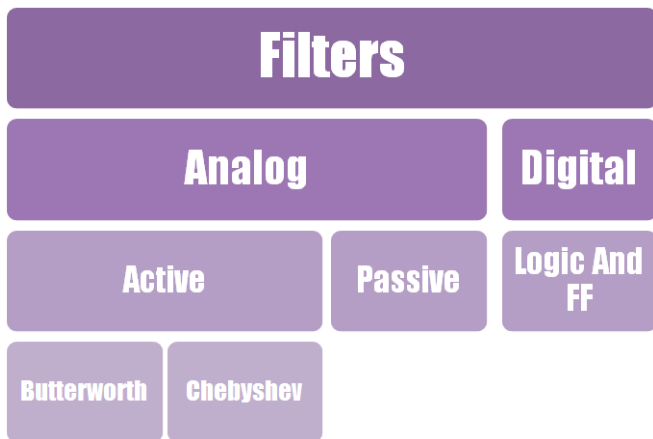


"Ideal Filters" Frequency domain

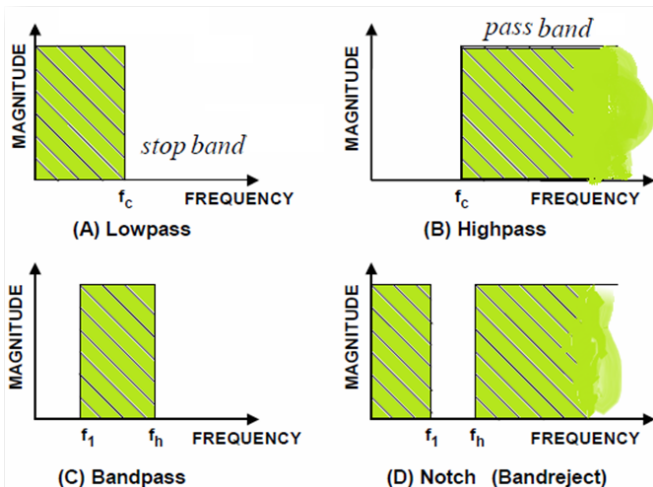

"Realistic Filters" Frequency domain

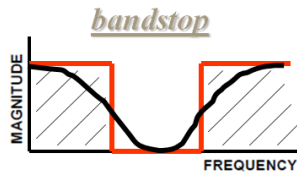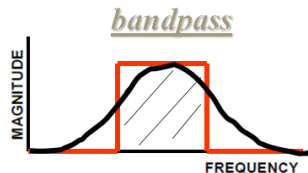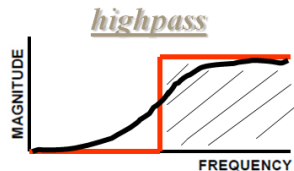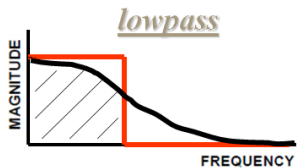

Key Filter Parameters

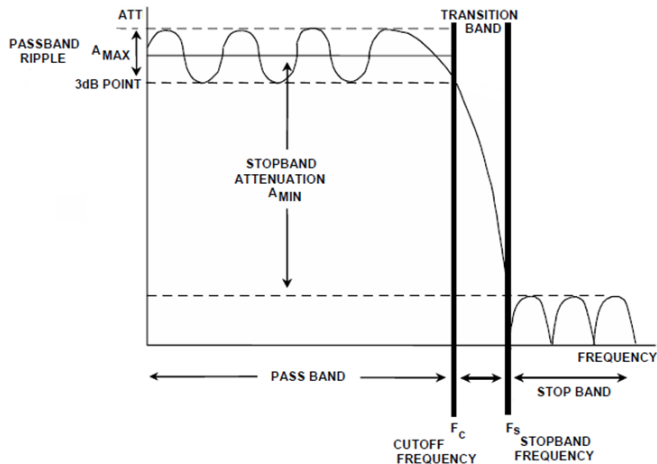

General form


$$T(s) = \frac{N(s)}{D(s)} = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}$$

$$T(s) = \frac{N(s)}{D(s)} = \frac{b_1 s + b_0}{a_1 s + a_0} \quad \text{First Order}$$

Conditions


- ▶ a_i and b_i are real numbers.
- ▶ a_i could be positive, negative, and zero.
- ▶ b_i could be positive.

Examples

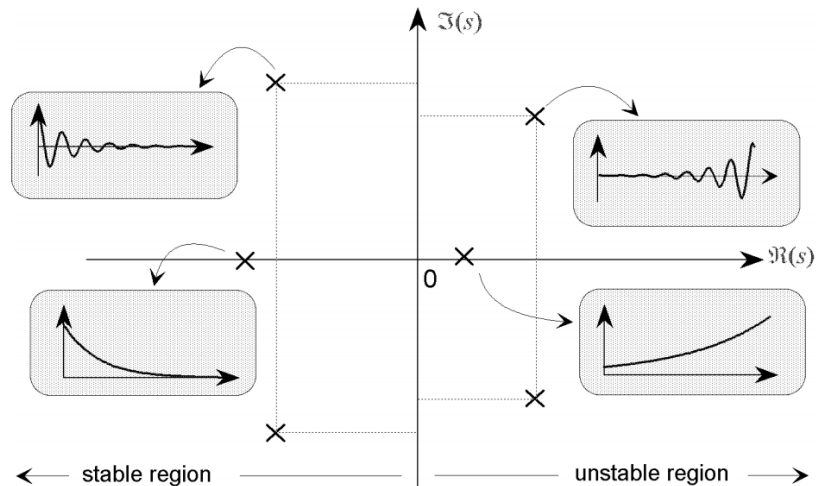


Examples

$$T_a(s) = K_a \frac{s + 3}{s + 1}$$

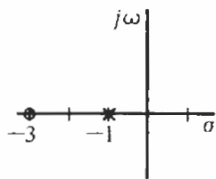


(a)

$$T_b(s) = K_b \frac{s + 1}{s + 4}$$

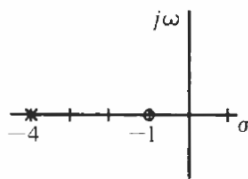


(b)

$$T_c(s) = K_c \frac{s - 2}{s + 2}$$

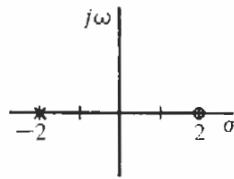

(c)

Examples

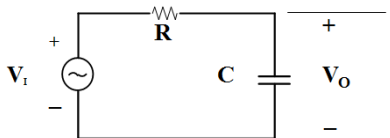

- ▶ Find the transfer function.
- ▶ compute magnitude, phase, pole, and zero , assume $R = 12k\Omega$ and $C = 100nf$.

Solution

Low Pass Filter


 $|T(S)|$

Magnitude


$$\alpha = 20 \log_{10} |T(S)|$$

$$f_c = \frac{1}{2\pi R_c} = \frac{1}{2 \times 3.14 \times 12k \times 100n}$$


$$= 132.6 \text{ Hz}$$

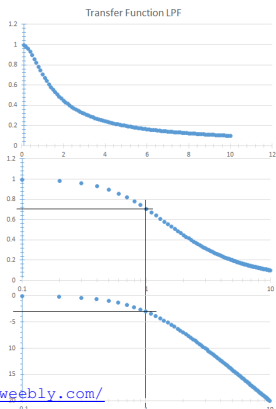


Low Pass Filter

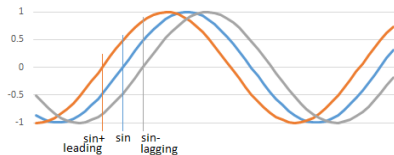 $\angle \theta(\omega)$ 

Phase

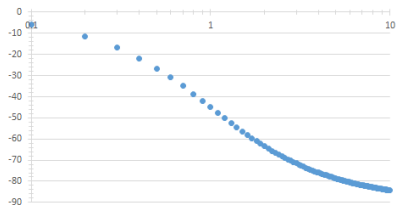

Examples

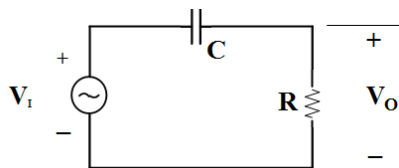

- ▶ Find the transfer function.
- ▶ compute magnitude, phase, pole, and zero , assume $R = 12k\Omega$ and $C = 100nf$.

Solution

High Pass Filter

 $|T(S)|$



$$\alpha = 20 \log_{10} |T(S)|$$

$$f_c = \frac{1}{2\pi R C}$$

$$= \frac{1}{2 \times 3.14 \times 12k \times 100n}$$

$$= 132.6 \text{ Hz}$$


Magnitude

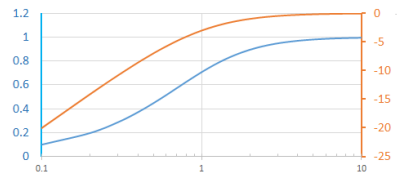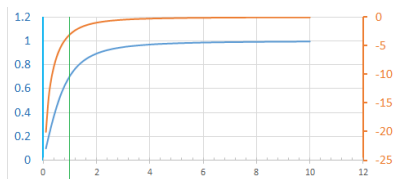

Excr 1:

Design a 1st order HPF with next specifications:

- ▶ $|T(0)| = 0.3$.
- ▶ $|T(\infty)| = 1$.
- ▶ there are a zero @
 $f_z = -159$.

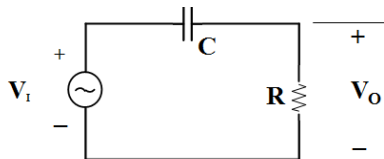


Solution

Example

- ▶ Find the transfer function.
- ▶ compute magnitude, phase.

The BPF cct.:

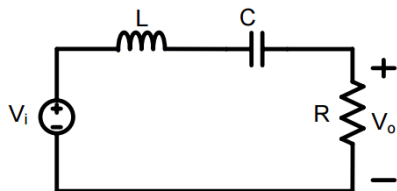

cont.


$$H(S) = \frac{R}{R + SL + \frac{1}{Sc}}$$

$$SL + \frac{1}{Sc} = 0$$

purely real

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

The BPF cct.:

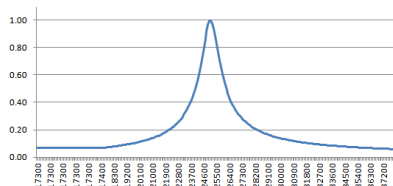


Band Pass Filter

- ▶ Therefore at the resonant frequency the impedance seen by the source is purely resistive.
- ▶ This implies that at resonance the inductor/capacitor combination acts as a short circuit.
- ▶ The current flowing in the system is in phase with the source voltage.

Max. and Min. Frequencies

The BPF cct.:

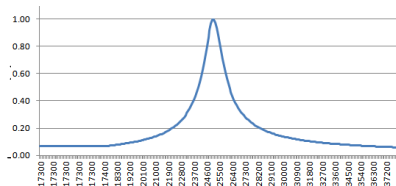

$$\begin{aligned}
 H(S) &= \frac{R}{R + SL + \frac{1}{SC}} \\
 &= \frac{SCR}{S^2LC + SCR + 1} \\
 &= \frac{S\frac{R}{L}}{S^2 + S\frac{R}{L} + \frac{1}{LC}} \\
 |T(j\omega)| &= \frac{\frac{R\omega}{L}}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\frac{\omega R}{L})^2}}
 \end{aligned}$$

$$\begin{aligned}
 |T(j\omega)| &= \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{(\frac{\omega L}{R} - \frac{1}{\omega RC})^2 + 1}} \\
 &+ 1 = \frac{\omega L}{R} - \frac{1}{\omega RC}
 \end{aligned}$$



Max. and Min. Frequencies

$$\omega_1 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\text{Band width} = \beta = \frac{R}{L}$$

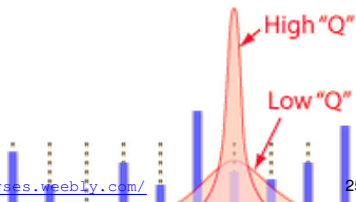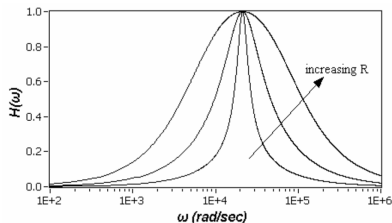
$$\text{Quality factor} = Q = \frac{\omega_0}{\beta}$$



Example

- ▶ Find the transfer function.
- ▶ compute magnitude, phase.

The BRF cct.:

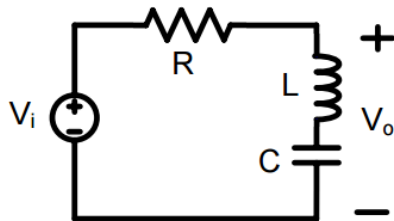

Band rejection Filter (BRF)

cont.


$$H(S) = \frac{SL + \frac{1}{Sc}}{R + SL + \frac{1}{Sc}}$$

$$SL + \frac{1}{Sc} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


purely real

The BRF cct.:

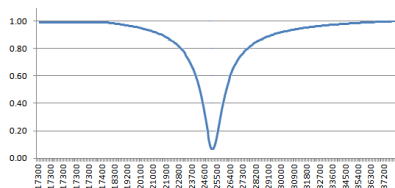

Max. and Min. Frequencies

The BRF cct.:

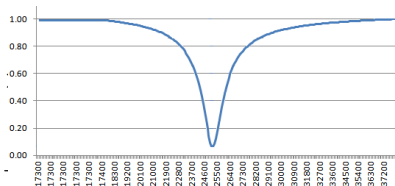

$$\begin{aligned}
 H(S) &= \frac{SL + \frac{1}{Sc}}{R + SL + \frac{1}{Sc}} \\
 &= \frac{S^2LC + 1}{S^2LC + SCR + 1} \\
 &= \frac{S^2 + \frac{1}{LC}}{S^2 + S\frac{R}{L} + \frac{1}{LC}} \\
 |T(j\omega)| &= \frac{\sqrt{(\frac{1}{LC} - \omega^2)^2}}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\frac{\omega R}{L})^2}}
 \end{aligned}$$

$$|T(j\omega)| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{(\frac{\omega R}{L})^2 + 1}}$$

Max. and Min. Frequencies

$$\omega_1 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$



$$\omega_2 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\text{Band width} = \beta = \frac{R}{L}$$

$$\text{Quality factor} = Q = \frac{\omega_0}{\beta}$$

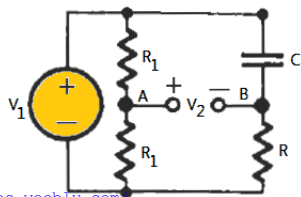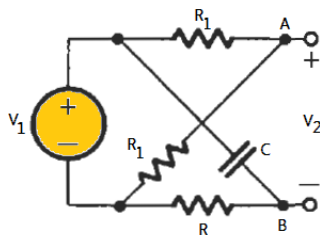Example

- ▶ Find the transfer function.
- ▶ compute magnitude, phase.



cont.


$$V_A = V_1 \frac{R_1}{2R_1} = \frac{1}{2} V_1$$

$$V_B = V_1 \frac{SCR}{SCR + 1}$$

$$V_2 = V_A - V_B = V_1 \left(\frac{1}{2} - \frac{SCR}{SCR + 1} \right)$$

$$\omega_c = \frac{1}{RC}$$


$$H(S) = \frac{1}{2} \times \frac{1 - SCR}{1 + SCR}$$

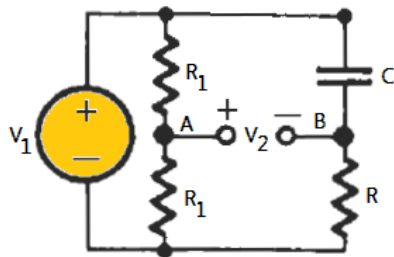The APF cct.:

Max. and Min. Frequencies

$$|T(j\omega)| = \frac{1}{2} \quad \text{for all } \omega$$

$$\theta = -2 \tan^{-1} \frac{\omega}{\omega_c}$$

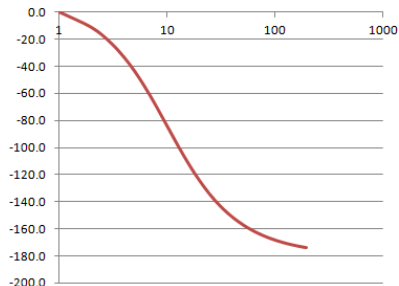

Example 3.1:

By using voltage divider:

$$V_o = V_i \frac{\frac{1}{sC}}{R + \frac{1}{sC}}$$

× SC

$$\frac{V_o}{V_i} = \frac{1}{1 + sRC} = \frac{1}{1 + j\omega Rc}$$

To find the pole of TF

(Dnum = 0):

$$|T(s)| = \frac{1}{\sqrt{(1)^2 + (\omega Rc)^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{Rc}$$

To find the zero of TF

(Num = 0):

zero = ∞

To find the magnitude of TF:

$$|T(s)| = \frac{1}{\sqrt{(1)^2 + (\omega Rc)^2}} \quad \text{use } \omega_c$$

$$|T(s)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

To find the phase of TF:

$$\theta(\omega) = 0 - \tan^{-1}\left(\frac{\omega Rc}{1}\right) = \tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$

Example 3.3:

By using voltage divider:

$$V_o = V_i \frac{R}{R + \frac{1}{sC}} \quad \times SC$$

$$\frac{V_o}{V_i} = \frac{SRC}{1 + SRC} = \frac{j\omega Rc}{1 + j\omega Rc}$$

To find the pole of TF
(Dnum = 0):

$$|T(S)| = \frac{1}{\sqrt{(1)^2 + (\omega Rc)^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{Rc}$$

To find the magnitude of TF:

$$|T(S)| = \frac{(\omega Rc)^2}{\sqrt{(1)^2 + (\omega Rc)^2}} \quad \text{use } \omega_c$$

$$|T(S)| = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$


To find the phase of TF:

$$\begin{aligned} \theta(\omega) &= \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega Rc}{1}\right) \\ &= \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega}{\omega_c}\right) \end{aligned}$$

Example 3.4:

To realize $|T(0)| = 0.3$:

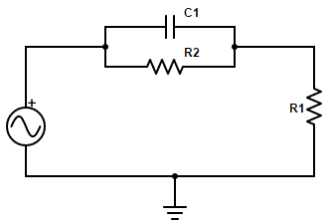a pure capacitor will not meet this condition we need to add shunt resistor, the expected cct.:



Back to [Example34](#).

$$V_o = V_i \frac{ScR_1R_2 + R_2}{ScR_1R_2 + (R_1 + R_2)} \quad (4)$$

$$|T(S)|_{\omega=0} = \frac{R_1}{R_1 + R_2} \quad (5)$$

To find the pole of TF (Dnum = 0):

$$ScR_1R_2 + R_2 = 0 \Rightarrow \omega = \frac{1}{cR_1} \quad (6)$$

From 4 and 6 assume $c = 1 \mu f$

$$\therefore R_1 = 1K\Omega \text{ and } R_2 = 429\Omega$$