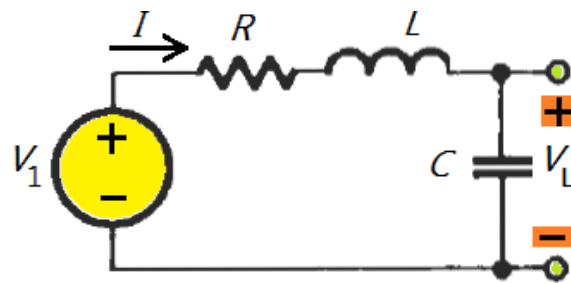




ANSWER THE FOLLOWING QUESTIONS:

1. A Second-order passive lowpass filter is designed with: [10 marks] [A_a, C_p]
 $R = 120\Omega$, $L = 16mH$, and $C = 0.05\mu F$.
- Drive the transfer function.
 - Calculate ω_o and Q .
 - Redesign the circuit to raise its quality factor to 12 without changing ω_o . Draw the wiring diagram of the circuit.

Solution: Q1.(a)



$$H(S) = \frac{\frac{1}{Sc}}{R + SL + \frac{1}{Sc}} \quad \times SC$$

$$H(S) = \frac{1}{S^2LC + SCR + 1} \quad \div LC$$

$$= \frac{\frac{1}{LC}}{S^2 + S\frac{R}{L} + \frac{1}{LC}}$$

$$= \frac{\omega_0^2}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$

$$\text{Quality factor} = Q = \frac{\omega_0}{\beta} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \beta = \frac{R}{L}$$

(b)

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{16m \times 0.05\mu}} = 35.35 \text{ krad/sec}$$

$$Q = \frac{\omega_0}{\beta} = \frac{1}{\sqrt{LC}} \times \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} = 4.71$$

(c)

$\therefore \omega_o$ depends on L, C

$\therefore \frac{\omega_o}{Q} = \frac{R}{L} \Rightarrow$ the only parameter i could change without affecting ω_o is R

$$\therefore R = \frac{L\omega_o}{Q} = 47.13\Omega$$

[Total Marks is 30]

2. For 7th order Butterworth. Find the pole locations.

[5 marks] [B_a, A_d, A_q]

Solution:

$$\psi = \frac{180}{7} = 25.71^\circ$$

$$B = (S + 1)(S^2 + 2 \cos 25.71S + 1)$$

$$(S^2 + 2 \cos 51.43S + 1)$$


$$(S^2 + 2 \cos 77.14S + 1)$$

$P_1 = -1$
 $P_{2,3} = \cos 25.71 \pm j \sin 25.71 = -0.9 \pm j0.43$
 $P_{4,5} = \cos 51.43 \pm j \sin 51.43 = -0.62 \pm j0.78$
 $P_{6,7} = \cos 77.14 \pm j \sin 77.14 = -0.22 \pm j0.97$

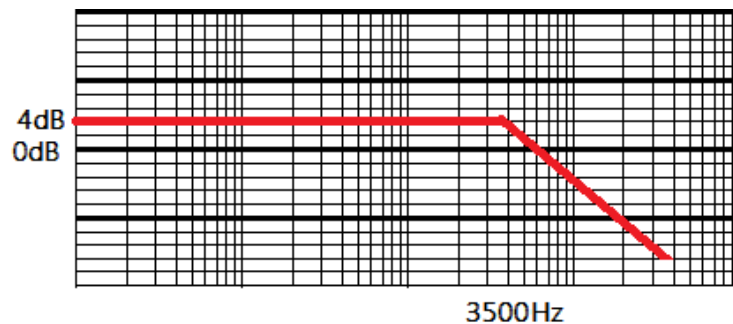3. Consider the Bode asymptotic plot in the next Figure.

[15 marks] [B_a, A_d, A_q]

- Determine $T(s)$ and plot the phase of $T(s)$.
- Drive an expression for transfer function of Sallen-key.
- Find the Sallen-key circuit that will realize the given specifications. Find the proper values of the circuit components.
- Calculate the error percentage of Q if the R_F increased 10%.




Solution:

From the bode plot:
Gain = 4dB, maximum flat $\Rightarrow Q = 0.707, \quad \omega_o = 2\pi \times 3500 = 21.98k \text{ rad/sec}$

(a)

$$k = 10^{\frac{4}{20}} = 1.58$$
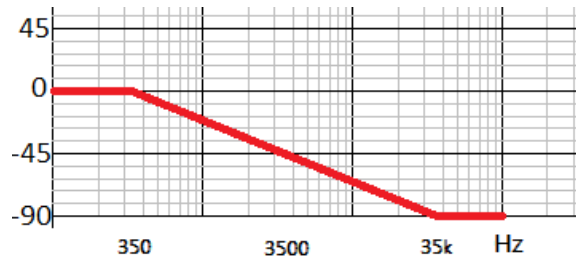
$$T(S) = \frac{1.58}{\left(\left(\frac{S}{21.98k}\right) + 1\right)}$$



(b)

$$V^-(1 + \frac{R_F}{R}) = V^-K = V_{out}V_x \quad :$$

$$\frac{V_{in} - V_x}{Z_1} = \frac{V_x - V^-}{Z_2} + \frac{V_x - V_{out}}{Z_3}$$

$$\frac{V_x - V^-}{Z_2} = \frac{V^-}{Z_4}$$

$$\therefore V_x = V^- \left(\frac{Z_2}{Z_4} + 1 \right)$$

$$V_{in} - V_x = V_x \frac{Z_1}{Z_2} - V^- \frac{Z_1}{Z_2} + V_x \frac{Z_1}{Z_3} - V_{out} \frac{Z_1}{Z_3}$$

$$V_{in} = V_x \left(\frac{Z_1}{Z_2} + \frac{Z_1}{Z_3} + 1 \right) - V^- \frac{Z_1}{Z_2} - V_{out} \frac{Z_1}{Z_3}$$

$$V_{in} = \frac{V_{out}}{K} \left(\frac{Z_2}{Z_4} + 1 \right) \left(\frac{Z_1}{Z_2} + \frac{Z_1}{Z_3} + 1 \right) - \frac{V_{out}}{K} \frac{Z_1}{Z_2} - V_{out} \frac{Z_1}{Z_3}$$

$$\frac{V_{in}}{V_{out}} = \frac{1}{K} \left(\frac{Z_1}{Z_4} + \frac{Z_1 Z_2}{Z_4 Z_3} + \frac{Z_2}{Z_4} + \frac{Z_1}{Z_2} + \frac{Z_1}{Z_3} + 1 - \frac{Z_1}{Z_2} \right) - \frac{Z_1}{Z_3}$$

$$= \frac{Z_1 Z_3 + Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_4 + Z_3 Z_4 - K Z_1 Z_4}{K Z_3 Z_4}$$

$$\frac{V_{out}}{V_{in}} = \frac{K Z_3 Z_4}{Z_1 Z_3 + Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_4 + Z_3 Z_4 - K Z_1 Z_4}$$

(c)

For Low pass filter: Z_3, Z_4 are capacitors and Z_1, Z_2 are resistors

$$\frac{V_{out}}{V_{in}} = \frac{K \frac{1}{sC_3} \frac{1}{sC_4}}{R_1 \frac{1}{sC_3} + R_1 R_2 + R_2 \frac{1}{sC_3} + R_1 \frac{1}{sC_4} + \frac{1}{sC_3} \frac{1}{sC_4} - K R_1 \frac{1}{sC_4}} \quad \times S^2 C_4 C_3$$

$$= \frac{K}{R_1 s C_4 + s^2 C_3 C_4 R_1 R_2 + R_2 s C_4 + R_1 s C_3 + 1 - K R_1 s C_3} \quad \div C_3 C_4 R_1 R_2$$

$$= \frac{\frac{K}{C_3 C_4 R_1 R_2}}{s^2 + s \frac{R_1 C_4 + R_2 C_4 + R_1 C_3 - K R_1 C_3}{C_3 C_4 R_1 R_2} + \frac{1}{C_3 C_4 R_1 R_2}} \quad C_3 = C_4 = C$$

$$T(S) = \frac{\frac{K}{C^2 R_1 R_2}}{s^2 + s \frac{R_2 + R_1(2-K)}{C R_1 R_2} + \frac{1}{C^2 R_1 R_2}}$$

$$\omega_o = \frac{1}{C\sqrt{R_1R_2}} \quad Q = \frac{\sqrt{R_1R_2}}{R_2 + R_1(2 - K)}$$

it is obvious that Q depends on R_1, R_2 , and k which is equal 1.58
 $\omega_o = 3500\text{rad/sec}$ depends on R_1, R_2 , and C .

So we will use R_1, R_2 to control Q and C to tune the ω_o .

$$Q = \frac{\sqrt{R_1R_2}}{R_2 + R_1(2 - K)}$$

$$0.707 = \frac{\sqrt{R_1R_2}}{R_2 + 0.42R_1}$$

$$0.707R_2 + 0.3R_1 = \sqrt{R_1R_2}$$

$$\text{let } R_1 = 10k\Omega$$

$$0.707R_2 + 3k = 100\sqrt{R_2}$$

$$(0.707R_2 + 3k)^2 = 10000R_2$$

$$0.5R_2^2 - 5859R_2 + 9 \times 10^6 = 0$$

$$R_2 \approx 9900\Omega \text{ or } R_2 \approx 1818\Omega$$

To find C :

$$C = \frac{1}{\omega_o\sqrt{R_1R_2}}$$

by substituting $R_1 = 10k\Omega, \omega_o = 3500\text{rad/sec}, R_2 = 9900/1818\Omega$



$$\therefore C = 287\mu F \text{ or } 670\mu F$$

To find R_i, R_F

$$R_F = (k - 1)R_i$$

$$\text{let } k = 1.58, R_i = 10k\Omega$$

$$R_F = 5.8k\Omega$$

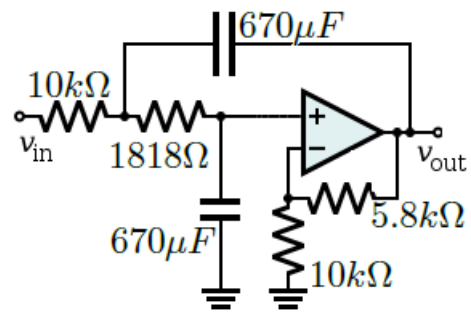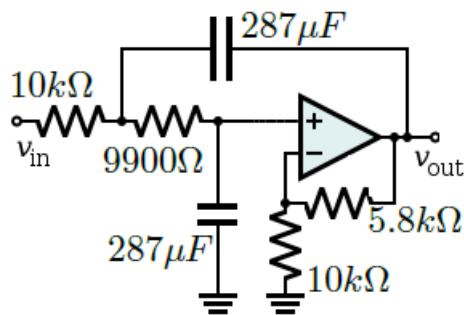

(d)

$$R_F = 5800 + 580 = 6380\Omega$$

$$K = 1 + \frac{R_F}{R_i} = 1.638$$

$$Q = \frac{\sqrt{R_1R_2}}{R_2 + R_1(2 - K)}$$

- $@R_2 = 9800 \Rightarrow Q = 0.735 \Rightarrow error = 4\%$
- $@R_2 = 1818 \Rightarrow Q = 0.784 \Rightarrow error = 10\%$

