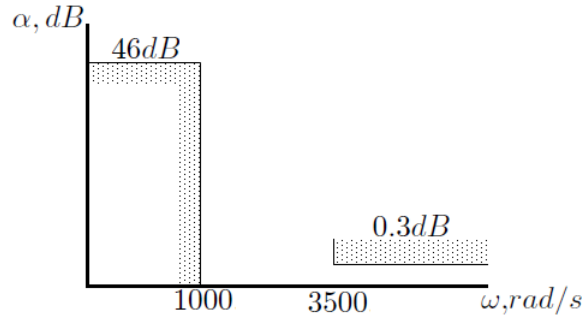




**ANSWER THE FOLLOWING QUESTIONS:**

1. Design a passive switched capacitor high pass filter with maximum flat response to meet at-  
 tenuation specification given in next Figure. [10 marks] [ $B_k, C_o$ ]  
 (a) The available capacitor is  $10\mu F$ .



Order	$R_S$	$C_1$ $a_1$	$L_2$ $a_2$	$C_3$ $a_3$	$L_4$ $a_4$	$C_5$ $a_5$	$L_6$ $a_6$	$C_7$ $a_7$
1	1.0	2.0000						
2	1.0	1.4142	1.4142					
3	1.0	1.0000	2.0000	1.0000				
4	1.0	0.7654	1.8478	1.8478	0.7654			
5	1.0	0.6180	1.6180	2.0000	1.6180	0.6180		
6	1.0	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176	
7	1.0	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450

**Solution:** Q1.(1) Find the normalized LPF

$$n = \frac{\log \frac{10^{0.1\alpha_{min}} - 1}{10^{0.1\alpha_{max}} - 1}}{2 \log \frac{\omega_s}{\omega_p}} = \frac{\log \frac{10^{4.6} - 1}{10^{0.03} - 1}}{2 \log \frac{3.5}{1}} = 5.28 \approx 6$$

(2) Pickup the values of N-LPF from ladder table

RS	C1	L2	C3	L4	C5	L6
1	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176

(3) Transform the values of N-LPF to N-HPF by  $C = \frac{1}{L}$  and  $L = \frac{1}{C}$

RS	L1	C2	L3	C4	L5	C6
1	1.931994	0.707114	0.517625	0.517625	0.707114	1.931994


(4) Available  $C = 10\mu F$ ,  $k_f = 3500$  and  $C = \frac{c_n}{k_m k_f} \Rightarrow k_m = \frac{c_n}{c k_f} = \frac{c_n}{10\mu \times 3500}$

RS	L1	C2	L3	C4	L5	C6
1	1.931994	0.707114	0.517625	0.517625	0.707114	1.931994
$k_m$		20.20324		14.78929		55.19982

(5) Select  $k_m = 55.2$


RS=RL	L1	C2	L3	C4	L5	C6
1	1.931993818	0.707114	0.517625	0.517625	0.707114	1.931994
55.2	31mH	3.66 $\mu F$	8mH	2.68 $\mu F$ $\phi_1 \phi_2$	11mH	10 $\mu F$

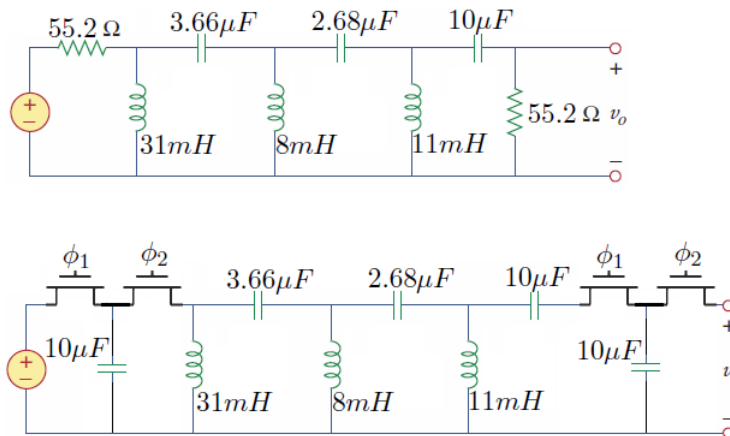(5) Switched Capacitor  $f_c = \frac{1}{RC} \Rightarrow f_c = \frac{1}{55.2 \times 10\mu} = 1811.6 Hz$ . we need non-overlap clock signals with frequency = 1811.6 Hz





2. Design a band pass filter with maximum flat response to meet attenuation specification given in next Figure. [10 marks] [ $C_o, A_m$ ]

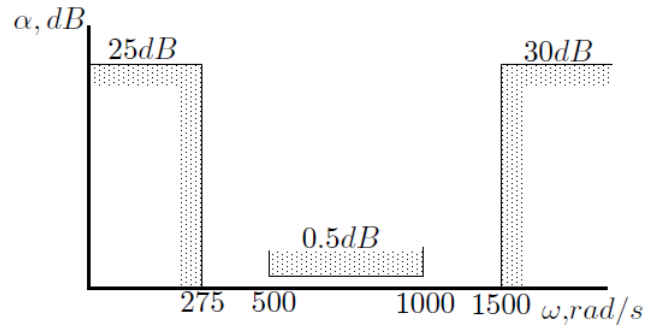(a) The available capacitor is  $0.1\mu F$ .



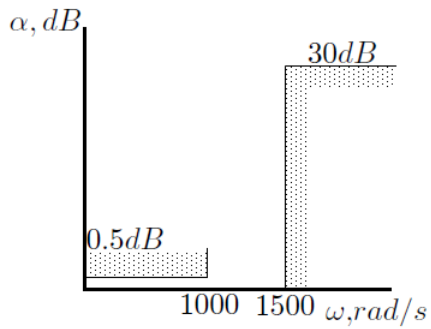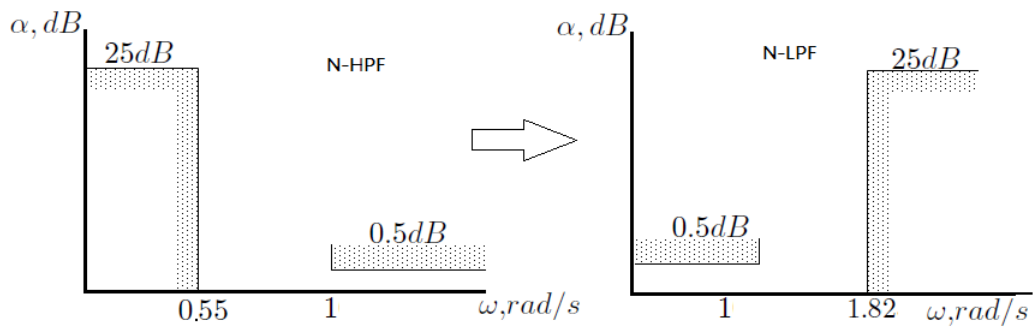**Solution:** Q1.(1) Find the normalized LPF for HPF



$$n_{NLPF} = \frac{\log \frac{10^{0.1\alpha_{min}} - 1}{10^{0.1\alpha_{max}} - 1}}{2 \log \frac{\omega_s}{\omega_p}} = \frac{\log \frac{10^{2.5} - 1}{10^{0.05} - 1}}{2 \log \frac{3.51.82}{1}} = 6.56 \approx 7$$

$$n_{LPF} = \frac{\log \frac{10^{0.1\alpha_{min}} - 1}{10^{0.1\alpha_{max}} - 1}}{2 \log \frac{\omega_s}{\omega_p}} = \frac{\log \frac{10^3 - 1}{10^{0.05} - 1}}{2 \log \frac{1500}{1000}} = 11.11 \approx 12$$

(2) Analysis of (N-LPF)  $\psi = \frac{180}{7} = 25.71$

$$\omega_B = \varepsilon^{\frac{-1}{n}} \omega_p = 1.17 \text{rad/sec}$$

$$R_1 = R_2 = \frac{1}{\omega_B C} = 0.85 \Omega \quad \text{assume } c = 1F$$

#	$\phi$	location	$\frac{1}{Q}$	$Q$	$k = 3 - \frac{1}{Q}$	$R_F = (k - 1)R$
pole 2,3	25.71	$-0.901 \pm j0.434$	1.802	0.55	1.198	0.15
pole 4,5	51.43	$-0.624 \pm j0.782$	1.248	0.8	1.752	0.56
pole 6,7	77.14	$-0.223 \pm j0.975$	0.446	2.24	2.554	1.15

(3) Transform the values of N-LPF to HPF. Available  $C = 0.1 \mu F$ ,  $k_f = 500$   
 $\therefore C = \frac{c_n}{k_m k_f} \Rightarrow k_m = \frac{c_n}{c k_f} = \frac{c_n}{0.1 \mu \times 500} = 20000$

$$C = 0.1 \mu F \quad R = 0.85 * 20000 = 17K \Omega \quad R_{F1} = 0.15 k_m = 3K \Omega$$

$$R_{F2} = 0.56 k_m = 11.2K \Omega \quad R_{F3} = 1.15 k_m = 23K \Omega$$

	non-Normalized (assume C=0.1uF)	Normalized (assume C= 1F)
$\omega_B$	430.189	0.8604
$R_n$		1.1623
$k_m$		20000.00
$R$	23245.5967	23246

(2) Analysis of (LPF)  $\psi = \frac{180}{12} = 15$

$$\omega_B = \varepsilon^{\frac{-1}{n}} \omega_p = 1091.68 \text{rad/sec}$$

$$R_1 = R_2 = \frac{1}{\omega_B C} = 9160.14 \Omega \quad \text{assume } c = 0.1 \mu F$$

#	$\phi$	location	$\frac{1}{Q}$	$Q$	$k = 3 - \frac{1}{Q}$	$R_F = (k - 1)R$
pole 1,2	7.50	$-0.991 \pm j0.13$	1.98	0.50	1.02	156.6
pole 3,4	22.50	$-0.924 \pm j0.382$	1.85	0.54	1.15	1393.15
pole 5,6	37.50	$-0.794 \pm j0.608$	1.59	0.63	1.41	3782.12
pole 7,8	52.50	$-0.609 \pm j0.793$	1.22	0.82	1.78	7160.85
pole 9,10	67.50	$-0.383 \pm j0.924$	0.77	1.30	2.23	11299.30
pole 11,12	82.50	$-0.131 \pm j0.991$	0.26	3.81	2.74	15915.75