

Second Order Analog Filters

Dr. M. Shiple

Shaping Circuits (EEC 242), 2015

Outline

Introduction

Second order Circuit

Low Pass Filter

Transfer Function

Frequency Response

High Pass Filter

Transfer Function

Frequency Response

Bandpass Filter

Transfer Function

Frequency response



Summary

Example

- Find the transfer function.

$$T(S) = \frac{Z_1}{Z_1 + Z_2}$$

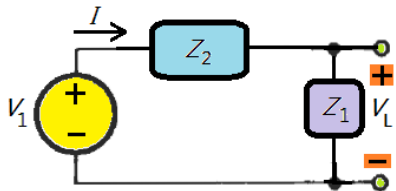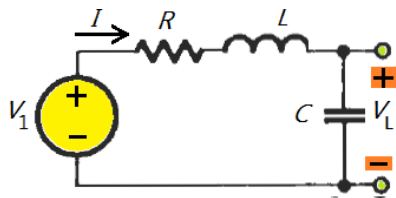Hint: By changing Z_1 , Numerator will take different forms and denominator will kept static.



cont.

$$H(S) = \frac{\frac{1}{S_c}}{R + SL + \frac{1}{S_c}}$$

$$SL + \frac{1}{S_c} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (1)$$

$$\text{Band width} = \beta = \frac{R}{L} \quad (2)$$

$$H(S) = \frac{1}{S^2 LC + SCR + 1} \quad \div LC$$

$$= \frac{\frac{1}{LC}}{S^2 + S\frac{R}{L} + \frac{1}{LC}}$$

$$= \frac{\omega_0^2}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$

$$\text{Quality factor} = Q = \frac{\omega_0}{\beta} \quad (3)$$

Magnitude and phase

- Replace ALL S by $j\omega$

$$H(S) = \frac{\omega_0^2}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$

$$T(j\omega) = \frac{\omega_0^2}{(j\omega)^2 + j\omega\frac{\omega_0}{Q} + \omega_0^2}$$

$$|T(j\omega)| = \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega\frac{\omega_0}{Q})^2}}$$

$$\phi(j\omega) = -\tan^{-1} \frac{\omega\frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$

Frequency response (FS) graph

$$|T(j\omega)| = \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega \frac{\omega_0}{Q})^2}}$$

1. @ $\omega = \text{zero} \Rightarrow$

$$|T(j\omega)| = \frac{\omega_0^2}{\sqrt{(\omega_0^2)^2}} = 1$$



2. @ $\omega = \omega_0 \Rightarrow$

$$|T(j\omega)| = \frac{\omega_0^2}{\sqrt{(\frac{\omega_0^2}{Q})^2}} = Q$$


$$\phi(j\omega) = -\tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$

1. @ $\omega = \text{zero} \Rightarrow \phi = 0$
2. @ $\omega = \omega_0 \Rightarrow \phi = -90$
3. @ $\omega = \infty \Rightarrow \phi = -180$

Effect of Q

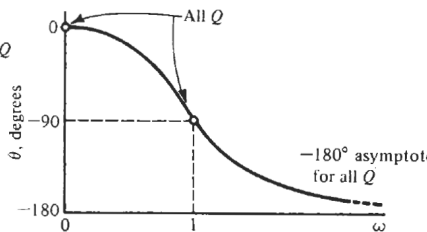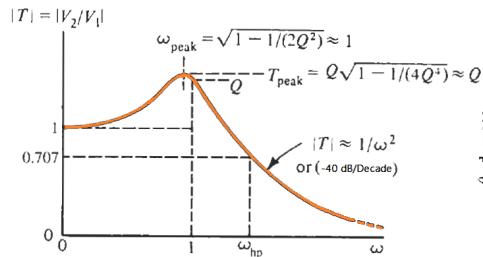


Effect of Q (Magnitude)

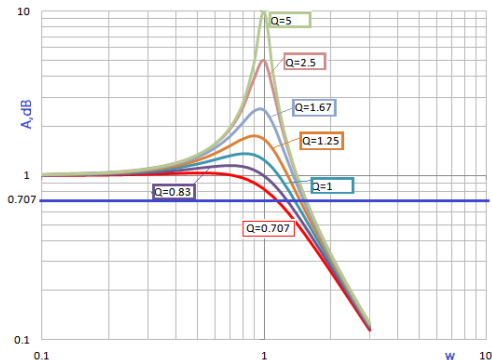

Hint: at $Q = 0.707$ (Flat magnitude) $\omega_0 = \omega_c$

Effect of Q (phase)

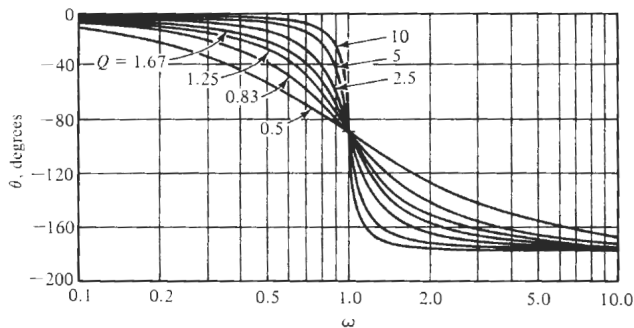



Hint: @ ALL Q $\phi = 0$ @ $\omega = 0$ and $\phi = -90$ @ $\omega = \omega_0$

Example

- Find the transfer function.

$$T(S) = \frac{Z_1}{Z_1 + Z_2}$$

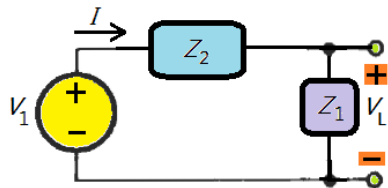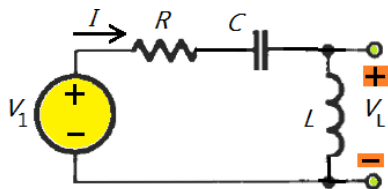Hint: By changing Z_1 , Numerator will take different forms and denominator will kept static.



cont.

$$H(S) = \frac{SL}{R + SL + \frac{1}{Sc}}$$

$$SL + \frac{1}{Sc} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (4)$$

$$\text{Band width} = \beta = \frac{R}{L} \quad (5)$$

$$H(S) = \frac{S^2 LC}{S^2 LC + SCR + 1} \quad \div LC$$

$$= \frac{S^2}{S^2 + S \frac{R}{L} + \frac{1}{LC}}$$

$$= \frac{S^2}{S^2 + S \frac{\omega_0}{Q} + \omega_0^2}$$

$$\text{Quality factor} = Q = \frac{\omega_0}{\beta} \quad (6)$$

Magnitude and phase

- ▶ Replace ALL S by $j\omega$

$$H(S) = \frac{s^2}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$

$$T(j\omega) = \frac{(j\omega)^2}{(j\omega)^2 + j\omega\frac{\omega_0}{Q} + \omega_0^2}$$

$$|T(j\omega)| = \frac{-\omega^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega\frac{\omega_0}{Q})^2}}$$

$$\phi(j\omega) = 180 - \tan^{-1} \frac{\omega\frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$



Frequency response (FS) graph

$$|T(j\omega)| = \frac{\omega^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega \frac{\omega_0}{Q})^2}}$$

1. @ $\omega = \text{zero} \Rightarrow$

$$|T(j\omega)| = 0$$

2. @ $\omega = \omega_0 \Rightarrow$

$$|T(j\omega)| = \frac{\omega_0^2}{\sqrt{(\frac{\omega_0^2}{Q})^2}} = Q$$


$$\phi(j\omega) = 180 - \tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$

1. @ $\omega = \text{zero} \Rightarrow \phi = 180$

2. @ $\omega = \omega_0 \Rightarrow \phi = 90$

3. @ $\omega = \infty \Rightarrow \phi = 0$

Effect of Q (Magnitude)

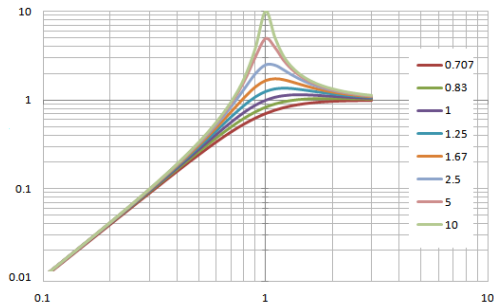


Hint: at $Q = 0.707$ (Flat magnitude) $\omega_0 = \omega_c$

Example

- ▶ Find the transfer function.
- ▶ compute magnitude, phase.

The BPF cct.:

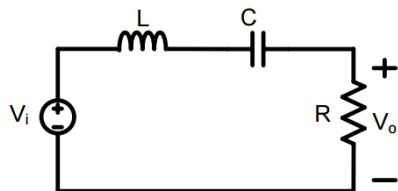

cont.


$$H(S) = \frac{R}{R + SL + \frac{1}{Sc}}$$

$$SL + \frac{1}{Sc} = 0$$

purely real

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

The BPF cct.:

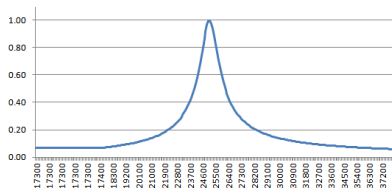


Max. and Min. Frequencies

The BPF cct.:

$$\begin{aligned}
 H(S) &= \frac{R}{R + SL + \frac{1}{Sc}} \\
 &= \frac{SCR}{S^2LC + SCR + 1} \\
 &= \frac{S\frac{R}{L}}{S^2 + S\frac{R}{L} + \frac{1}{LC}} \\
 &= \frac{S\frac{\omega_0}{Q}}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}
 \end{aligned}$$

× Sc
÷ LC

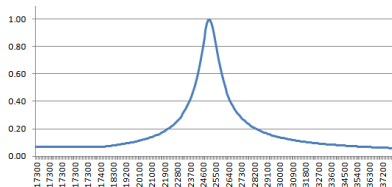

$$\phi(j\omega) = 90 - \tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$



Max. and Min. Frequencies


$$\omega_1 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\text{Band width} = \beta = \frac{R}{L}$$
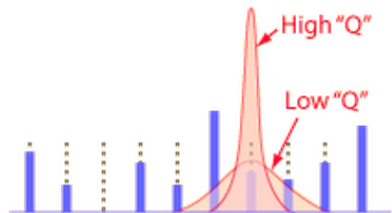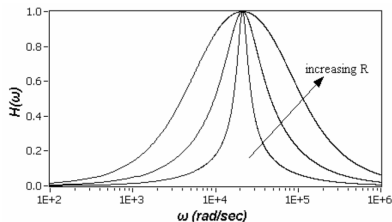
$$\text{Quality factor} = Q = \frac{\omega_0}{\beta}$$



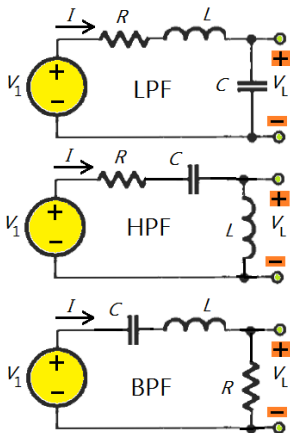

$$H(S) = \frac{\omega_0^2}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$

$$\phi(j\omega) = -\tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$

$$= \frac{s^2}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$

$$= 180 - \tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$

$$= \frac{S\frac{\omega_0}{Q}}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$

$$= 90 - \tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$