

# Second Order Biquadratic topologies

Dr. M. Shiple

Shaping Circuits (EEC 242), 2015

## 1 Introduction

## 2 Tow Thomas

- Circuit Diagram
- Mathematical Derivative

## 3 Sallen Key Topology

- Circuit Diagram
- Mathematical Derivative
- Disadvantages

## 4 Sallen Key designs


- Introduction
- Design 4
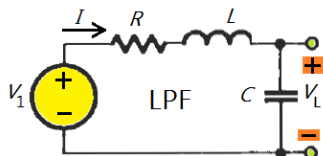
# Introduction

Thomas submitted  
his paper in 1 July 1969




Tow published his paper  
in December 1969




$$H(S) = \frac{\omega_0^2}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$
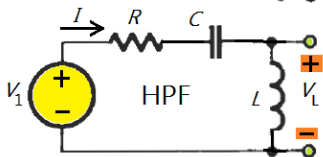
$$\phi(j\omega) = -\tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$



$$= \frac{S^2}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$
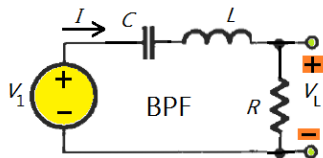
$$= 180 - \tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$



$$= \frac{S\frac{\omega_0}{Q}}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$



$$= 90 - \tan^{-1} \frac{\omega \frac{\omega_0}{Q}}{\omega_0^2 - \omega^2}$$
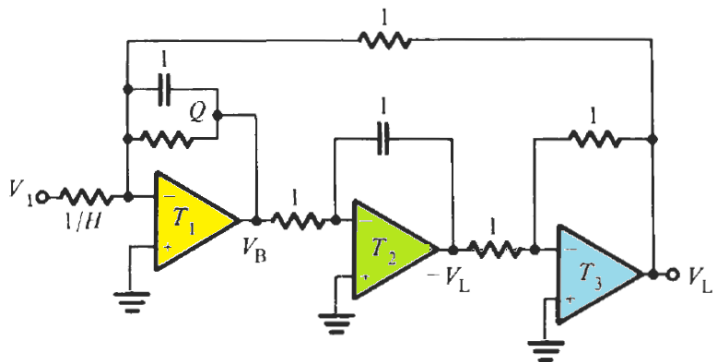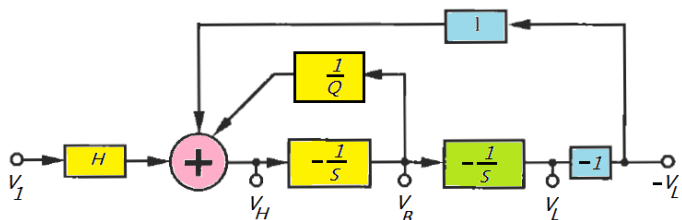
## Tow Thomas


Thomas submitted  
his paper in 1 July 1969



Tow published his paper  
in December 1969



## wiring diagram

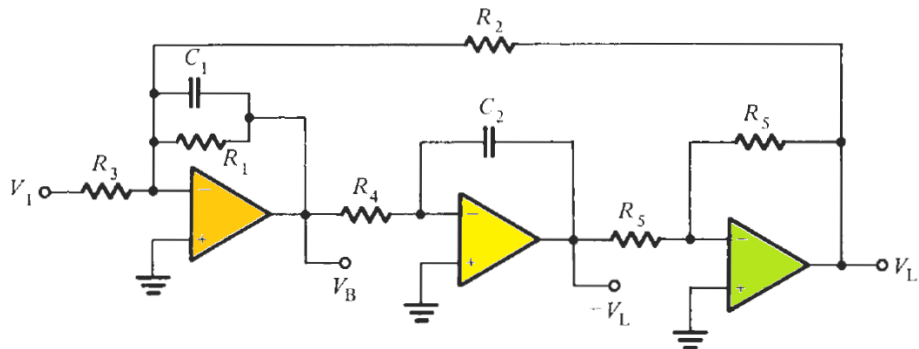

## Wiring Diagram:

$$V_B = -\frac{Z_F}{Z} V_1 - \frac{Z_F}{Z} V_L$$

$$Z_F = (Z_{C_1} \parallel Z_{R_1}) = \frac{R_1}{1 + SC_1 R_1}$$

$$(1 + SC_1 R_1) V_B = -\frac{R_1}{R_3} V_1 - \frac{R_1}{R_2} V_L$$



$$\therefore V_L = \frac{1}{SC_2 R_4} V_B$$

$$(1 + SC_1 R_1 + \frac{R_1}{SC_2 R_2 R_4}) V_B = -\frac{R_1}{R_3} V_1$$

$$\frac{V_B}{V_1} = \frac{-\frac{R_1}{R_3} SC_2 R_2 R_4}{SC_2 R_2 R_4 + S^2 C_1 C_2 R_1 R_2 R_4 + R_1}$$

$$\frac{V_B}{V_1} = \frac{\left(-\frac{R_1}{R_3}\right) S \frac{1}{C_1 R_1}}{S^2 + S \frac{1}{C_1 R_1} + \frac{1}{C_1 C_2 R_2 R_4}}$$
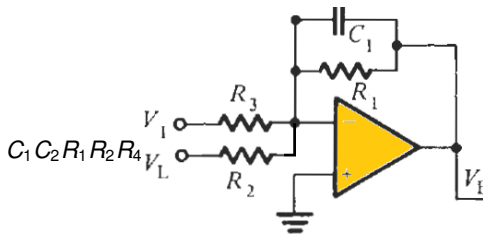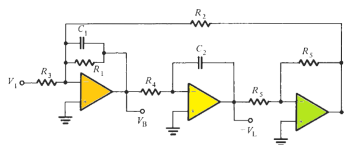
$$\therefore \omega_0 = \frac{1}{\sqrt{C_1 C_2 R_2 R_4}} \text{ and } Q = \frac{R_1}{\sqrt{R_2 R_4}} \sqrt{\frac{C_1}{C_2}}$$






# Sallen Key Topology



E. L. Key

R. P. Sallen

## wiring diagram

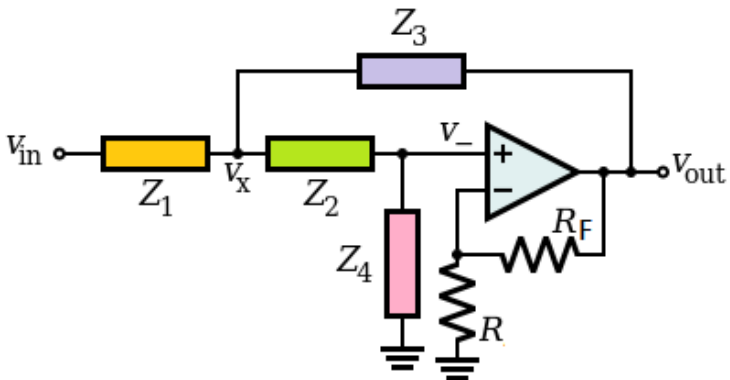

## KCL:


$$V^-(1 + \frac{R_F}{R}) = V^-K = V_{out}$$

 $V_x :$ 

$$\frac{V_{in} - V_x}{Z_1} = \frac{V_x - V^-}{Z_2} + \frac{V_x - V_{out}}{Z_3}$$

$$\frac{V_x - V^-}{Z_2} = \frac{V^-}{Z_4}$$
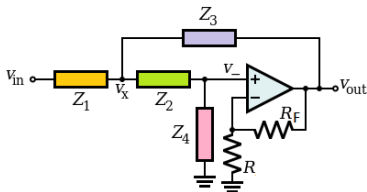
$$\therefore V_x = V^- \left( \frac{Z_2}{Z_4} + 1 \right)$$



$$\frac{V_{out}}{V_{in}} = \frac{KZ_3Z_4}{Z_1Z_3 + Z_1Z_2 + Z_2Z_3 + Z_1Z_4 + Z_3Z_4 - KZ_1Z_4}$$

(1)

## Cont.


 $V_x :$ 

$$V_{in} - V_x = V_x \frac{Z_1}{Z_2} - V^- \frac{Z_1}{Z_2} + V_x \frac{Z_1}{Z_3} - V_{out} \frac{Z_1}{Z_3}$$

$$V_{in} = V_x \left( \frac{Z_1}{Z_2} + \frac{Z_1}{Z_3} + 1 \right) - V^- \frac{Z_1}{Z_2} - V_{out} \frac{Z_1}{Z_3}$$

$$V_{in} = \frac{V_{out}}{K} \left( \frac{Z_2}{Z_4} + 1 \right) \left( \frac{Z_1}{Z_2} + \frac{Z_1}{Z_3} + 1 \right) - \frac{V_{out}}{K} \frac{Z_1}{Z_2} - V_{out} \frac{Z_1}{Z_3}$$
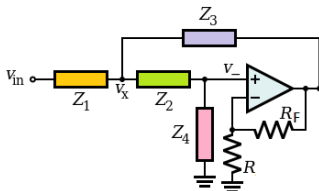
$$\begin{aligned} \frac{V_{in}}{V_{out}} &= \frac{1}{K} \left( \frac{Z_1}{Z_4} + \frac{Z_1 Z_2}{Z_4 Z_3} + \frac{Z_2}{Z_4} + \frac{Z_1}{Z_2} + \frac{Z_1}{Z_3} + 1 - \frac{Z_1}{Z_2} \right) - \frac{Z_1}{Z_3} \\ &= \frac{Z_1 Z_3 + Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_4 + Z_3 Z_4 - K Z_1 Z_4}{K Z_3 Z_4} \end{aligned}$$



# Low Pass Filter

$$\frac{V_{out}}{V_{in}} = \frac{KZ_3Z_4}{Z_1Z_3 + Z_1Z_2 + Z_2Z_3 + Z_1Z_4 + Z_3Z_4 - KZ_1Z_4}$$


$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{K \frac{1}{sC_3} \frac{1}{sC_4}}{R_1 \frac{1}{sC_3} + R_1R_2 + R_2 \frac{1}{sC_3} + R_1 \frac{1}{sC_4} + \frac{1}{sC_3} \frac{1}{sC_4} - KR_1 \frac{1}{sC_4}} && \times s^2 C_4 C_3 \\ &= \frac{K}{R_1 s C_4 + s^2 C_3 C_4 R_1 R_2 + R_2 s C_4 + R_1 s C_3 + 1 - K R_1 s C_3} && \div C_3 C_4 R_1 R_2 \\ &= \frac{\frac{K}{C_3 C_4 R_1 R_2}}{s^2 + s \frac{R_1 C_4 + R_2 C_4 + R_1 C_3 - K R_1 C_3}{C_3 C_4 R_1 R_2} + \frac{1}{C_3 C_4 R_1 R_2}} && C_3 = C_4 = C \end{aligned}$$

# Low Pass Filter

$$T(S) = \frac{\frac{K}{C^2 R_1 R_2}}{s^2 + S \frac{R_2 + R_1(2-K)}{C R_1 R_2} + \frac{1}{C^2 R_1 R_2}}$$

$$\omega_0 = \frac{1}{C\sqrt{R_1 R_2}}, Q = \frac{\sqrt{R_1 R_2}}{R_2 + R_1(2-K)} \quad R_1 = R_2 = R$$
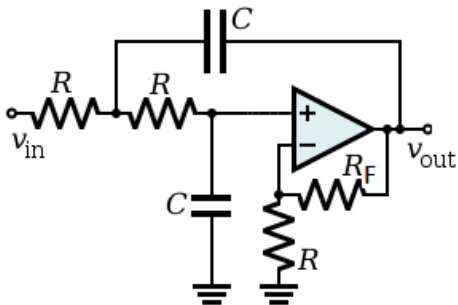
$$\omega_0 = \frac{1}{RC}, \quad Q = \frac{1}{(3-K)}, \quad K = 1 + \frac{R_F}{R}$$



$$\omega_0 = \frac{1}{RC}$$

$$Q = \frac{1}{(3 - K)}$$

$$K = 1 + \frac{R_F}{R}$$

## Sensitivity

- Sensitivity:

$$Q = \frac{1}{(3 - K)}$$

$$\frac{dQ(K)}{dK} = \frac{1}{(3 - K)^2} = Q^2$$

$$\therefore dQ(K) = Q^2 dK$$

$$\frac{dQ(K)}{Q} = Q dK \quad \times \frac{K}{K}$$

$$\frac{dQ(K)}{Q} = KQ \frac{dK}{K}$$

- Gain adjustment:

$$K = 3 - \frac{1}{Q}$$



## Sallan Key designs



E. L. Key

R. P. Sallen

## Quality Factor (Q) or Damping Ratio( $\zeta$ )

$$Q = \frac{1}{2\zeta}$$


$$H(S) = \frac{\omega_0^2}{S^2 + \frac{\omega_0}{Q}S + \omega_0^2} = \frac{\omega_0^2}{S^2 + 2\zeta\omega_0 S + \omega_0^2}$$

$$S_{1,2} = -\zeta\omega_0 \pm \omega_0\sqrt{\zeta^2 - 1} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$S_{1,2} =$$

$\zeta > 1$ or $Q < 0.5$ ,	Distinct real roots	Overdamped 1 <sup>st</sup> order
$\zeta = 1$ or $Q = 0.5$ ,	Identical real roots	Critically damped
$\zeta < 1$ or $Q > 0.5$ ,	Distinct complex roots	Underdamped
$\zeta = 0$ or $Q = \infty$ ,	Oscillator	


## Root Locus of Q

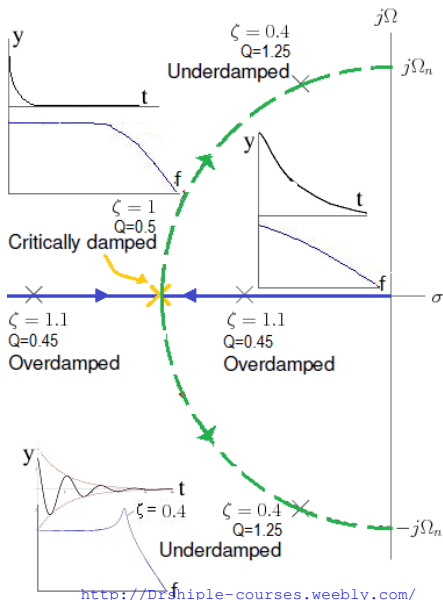
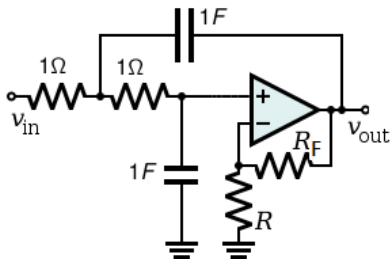
## Design 1/Simplification 1: Set Filter Components Equal

Features:

- 1  $1 < K < 3$
- 2 Avoid  $k=1 \Rightarrow Q = 0.5$
- 3 Avoid  $k=3 \Rightarrow Q = \infty$
- 4 ALL components are = 1,  
 $R_1 = R_2 = 1\Omega \quad C_3 = C_4 = 1F$
- 5 Very sensitive.



$$T(S) = \frac{k \frac{1}{R_1 R_2 C_3 C_4}}{S^2 + \left[ \frac{1}{R_1 C_3} + \frac{1}{R_2 C_3} + \frac{1}{R_2 C_4} - \frac{k}{R_2 C_4} \right] S + \frac{1}{R_1 R_2 C_3 C_4}}$$

assume  $R_1 = R_2 = C_3 = C_4 = \omega_0 = 1$


$$= \frac{k}{S^2 + [3 - K]S + 1}$$

$$K = 3 - \frac{1}{Q} = 1 + \frac{R_a}{R_b}$$
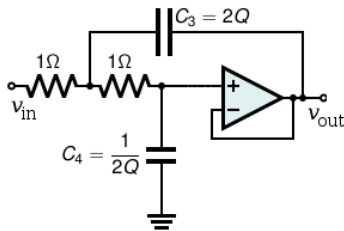
## Design 2/Simplification 2:Set Filter Components as Ratios and Gain = 1

Features:

- 1  $k=1$
- 2  $Q$  is independent on  $K$ .
- 3  $R_1 = R_2 = 1\Omega$  and  $C_3 = \frac{1}{C_4}$



$$T(S) = \frac{k \frac{1}{R_1 R_2 C_3 C_4}}{S^2 + \left[ \frac{1}{R_1 C_3} + \frac{1}{R_2 C_3} + \frac{1}{R_2 C_4} - \frac{k}{R_2 C_4} \right] S + \frac{1}{R_1 R_2 C_3 C_4}}$$


assume  $R_1 = R_2 = 1\Omega$  and  $C_3 = \frac{1}{C_4}$

$$= \frac{1}{S^2 + \frac{2}{C_3} S + 1} \quad \Rightarrow \quad C_3 = 2Q \quad C_4 = \frac{1}{2Q}$$
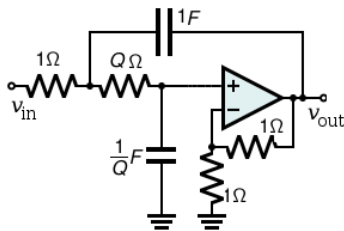
## Design 3/Simplification 3: Set Filter Components as Ratios and Gain = 2

Features:

- 1  $k=2 \Rightarrow R_a = R_b = 1\Omega$
- 2  $Q$  is independent on  $K$ .
- 3  $R_1 = 1\Omega$ ,  $C_3 = 1F$  and  $R_2 = \frac{1}{C_4}$



$$T(S) = \frac{k \frac{1}{R_1 R_2 C_3 C_4}}{S^2 + \left[ \frac{1}{R_1 C_3} + \frac{1}{R_2 C_3} + \frac{1}{R_2 C_4} - \frac{k}{R_2 C_4} \right] S + \frac{1}{R_1 R_2 C_3 C_4}}$$


assume  $R_1 = 1\Omega$  and  $R_2 = \frac{1}{C_4}$

$$= \frac{2}{S^2 + \frac{1}{R_2} S + 1} \Rightarrow R_2 = Q = \frac{1}{C_4}$$
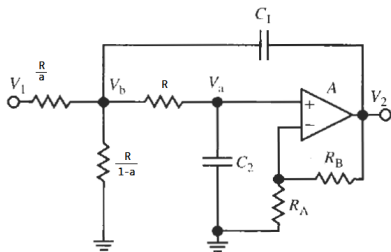
## Resistive Gain Reduction

Features:

- 1 could be applied to all simplifications.




$$R_1 = \left( \frac{R}{a} \parallel \frac{R}{1-a} \right)$$
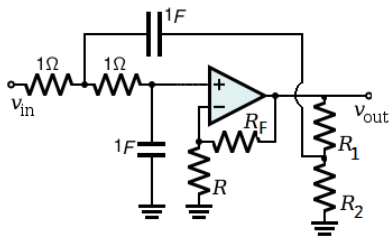
## Resistive Gain Enhancement

Features:

- 1 ALL components are = 1,  
 $R_1 = R_2 = 1\Omega$   $C_3 = C_4 = 1F$



$$T(S) = \frac{k \frac{1}{R_1 R_2 C_3 C_4}}{S^2 + \left[ \frac{1}{R_1 C_3} + \frac{1}{R_2 C_3} + \frac{1}{R_2 C_4} - \frac{k k_d}{R_2 C_4} \right] S + \frac{1}{R_1 R_2 C_3 C_4}}$$

assume  $R_1 = R_2 = C_3 = C_4 = \omega_0 = 1$

$$= \frac{k}{S^2 + [3 - K K_d] S + 1} \Rightarrow K_d = \frac{R_2}{R_1 + R_2}$$

$$K K_d = 3 - \frac{1}{Q}$$