

Scaling and Transformation

Dr. M. Shiple

Shaping Circuits (EEC 242), 2015

1 **Scaling**

- Magnitude Scaling (Impedance Scaling)
- Frequency Scaling
- Full Normalization
- Normalization Examples

2 **Frequency Transformation**

- Lowpass-to-Highpass Transformation
- Examples
- Lowpass-to-Bandpass Transformation

3 **Ladder filter**

- Filter Transformation

Section 1

Scaling


Subsection 1

Magnitude Scaling (Impedance Scaling)

Impedance Scaling

Magnitude scaling

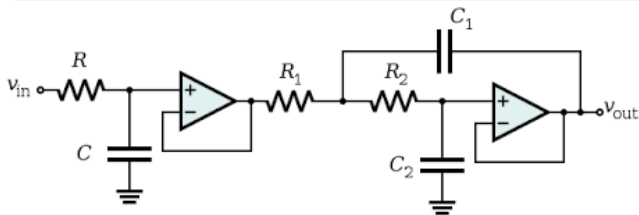is the process of increasing all impedances in a network by a factor, the frequency response remaining unchanged.



R	R ₁	R ₂	α_{\max}	ω_c	C	C ₁	C ₂

$$10^3 \cdot 10^3 \cdot 10^3 \cdot 10^2 \cdot 10 \cdot 10^3 = 10^{14}$$

The impedance of passive components

$$Z_R = R \quad Z_L = SL \quad Z_C = \frac{1}{SC}$$

Let the frequency remain constant

$$Z'_R = K_m R \quad Z'_L = K_m SL \quad Z'_C = K_m \frac{1}{SC}$$

Therefore :

$$R' = K_m R \quad L' = k_m L \quad C' = \frac{C}{K_m}$$

Test the frequency:

$$\omega'_o = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{k_m L \frac{C}{K_m}}}$$

$$\omega'_o = \frac{1}{\sqrt{LC}} = \omega_o$$

Subsection 2

Frequency Scaling

Frequency Scaling

is the process of shifting the frequency response of a network up or down the frequency axis while leaving the impedance the same.



The impedance of passive components

$$Z_R = R \text{ (not affected by frequency)} \quad Z_L = j\omega L \quad Z_C = \frac{1}{j\omega C}$$

$$Z'_L = j(\omega K_f)L \quad Z'_C = \frac{1}{j(\omega K_f)C}$$

Therefore :

$$R' = R \quad L' = \frac{L}{K_f} \quad C' = \frac{C}{K_f}$$

Test the frequency:

$$\omega'_o = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\frac{L}{K_f} \frac{C}{K_f}}}$$

$$\omega'_o = \frac{K_f}{\sqrt{LC}} = K_f \omega_o$$

Subsection 3

Full Normalization

Magnitude and Frequency Scaling

The general normalize rule:

$$R = \frac{R}{k_m} \quad L = \frac{K_f}{K_m} L' \quad C = K_m K_f C'$$

The general De-normalize rule:


$$R' = k_m R \quad L' = \frac{K_m}{K_f} L \quad C' = \frac{1}{K_m K_f} C$$

Subsection 4

Normalization Examples

Magnitude and Frequency Scaling

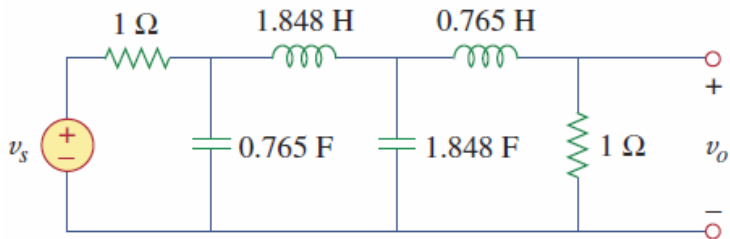Q1: A fourth order lowpass filter is shown. The filter is designed such that the cutoff frequency $\omega_o = 1 \text{ rad/s}$. Scale the circuit for a cutoff frequency of 50 kHz using $10 \text{ k}\Omega$ resistors.



Magnitude and Frequency Scaling

Q1: A fourth order lowpass filter is shown. The filter is designed such that the cutoff frequency $\omega_o = 1 \text{ rad/s}$. Scale the circuit for a cutoff frequency of 50 kHz using $10 \text{ k}\Omega$ resistors.

$$\omega'_c = 2\pi(50\text{k}) = 100\text{k}\pi$$

$$k_f = \frac{\omega'_c}{\omega_o} = \frac{100\text{k}\pi}{1} = \pi \times 10^5 \quad k_m = \frac{10\text{k}}{1} = 10\text{k}$$

Therefore : $R' = k_m R = 10\text{k}\Omega$


$$L'_1 = \frac{K_m}{k_f} L = \frac{10^4}{\pi \times 10^5} (1.848) = 58.82\text{mH}$$

$$L'_2 = \frac{10^4}{\pi \times 10^5} (0.765) = 24.35\text{mH}$$

$$C'_1 = \frac{1}{K_f K_m} C = \frac{1}{\pi \times 10^9} 0.765 = 243.5\text{pF}$$

$$C'_2 = \frac{1}{K_f K_m} C = \frac{1}{\pi \times 10^9} 1.848 = 588.2\text{pF}$$

Example 1

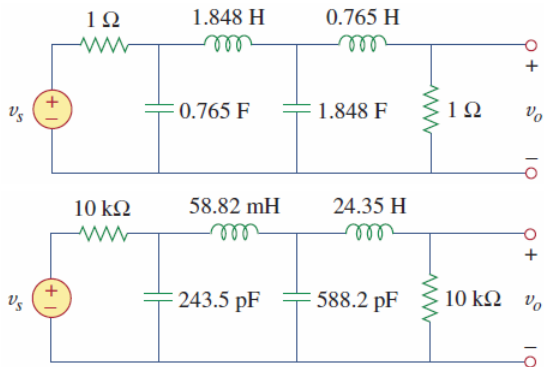


Section 2

Frequency Transformation

Subsection 1

Lowpass-to-Highpass Transformation

LP-HP procedure:




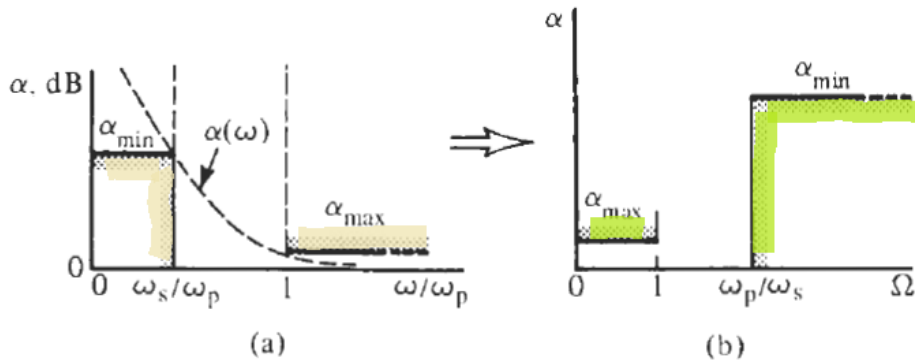


- 1 Normalize the frequency axis of HPF by passband corner frequency ω_p .
- 2 Use $\Omega = \frac{1}{\omega}$ and consider the attenuation values.
- 3 Find the degree n of LPF.
- 4 Compute the LPF transfer function $T_L(S)$.
- 5 Compute the HPF transfer function $T_H(S)$ by replacing S by $\frac{1}{S}$.
- 6 Realize $T_H(S)$.


Subsection 2

Examples

Example 1:

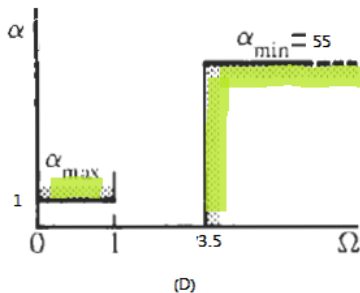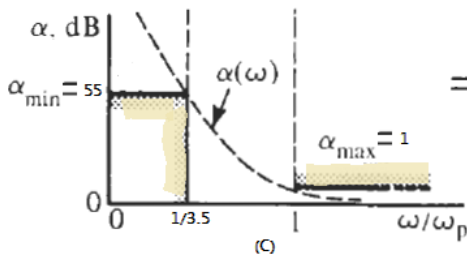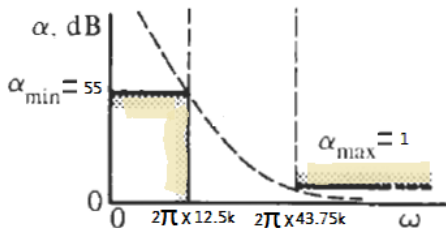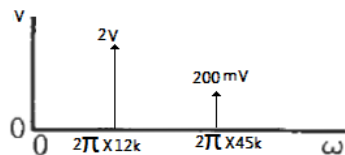

Example 1:

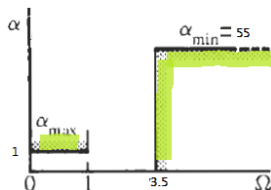

3

$$n = \frac{\log \left(\frac{10^{\frac{\alpha_{min}}{10}} - 1}{10^{\frac{\alpha_{max}}{10}} - 1} \right)}{2 \log \frac{\omega_S}{\omega_P}} = 5.5 \approx 6 \quad (1)$$

$$\epsilon = \sqrt{10^{\frac{\alpha_{max}}{10}} - 1} = 0.51 \quad (2)$$

$$\omega_B = \epsilon^{-\frac{1}{n}} \omega_P = 1.12 \text{ rad/sec} \quad (3)$$


$$R_1 = R_2 = \frac{1}{\omega_B C} = 0.89 \Omega \quad \text{assume } c = 1F \quad (4)$$

Example 1 (Cont.):

4

$$T_L(S) = \frac{1}{(S^2 + 1.93S + 1)(S^2 + 1.41S + 1)(S^2 + 0.52S + 1)}$$

$\frac{1}{Q}$	Q_n	K	$R_F = (k - 1)R$
1.93	0.518135	1.07	0.0623
1.41	0.70922	1.59	0.5251
0.52	1.923077	2.48	1.3172

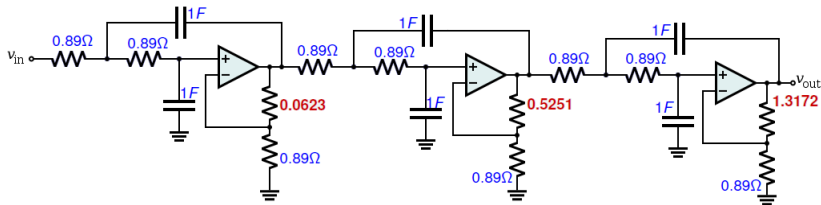


Example 1 (Cont.):

5

$$T_H(S) = \frac{1}{(S^{-2} + 1.93S^{-1} + 1)(S^{-2} + 1.41S^{-1} + 1)(S^{-2} + 0.52S^{-1} + 1)} \times (S^2 S^2 S^2)$$


$$T_H(S) = \frac{S^6}{(1 + 1.93S + S^2)(S^{-2} + 1.41S + S^2)(S^{-2} + 0.52S + S^2)}$$

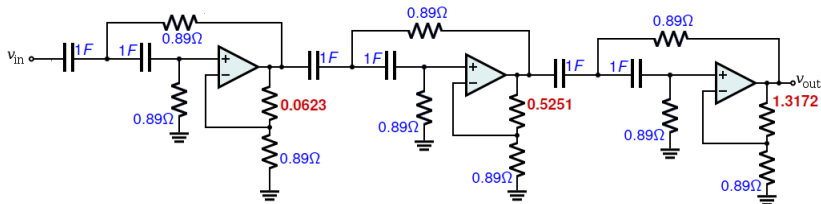6 Realize $T_H(S)$.

$$R = k_m R \Rightarrow R = 8.9K\Omega \quad R_{f1} = 623\Omega \quad R_{f2} = 5.25K\Omega \quad R_{f1} = 13.17k\Omega \quad \therefore K_M = 10K$$

$$C = \frac{1}{K_m K_F} C = \frac{1}{10k \cdot 2\pi 43.75k} = 3.64\mu F$$


Example 1 (Cont.):

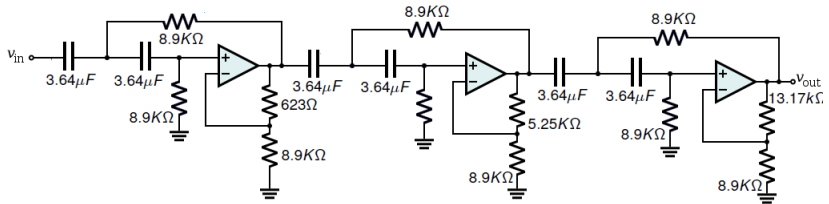

Subsection 3


Lowpass-to-Bandpass Transformation

LP-BP procedure:

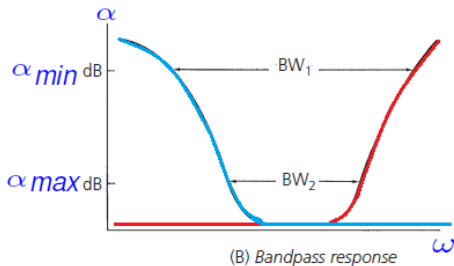

- 1 Discriminate between HPF and LPF.
- 2 Normalize the frequency axis of HPF by passband corner frequency ω_p .
- 3 Use $\Omega = \frac{1}{\omega}$ and consider the attenuation values.
- 4 Find the degree n of LPF.
- 5 Compute the LPF transfer function $T_L(S)$.
- 6 Compute the HPF transfer function $T_H(S)$ by replacing S by $\frac{1}{S}$.
- 7 Realize $T_H(S)$.

Example 1:

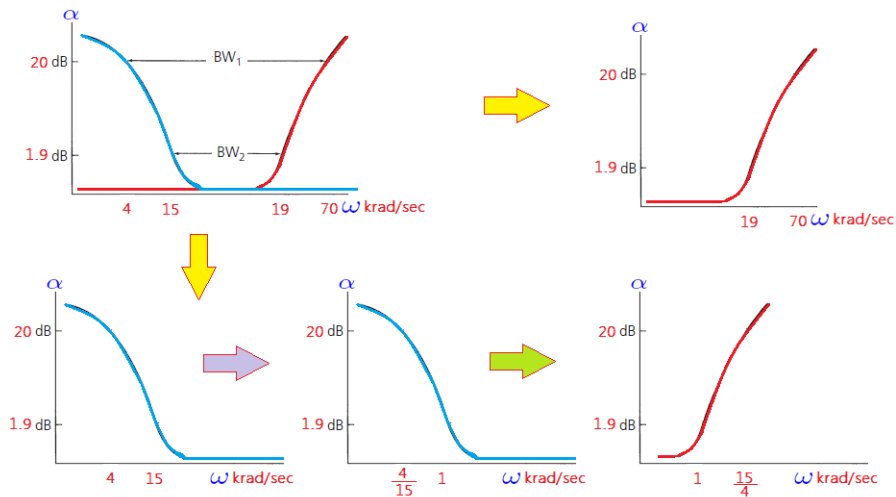

Section 3

Ladder filter

Normalized Filters




Order	R_S	C_1 a_1	L_2 a_2	C_3 a_3	L_4 a_4	C_5 a_5	L_6 a_6	C_7 a_7
1	1.0	2.0000						
2	1.0	1.4142	1.4142					
3	1.0	1.0000	2.0000	1.0000				
4	1.0	0.7654	1.8478	1.8478	0.7654			
5	1.0	0.6180	1.6180	2.0000	1.6180	0.6180		
6	1.0	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176	
7	1.0	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450

Normalized Filters

Table: Filter Table

Order	RS	C1	L2	C3	L4
3	1	1	2	1	

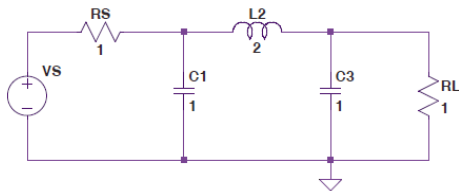


Examples

Design a Butterworth LPF of order $n = 3$ with $-3dB$ frequency $f_r = 1kHz$ and $R_S = R_L = 600\Omega$.

Solution: We find that $\omega_r = 2\pi 1000 = 6283.2rad/s$.

Order	k_m	k_f	Rule	Realization
RS	600	6283.2	$k_m R_n$	600Ω
C1	600	6283.2	$\frac{1}{k_m k_f} L_n$	$265.25nF$
L2	600	6283.2	$\frac{k_m}{k_f} L_n$	$191mH$
C3	600	6283.2	$\frac{1}{k_m k_f} L_n$	$265.25nF$
RL	600	6283.2	$k_m R_n$	600Ω

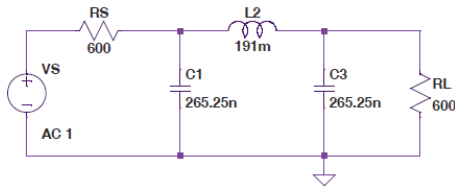

Subsection 1

Filter Transformation

LPF to HPF


The substitution $s = \frac{1}{s}$ affects the C and L elements of the LPF as follows:

$$Z_C = \frac{1}{sC} \Rightarrow Z_C = \frac{1}{\frac{1}{s}C} = s\frac{1}{C} \quad (C \Rightarrow L = \frac{1}{C})$$

$$Z_L = sL \Rightarrow Z_C = \frac{1}{s}L = \frac{L}{s} \quad (L \Rightarrow C = \frac{1}{L})$$

LPF to BPF

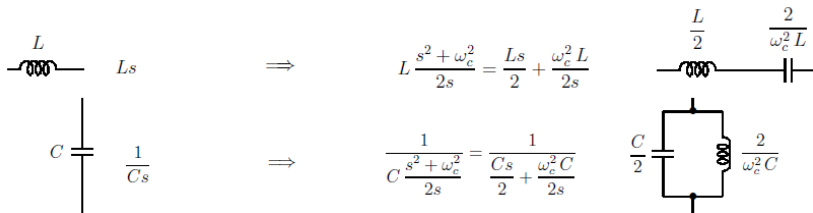The substitution $s = \frac{s^2 + \omega_c^2}{2s}$ affects the C and L elements of the LPF as follows:



Example

Example: Butterworth BPF of order $n = 6$ with bandwidth 100 kHz, center frequency $f_c = 1\text{ MHz}$, and $R_S = R_L = 50 \Omega$. Start from a normalized Butterworth LPF of order $n = 3$ with $C_1 = C_3 = 1\text{ F}$ and $L_2 = 2\text{ H}$. Then use frequency and impedance scaling factors

