

# Component Converter

Dr. M. Shiple

Shaping Circuits (EEC 242), 2015

### 1 Switched Capacitor Filters (SC-filters)

- Introduction
- MOSFET
- Switched Capacitor
- Challenges
- Implementation

### 2 Generalized impedance Converter (GIC)


## Section 1

# Switched Capacitor Filters (SC-filters)


## Subsection 1

# Introduction


## What are the wafer and Die?

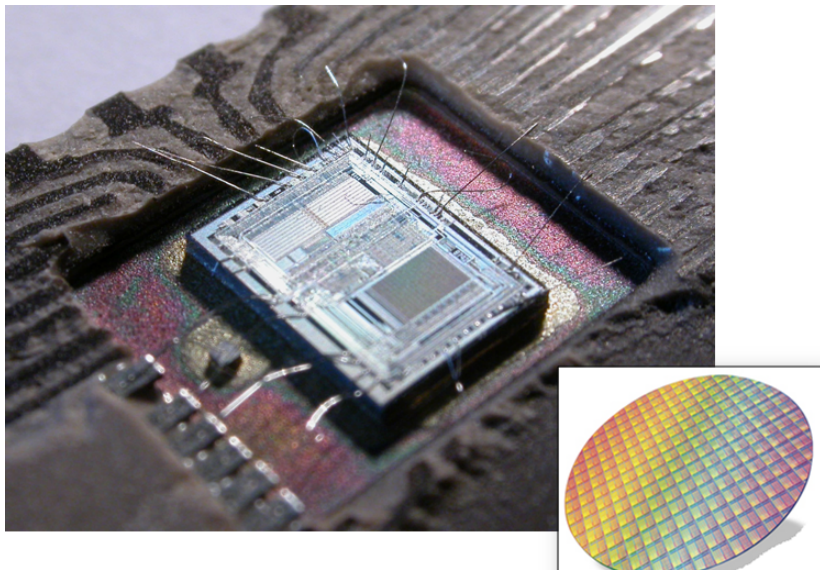

## 7555 is a CMOS version of 555 timer


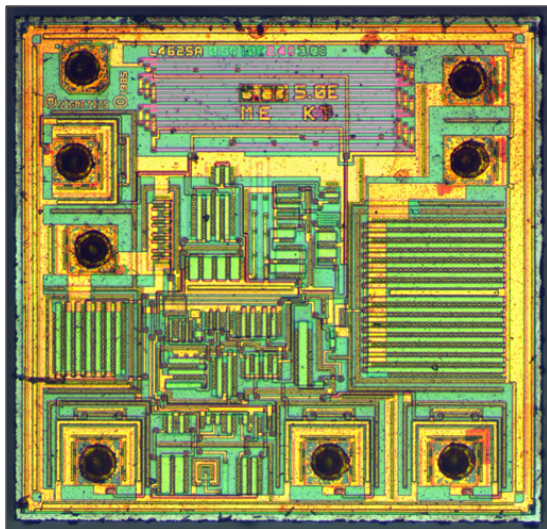


## Resistor vs. Transistor vs. Pad

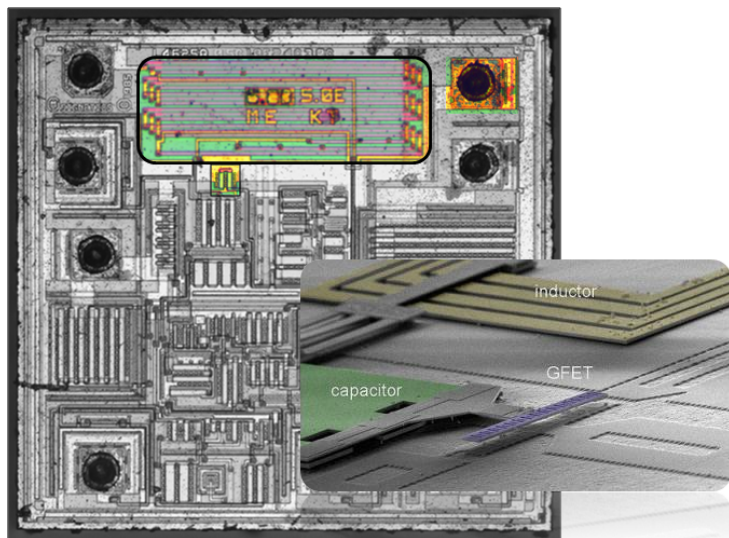
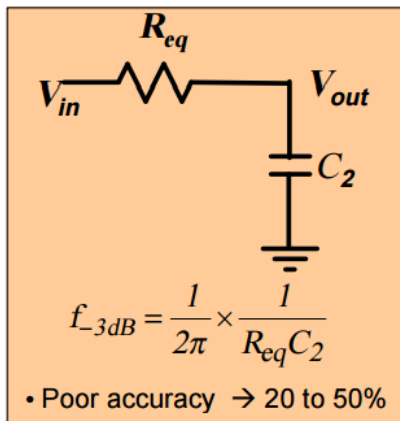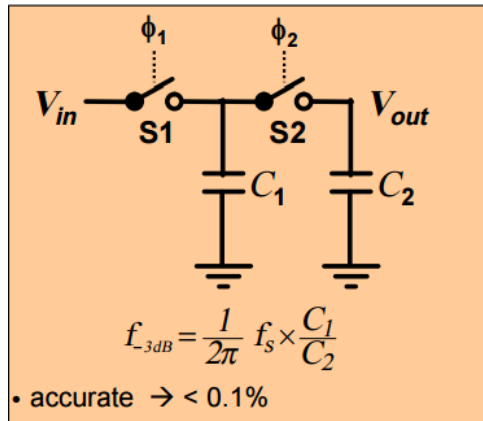
## Switched Capacitor Features

- Suitable for IC design.
- inherent corner frequency accuracy (tight tolerance less than 0.1%).
- Very low power consumption.







## Subsection 2

# MOSFET

## Enhancement Type
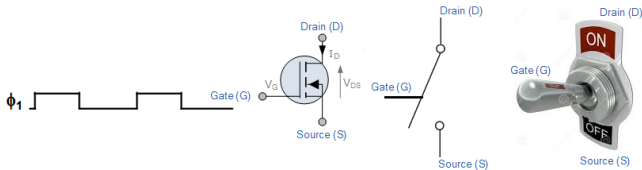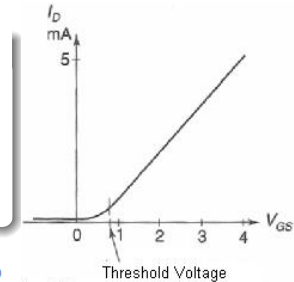
### Operation

- The enhancement MOSFET is on at  $V_{GS} > V_T$ .
- The enhancement MOSFET is off at  $V_{GS} < V_T$ .



## Subsection 3

# Switched Capacitor

## Equivalent resistor

@  $\phi_1$  (Charging):

$$q_1 = CV_{in}$$

@  $\phi_2$  (Discharging):

$$q_2 = CV_{out}$$

$$\Delta q = C(V_{in} - V_{out}) \quad \div T$$



$$i \approx \frac{\Delta q}{T} = \Delta q f_c = Cf_c(V_{in} - V_{out})$$

$$R_{eq} = \frac{(V_{in} - V_{out})}{i} = \frac{1}{Cf_c}$$



## Subsection 4

# Challenges



## Parasitic Capacitance of the MOSFET

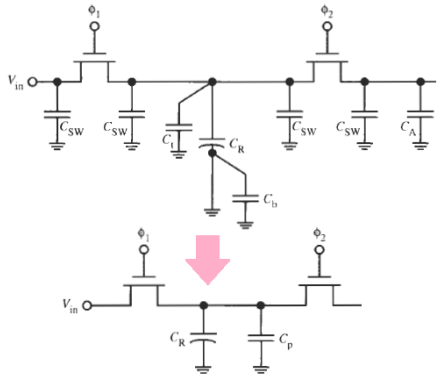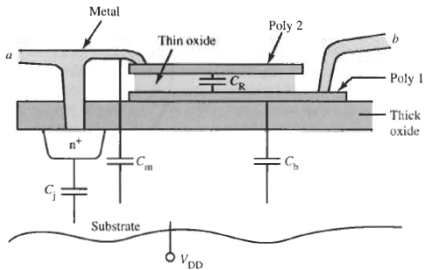

## Parasitic insensitive circuits

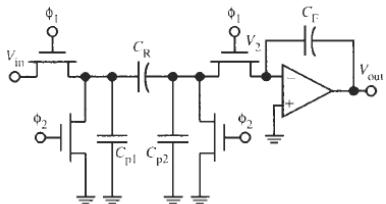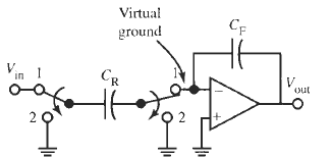

(a)


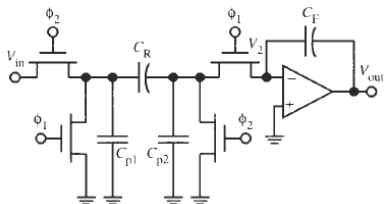
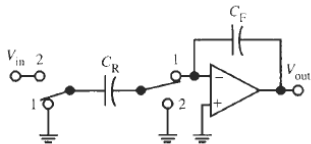


## Subsection 5

# Implementation




## Redundant switches

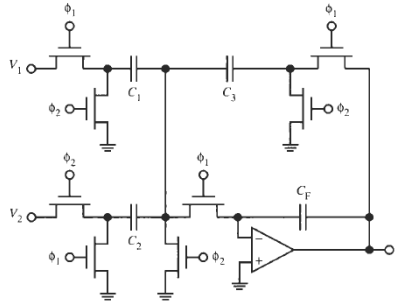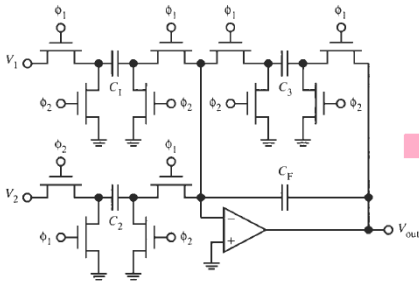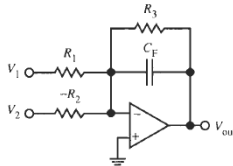

## Section 2

# Generalized impedance Converter (GIC)

## GIC circuit

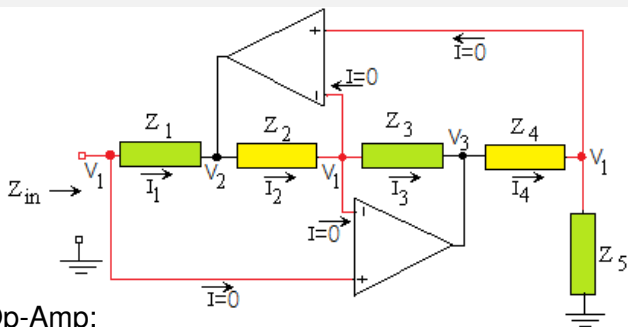

For ideal Op-Amp:

$$V_o = A(V^+ - V^-)$$

$$A = \infty$$

$$V^- = V^+$$

$$I_2 = I_3 \Rightarrow \frac{V_2 - V_1}{Z_2} = \frac{V_1 - V_3}{Z_3} \Rightarrow \boxed{V_2 = \left(1 + \frac{Z_2}{Z_3}\right)V_1 - \frac{Z_2}{Z_3}V_3} \quad (1)$$

$$I_4 = I_5 \Rightarrow \frac{V_3 - V_1}{Z_4} = \frac{V_1}{Z_5} \Rightarrow \boxed{V_3 = \left(1 + \frac{Z_4}{Z_5}\right)V_1} \quad (2)$$

Calculate  $Z_{in}$ 

$$v_2 = \left(1 + \frac{Z_2}{Z_3}\right)v_1 - \frac{Z_2}{Z_3}v_3 \quad (1)$$

$$v_3 = \left(1 + \frac{Z_4}{Z_5}\right)v_1 \quad (2)$$

By substituting (2) in (1):

$$v_2 = \left(1 + \frac{Z_2}{Z_3}\right)v_1 - \frac{Z_2}{Z_3}\left(1 + \frac{Z_4}{Z_5}\right)v_1$$

$$v_1 - v_2 = \frac{Z_2 Z_4}{Z_3 Z_5} v_1$$

$$\frac{v_1 - v_2}{Z_1} = \frac{Z_2 Z_4}{Z_1 Z_3 Z_5} v_1 = I_1$$

$$\therefore Z_{in} = \frac{v_1}{I_1}$$

$$\therefore Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4} = \frac{\text{odd}}{\text{even}}$$

## L to GIC

$$Z_{in} = \frac{z_1 z_3 z_5}{z_2 z_4} = \frac{\text{odd}}{\text{even}}$$

Select  $z_4$  or  $z_2 = \frac{1}{sC}$  and rest of  $z=R$   $\therefore z_{in} = S \frac{R_1 R_3 R_5 C_4}{R_2}$

For sake of normalization:

$$R_1 = R_2 = R_3 = 1\Omega \text{ and } C_4 = 1F \Rightarrow z_{in} = SR_5 = SL \Rightarrow L = R_5$$

## example

## Example

MUST BE EARTHED COIL ONLY