

BJT Current Sources

Dr. M. Shiple

Advanced Electronic Circuits (EEI 184), 2018

Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

1 Introduction

2 Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

EEI 184

Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers



Introduction




Discrete Circuit Biasing

Independent on β

Introduction

Current Sources

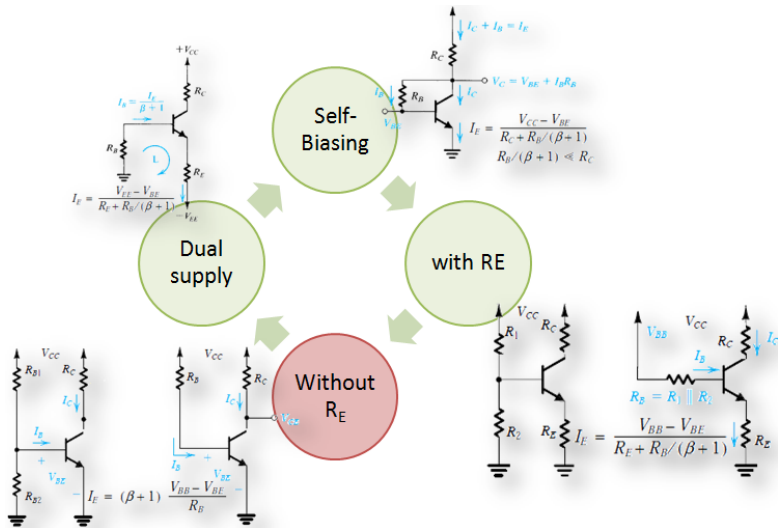
- Problem Definition
- β Dependence
- r_o Output Resistance
- Low output currents
- Multi-transistor
- Current Amplifiers



Introduction

Current Sources

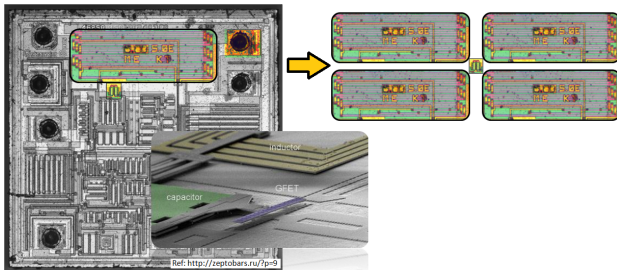- Problem Definition
- β Dependence
- r_o Output Resistance
- Low output currents
- Multi-transistor
- Current Amplifiers



- Resistors require relatively large areas.
- Resistor biasing technique uses coupling and bypass capacitors.



Current Sources





Problem Definition




Introduction

Current Sources

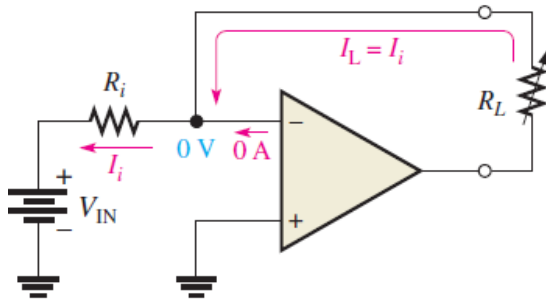Problem Definition

- β Dependence
- r_o Output Resistance
- Low output currents
- Multi-transistor
- Current Amplifiers



Constant-current source delivers a load current that remains constant when the load resistance changes

Two-Transistor Current Source

Introduction

Current Sources

Problem Definition


β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

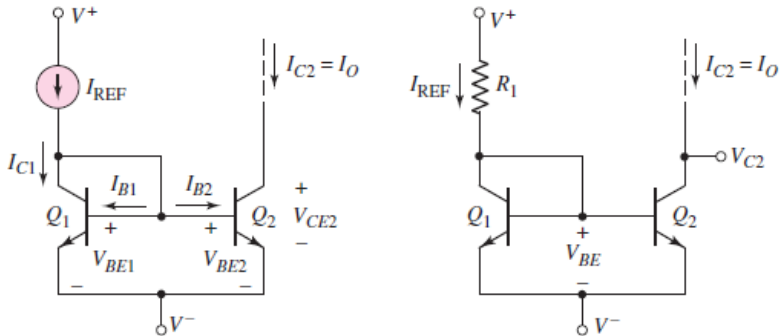

- Identical transistors Q_1 and Q_2 .
- Operating at the same temperature.
- B-E voltage equal in Q_1 and Q_2 .



$$I_{Ref} = \frac{V^+ - V_{BE} - V^-}{R_1}$$

Cont.:Two-Transistor Current Source

Introduction

Current Sources

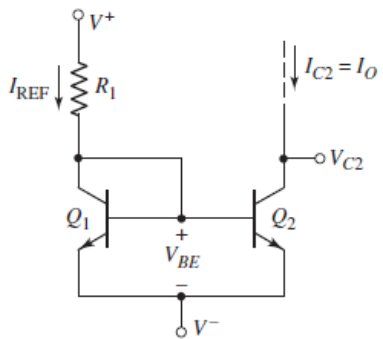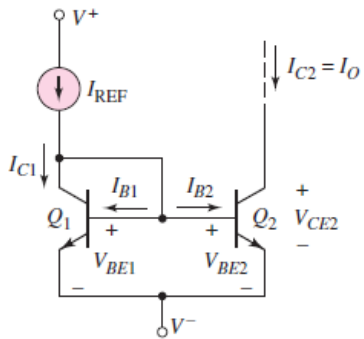- Problem Definition
- β Dependence
- r_o Output Resistance
- Low output currents
- Multi-transistor
- Current Amplifiers



According to matching transistor $I_{C2} = I_{C1}$

$$\begin{aligned} I_{Ref} &= I_{C1} + 2I_B \\ &= I_{C2} \left(1 + \frac{2}{\beta} \right) \end{aligned}$$

$$I_{B1} = I_{B2}$$

$$I_{C2} = \frac{I_{Ref}}{\left(1 + \frac{2}{\beta} \right)} \quad I_{Ref} = \frac{V^+ - V_{BE} - V^-}{R_1}$$



β Dependence



Introduction

Current Sources

Problem Definition



β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

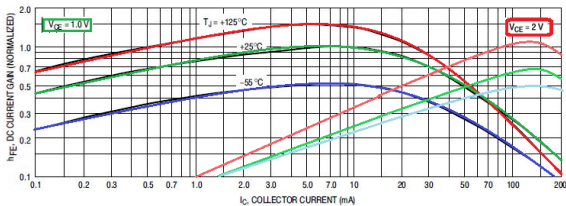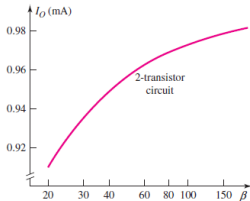

$$I_{C2} = \frac{I_{Ref}}{1 + \frac{2}{\beta}}$$

Design Example

Introduction

Current Sources

Problem Definition


β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

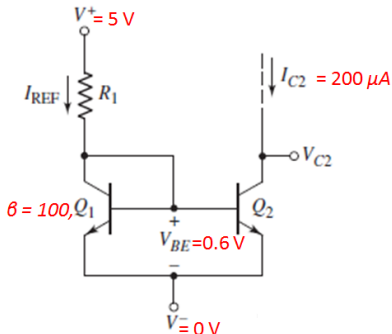

Find R_1

$$I_{Ref} = I_{C2} \left(1 + \frac{2}{\beta} \right) = 204 \mu A$$

$$R_1 = \frac{V^+ - V_{BE} - V^-}{I_{Ref}} = 21.6 K\Omega$$

Three-Transistor Current Source

Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

$$I_{Ref} = I_{C1} + I_{B3}$$

$$I_{E3} = (1 + \beta)I_{B3}$$

$$I_{E3} = 2I_B$$


$$I_{C2} = \beta I_B$$

$$\therefore I_{Ref} = I_{C1} + \frac{I_{E3}}{(1 + \beta)}$$

$$I_{Ref} = I_{C1} + \frac{2I_B}{(1 + \beta)}$$

$$= I_{C1} + \frac{2I_{C2}}{\beta(1 + \beta)}$$
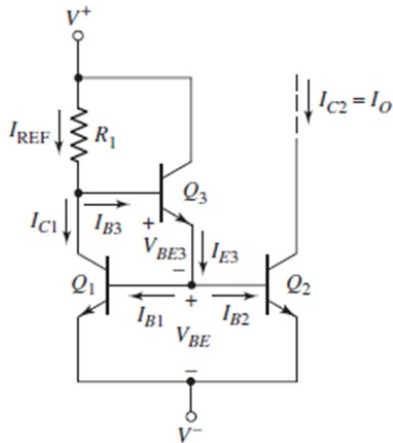
$$= I_{C2} \left(1 + \frac{2}{\beta(1 + \beta)} \right)$$



$$I_{C2} = \frac{I_{Ref}}{\left(1 + \frac{2}{\beta(1 + \beta)} \right)}$$

Introduction

Current Sources

Problem Definition


β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

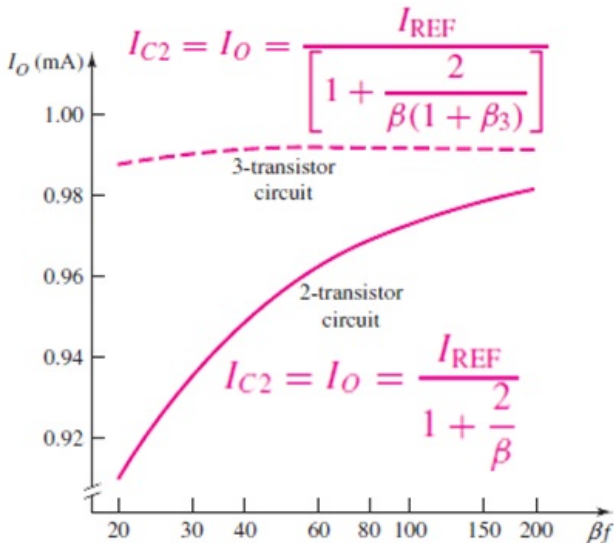

EEI 184

Introduction

Current
Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor


Current Amplifiers




r_o Output Resistance




Output Resistance

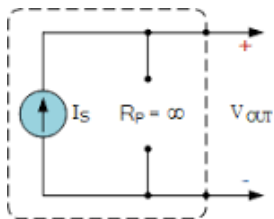


Ideal Current Source

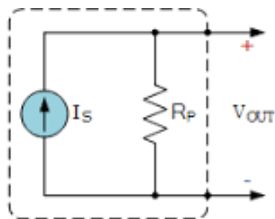

Practical Current Source

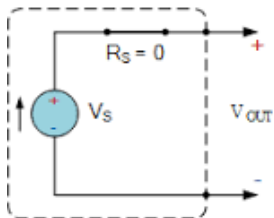

Ideal Voltage Source

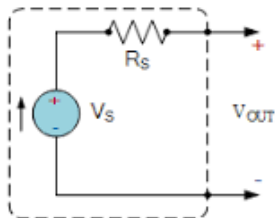

Practical Voltage Source

Output Resistance Two/Three transistors

Introduction

Current Sources

Problem Definition


β Dependence

r_o Output Resistance

Low output currents


Multi-transistor

Current Amplifiers

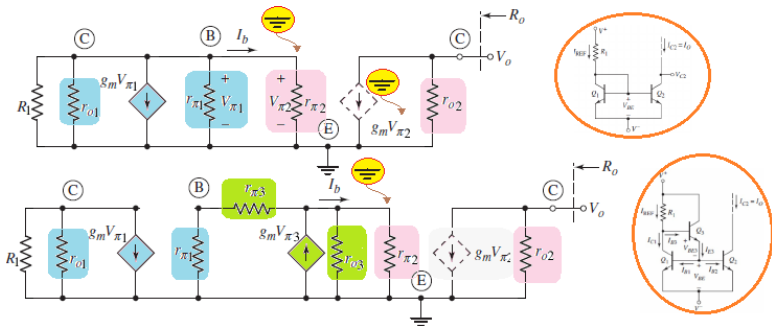

For constant biasing $V_{\pi 2} = 0$

$$R_o = \frac{V_o}{I_o} = r_{o2}$$

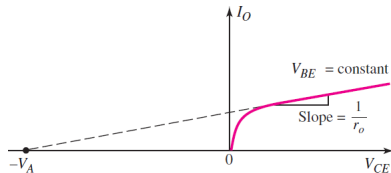


Wilson Current Source

Introduction

Current Sources

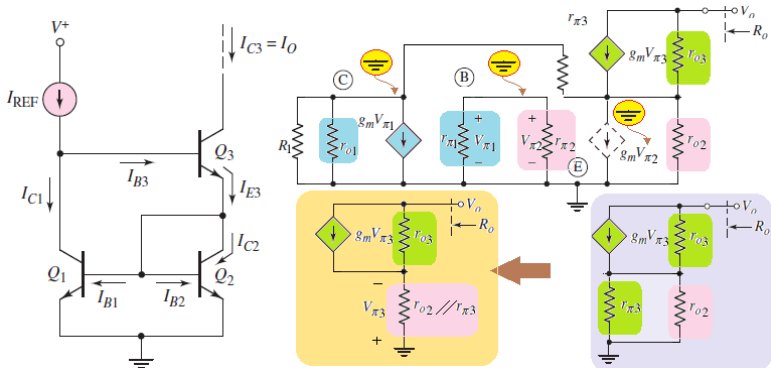- Problem Definition
- β Dependence
- r_o Output Resistance
- Low output currents
- Multi-transistor
- Current Amplifiers



For constant biasing $V_{\pi 2} = 0$

Wilson: Output Resistance

Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

$$I_o = g_m V_{\pi 3} + \left(\frac{V_o - I_o(r_{o2} \parallel r_{\pi 3})}{r_{o3}} \right)$$

$$\therefore V_{\pi 3} = -I_o(r_{o2} \parallel r_{\pi 3})$$


$$r_{o3} I_o = -r_{o3} g_m I_o(r_{o2} \parallel r_{\pi 3}) + V_o - I_o(r_{o2} \parallel r_{\pi 3})$$

$$\frac{V_o}{I_o} = r_{o3} + r_{o3} g_m (r_{o2} \parallel r_{\pi 3}) + (r_{o2} \parallel r_{\pi 3})$$

assume $r_{\pi 3} \ll r_{o2}$

$$= r_{o3} + r_{o3} g_m r_{\pi 3} + \cancel{r_{\pi 3}} \approx 0$$
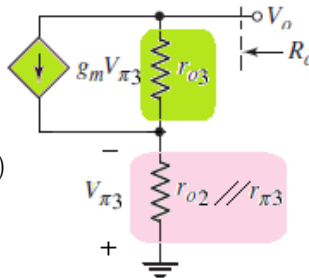
$$\cong r_{o3}(1 + \beta) \cong \beta r_{o3} \uparrow$$



Wilson Current Source

Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers



George R. Wilson

Wilson devised this configuration in 1967 when he and Barrie Gilbert challenged each other to find an improved current mirror overnight that would use only three transistors. Wilson won the challenge.

Wilson Current Source

Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers


$$I_{Ref} = I_{C1} + I_{B3}$$

$$I_{E3} = I_{C2} + 2I_B = I_{C2} \left(1 + \frac{2}{\beta} \right)$$
$$= I_{C2} + 2I_B = I_{C2} \left(1 + \frac{2}{\beta} \right)$$

$$I_{C2} = \frac{I_{E3}}{1 + \frac{2}{\beta}} = \frac{(1 + \beta)}{(2 + \beta)} I_{C3}$$

$$I_{Ref} = \frac{(1 + \beta)}{(2 + \beta)} I_{C3} + \frac{I_{C3}}{\beta}$$
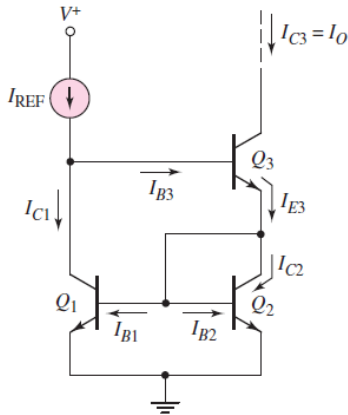
$$I_o = I_{Ref} \left(\frac{1}{1 + \left(\frac{2}{\beta(2+\beta)} \right)} \right)$$



Further improvement (full Wilson Mirror)

Introduction

Current Sources

Problem Definition


β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

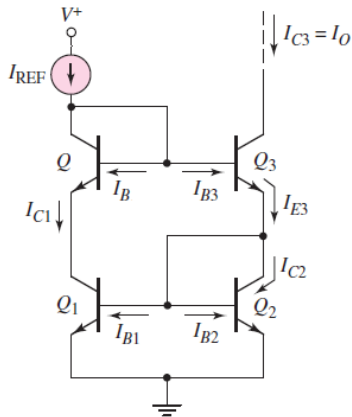

EEI 184

Introduction

Current
Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers



Low output currents



Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers





Bob Widlar

- Widlar current source
- bandgap voltage reference
- voltage regulator ICs ($\mu A723$)
 - operational amplifier ICs ($\mu A702$, $\mu A709$)
- Active loads in the LM101A op amp (1967)



(1937 – 1991)

Problem

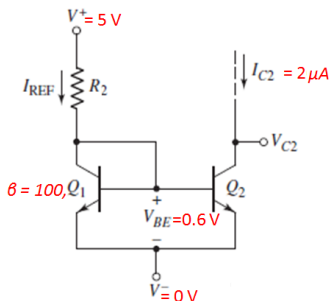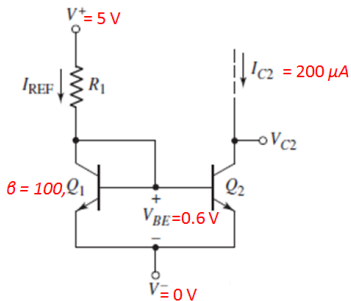

Find R_1 and R_2

$$I_{Ref} = I_{C2} \left(1 + \frac{2}{\beta} \right) = 204 \mu A \quad \text{and} \quad 2.02 \mu A$$

$$R_1 = \frac{V^+ - V_{BE} - V^-}{I_{Ref}} = 21.6 K\Omega \quad \text{and} \quad \boxed{2.17 M\Omega}$$

Widlar Current Source

Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

$$I_o = I_S e^{\frac{V_{BE2}}{V_T}}$$

$$V_{BE2} = V_T \ln \left(\frac{I_o}{I_S} \right)$$

$$I_{Ref} = I_S e^{\frac{V_{BE1}}{V_T}}$$

$$V_{BE1} = V_T \ln \left(\frac{I_{Ref}}{I_S} \right)$$


$$V_{BE1} = V_{BE2} + I_o R_E$$

$$V_{BE1} - V_{BE2} = V_T \ln \left(\frac{I_{Ref}}{I_o} \right)$$

$$\therefore I_o R_E = V_T \ln \left(\frac{I_{Ref}}{I_o} \right)$$

$$R_1 = \frac{V^+ - V_{BE} - V^-}{I_{Ref}}$$

$$\therefore I_o \approx I_E$$

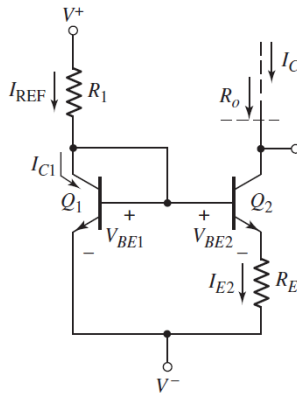

Example: Widlar Vs. Two Transistor

Introduction

Current Sources

Problem Definition



β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

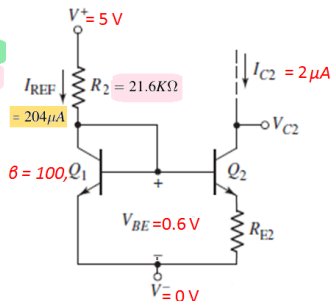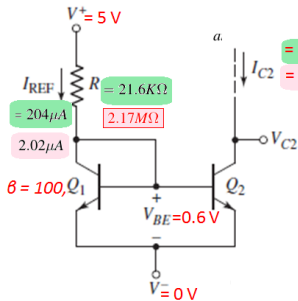


Find R_{E2} assume $R_2 = 21.6K$

$$R_2 = \frac{V^+ - V_{BE} - V^-}{I_{Ref}} \Rightarrow I_{Ref} = 203.7 \mu A \approx 204 \mu A$$

$$\therefore I_o R_E = V_T \ln \left(\frac{I_{Ref}}{I_o} \right) \Rightarrow R_E = 60.1 K \Omega \approx 60 K \Omega$$

Widlar Output Resistor

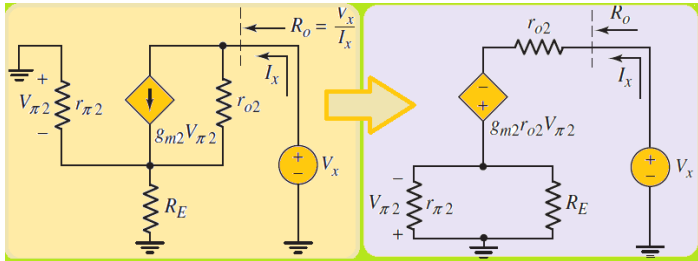

$$R_o = \frac{V_x}{I_x} \Rightarrow V_x = I_x r_{o2} - g_{m2} r_{o2} V_{\pi 2} + V_{\pi 2}$$

$$V_{\pi 2} = I_x (R_E || r_{\pi 2}) \Rightarrow V_x = I_x (r_{o2} + g_{m2} r_{o2} (R_E || r_{\pi 2}) + (R_E || r_{\pi 2}))$$

$$R_o = r_{o2} \left(1 + g_{m2} (R_E || r_{\pi 2}) + \frac{(R_E || r_{\pi 2})}{r_{o2}} \right)$$

$$\because (1/r_{o2}) \ll g_{m2};$$

$$\therefore R_o \approx r_{o2} (1 + g_{m2} (R_E || r_{\pi 2})) \quad \text{compare with } R_{O2tran} = r_{o2}$$

EEI 184

Introduction

Current
Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers



Multi-transistor



Multitransistor Current Mirrors

Introduction

Current Sources

Problem Definition

β Dependence


r_o Output Resistance

Low output currents


Multi-transistor

Current Amplifiers
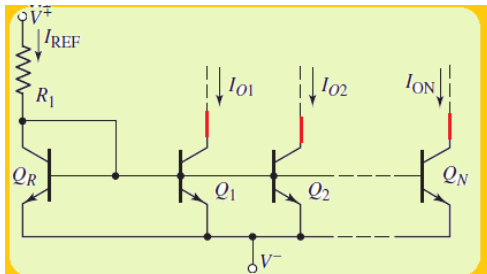
$$I_{O1} = I_{O2} = I_{ON} = \frac{I_{Ref}}{1 + \frac{1+N}{\beta}}$$


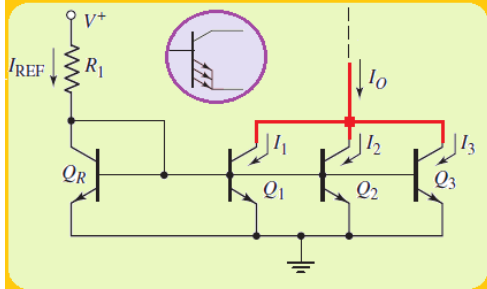
$$I_O = N \frac{I_{Ref}}{1 + \frac{1+N}{\beta}}$$



Examples: Multitransistor

Introduction

Current Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor


Current Amplifiers

$$I_{O3} = \frac{1}{2} I_{REF}$$

$$I_{O4} = \frac{3}{2} I_{REF}$$

$$I_{O1} = I_{REF}$$

$$I_{O2} = 2 I_{REF}$$

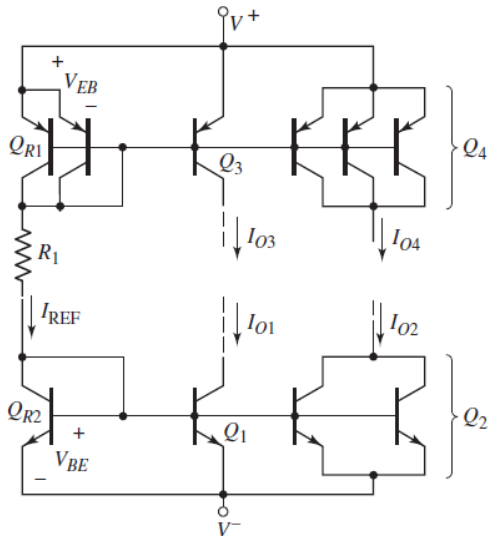

EEI 184

Introduction

Current
Sources

Problem Definition

β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers



Current Amplifiers



Introduction

Current Sources

Problem Definition


β Dependence

r_o Output Resistance

Low output currents

Multi-transistor

Current Amplifiers

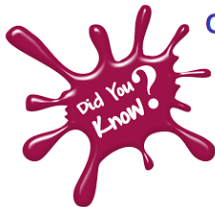

Current amplifiers

- Current amplifiers are occasionally used in analog systems.
- 1990s: analog designers promoted the notion of "current-mode circuits".

Mismatched Transistors

Introduction

Current Sources

- Problem Definition
- β Dependence
- r_o Output Resistance
- Low output currents
- Multi-transistor
- Current Amplifiers

- The parameters I_{S1} and I_{S2} contain both the electrical and geometric parameters of Q_1 and Q_2 .
- If Q_1 and Q_2 are not identical, then $I_{S1} \neq I_{S2}$.

$$I_{REF} = I_{S1} e^{\frac{V_{BE}}{V_T}}$$

$$I_o = I_{S2} e^{\frac{V_{BE}}{V_T}}$$

$$\therefore I_o = I_{REF} \left(\frac{I_{S2}}{I_{S1}} \right)$$

$$I_o = n \times I_{REF}$$

