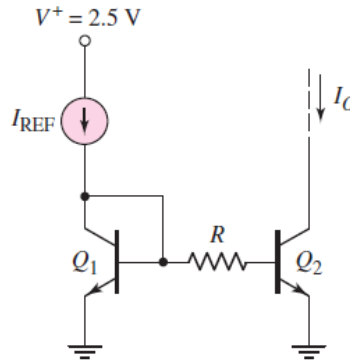




ANSWER THE FOLLOWING QUESTIONS:

1. Consider the circuit shown in next Figure. Assume $I_{REF} = 200\mu A$ and $R = 2k\Omega$. The transistor parameters are $\beta = 40$, $I_{S1} = I_{S2} = 5 \times 10^{-15} A$. Find V_{BE1} , V_{BE2} , and I_O .



Solution:

- (a) We know from two transistor current source that $I_{C1} = I_{C2}$ and both have a relation with I_{REF} as follows:

$$I_{C1} = \frac{I_{Ref}}{\left(1 + \frac{2}{\beta}\right)}$$

$$= \frac{200\mu}{\left(1 + \frac{2}{40}\right)} = 190.48\mu A$$

$$\therefore I_C = \beta I_B \Rightarrow I_{B1} = 4.762\mu A$$

$$\therefore V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) = 0.63345V \quad \text{where } V_T = 0.026V$$


$$I_{Ref} = I_{B1} + I_{B2} + I_{C1} \Rightarrow I_{B2} = I_{Ref} - I_{C1} - I_{B1} = 4.758\mu A$$

- (b)

$$V_{BE1} = I_{B2}R + V_{BE2} \Rightarrow V_{BE2} = 0.624V \quad I_O = I_{S2} e^{\frac{V_{BE2}}{V_T}} = 132.4\mu A$$

2. The values of β for the transistors in next Figure are very large.
- (a) If Q_1 is diode-connected with $I_1 = 0.5mA$, determine the collector currents in the other two transistors.
- (b) Repeat part (a) if Q_2 is diode-connected with $I_2 = 0.5mA$.
- (c) Repeat part (a) if Q_3 is diode-connected with $I_3 = 0.5mA$.

□

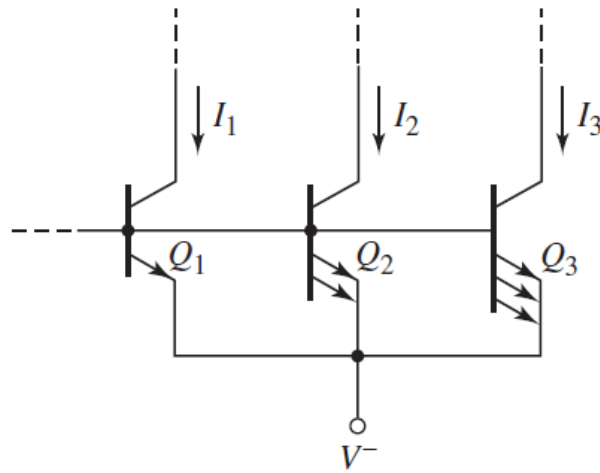**Solution:**

(a)

$$I_2 = 2I_1 \text{ and } I_3 = 3I_1$$

$$I_2 = 1.0 \text{ mA}, I_3 = 1.5 \text{ mA}$$

(b)

$$I_1 = 0.5I_2 \text{ and } I_3 = 3(0.5I_2)$$


$$I_2 = 0.25 \text{ mA}, I_3 = 0.75 \text{ mA}$$

(c)

$$I_1 = \frac{I_3}{3} \text{ and } I_2 = 2\left(\frac{I_3}{3}\right)$$

$$I_2 = 0.167 \text{ mA}, I_3 = 0.333 \text{ mA}$$

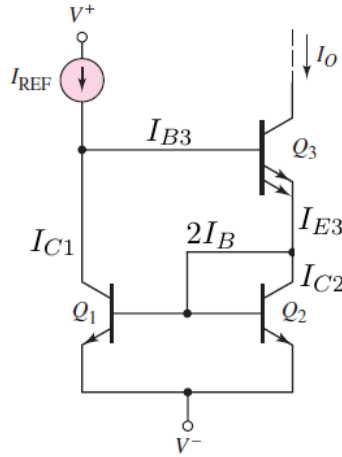3. Consider the Wilson current source in next Figure . The transistors have a finite β and an infinite Early voltage. Derive the expression for I_O in terms of I_{REF} and β .




Solution:

$$\begin{aligned}
 I_{Ref} &= I_{C1} + I_{B3} \\
 I_{E3} &= I_{C2} + 2I_B = I_{C2} \left(1 + \frac{2}{\beta} \right) \\
 &= I_{C2} + 2I_B = I_{C2} \left(1 + \frac{2}{\beta} \right) \\
 I_{C2} &= \frac{I_{E3}}{1 + \frac{2}{\beta}} = \frac{(1 + \beta)}{(2 + \beta)} I_{C3} \\
 I_{Ref} &= \frac{(1 + \beta)}{(2 + \beta)} I_{C3} + \frac{I_{C3}}{\beta} \\
 I_o &= I_{Ref} \left(\frac{1}{1 + \left(\frac{2}{\beta(2 + \beta)} \right)} \right)
 \end{aligned}$$

4. Consider the circuit in next Figure. Neglect base currents and assume $V_A = \infty$.
- Derive the expression for I_O in terms of I_{Ref} and R_E .
 - Determine the value of R_E such that $I_O = I_{Ref} = 100\mu A$. Assume $V_{BE} = 0.7V$ at a collector current of 1 mA.

Solution:

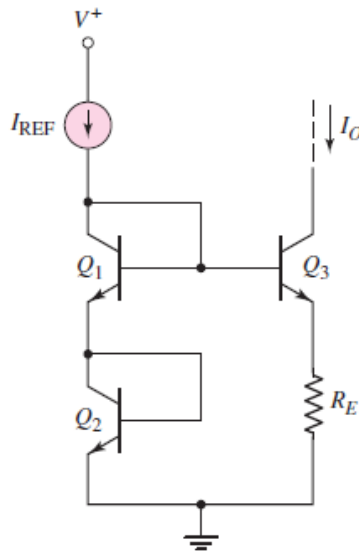

(a)

$$2V_{BE} = V_{BE} + I_o R_E$$

$$V_{BE} = I_o R_E$$

$$V_T \ln\left(\frac{I_{Ref}}{I_S}\right) = I_o R_E$$

(b)

$$I_S = \frac{I_C}{e^{\frac{V_{BE}}{V_T}}} = 2.03 \times 10^{-15} \text{ A}$$

$$V_T \ln\left(\frac{I_{Ref}}{I_S}\right) = I_o R_E \Rightarrow R_E = 6.4 \text{ K}\Omega$$


5. Consider the circuit in next Figure. The transistor parameters are: $\beta = \infty$, $V_A = \infty$, and $V_{BE} = 0.7 \text{ V}$. Design the circuit such that the BE voltages of $Q_1, Q_2,$ and Q_3 are identical to that of Q_R . What are the values of $I_{O1}, I_{O2},$ and I_{O3} ?

Solution:

To keep BE voltages of $Q_1, Q_2,$ and Q_3 are identical to that of Q_R , therefore voltages of R_{ER}, R_{E1}, R_{E2} and R_{E3} must be identical too.

$$V_{R_{ER}} = I_{Ref} R_{ER} = \frac{V^+ - 0.7}{6.3 \text{ K} + 3 \text{ K}} \times 3 \text{ K} = 3 \text{ V}$$
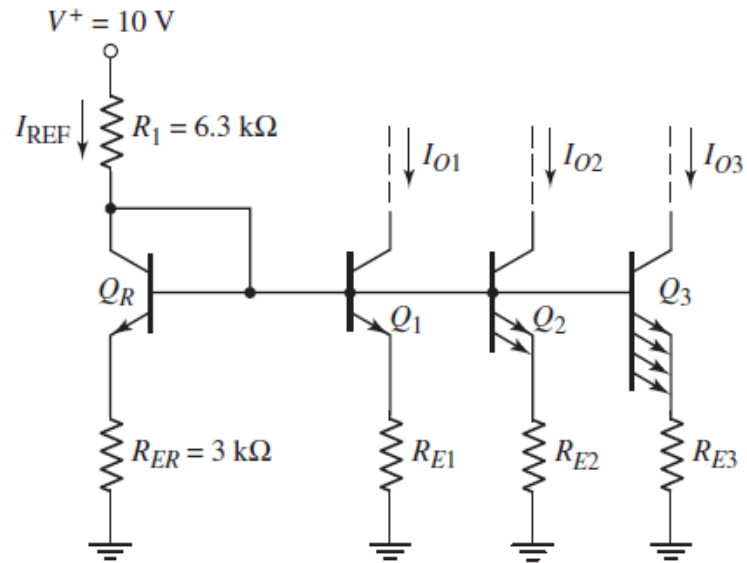
$$V_{R_{E1}} = I_{O1} R_{E1} \Rightarrow R_{E1} = \frac{3}{1 \text{ m}} = 3 \text{ K}\Omega \quad I_{O1} = I_{Ref}$$



$$V_{R_{E2}} = I_{O2} R_{E2} \Rightarrow R_{E2} = \frac{3}{2m} = 1.5K\Omega$$

$$I_{O2} = 2I_{Ref}$$

$$V_{R_{E3}} = I_{O3} R_{E3} \Rightarrow R_{E3} = \frac{3}{4m} = 0.75K\Omega$$

$$I_{O3} = 4I_{Ref}$$