

BJT with Active Loads

Dr. M. Shiple

Advanced Electronic Circuits (EEI 184), 2018

1. Introduction

2. BJT Active Load Circuits

- Replacing R_E
- Replacing R_C
- Examples

3. FET Active Load Circuits

- Examples




1.Introduction



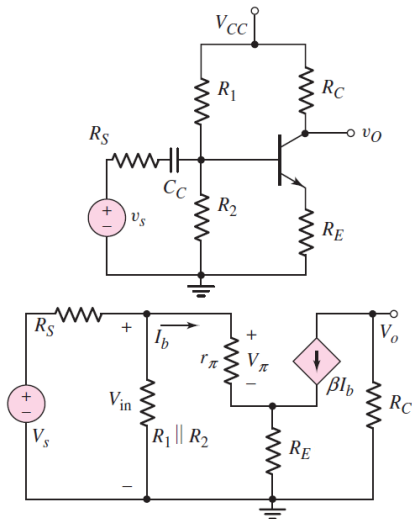
Problem

$$\frac{V_o}{V_s} = -\frac{\beta R_C}{r_\pi + (1 + \beta)R_E}$$

which resistor should be replaced ,
 R_E , or R_C



Problem

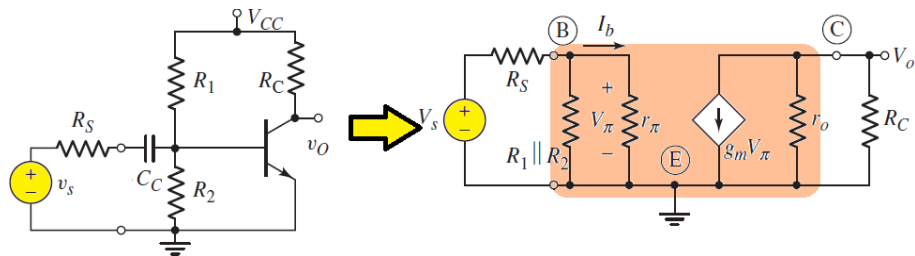


For $R_S = 0$ and $r_o = \infty$: $g_m = \frac{I_C}{V_A}$

$$A_v = -g_m R_C \quad \text{and} \quad g_m = \frac{I_C}{V_A} \quad \text{and} \quad V_O = V_{CC} - I_C R_C$$

- 1 To increase gain $\therefore R_C \uparrow$, But on the other hand $V_O \downarrow$.
- 2 To increase gain $\therefore R_C \uparrow$, BOTOH $I_C \downarrow$ (driving current ☹).
- 3 To increase gain $\therefore R_C \uparrow$, BOTOH area occupation on die \uparrow

R Equivalent model

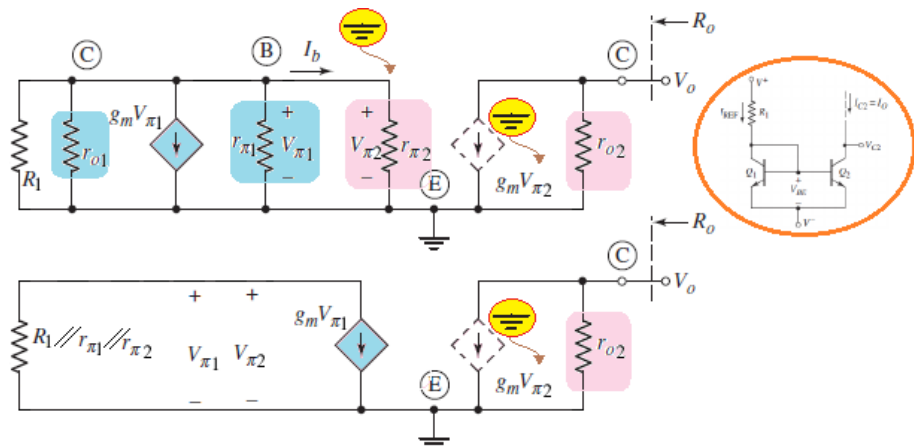

$$V_{\pi 1} = V_{\pi 2} = -g_m V_{\pi 1} (R_1 \parallel r_{\pi 1} \parallel r_{\pi 2})$$

$$0 = V_{\pi 1} (1 + g_m (R_1 \parallel r_{\pi 1} \parallel r_{\pi 2}))$$

$\therefore 0 = V_{\pi 1} = V_{\pi 2} \Rightarrow$ Current sources could be replaced by r_o




2.BJT Active Load Circuits




R Equivalent model

NMOS Version:

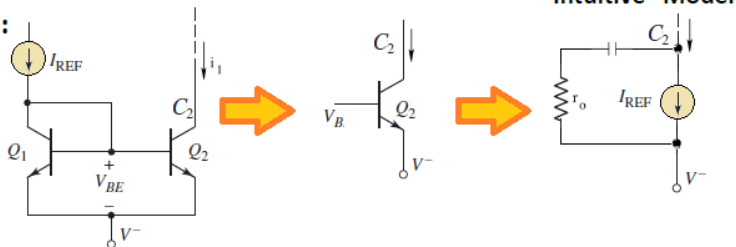

PMOS Version:

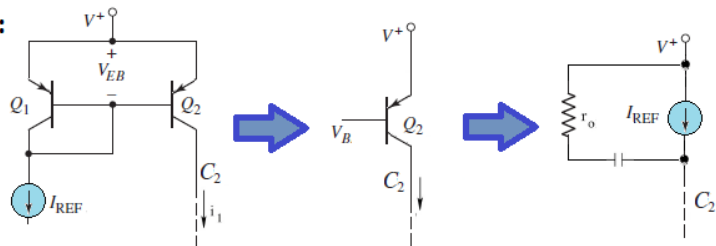




Replacing R_E



Biasing Common Emitter Amplifier (R_E)

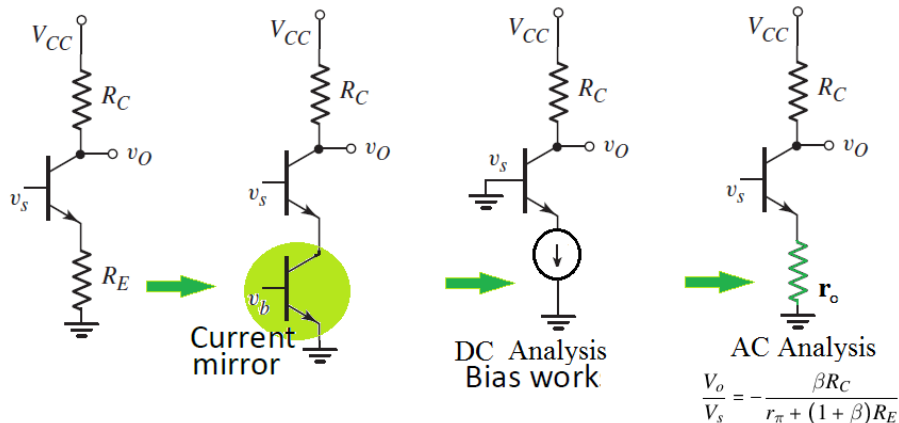

Its Clear $r_o \uparrow$ therefore, gain will be reduced.


Do Not Place A CURRENT SOURCE at Emitter OF CE AMPLIFIER



Replacing R_c







Biased Common Emitter Amplifier (R_C)

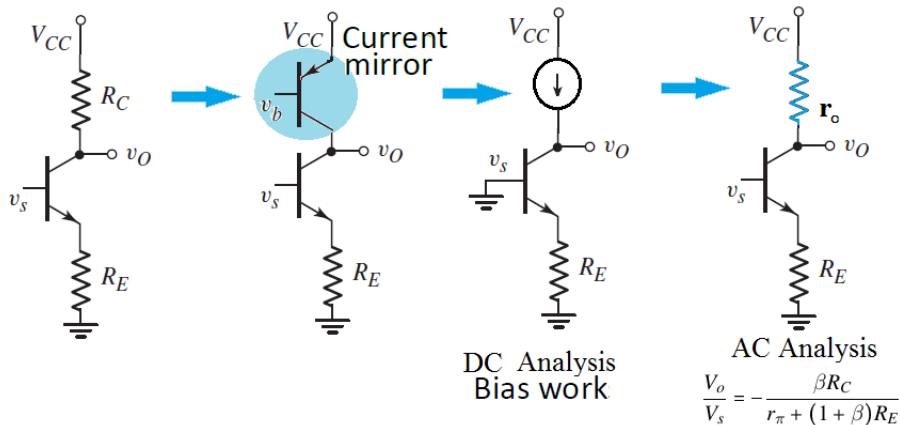



Its Clear $r_o \uparrow$ therefore, gain will be increase.

Place A CURRENT SOURCE at Collector OF CE AMPLIFIER


Active load circuits

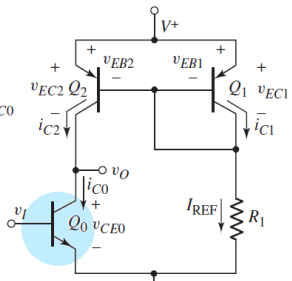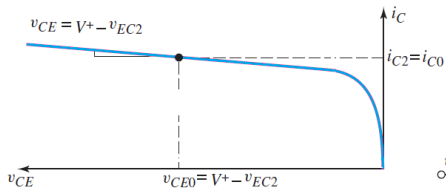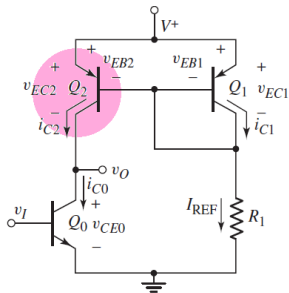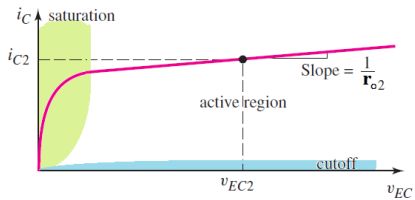

Active load circuits


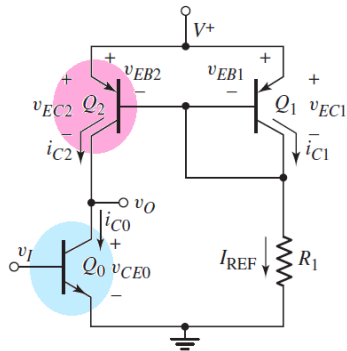
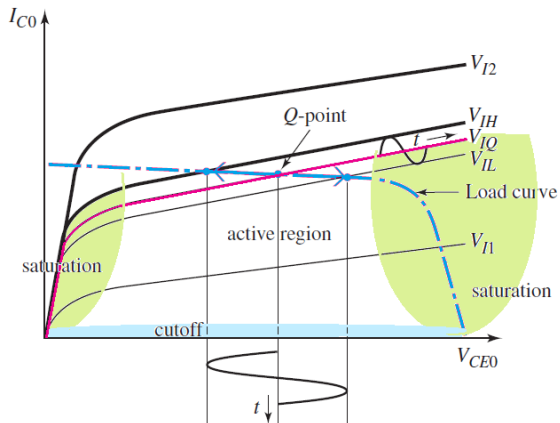


Active load circuits

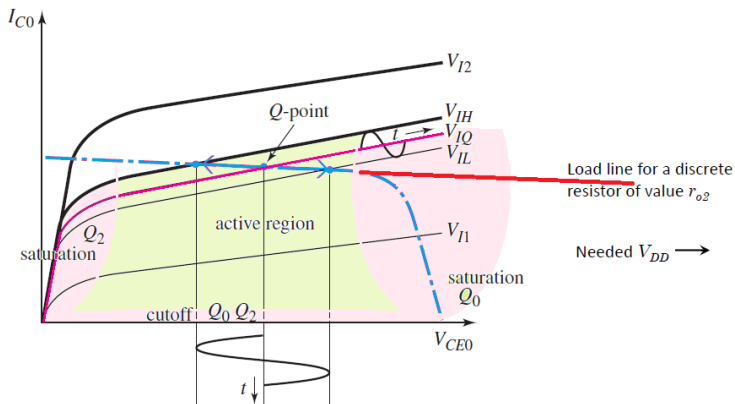

a very large R_C without increasing V_{DD}

Active load circuits

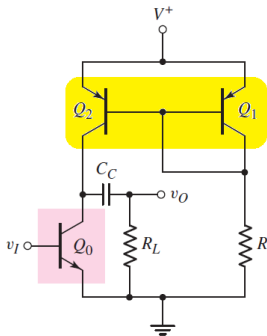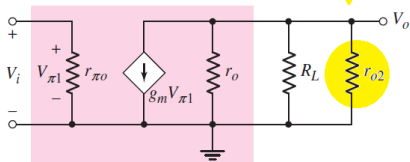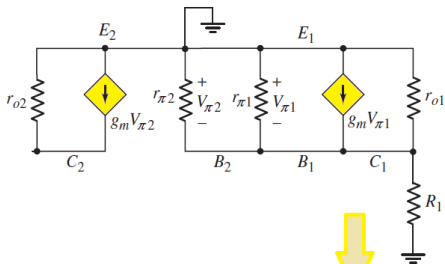

$$A_v = \frac{V_o}{V_i} = -g_m (r_o \parallel R_L \parallel r_{o2})$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{\beta}{r_{\pi}}$$

Conclusion

However, it is important to understand how narrow the input transition width is such that the transistors are biased correctly. For this reason, the use of active loads in discrete circuits is almost impossible.



Examples




Ex1:

$$g_m = \frac{I_{CQ}}{V_T} = 7.69 \text{ A/V}$$

$$A_v = -g_m(r_o \parallel R_L \parallel r_{o2}) = -1846 \quad R_L = \infty$$

$$A_v = -839 \quad R_L = 200 \text{ k}\Omega$$
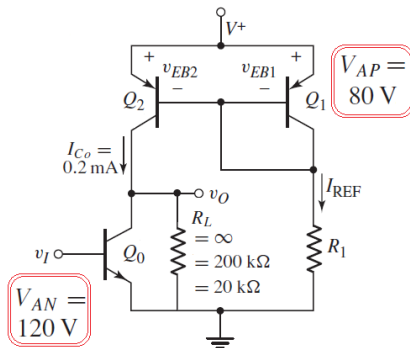
$$A_v = -142 \quad R_L = 20 \text{ k}\Omega$$



Comment:



The small-signal voltage gain is a strong function of the R_L . Therefore, the R_{in} of the next stage must be large in order to minimize the loading effect.



3.FET Active Load Circuits



Active load circuits

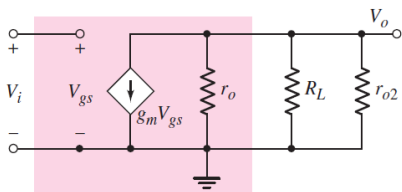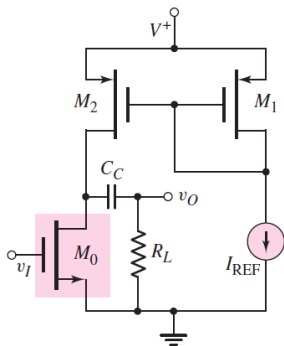

$$A_v = \frac{V_o}{V_i} = -g_m(r_o \parallel R_L \parallel r_{o2})$$

$$g_m = 2\sqrt{K_n I_{REF}} = K_n (V_{ov})$$

Comment:

Gain is smaller than equivalent bipolar circuits, because of the smaller (g_m) transconductance for the MOSFET.




Examples



Ex1:

$$g_m = \sqrt{2K'_n I_{REF} \left(\frac{W}{L}\right)} = 0.63 \text{ mA/V}$$
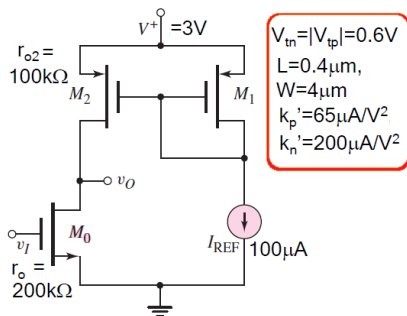
$$A_v = -g_m (r_{on} \parallel r_{op}) = -42$$



Comment:

The small-signal voltage gain is a strong function of the R_L . Therefore, the R_{in} of the next stage must be large in order to minimize the loading effect.