

EEI 184

Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

THE DIFFERENTIAL AMPLIFIER

Dr. M. Shipley

Advanced Electronic Circuits (EEI 184), 2018

Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

1 Intro. to DA

2 Large Signal Analysis

3 Small Signal Analysis

DA: Find Linear Region boundary


Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

Intro. to DA

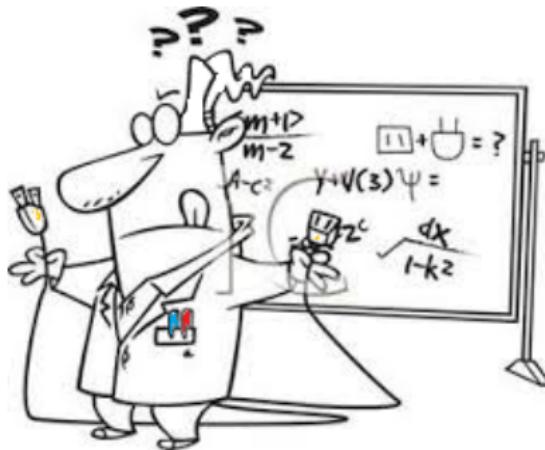


Problem

Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

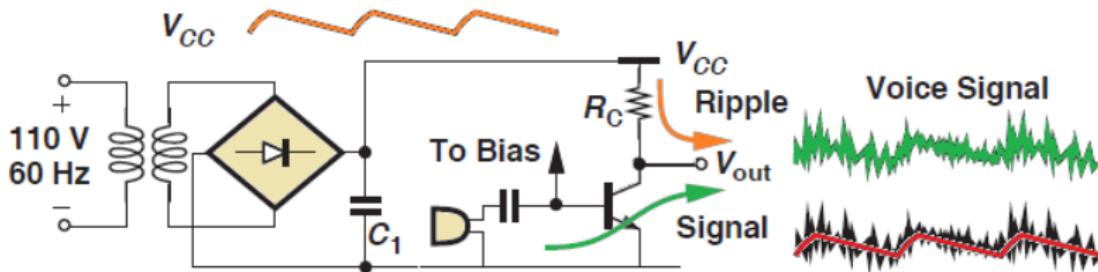


$$V_{out} = (V_{CC} + \text{Noise}) - i_C R_C \Rightarrow= (V_{CC} - i_C R_C) + \text{Noise}$$

Hum example

First Glance Solution

Intro. to DA

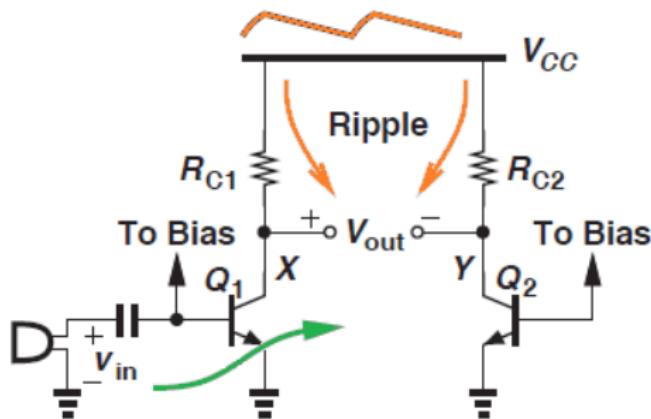Large Signal
AnalysisSmall Signal
AnalysisDA: Find Linear
Region boundary

$$V_{out}^+ = (V_{CC} - i_C R_C) + \text{Noise} \quad V_{out}^- = (V_{CC} - I_C R_C) + \text{Noise}$$

$$V_{out}^+ - V_{out}^- = (V_{CC} - i_C R_C) + \text{Noise} - [(V_{CC} - I_C R_C) + \text{Noise}]$$

$$V_{out} = -i_C R_C + I_C R_C = -(I_C + i_c) R_C = -i_C R_C$$

Duplicate stage consisting of Q2 and RC2 remains "idle", thereby "wasting" current.


Improve Solution (Common Mode)

Intro. to DA

Large Signal Analysis

Small Signal Analysis

DA: Find Linear Region boundary

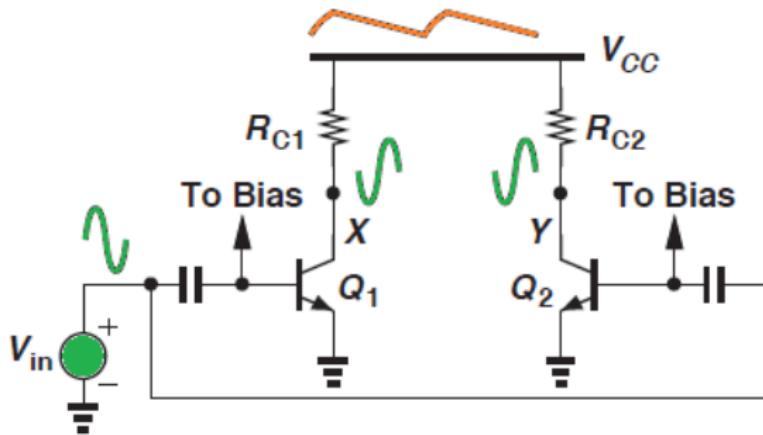


$$V_{out}^+ = (V_{CC} - i_C R_C) + \text{Noise} \quad V_{out}^- = (V_{CC} - i_C R_C) + \text{Noise}$$

$$V_{out}^+ - V_{out}^- = (V_{CC} - i_C R_C) + \text{Noise} - [(V_{CC} - i_C R_C) + \text{Noise}]$$

$$V_{out} = 0$$

Cont. Improve Solution (Differential Mode)

Intro. to DA

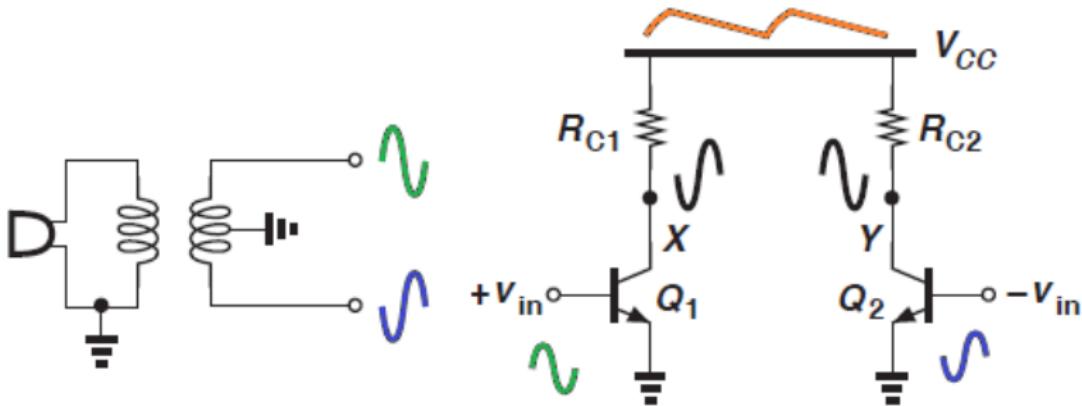Large Signal
AnalysisSmall Signal
AnalysisDA: Find Linear
Region boundary

$$\begin{aligned} V_{out}^+ &= (V_{CC} - i_C R_C) + \text{Noise} & V_{out}^- &= (V_{CC} - (-i_C) R_C) + \text{Noise} \\ V_{out}^+ - V_{out}^- &= (V_{CC} - i_C R_C) + \text{Noise} - [(V_{CC} - (-i_C) R_C) + \text{Noise}] \\ V_{out} &= -i_c R_C - i_c R_C = -2i_c R_C \end{aligned}$$

Intro. to DA

Large Signal
Analysis

Small Signal
Analysis



DA: Find Linear
Region boundary

Differential Amplifier

is an amplifier that produces outputs that are a function of the difference between two input voltages.

DA Modes:

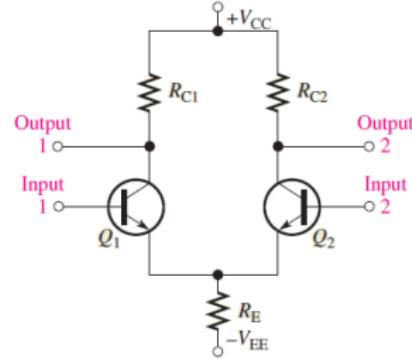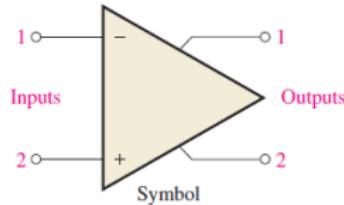- Two inputs are different (Differential).
- Two inputs are the same (Common mode).



Intro. to DA

Large Signal
Analysis


Small Signal
Analysis

DA: Find Linear
Region boundary

Did you know?

An important application of the differential pair is at the input of op amps, where inverting and noninverting input terminals are necessary.

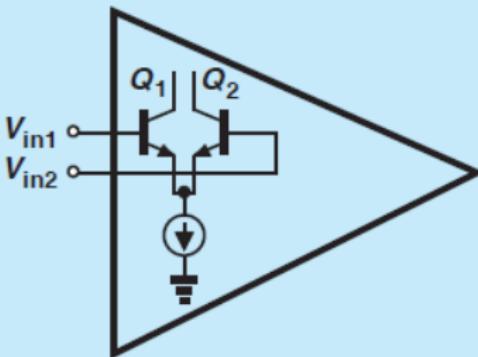Without this second input, many op-amp-based functions would be difficult to realize. For example, the noninverting amplifier utilize both inputs.



Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

Large Signal Analysis




Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

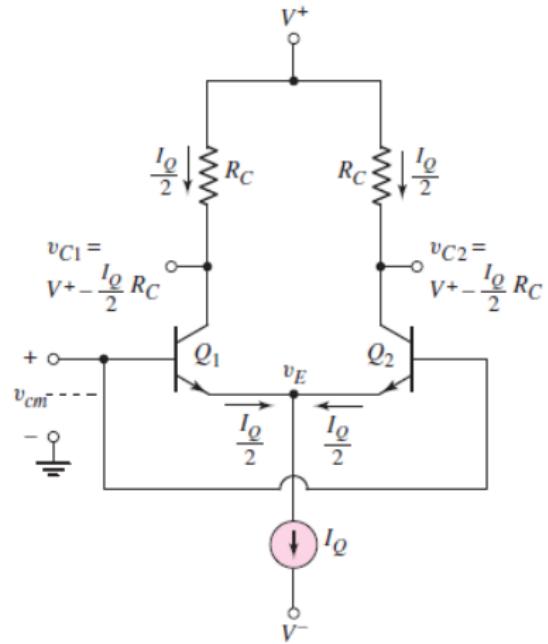

"tail current source", "emitter-coupled pair" or the "long-tailed pair."

$$i_{C1} = I_S e^{v_{BE1}/V_T}$$

$$i_{C2} = I_S e^{v_{BE2}/V_T}$$

$$I_Q = i_{C1} + i_{C2}$$

$$= I_S \left(e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T} \right)$$



$$\frac{i_{C1}}{I_Q} = \frac{1}{1 + e^{(v_{BE2} - v_{BE1})/V_T}}$$

$$\frac{i_{C2}}{I_Q} = \frac{1}{1 + e^{-(v_{BE2} - v_{BE1})/V_T}}$$

$$\therefore v_{BE2} - v_{BE1} = v_d$$

$$c \frac{i_{C2}}{I_Q} = \frac{1}{1 + e^{-(v_d)/V_T}}$$

large-signal operation

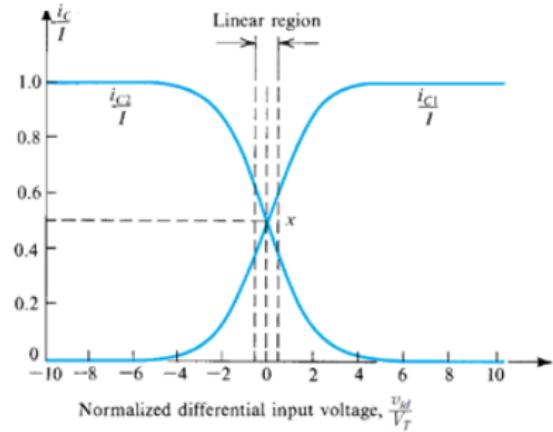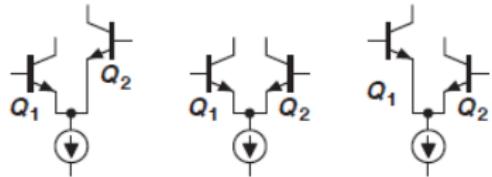


Intro. to DA

Large Signal Analysis

Small Signal Analysis

DA: Find Linear Region boundary

Differential BJT

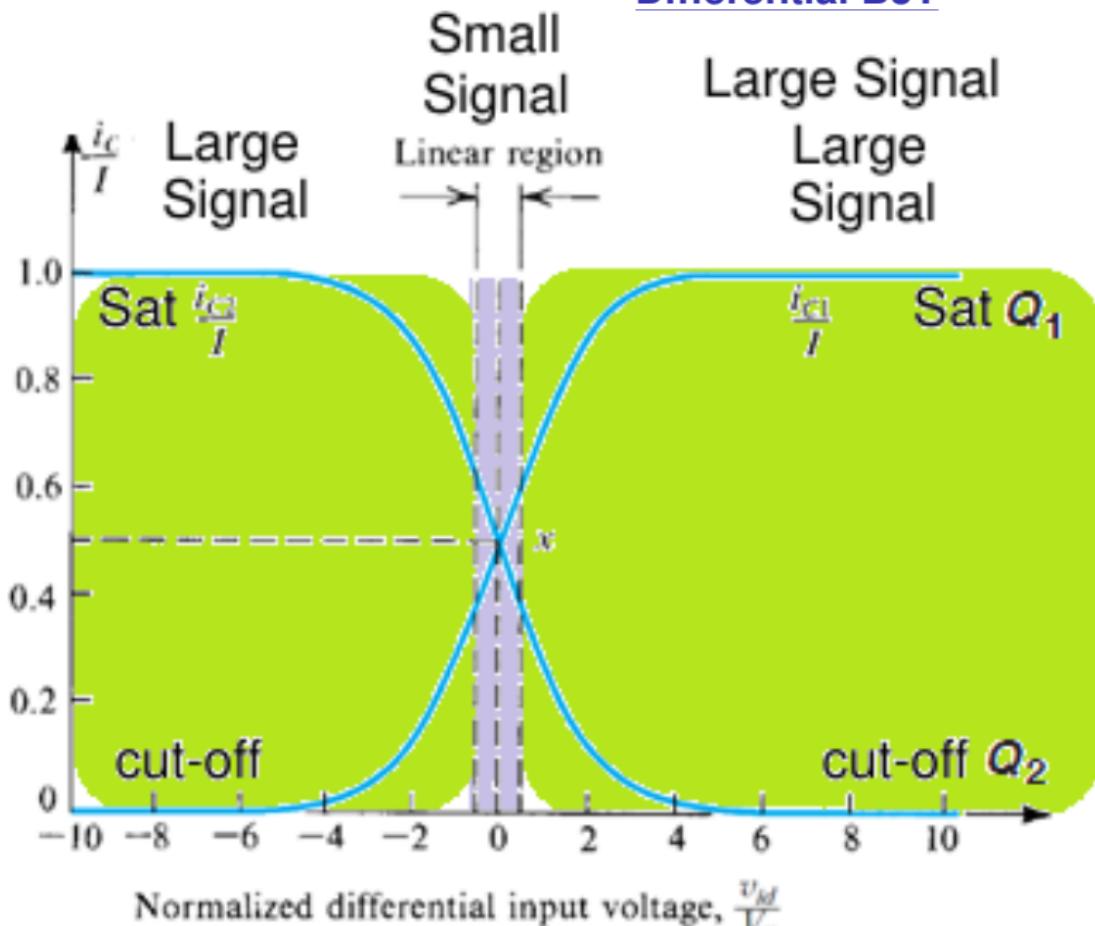


Large Signal Example

Intro. to DA

Large Signal Analysis

Small Signal Analysis

DA: Find Linear Region boundary

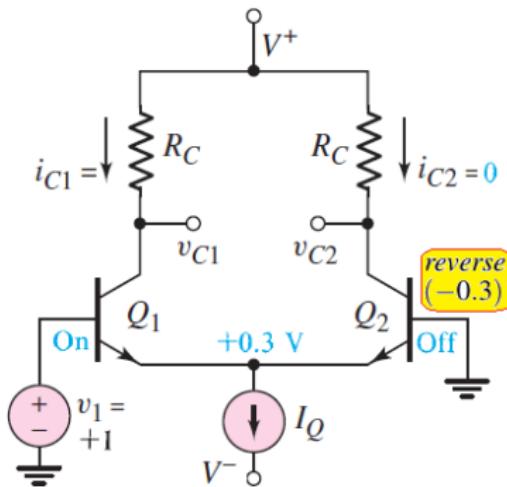

$$\begin{aligned}
 V_E &= V_B - V_{BE} \\
 &= 1 - 0.7 = 0.3 \quad \text{to be active} \\
 \therefore V_{BE2} &= -0.3 \quad \text{Reverse}
 \end{aligned}$$

$$\begin{aligned}
 V_E &= V_B - V_{BE} \\
 &= 0 - 0.7 = -0.3 \\
 \therefore V_{BE1} &= -0.3
 \end{aligned}$$


Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

Small Signal Analysis

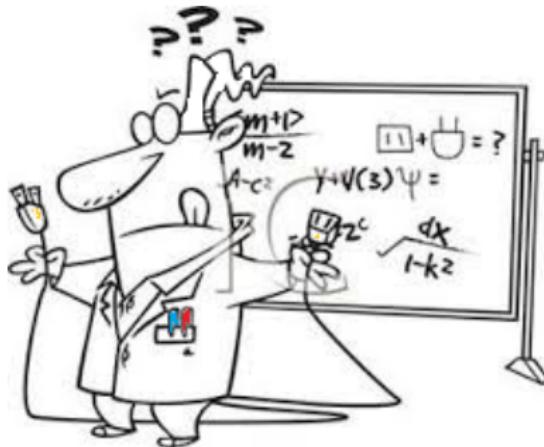

Active Differential BJT

Intro. to DA

Large Signal
AnalysisSmall Signal
AnalysisDA: Find Linear
Region boundary

Active means both transistors in active region, linear region, difference input voltages is small signal.

\therefore transistors are matched,


$$v_{BE1} = v_{BE2}$$

$$i_{E1} = i_{E2} = \frac{I_Q}{2}$$

$$i_{C1} = i_{C2} \quad \therefore i_C \approx i_E$$

$$\therefore v_{C1} = V^+ - \frac{I_Q}{2} R_C = v_{C2}$$

$$v_d = V_{C1} - V_{C2} = 0 \#$$

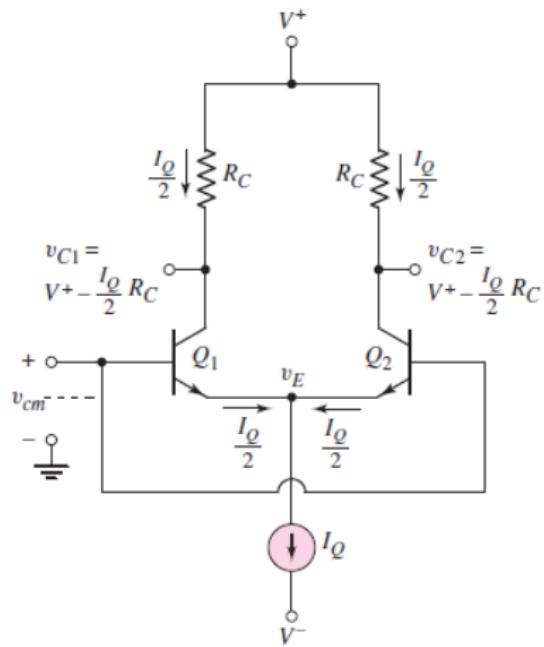

Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

Active Differential BJT

Two inputs are equal
and inverted

$$v_{in1} = -v_{in2}$$

$$v_d = v_{in1} - v_{in2}$$


$$v_d = v_{in1} + v_{in2}$$

$$\Rightarrow v_{in1} = -v_{in2} = \frac{v_d}{2}$$

$$\therefore I_{E1} = \frac{I_Q}{2} + \Delta I$$

$$v_{C1} = V^+ - \left(\frac{I_Q}{2} + \Delta I \right) R_C \quad v_{C2} = V^+ - \left(\frac{I_Q}{2} - \Delta I \right) R_C$$
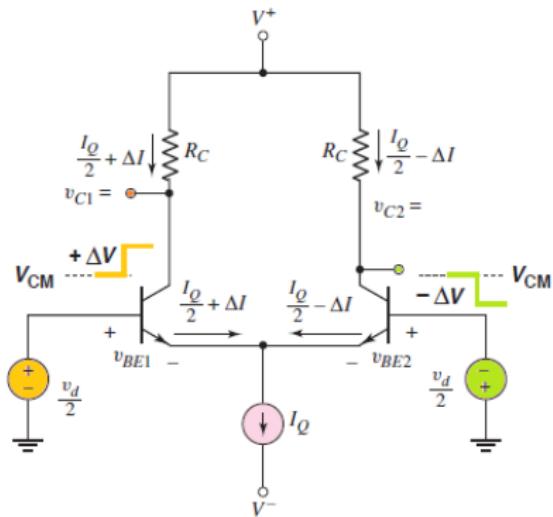
$$v_d = V_{C1} - V_{C2} = 2\Delta I R_C$$



ΔI : proportional to the difference input voltage


Intro. to DA

Large Signal
Analysis


Small Signal
Analysis

DA: Find Linear Region boundary

DA: Find Linear Region boundary

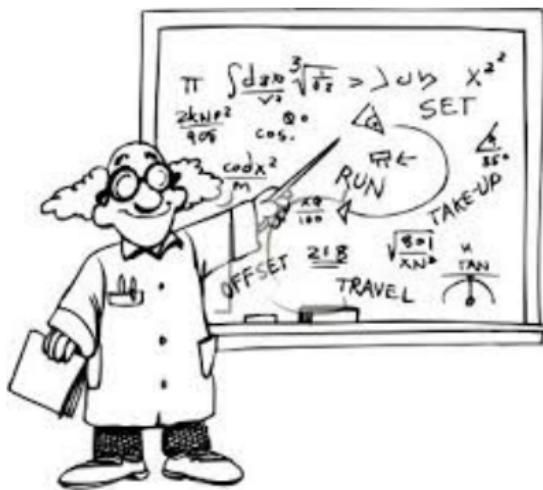

Small Signal Analysis

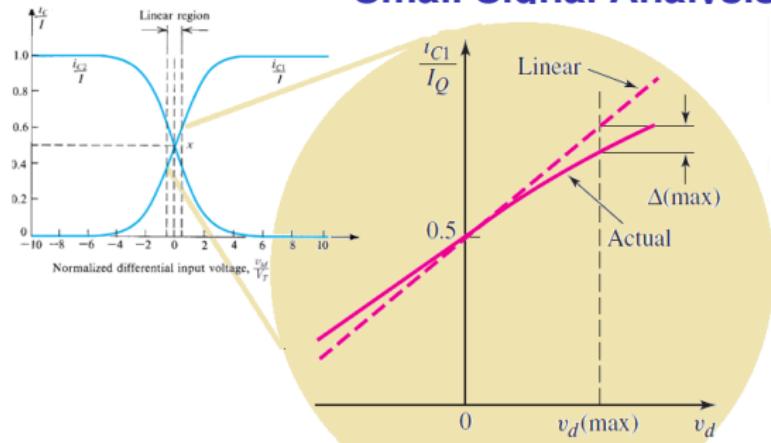

$$i_{C1} = \frac{I_Q}{1 + e^{(-v_d)/V_T}} = I_Q(1 + e^{(-v_d)/V_T})^{-1}$$

$$\frac{di_{C1}}{d(v_d)} = I_Q(-1)(1 + e^{(v_d)/V_T})^{-2} \left(\frac{-1}{V_T} e^{(-v_d)/V_T} \right)$$

$$= \frac{I_Q e^{(-v_d)/V_T}}{V_T (1 + e^{(-v_d)/V_T})^2} \Big|_{v_d=0} = \frac{I_Q}{4V_T}$$


Small Signal Analysis

Intro. to DA


Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

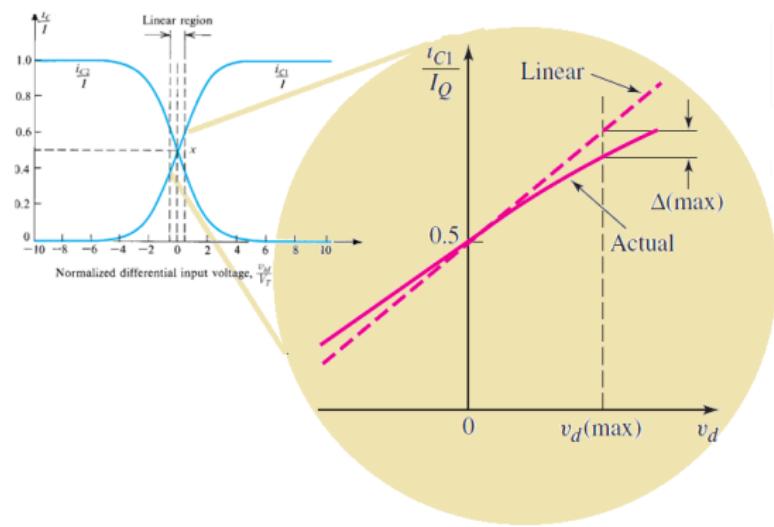

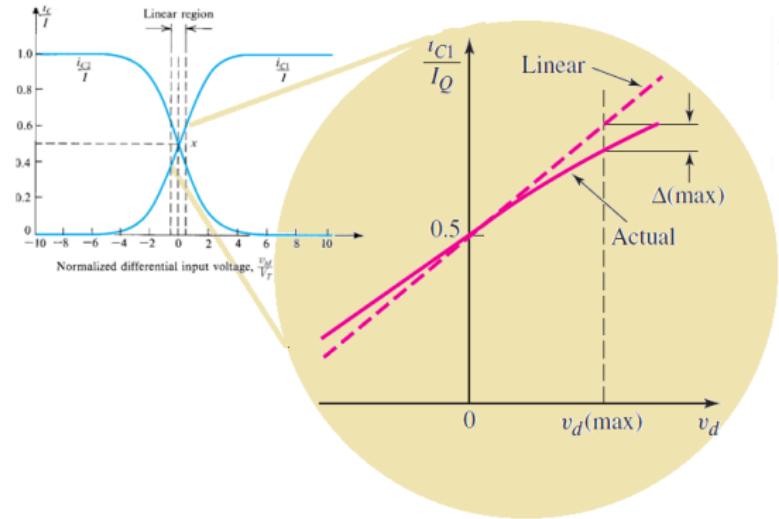Therefore the equation of a line passes through $I_c = 0.5I_Q$ and slope $\frac{I_Q}{4V_T}$ is $I_c = 0.5I_Q + \left(\frac{I_Q}{4V_T}\right)v_d$



$$\frac{i_{C(\text{linear})} - i_{C(\text{actual})}}{i_{C(\text{linear})}} = 0.01$$

or

$$\frac{\left(0.5I_Q + \left(\frac{I_Q}{4V_T}\right)v_d\right) - \frac{I_Q}{1 + e^{(-v_d)/V_T}}}{\left(0.5I_Q + \left(\frac{I_Q}{4V_T}\right)v_d\right)} = 0.01 \Rightarrow v_d \cong 18mv$$



Small Signal Analysis

Intro. to DA


Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

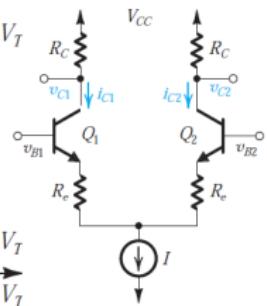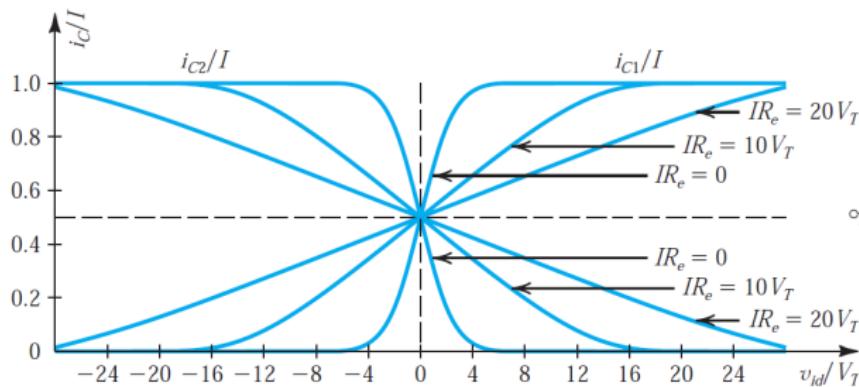

Recall BJT AC analysis

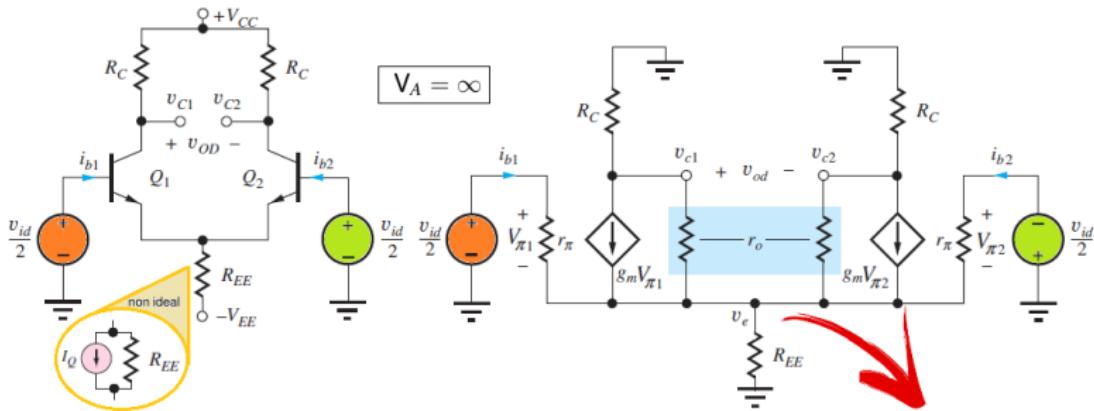

Apply KCL @ node v_e

$$\because V_A = \infty \therefore r_o = \infty$$

$$g_m V_{\pi 1} + i_{b1} + g_m V_{\pi 2} + i_{b2} = \frac{v_e}{R_{EE}}$$

$$g_m V_{\pi 1} + \frac{V_{\pi 1}}{r_{\pi}} + g_m V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi}} = \frac{v_e}{R_{EE}}$$

$$(g_m + \frac{1}{r_{\pi}})(V_{\pi 1} + V_{\pi 2}) = \frac{v_e}{R_{EE}}$$


Intro. to DA

Large Signal Analysis

Small Signal Analysis

DA: Find Linear Region boundary

DA: Virtual Ground

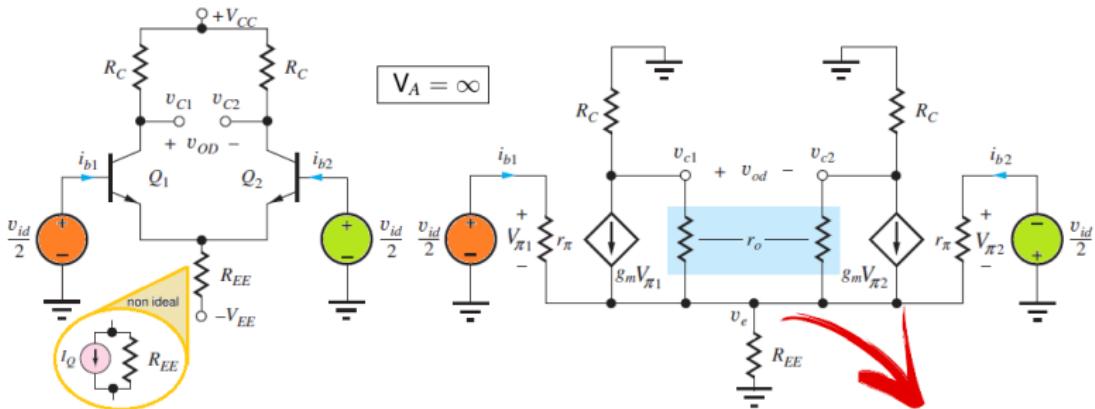

$$(g_m + \frac{1}{r_\pi})(V_{\pi 1} + V_{\pi 2}) = \frac{v_e}{R_{EE}}$$

$$(g_m + \frac{1}{r_\pi})\left(\frac{v_{id}}{2} - v_e + \left(\frac{-v_{id}}{2} - v_e\right)\right) = \frac{v_e}{R_{EE}}$$


$$(g_m + \frac{1}{r_\pi})(-2v_e) = \frac{v_e}{R_{EE}}$$

$$v_e(2g_m + 2\frac{1}{r_\pi} + \frac{1}{R_{EE}}) = 0$$



DA: Gain

Intro. to DA

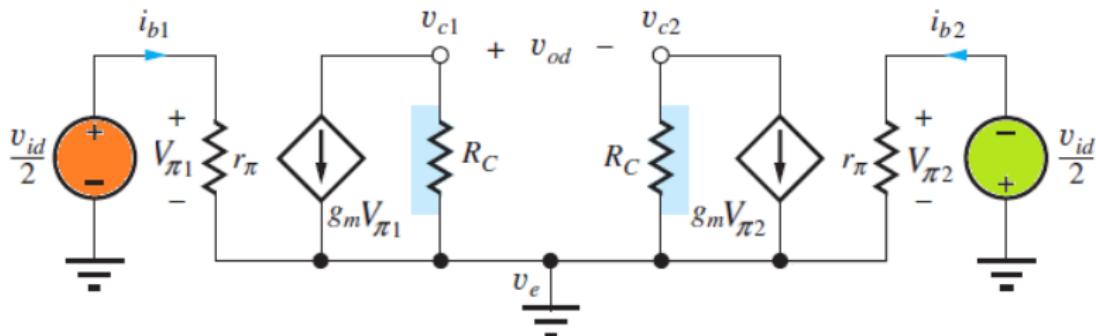Large Signal
AnalysisSmall Signal
AnalysisDA: Find Linear
Region boundary

$$v_{c1} = -g_m v_{\pi 1} R_C \quad v_{c2} = -g_m v_{\pi 2} R_C$$

$$v_{c1} = -g_m \frac{v_{id}}{2} R_C \quad v_{c2} = -g_m \frac{-v_{id}}{2} R_C$$

$$v_{od} = v_{c1} - v_{c2} = -g_m R_C v_{id}$$

$$Gain = \frac{v_{od}}{v_{id}} = -g_m R_C$$

$$R_{id} = \frac{v_{id}}{i_{b1}} = 2r_\pi$$

$$R_{od} = 2R_C |_{\text{differential}}$$


$$R_{out} = R_C |_{\text{single ended}}$$

Intro. to DA

Large Signal
Analysis

Small Signal
Analysis

DA: Find Linear
Region boundary

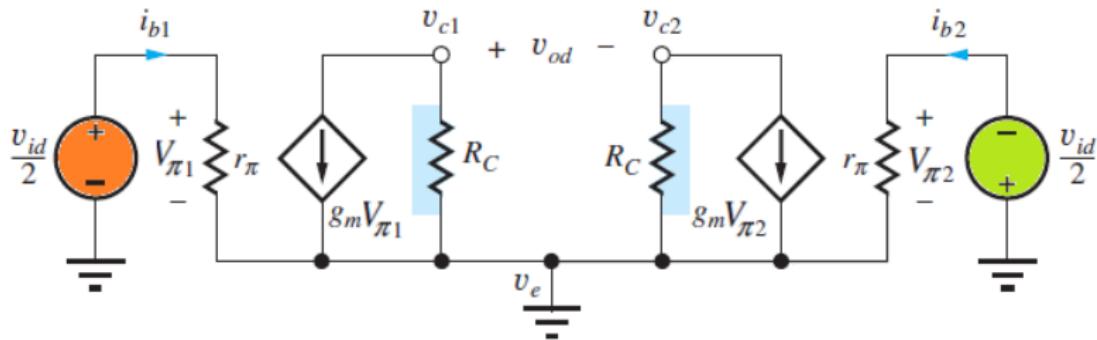

$$i_c = -g_m v_{id} \quad I_C = I_Q/2$$

$$v_C = V_{CC} - i_C R_C = V_{CC} - \frac{I_Q}{2} R_C + g_m v_{id} R_C$$

Example

Design

a bipolar differential pair for a gain of 10 and a power budget of 1 mW, 0.5 mW with a supply voltage of 2 V.

$$\text{recall } P = IV \quad g_m = \frac{I_C}{V_T}$$

$$I = \begin{cases} 0.5|_{1mW}, & I_C = 0.25mA, \quad g_m = 9.6m\text{S}, \quad R_C = 1041\Omega \\ 0.25|_{0.5mW}, & I_C = 0.125mA, \quad g_m = 4.8m\text{S}, \quad R_C = 2080\Omega \end{cases}$$


Intro. to DA

Large Signal Analysis

Small Signal Analysis

DA: Find Linear Region boundary

Low Input Resistance

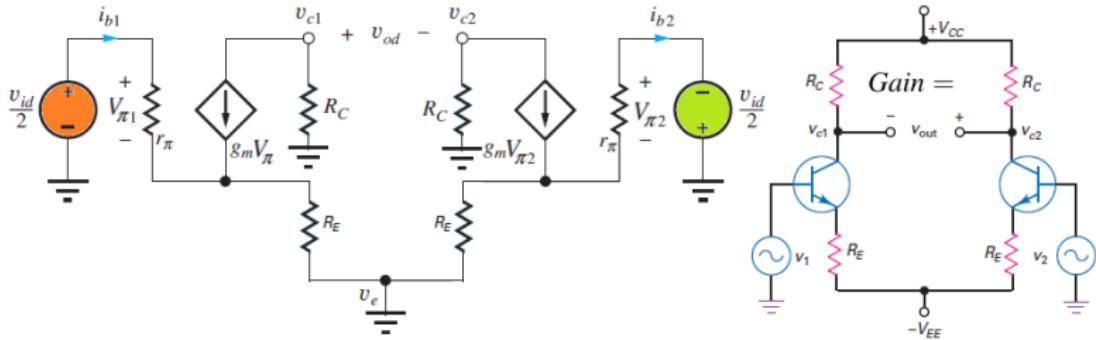

$$\text{Recall } R_{id} = \frac{v_{id}}{i_{b1}} = 2r_\pi$$

$$\frac{v_{id}}{2} = i_{b1}r_\pi + i_eR_E$$

$$\frac{v_{id}}{2} = i_{b1}r_\pi + (1 + \beta)i_{b1}R_E$$

$$\frac{v_{id}}{i_{b1}} = 2(r_\pi + (1 + \beta)R_E) = 2(r_\pi + (1 + \beta)R_E) \uparrow$$

Intro. to DA


Large Signal

Analysis

Small Signal Analysis

DA: Find Linear Region boundary

DA with R_E : Gain

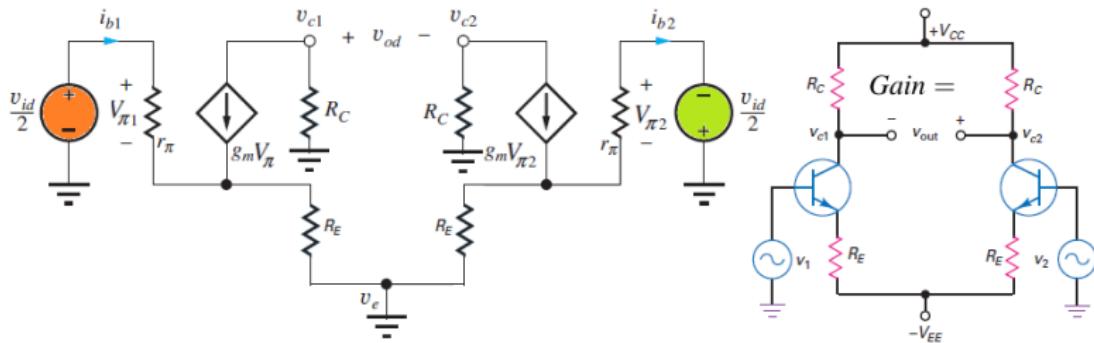

Recall $Gain = -g_m R_C$ $g_m r_\pi = \beta$

$$\frac{v_{id}}{2} = v_\pi + i_e R_E$$

$$\frac{v_{id}}{2} = v_\pi + \left(\frac{v_\pi}{r_\pi} + g_m v_\pi \right) R_E$$

$$v_{id} = 2v_\pi \left(1 + \left(\frac{1}{r_\pi} + \frac{\beta}{r_\pi} \right) R_E \right) \Rightarrow v_\pi = \frac{v_{id}}{2\left(1 + \frac{1+\beta}{r_\pi} R_E\right)}$$

$$v_{out} = v_{c1} - v_{c2} = -g_m R_C (V_{\pi 1} - V_{\pi 2})$$


Intro. to DA

Large Signal Analysis

Small Signal Analysis

DA: Find Linear Region boundary

Cont. :DA with R_E : Gain

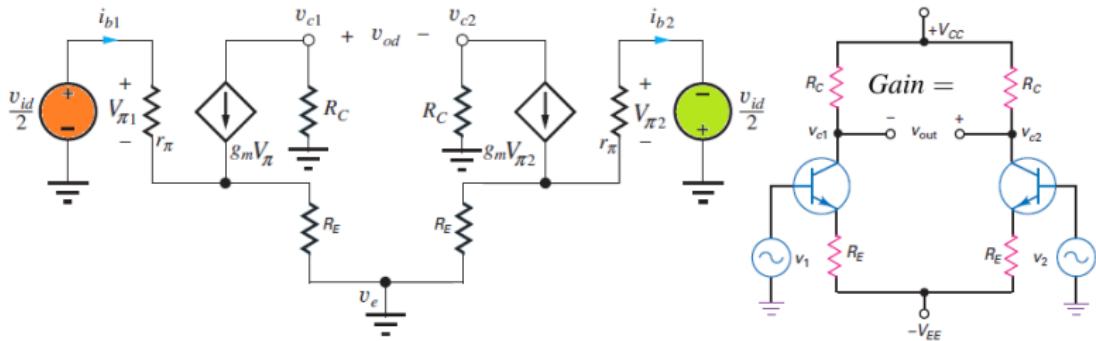

$$\text{Recall } \text{Gain} = -g_m R_C \quad g_m r_\pi = \beta$$

$$v_{out} = v_{c1} - v_{c2} = -g_m R_C (V_{\pi 1} - V_{\pi 2})$$

$$v_{out} = \frac{-g_m R_C}{2(1 + \frac{1+\beta}{r_\pi} R_E)} (v_{id} - (-v_{id})) =$$

$$\boxed{\text{Gain} = \frac{-g_m R_C}{(1 + \frac{1+\beta}{r_\pi} R_E)}}$$



$$\boxed{\text{Gain} = \frac{-\beta R_C}{r_\pi + (1 + \beta) R_E} \approx \frac{-R_C}{R_E}}$$