

EEI 184

1.Revision

2.Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current(Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source

FET Current Sources

Dr. M. Shiple

Advanced Electronic Circuits (EEI 184), 2018

1.Revision

2.Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current(Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source

- 1** 1.Revision
- 2** 2.Two-Tran. and current Amp.
- 3** 3. No Three-Transistor Current Source
Reference Current(Reduce resistors)
- 4** 4. r_o Output Resistance
Wilson Current Mirror
- 5** 5. Bias-Independent Current Source

EEI 184

1.Revision

2. Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current (Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



1.Revision




Channel Capacitance

Oxide capacitance:

$$= \frac{\text{permittivity of the silicon dioxide}(3.45 \times 10^{-11})(F/m)}{\text{thickness}(m)} = F/m^2$$
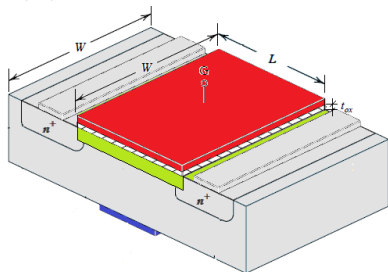
$$C_{OX} = \frac{\epsilon_{OX}}{t_{OX}}$$
$$C = C_{OX}WL = F$$



t_{OX} of $0.13\mu m$ technology = 2.7 nm, 45nm technology = 1.4 nm.

- 1.Revision
- 2. Two-Tran. and current Amp.
- 3. No Three-Transistor Current Source
- Reference Current(Reduce resistors)
- 4. r_o Output Resistance
- Wilson Current Mirror
- Bias-Independent Current Source

1. Revision

2. Two-Tran. and current Amp.

3. No Three-Transistor Current Source


Reference Current (Reduce resistors)

4. r_o Output Resistance

Wilson Current Mirror

Bias-Independent Current Source

Applying V_{DS}

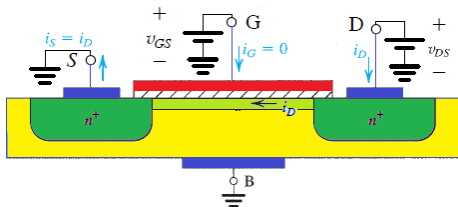

Process transconductance parameter (electron mobility μ_n)

$$k'_n = \mu_n C_{OX} = (m^2/V \cdot s)(F/m^2) = A/V^2$$

MOSFET transconductance parameter

$$K_n = k'_n \frac{W}{L} = A/V^2$$

Drain Current

$$I_D = 0.5K_n(V_{GS} - V_t)^2$$

Finite Output Resistance

1. Revision

2. Two-Trans. and current Amp.


3. No Three-Transistor Current Source

Reference Current (Reduce resistors)

4. r_o Output Resistance

Wilson Current Mirror

Bias-Independent Current Source

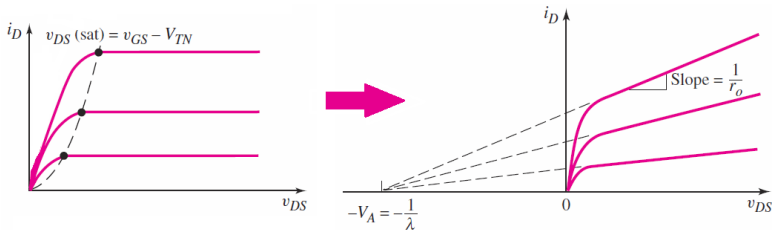

$$I_D = \frac{1}{2} K_n V_{OV}^2 (1 + \lambda V_{DS})$$

$$V_A = \frac{1}{\lambda} \quad r_o = \frac{V_A}{I_{DQ}}$$

λ : (lambda) is a positive quantity called the channel-length modulation parameter

EEI 184

1.Revision

2. Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current (Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



2. Two-Tran. and current Amp.



Two-Transistor Current Source

1. Revision

2. Two-Tran. and current Amp.

3. No Three-Transistor Current Source

Reference Current (Reduce resistors)

4. r_o Output Resistance

Wilson Current Mirror

Bias-Independent Current Source

- Identical transistors M_1 and M_2 .
- $V_{TN1} = V_{TN2}$.
- $K_{n1} = K_{n2}$.
- Both tran. @ saturation.


$$I_{REF} = 0.5K_{n1}(V_{GS} - V_{TN1})^2$$

$$V_{GS} = V_{TN2} + \sqrt{\frac{2I_{REF}}{K_{n1}}}$$

Therefore

$$I_o = 0.5K_{n2} \left(\left(V_{T2} + \sqrt{\frac{2I_{REF}}{K_{n1}}} \right) - V_{T2} \right)^2$$

$$\therefore I_o = I_{REF}$$

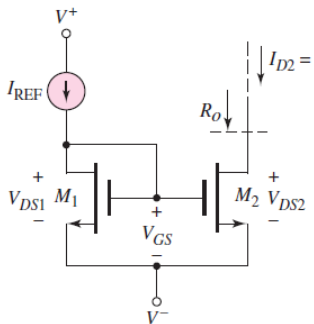

$$I_o = 0.5K_{n2}(V_{GS} - V_{TN2})^2$$

Current Amplifier

1. Revision

2. Two-Tran. and current Amp.

3. No Three-Transistor Current Source

Reference Current (Reduce resistors)

4. r_o Output Resistance


Wilson Current Mirror

Bias-Independent Current Source



- $V_{TN1} = V_{TN2}$.
- $K_{n1} \neq K_{n2}$.
- Both tran. @ saturation.

$$I_o = K_{n2} \left(\left(V_{TN2} + \sqrt{\frac{I_{REF}}{K_{n1}}} \right) - V_{TN2} \right)^2$$
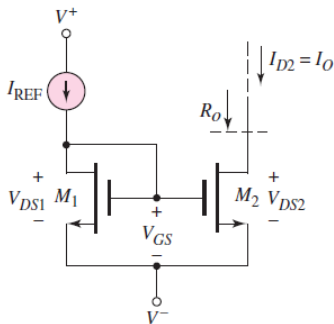
$$\therefore I_o = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} I_{REF}$$



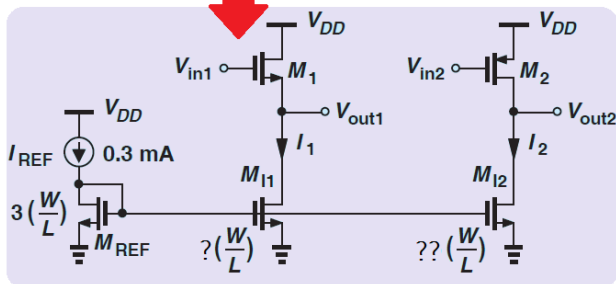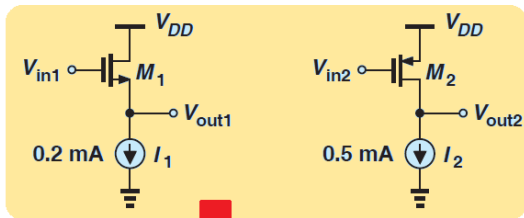- 1.Revision
- 2. Two-Tran. and current Amp.
- 3. No Three-Transistor Current Source
- Reference Current (Reduce resistors)
- 4. r_o Output Resistance
- Wilson Current Mirror
- Bias-Independent Current Source



$$I_o = \left(\frac{W}{L}\right)_2 \frac{I_{REF}}{\left(\frac{W}{L}\right)_1} \Rightarrow ? = 3 \frac{I_1}{I_{REF}} = 2 \quad ?? = 5$$

Output Resistance Two-Transistors

1. Revision

2. Two-Tran. and current Amp.



3. No Three-Transistor Current Source

Reference Current (Reduce resistors)

4. r_o Output Resistance


Wilson Current Mirror

Bias-Independent Current Source

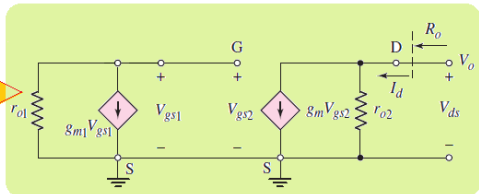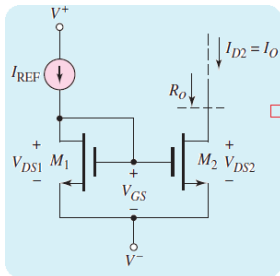

$$R_o = \frac{V_o}{I_o} = r_{o2}$$

$$V_A = \frac{1}{\lambda} \quad r_o = \frac{V_A}{I_{DQ}}$$

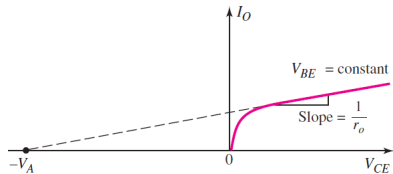

EEI 184

1.Revision

2. Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current (Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



3. No Three-Transistor Current Source



1.Revision

2.Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current(Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



MOS devices draw a negligible gate current

$$I_G = 0$$

On the other hand, channel-length modulation in the current-source transistors does lead to additional errors.

EEI 184

1.Revision

2. Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current(Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



Reference Current(Reduce resistors)



Replace Resistor

1. Revision

2. Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current (Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source

$$0.5K_{n1}(V_{GS1} - V_{T1})^2 = 0.5K_{n3}(V_{GS3} - V_{T3})^2$$

$$V_{GS1} + V_{GS3} = V^+ - V^- = V$$

$$\text{Assume } K'_{n1} = K'_{n3} \quad V_{T1} = V_{T3}$$

$$\left(\frac{W}{L}\right)_1 (V_{ov1})^2 = \left(\frac{W}{L}\right)_3 (V_{ov3})^2$$



$$\left(\frac{(W/L)_3}{(W/L)_1}\right) = x$$

$$V_{ov1} = \sqrt{x}V_{ov3} \Rightarrow$$

$$V_{GS1} = \sqrt{x}V_{GS3} + V_T(1 - \sqrt{x})$$

$$V_{GS1}(1 + \sqrt{x}) = \sqrt{x}V + V_T(1 - \sqrt{x})$$
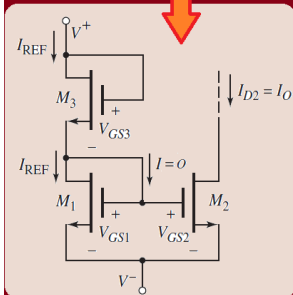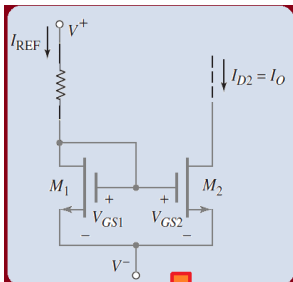
$$V_{GS1} = \frac{\sqrt{x}}{(1 + \sqrt{x})}V + \frac{(1 - \sqrt{x})}{(1 + \sqrt{x})}V_T$$



Cont.:Replace Resistor

1. Revision

2. Two-Trans.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current (Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror



Bias-
Independent
Current
Source

$$V_{GS1} = \frac{\sqrt{x}}{(1 + \sqrt{x})} V + \frac{(1 - \sqrt{x})}{(1 + \sqrt{x})} V_T = V_{GS2}$$

$$\therefore x = \left(\frac{(W/L)_3}{(W/L)_1} \right)$$

$$\therefore V = V^+ - V^-$$

$$I_O = 0.5K_{n2}(V_{GS2} - V_T)^2$$

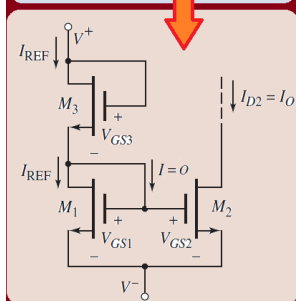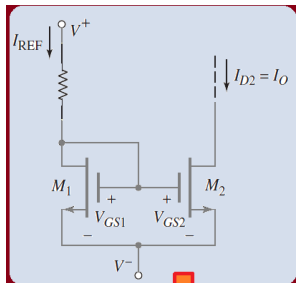

Example: Replace Resistor

1. Revision

2. Two-Tran. and current Amp.

3. No Three-Transistor Current Source

Reference Current (Reduce resistors)

4. r_o Output Resistance

Wilson Current Mirror

Bias-Independent Current Source

for saturation (M_2):

$$V_{DS2} \geq V_{GS2} - V_T \Rightarrow$$

$$V_{GS2} = V_{DS2} + V_T = 0.8V = V_{GS1}$$


$$\left(\frac{W}{L}\right)_2 = \frac{I_O}{0.5K_{n1}(V_{GS1} - V_T)^2} = 7.5$$

$$\left(\frac{W}{L}\right)_1 = 12.5$$

$$\therefore V_{GS1} + V_{GS3} = V^+ - V^- = 2.5$$

$$V_{GS3} = 1.7V$$

$$\left(\frac{W}{L}\right)_3 = 1.18$$

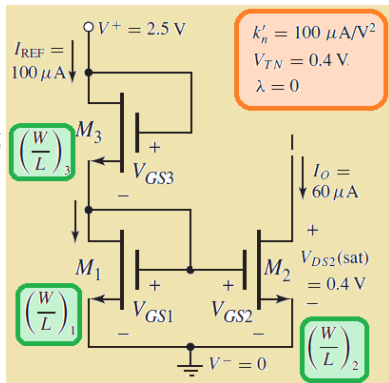

Example: Challenge your self

1. Revision

2. Two-Tran.
and current
Amp.


3. No Three-
Transistor
Current
Source

Reference
Current (Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source

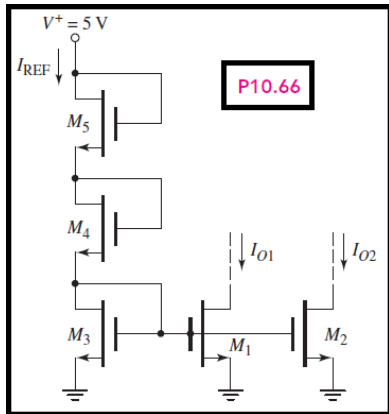

EEI 184

1.Revision

2. Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current(Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



4. r_o Output Resistance



EEI 184

1.Revision

2.Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current(Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



Wilson Current Mirror



1.Revision

2.Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current(Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



Cascode

is a shortened version of “*cas*caded *cat*hode”,
from the days of vacuum tubes .

Wilson Current Source

1. Revision

2. Two-Tran. and current Amp.


3. No Three-Transistor Current Source

Reference Current (Reduce resistors)

4. r_o Output Resistance

Wilson Current Mirror

Bias-Independent Current Source

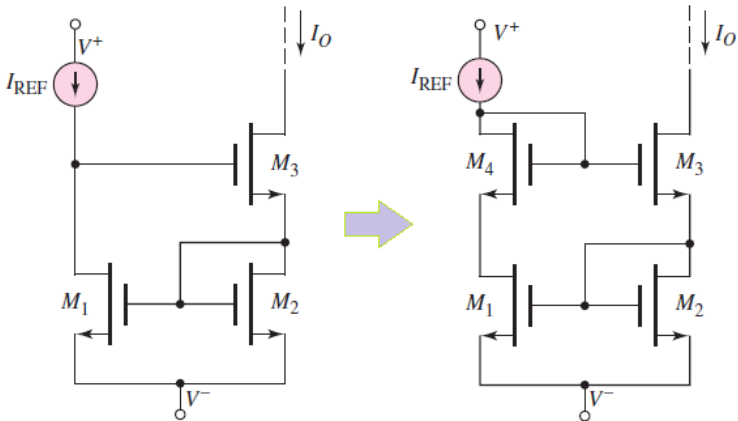

Since λ is not zero, the ratio $\frac{I_O}{I_{REF}}$ is slightly different from the aspect ratios. This problem is solved in the **modified Wilson current source**

Wilson Output resistance

1. Revision

2. Two-Tran. and current Amp.



3. No Three-Transistor Current Source

Reference Current (Reduce resistors)

4. r_o Output Resistance

Wilson Current Mirror

Bias-Independent Current Source

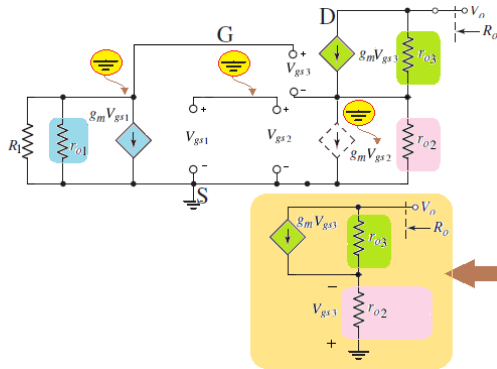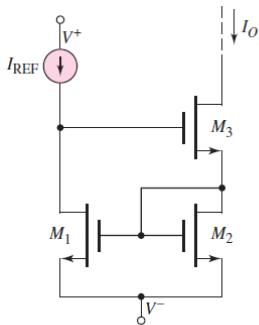

Wilson Current Mirror

1. Revision

2. Two-Tran. and current Amp.

3. No Three-Transistor Current Source

Reference Current (Reduce resistors)

4. r_o Output Resistance

Wilson Current Mirror

Bias-Independent Current Source

$$I_o = g_m V_{gs3} + \left(\frac{V_o - I_o r_{o2}}{r_{o3}} \right)$$

$$\therefore V_{gs3} = -I_o r_{o2}$$


$$r_{o3} I_o = -r_{o3} g_m I_o r_{o2} + V_o - I_o r_{o2}$$

$$\frac{V_o}{I_o} = r_{o3} + r_{o3} g_m r_{o2} + r_{o2}$$

$$\frac{V_o}{I_o} = r_{o3} + r_{o2} (g_m r_{o3} + 1)$$

$$\text{normally } g_m r_{o3} \gg 1$$

Therefore the R_o is improved.

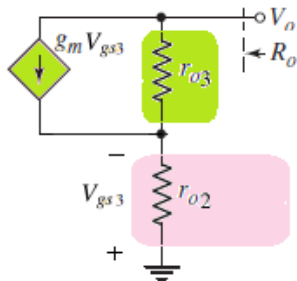

EEI 184

1.Revision

2. Two-Tran.
and current
Amp.

3. No Three-
Transistor
Current
Source

Reference
Current (Reduce
resistors)

4. r_o Output
Resistance

Wilson Current Mirror

Bias-
Independent
Current
Source



Bias-Independent Current Source



$$R = \frac{(1 - \sqrt{X})}{\sqrt{0.5K_n I_{D2}}}$$

The currents I_{D1} and I_{D2} are independent of the supply voltages V^+ and V^- as long as M_2 and M_3 are biased in the saturation region. As the difference, $V^+ - V^-$, increases, the values of V_{DS2} and V_{SD3} increase but the currents remain essentially constant.

Hum Noise Again!!

