

Shiple

Introduction to
Op Amp

Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

Operational Amplifier (Op-Amp)

Dr. M. Shiple

Refer to Electronic circuits ,Adel Sedra , 7th edition

Electronic Circuits (Elec I), 2023

Shiple

Introduction to
Op Amp

Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

- 1 Introduction to Op Amp**
- 2 Inverting Input circuits**
- 3 Non-Inverting Input circuits**
- 4 Op Amp applications**
- 5 Effect of Op-Amp Parameters**
 - Advanced Concepts on Op-Amp

Brief History

Shiple

Introduction to
Op Amp

Inverting Input
circuits


Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

Fairchild Lab:

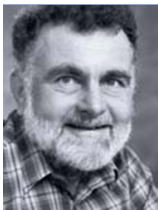

- 1964: **Bob Widlar** designs the first op-amp: the *702*.
 - Open-loop gain over 7000.
 - Using only 9 transistors and cost \$300 per op-amp.
- 1965: **He** designs also the *709* \equiv μ A741.
 - Open-loop gain around 70,000.
 - lack of short circuit protection.
- 1968: **Dave Fullagar** designs the *741*.
 - Add fixed internal compensation capacitor, that eliminates the external circuitry, unlike its predecessors.
 - Add extra transistors for short circuit protection.
 - Gain around 250,000.

Schematic of UA741 Op Amp

Shiple

Introduction to Op Amp


Inverting Input circuits

Non-Inverting Input circuits

Op Amp applications

Effect of Op-Amp Parameters

Advanced Concepts on Op-Amp

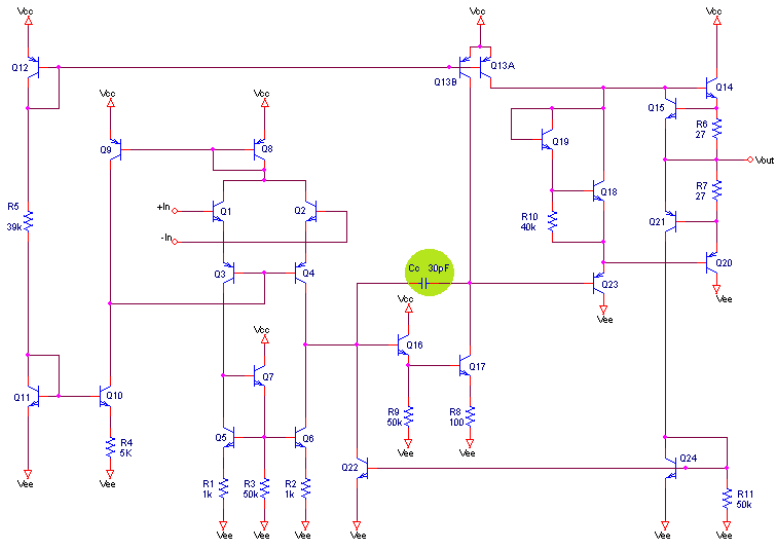

Terminals of Op Amp (2.1.1)

Shiple

Introduction to
Op Amp



Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

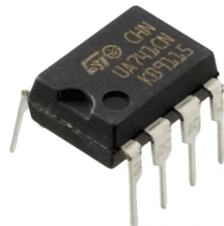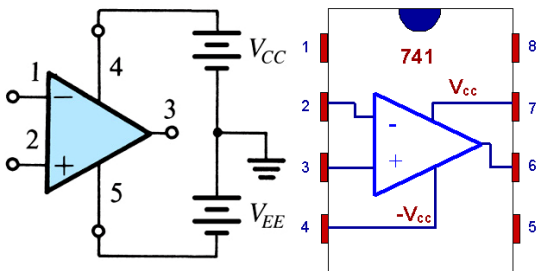

Characteristics of the Ideal Op Amp (2.1.2)

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

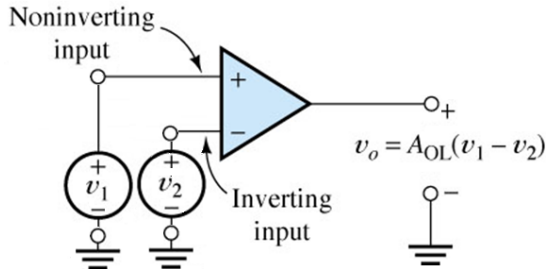

- Ideal gain is defined as $V_3 = A(V_2 - V_1)$
- Ideal input impedance is infinite.
- Ideal output impedance is zero.
- Differential gain; open-loop gain (A) is infinite
- Bandwidth gain is constant from dc to high frequencies

Characteristics of the Ideal Op Amp

Shiple

Introduction to Op Amp


Inverting Input circuits

Non-Inverting Input circuits

Op Amp applications

Effect of Op-Amp Parameters

Advanced Concepts on Op-Amp

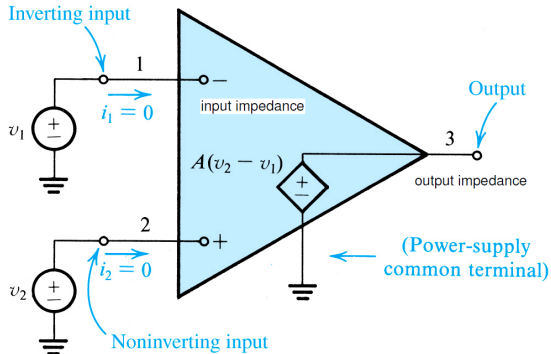

The Inverting Amplifier(2.2)

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

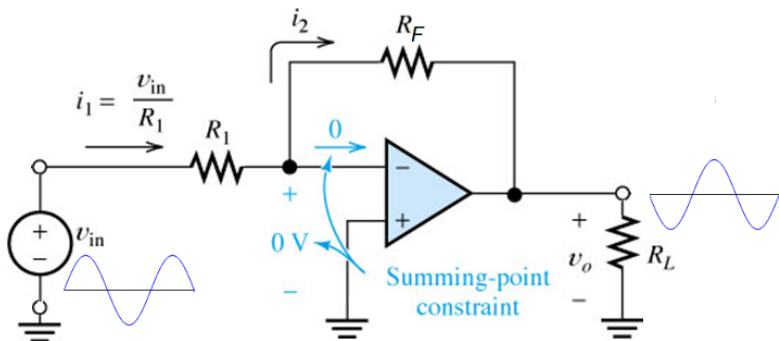

$$V_{out} = -\frac{R_F}{R_1} V_{in}$$

The Weighted Summer (2.2.4)

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

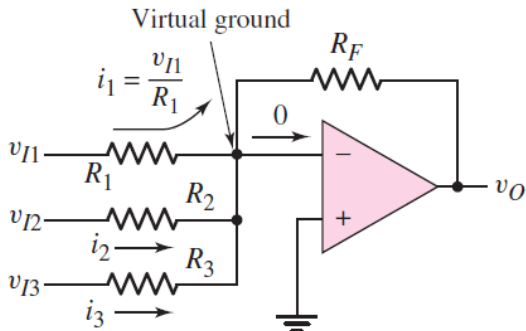

$$V_{out} = -\frac{R_F}{R_1} V_{I1} - \frac{R_F}{R_2} V_{I2} - \frac{R_F}{R_3} V_{I3}$$

The Non-Inverting Configuration(2.3)

Shiple

Introduction to
Op Amp



Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

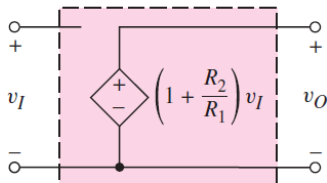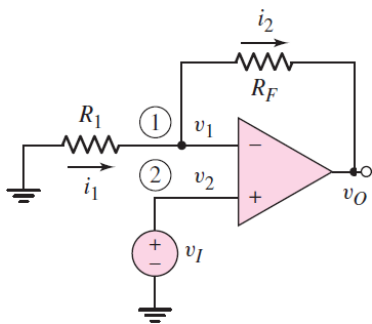

$$G = 1 + \frac{R_F}{R_1}$$

The Voltage Follower (Buffer) (2.3.4)

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

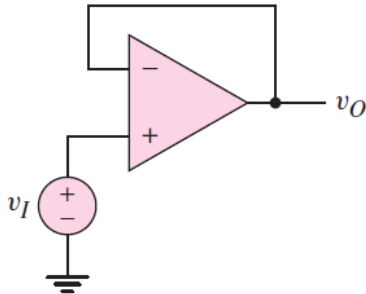

- unity-gain amplifier.
- impedance transformer.

The Voltage Follower (Cont.)

Shiple

Introduction to
Op Amp



Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

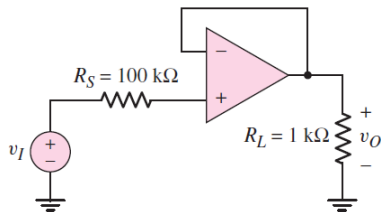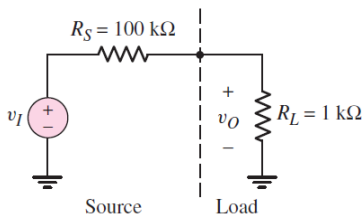

loading problem

Difference Amplifier (2.4)

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

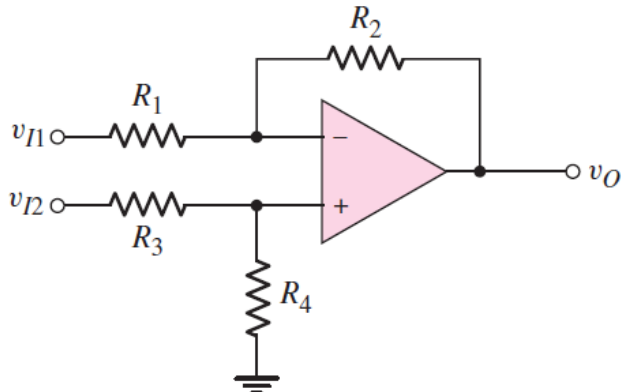

The inverting configuration suffers from a low input resistance. what about the R_F to save the gain!!!

Input Impedance of Difference Amplifier

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

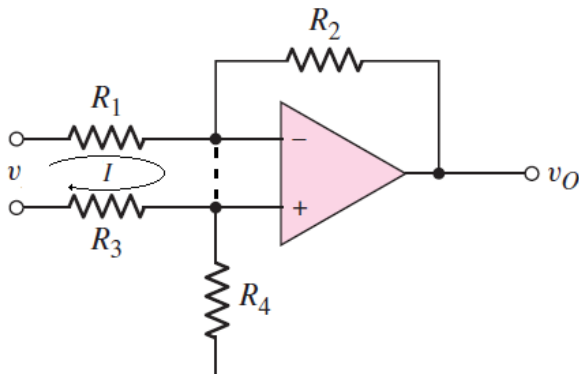

($R_i = 2R$) The difference configuration suffers from a low input resistance. Dilemma of input impedance and high gain !!! To change the gain two resistor should be changed and keep the resistors ratio too.

The Instrumentation Amplifier

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

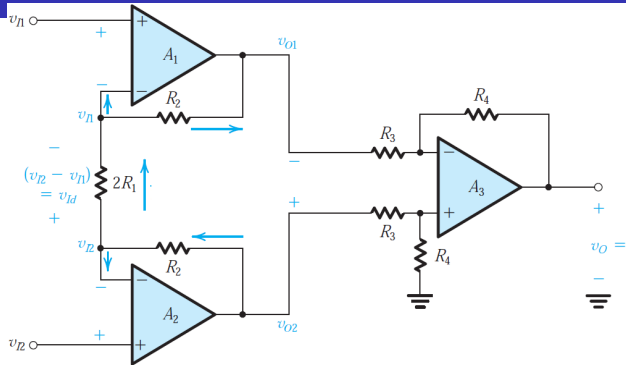

- To vary the differential gain A_d , two resistors have to be varied simultaneously (voltage follower).
- The two amplifier channels in the first stage are not perfectly matched.
- The input common-mode signal v_{ICM} is amplified in the first stage.

The Instrumentation Amplifier (2.4.2)

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

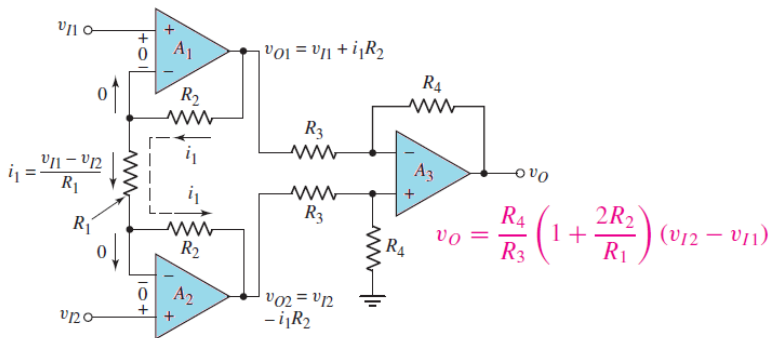

Change just one resistor to tune the gain!!!

The Effect of Finite Gain on Inverting Amplifier

Shiple

Introduction to
Op Amp

Inverting Input
circuits


Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

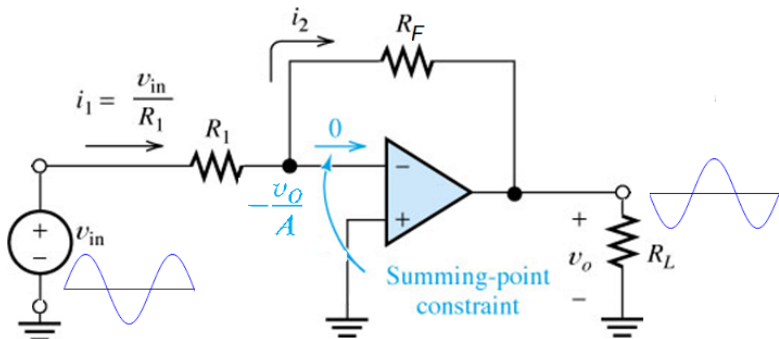Q: How does the gain expression change if open loop gain (A_{ol}) is not assumed to be infinite?



Input Resistances

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

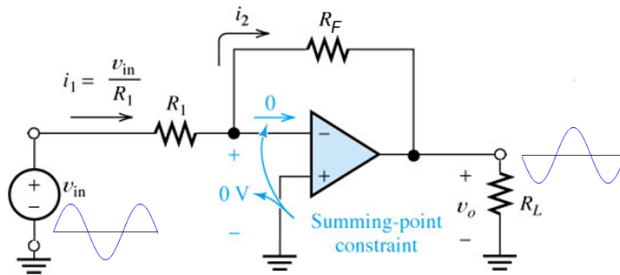

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{in}}{\frac{V_{in}}{R_1}} = R_1$$

The inverting configuration suffers from a low input resistance. what about the R_F to save the gain!!!

Percent gain error

Shiple

Introduction to
Op Amp

Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

$$\begin{aligned} PGE &= \frac{G_{ideal} - G_{finite}}{G_{ideal}} \\ &= \frac{1 + \frac{R_F}{R_1}}{A + 1 + \frac{R_F}{R_1}} \times 100 \end{aligned}$$

Common-Mode Rejection Ratio (CMRR)

Shiple

Introduction to
Op Amp


Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

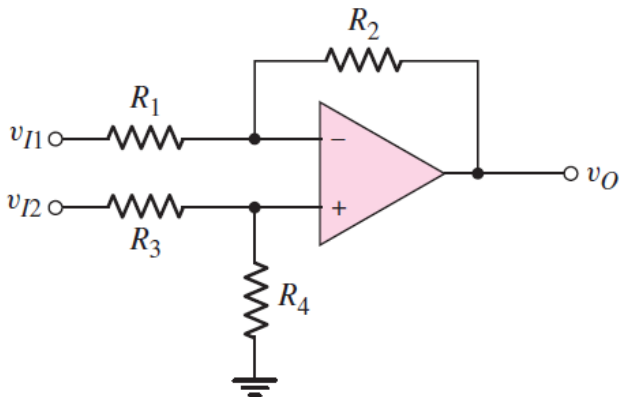

$$v_O = A_d v_{Id} + A_{cm} v_{Icm}$$

$$CMRR = 20 \log \frac{|A_d|}{|A_{cm}|}$$

Common Mode Input Signal

Shiple

Introduction to Op Amp


Inverting Input circuits

Non-Inverting Input circuits

Op Amp applications


Effect of Op-Amp Parameters

Advanced Concepts on Op-Amp

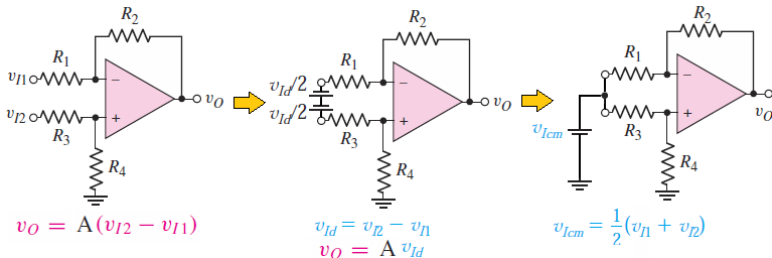

Difference amplifier

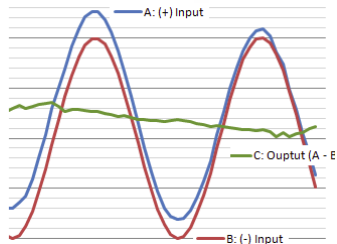is one that responds to the difference between the two signals applied at its input and ideally rejects signals that are common to the two inputs.



Differential and Common-Mode Signals

Shiple

Introduction to
Op Amp

Inverting Input
circuits


Non-Inverting
Input circuits

Op Amp
applications


Effect of
Op-Amp
Parameters

Advanced Concepts
on Op-Amp

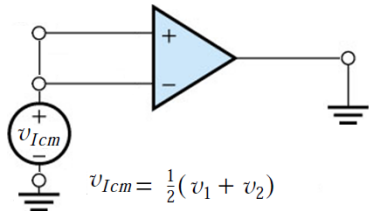- Ideal op amp has zero common-mode gain $\equiv \infty$ common mode rejection.


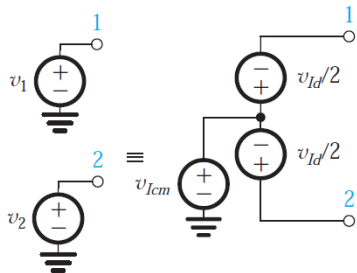
$$v_{Icm} = \frac{1}{2}(v_1 + v_2)$$
$$v_{Id} = v_2 - v_1$$



Common Mode Rejection Ratio

Shiple

Introduction to
Op Amp

Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters


Advanced Concepts
on Op-Amp

By applying superposition:

$$v_o = \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2 R_3}{R_1 R_4} \right) v_{cm}$$

$$A_{cm} = \frac{v_o}{v_{cm}} = \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2 R_3}{R_1 R_4} \right)$$
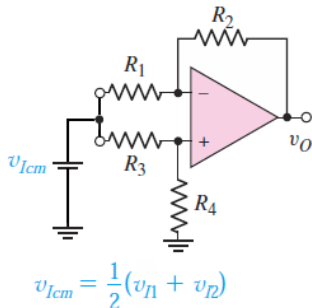
$$A_{cm} = \begin{cases} 0, & \frac{R_2}{R_1} = \frac{R_3}{R_4} \\ \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2 R_3}{R_1 R_4} \right) & \text{otherwise} \end{cases}$$



$$v_o = A_d v_{Id} + A_{cm} v_{cm}$$

$$CMRR = 20 \log \frac{A_d}{A_{cm}}$$

*cm=common mode

Op-Amp Parameters

Shiple

Introduction to
Op Amp

Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters



Advanced Concepts
on Op-Amp

Maximum Peak-to-Peak Output (MPP)

The output cannot swing all the way to the value of the supply voltages because there are small voltage drops in the final stage of the op amp.

Frequency Response

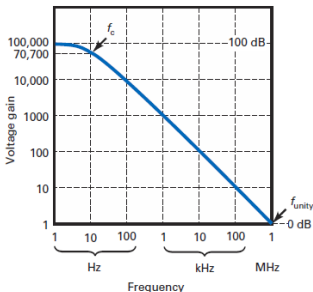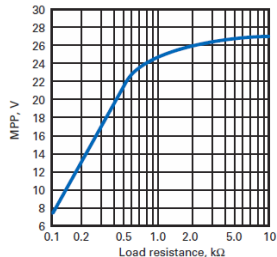The unity-gain frequency is the frequency at which the voltage gain equals 1.



Op-Amp Parameters

Shiple

Introduction to
Op Amp

Inverting Input
circuits

Non-Inverting
Input circuits

Op Amp
applications

Effect of
Op-Amp
Parameters


Advanced Concepts
on Op-Amp

Slew Rate

the charging and discharging of The compensating capacitor. This creates a speed limit on how fast the output of the op amp can change. $S_R = \frac{\Delta V_{out}}{\Delta t}$

Power Bandwidth

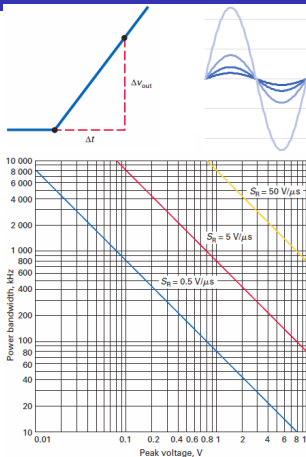where f_{max} is the highest frequency that can be amplified without slew-rate distortion



741 packaging

Shiple

Introduction to Op Amp

Inverting Input circuits

Non-Inverting Input circuits

Op Amp applications

Effect of Op-Amp Parameters

Advanced Concepts on Op-Amp

