
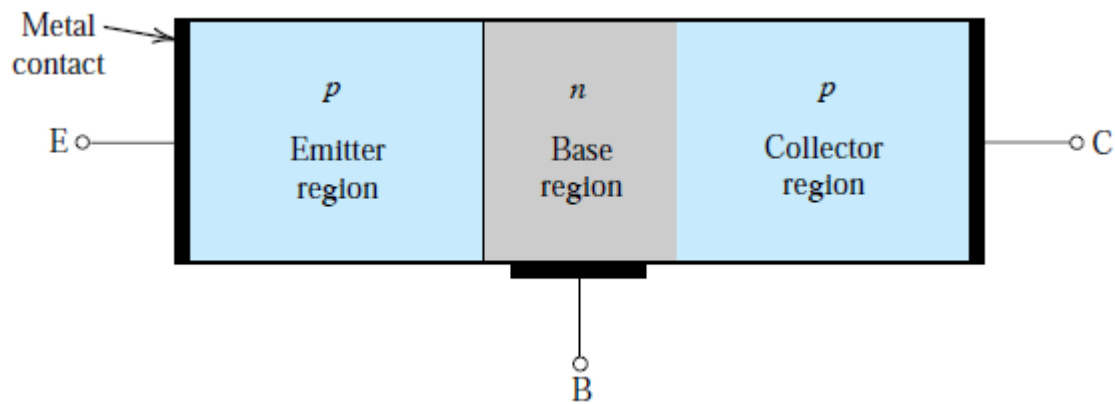



Bipolar Junction Transistor

BY:
Dr. M. Shiplo

Simplified Structure Of BJT

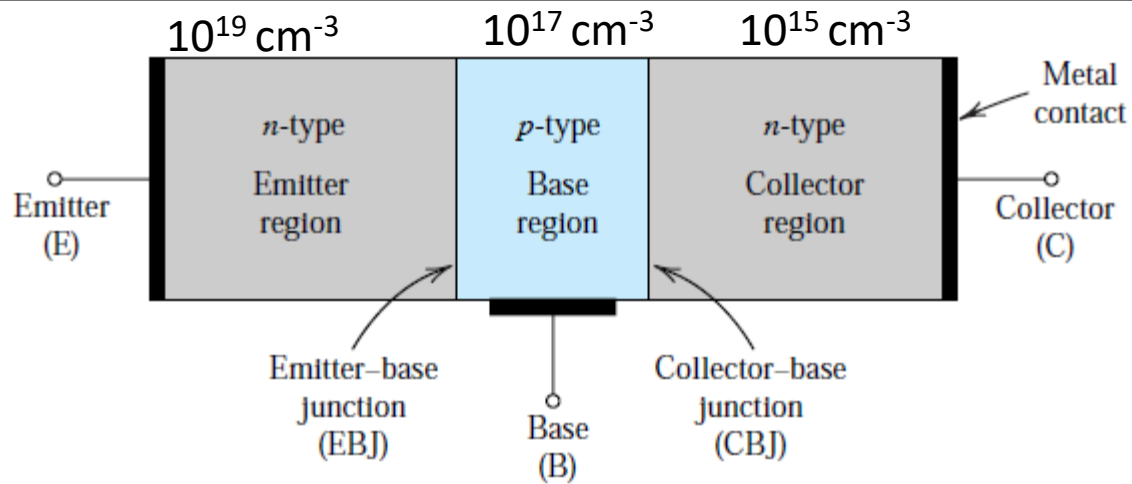

Current Flow in *NPN Transistor*

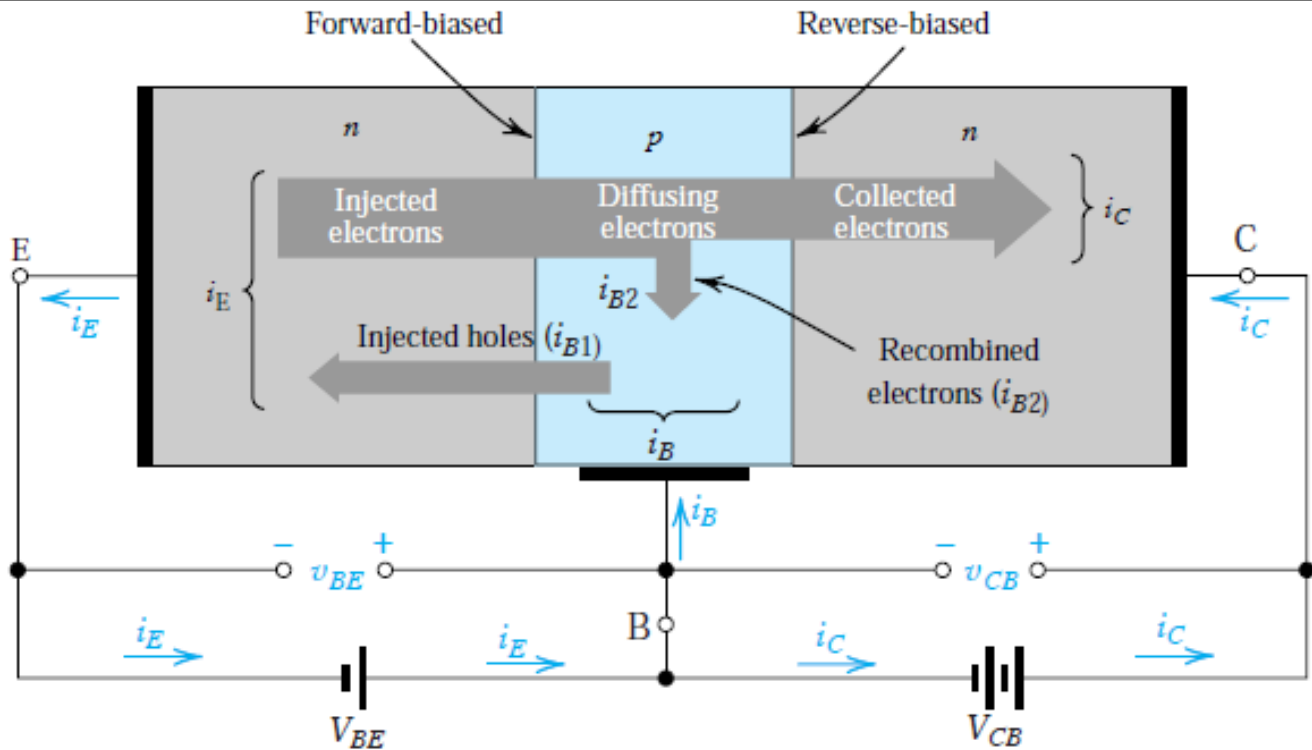


Saturation current

The Collector Current: $i_C = I_s e^{V_{BE}/V_T}$

thermal voltage = 25 mV



Current Flow in *NPN Transistor*

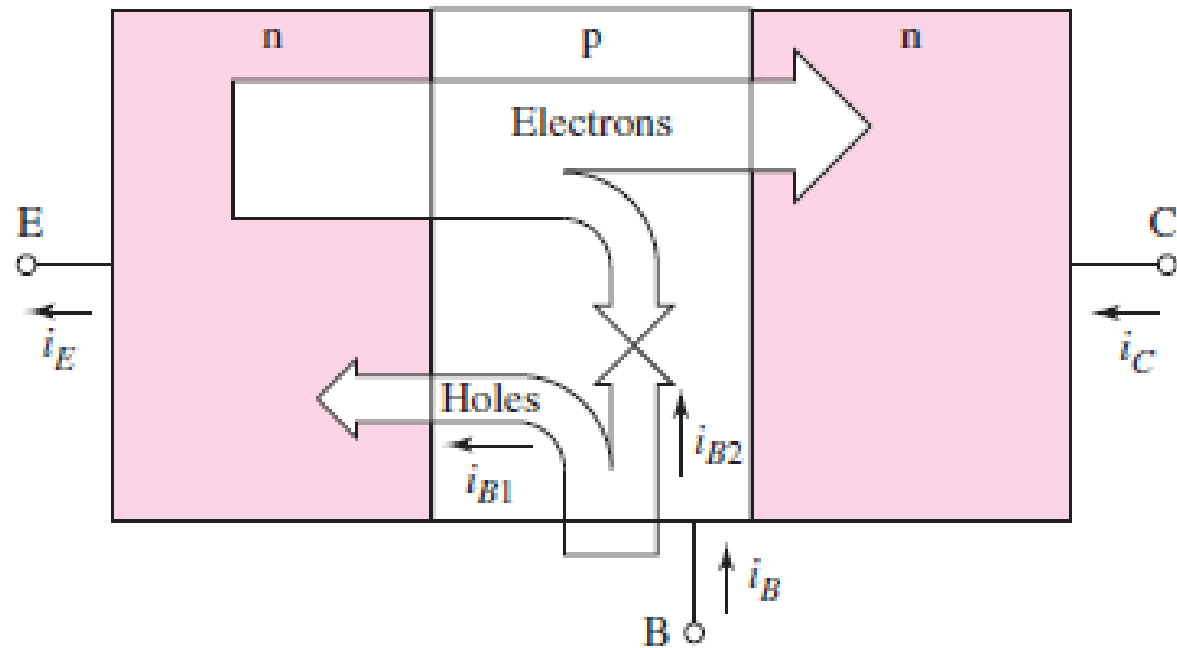

The Base Current:
$$i_B = \left(\frac{I_S}{\beta} \right) e^{v_{BE}/V} = \frac{i_C}{\beta}$$



Current Flow in *NPN Transistor*

Emitter Current:


$$i_E = i_C + i_B$$

$$i_C = \beta i_B$$

$$i_E = (1 + \beta) i_B$$

$$i_C = \left(\frac{\beta}{1 + \beta} \right) i_E$$

$$\alpha = \frac{\beta}{1 + \beta}$$

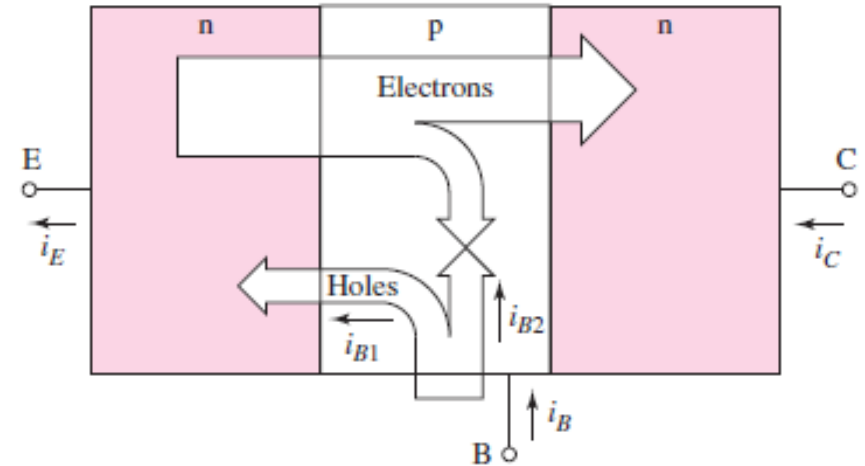

β : Common-emitter Current Gain

α : Common-base Current Gain





Summary of Current Relations

$$i_E = i_C + i_B$$

$$i_E = (1 + \beta)i_B$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$i_C = \beta i_B$$

$$i_C = \alpha i_E = \left(\frac{\beta}{1 + \beta} \right) i_E$$

$$\beta = \frac{\alpha}{1 - \alpha}$$



Example 6.2: pp 368 , Design

The transistor in the circuit has :

$$\beta = 100$$

v_{BE} of 0.7 V @ $i_C = 1$ mA.

$$I_C = 2 \text{ mA.}$$

$$V_C = +5 \text{ V}$$

$$i_E = i_C + i_B$$


$$i_C = \beta i_B$$

$$i_E = (1 + \beta) i_B$$

$$i_C = \alpha i_E = \left(\frac{\beta}{1 + \beta} \right) i_E$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

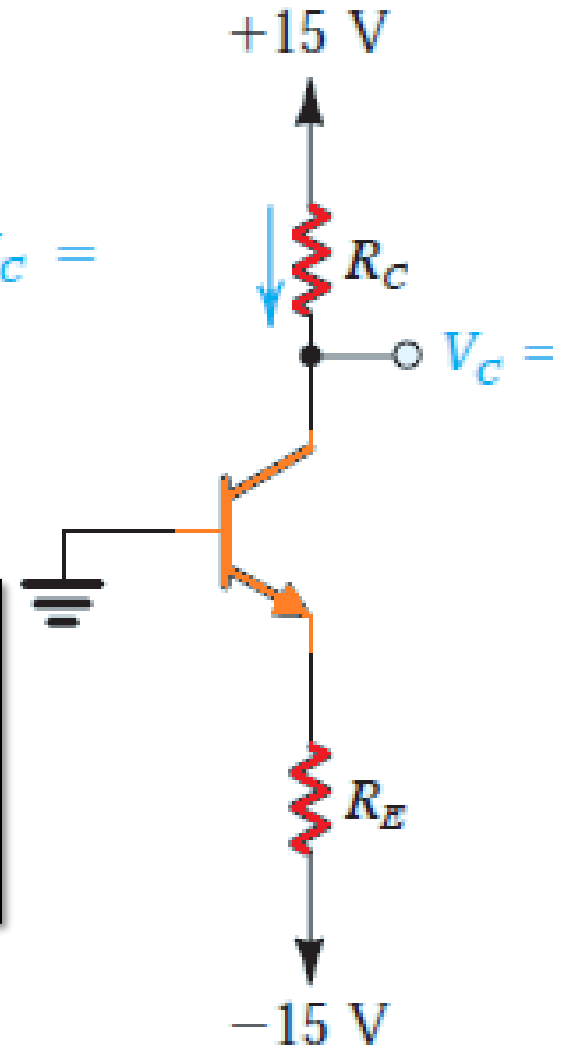

Example: Design

The transistor in the circuit has :

$$\beta = 100$$

v_{BE} of 0.7 V @ $i_C = 1$ mA.

$I_C = 2$ mA.

$$V_C = +5$$
 V

$$i_E = i_C + i_B$$


$$i_C = \beta i_B$$

$$i_E = (1 + \beta) i_B$$

$$i_C = \alpha i_E = \left(\frac{\beta}{1 + \beta} \right) i_E$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

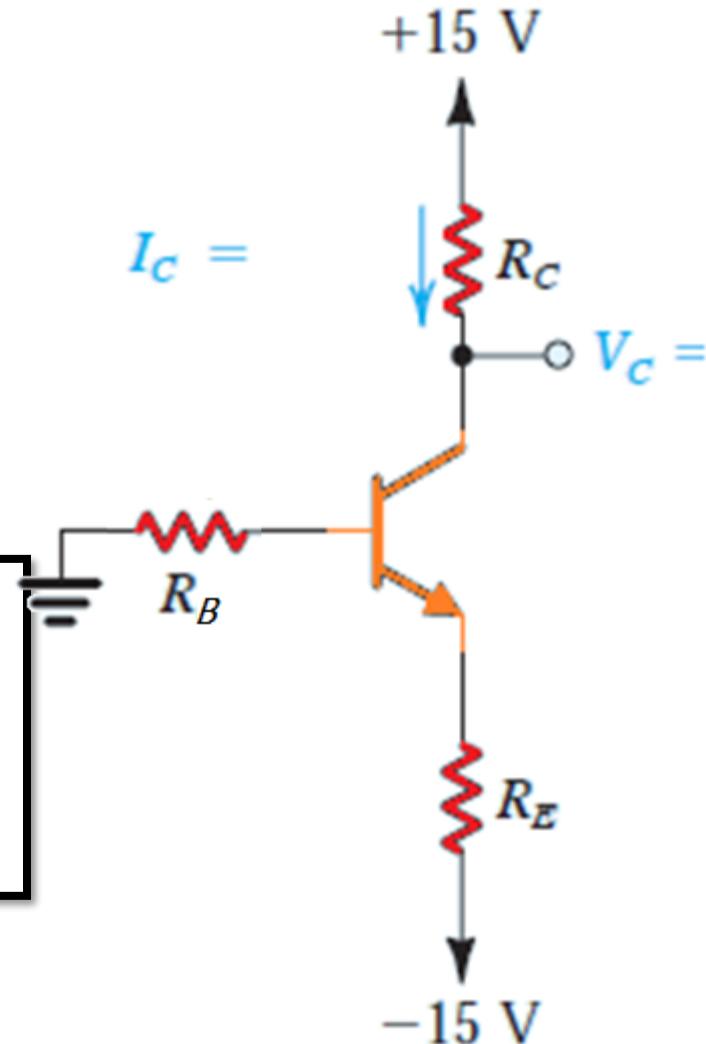

Homework




H.W : Exercise 6.13 &
Exercise 6.14 pp. 369






Current-Voltage Characteristics

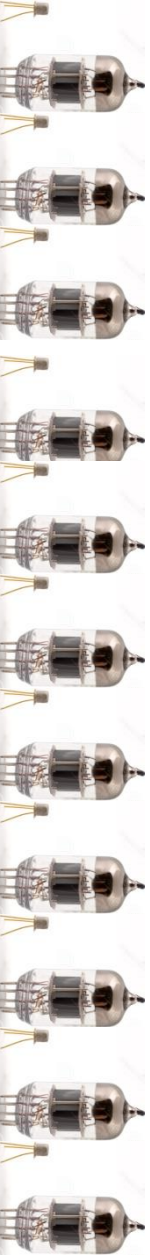

$i_C - v_{BE}, i_E - v_{BE}, i_B - v_{BE}$ characteristics


Diode

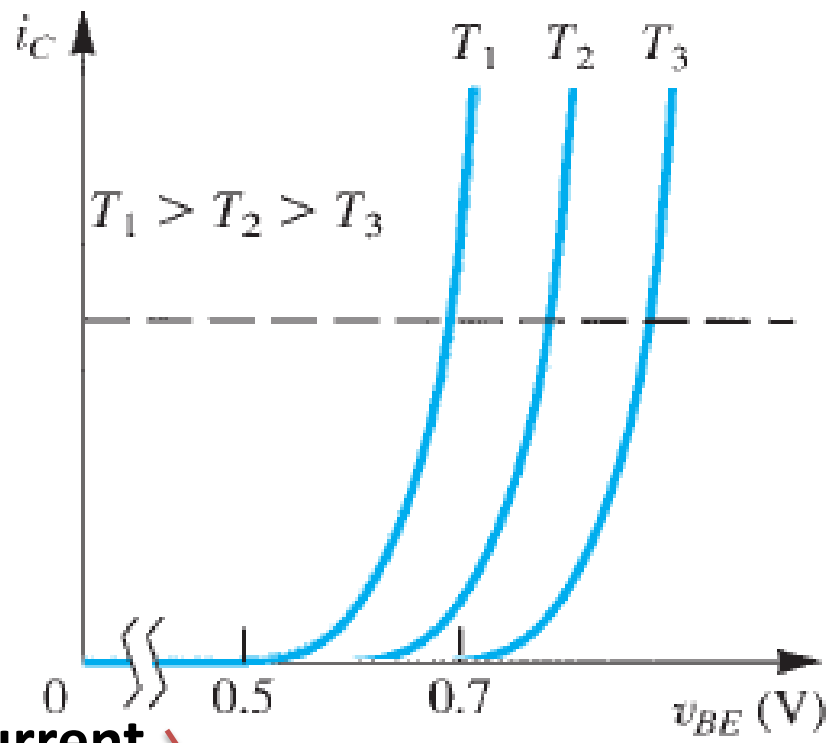

Saturation current

The Collector Current: $i_C = I_s e^{v_{BE}/V_T}$



thermal voltage = 25 mV

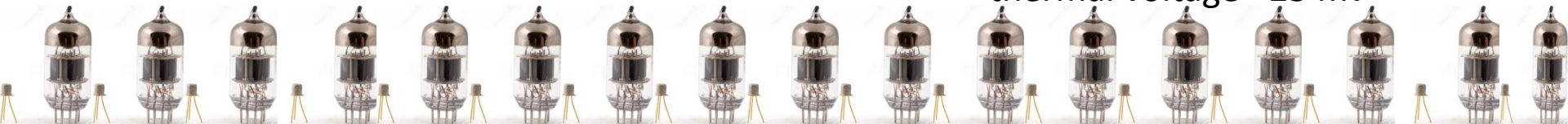

$i_C - v_{CE}$ characteristics Early Effect




common-emitter Characteristics


$$r_o = \frac{V_A}{I_C}$$

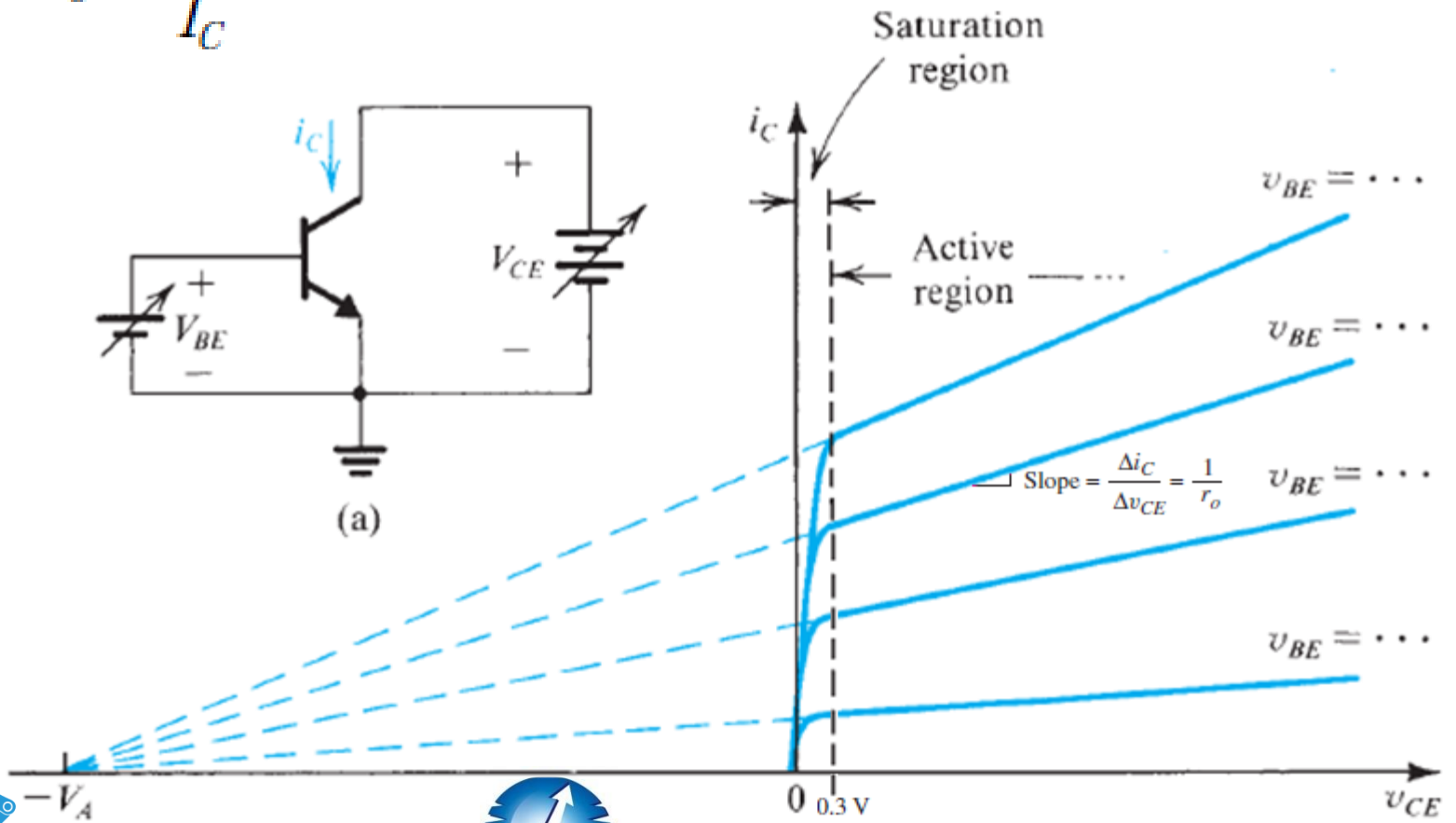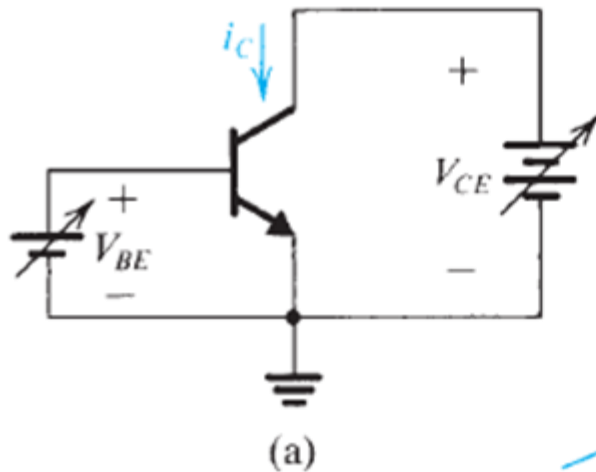



Load Line & Q-point

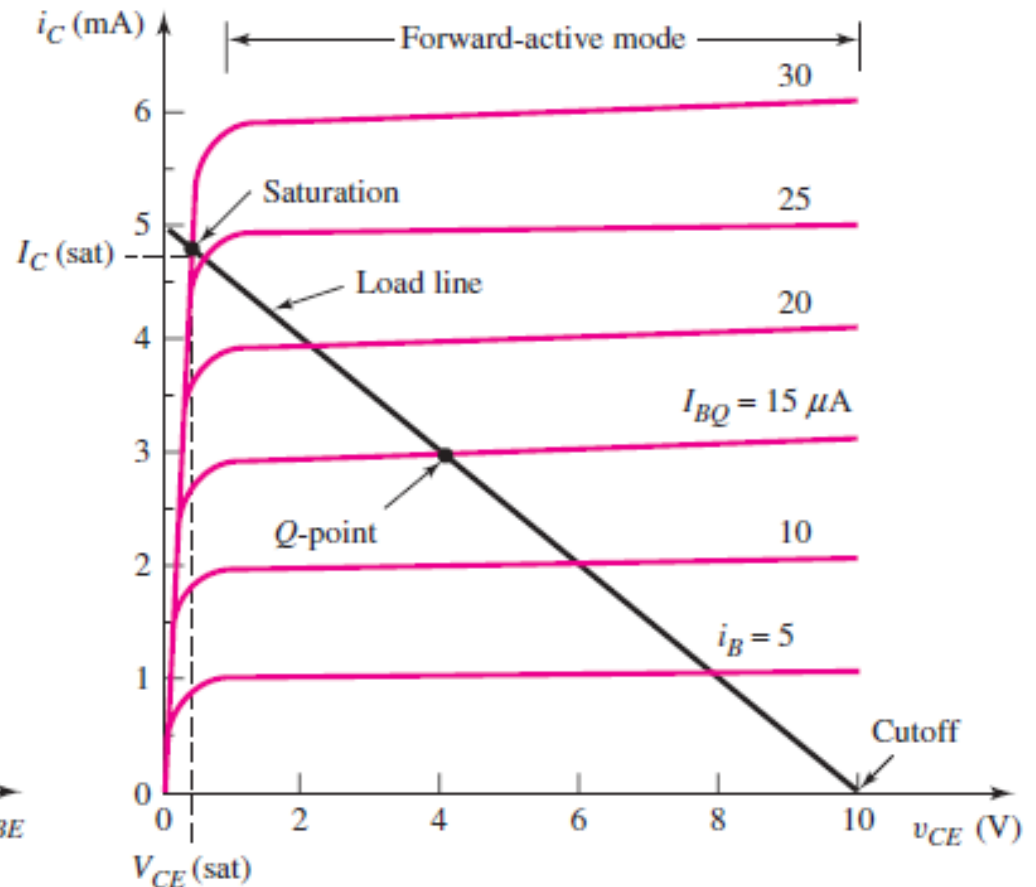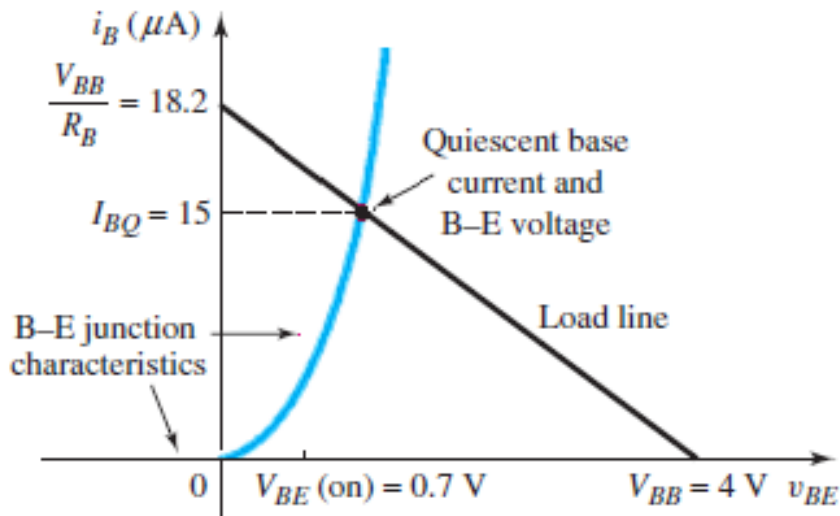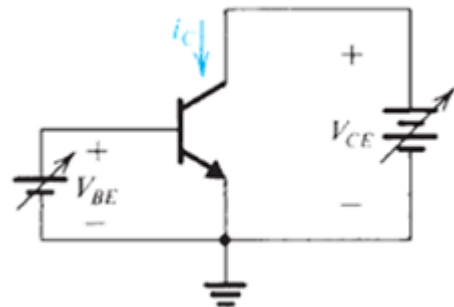

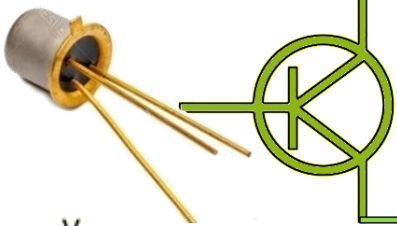


Example: by using BC107A NPN transistor ($\beta = 195$)

$$\frac{V_{CC}}{R_C + R_E}$$

7.5


$$\text{Slope} = -\frac{1}{R_C}$$

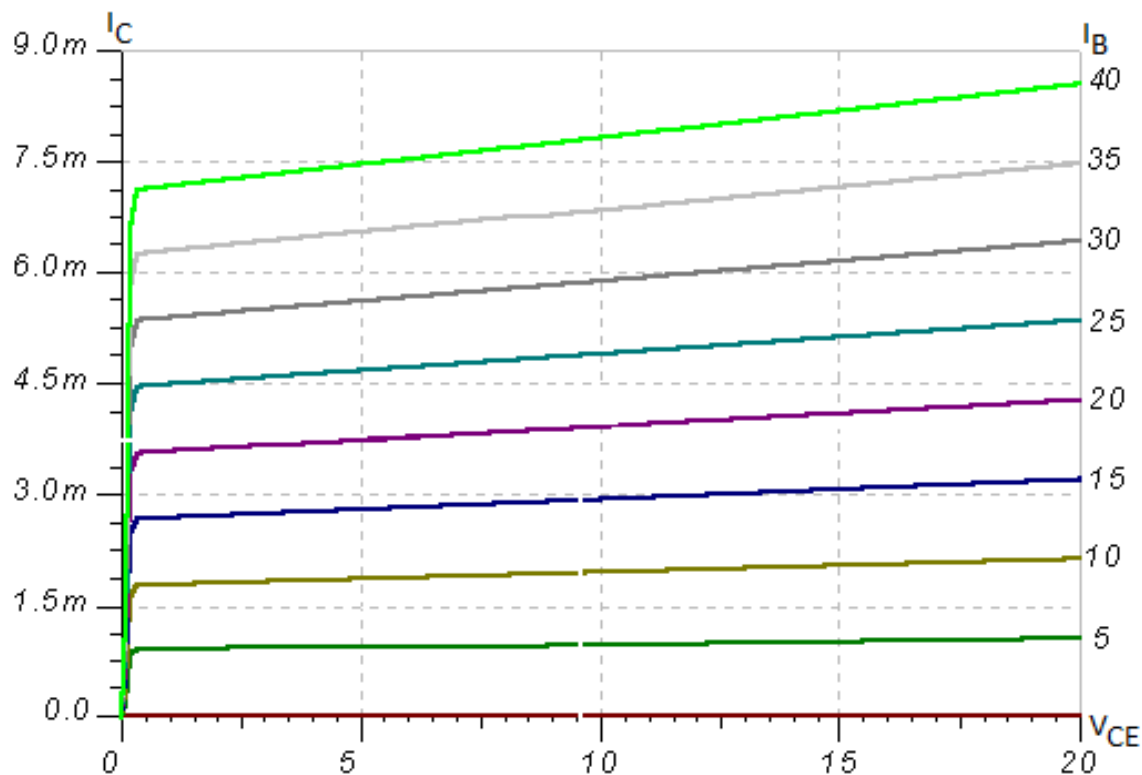

$I_B = 0.01$

$I_C = 1.95$

$V_{CE} = 11.1$

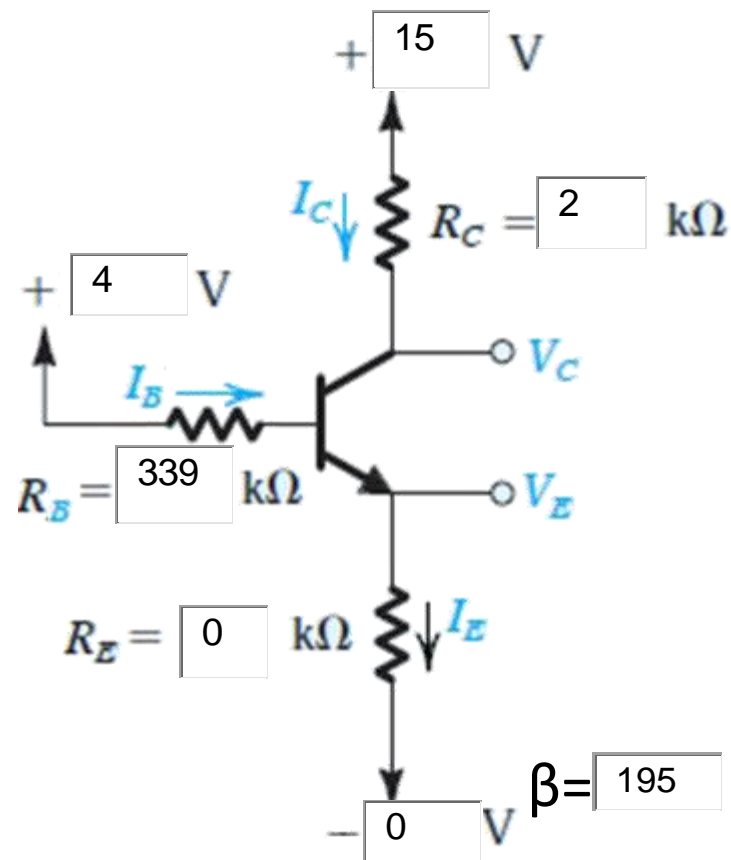



Example: by using BC107A NPN

$$\frac{V_{CC}}{R_C + R_E}$$



5


Design an amplifier to allocate Q point at the center with following specs $V_{BB}=V_{CC}=20\text{ v}$

(a) in the active mode with $V_{CE} = 5$


(b) at the edge of saturation

(c) deep in saturation with $\beta = 10$

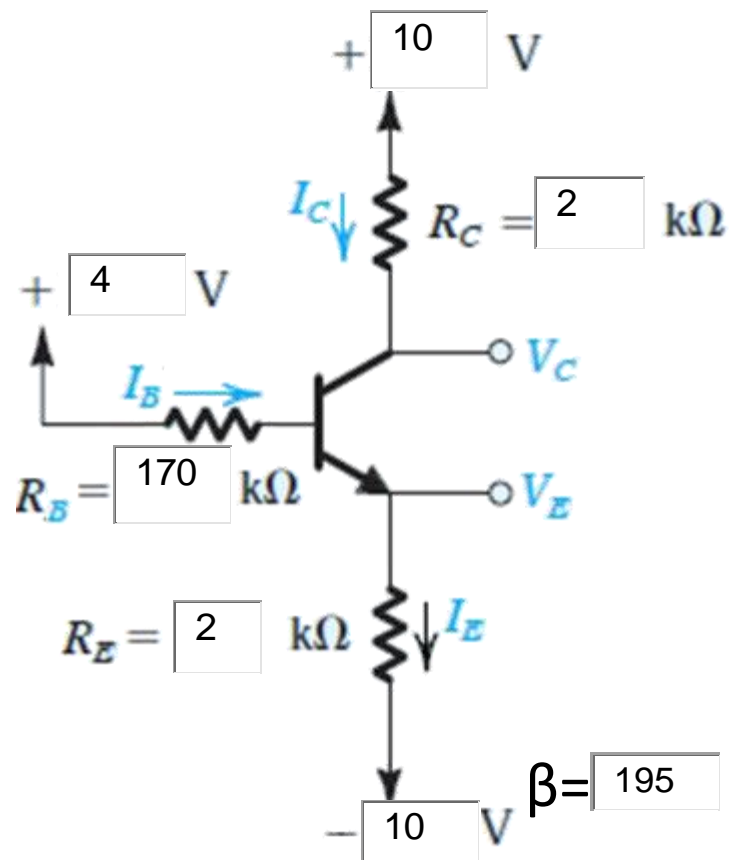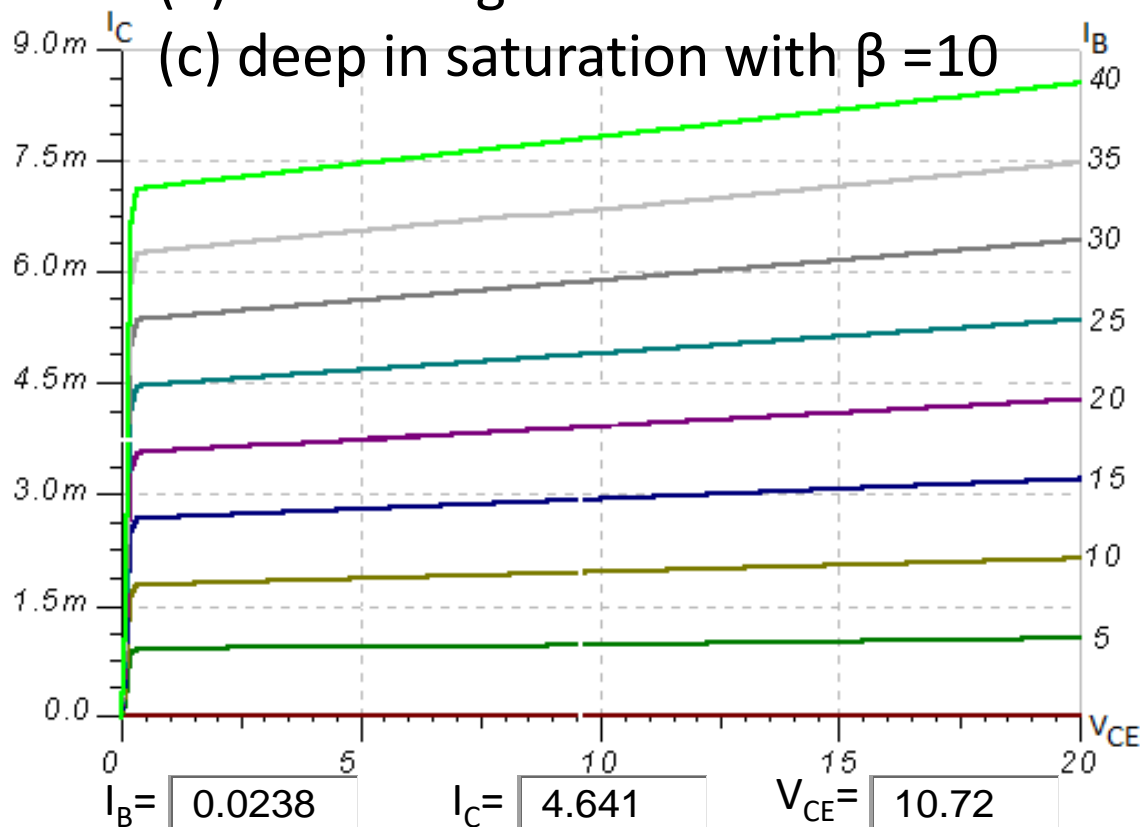


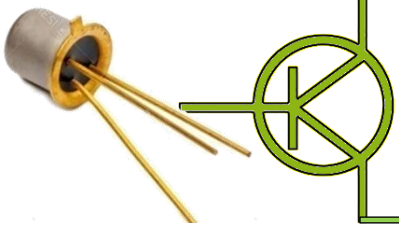


Conditions of the BJT in Various Modes

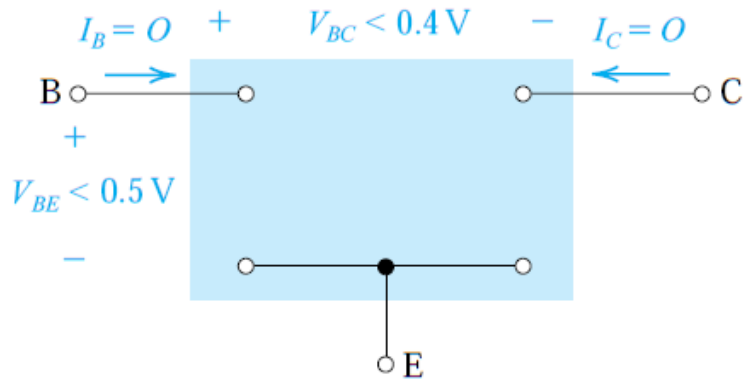

Cut off

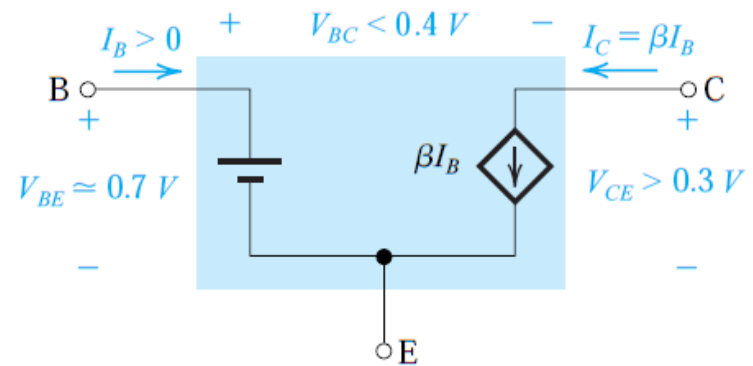

Active

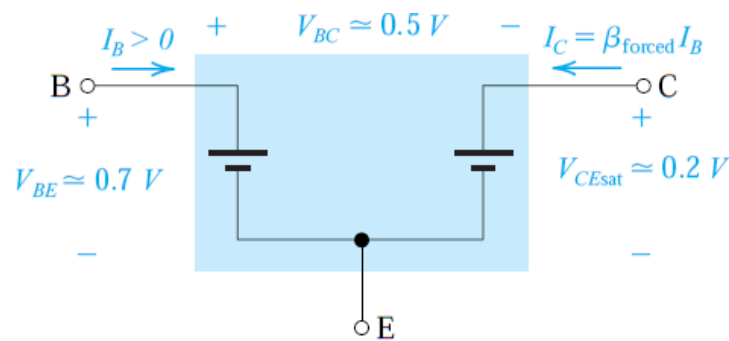

Saturation

