



Finite State Machines in VHDL

Dr. M. M. Shiple



Quote of the Day

Definitions

- **A** finite state machine (FSM) is a sequential circuit with “random” next-state logic.




Introduction


- The models selected will influence a design but there are no general indications as to which model is better.

Moore FSM

Process (clock, reset)

 


**concurrent
statements**

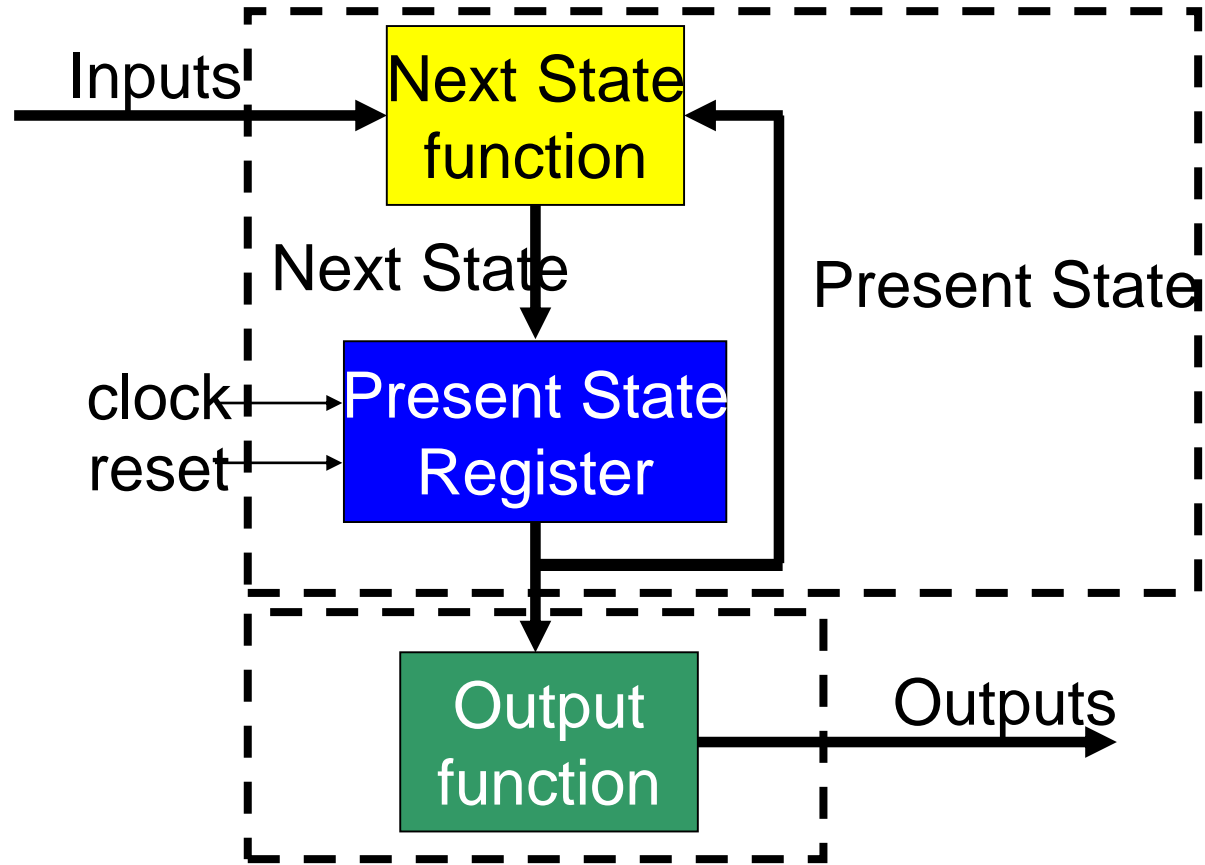


Mealy FSM

Process (clock, reset)

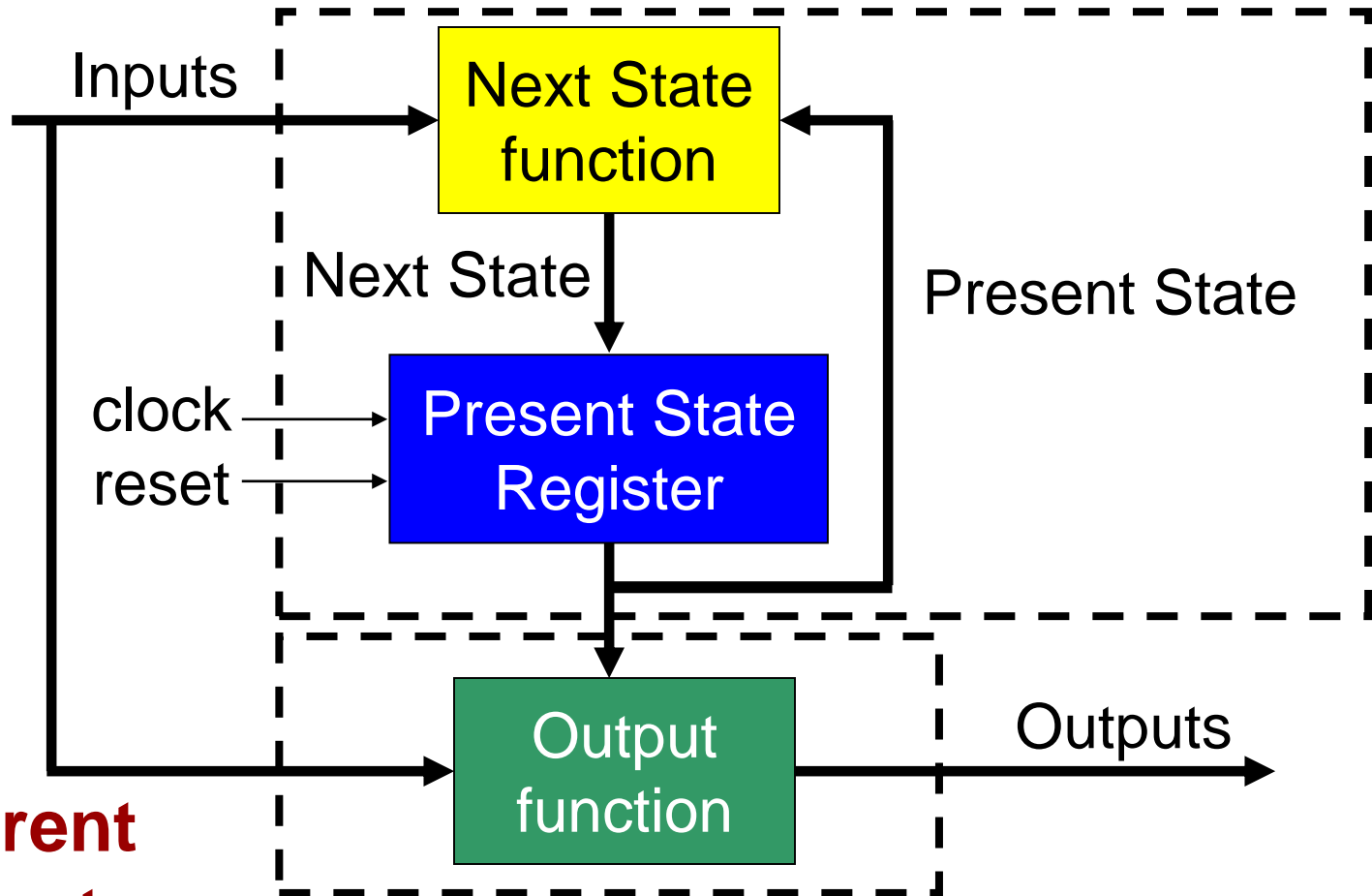

**concurrent
statements**

Moore vs. Mealy

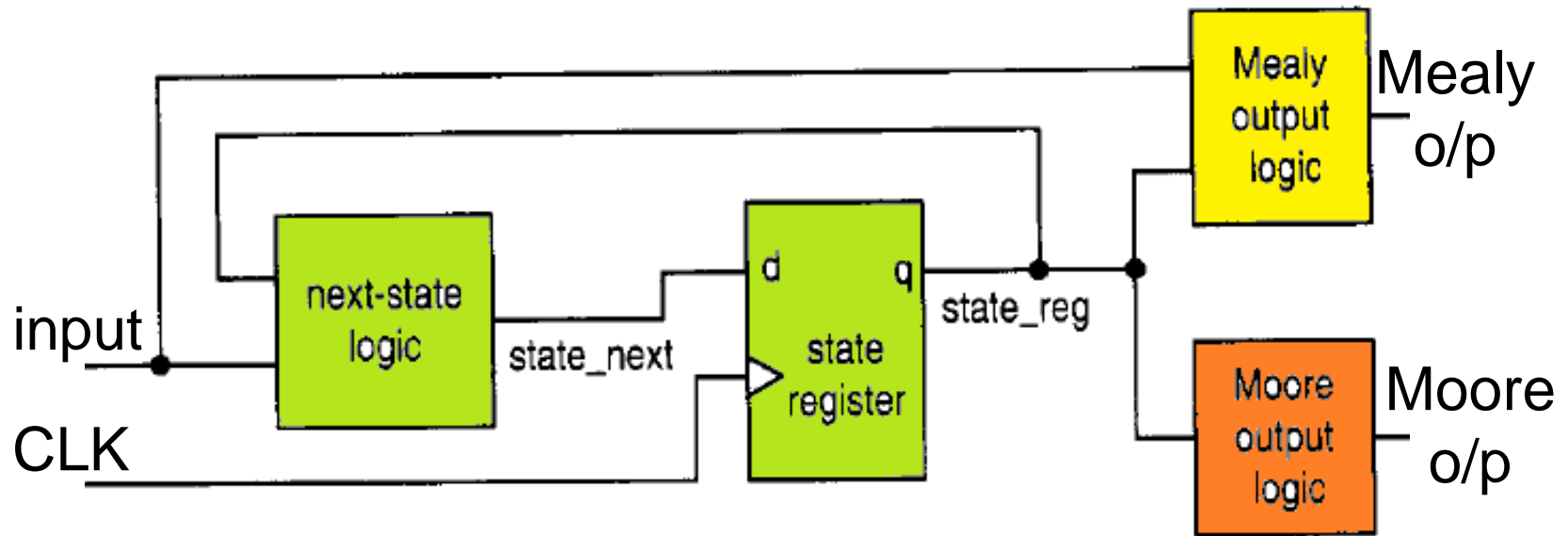




State Diagram by example


Moore FSM - Example 1

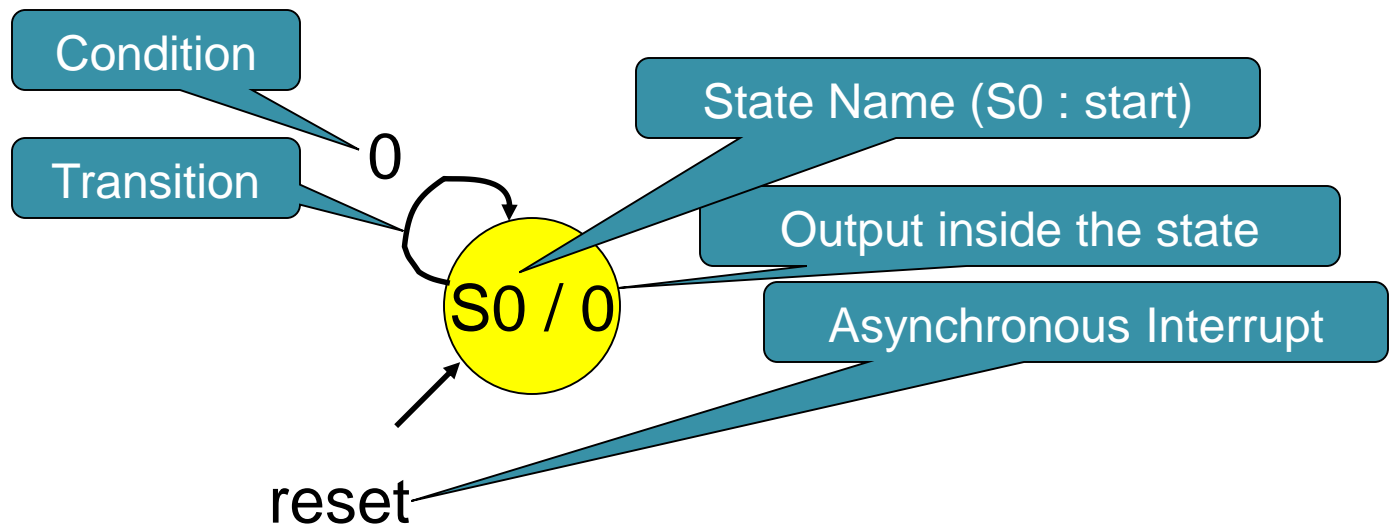- Draw Moore Recognizes Sequence “1 then 0”




Moore FSM - Example 1

- Define the output if the input='1';

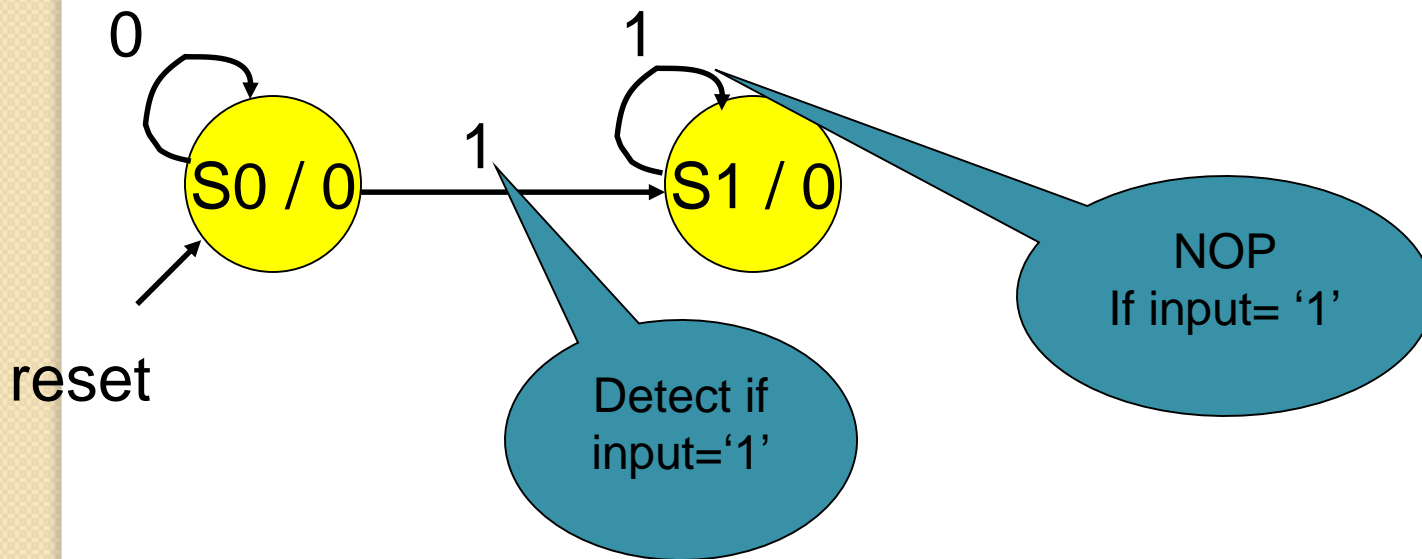


Moore FSM - Example 1

- The sequence complete perfectly

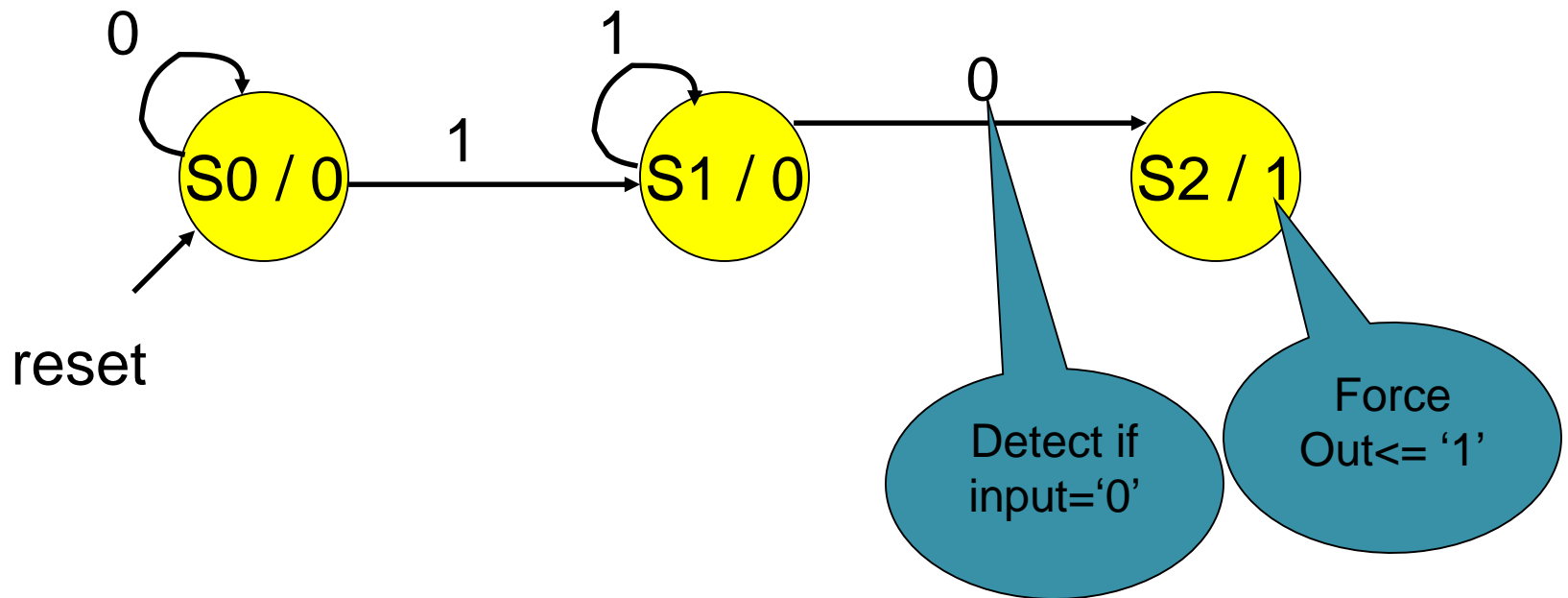

Moore FSM - Example I

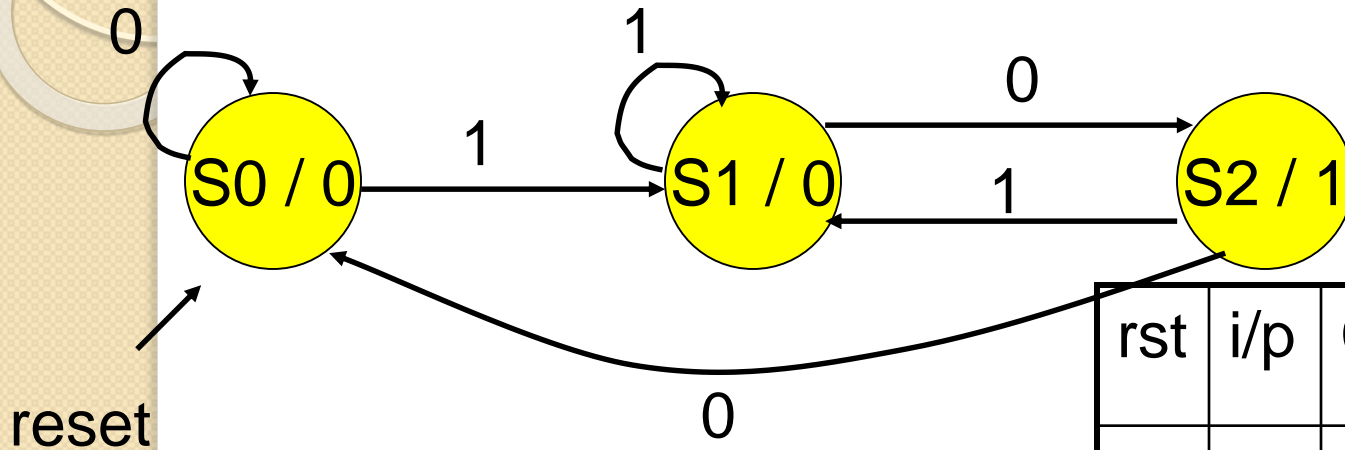


Each output cases need unique state


rst	i/p	Crt st	Nxt st	o/p
1	-	-	S0	0
0	0	S0	S0	0
0	1	S0	S1	0
0	0	S1	S2	1
0	1	S1	S1	0
0	0	S2	S0	0
0	1	S2	S1	0

Mealy FSM - Example I

- Draw sequence recognition with mealy

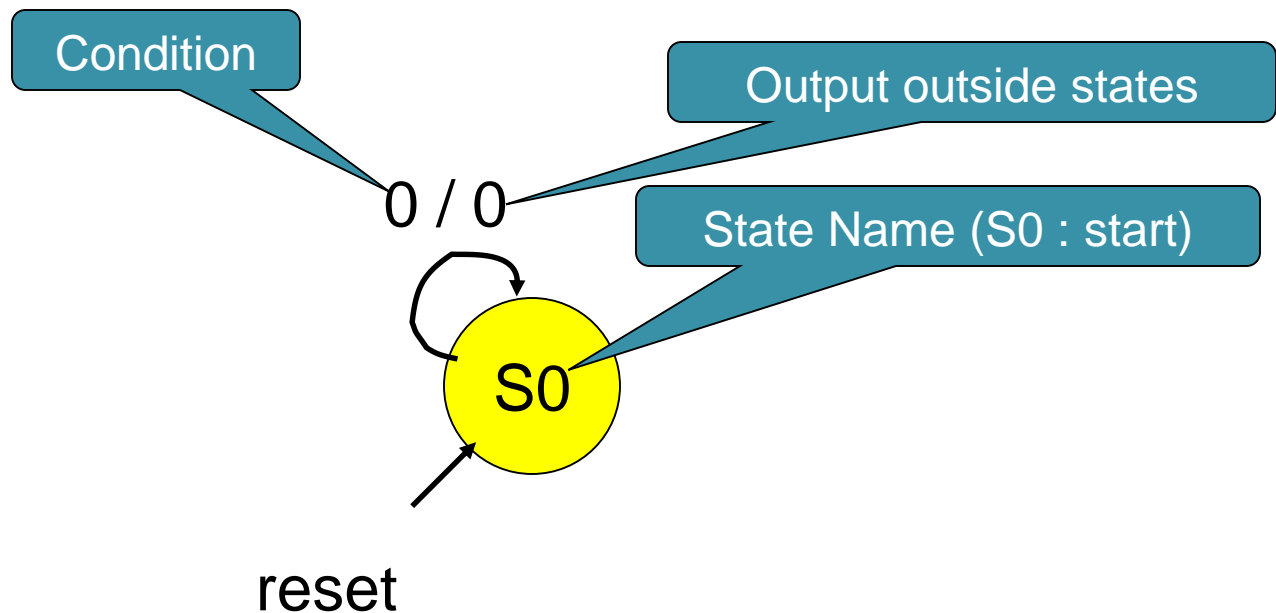

Mealy FSM - Example I

 

rst	i/p	Crt st	Nxt st	o/p
1	-	-	S0	0
0	0	S0	S0	0
0	1	S0	S1	0
0	0	S1	S0	1
0	1	S1	S1	0




Algorithmic State Machine (ASM)



by example

<http://Drshiple-courses.weebly.com/>



ASM Symbols

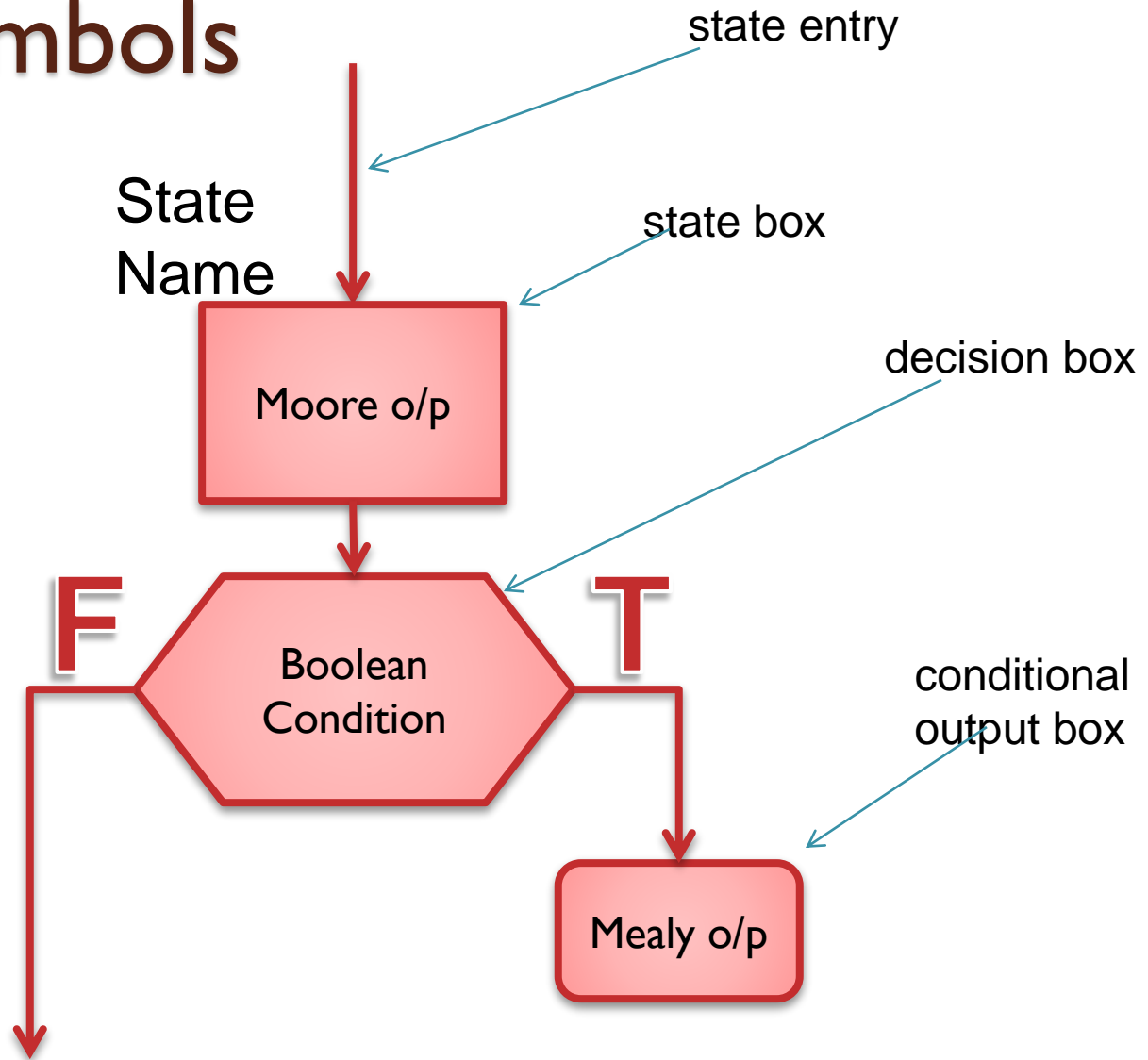



Moore ASM

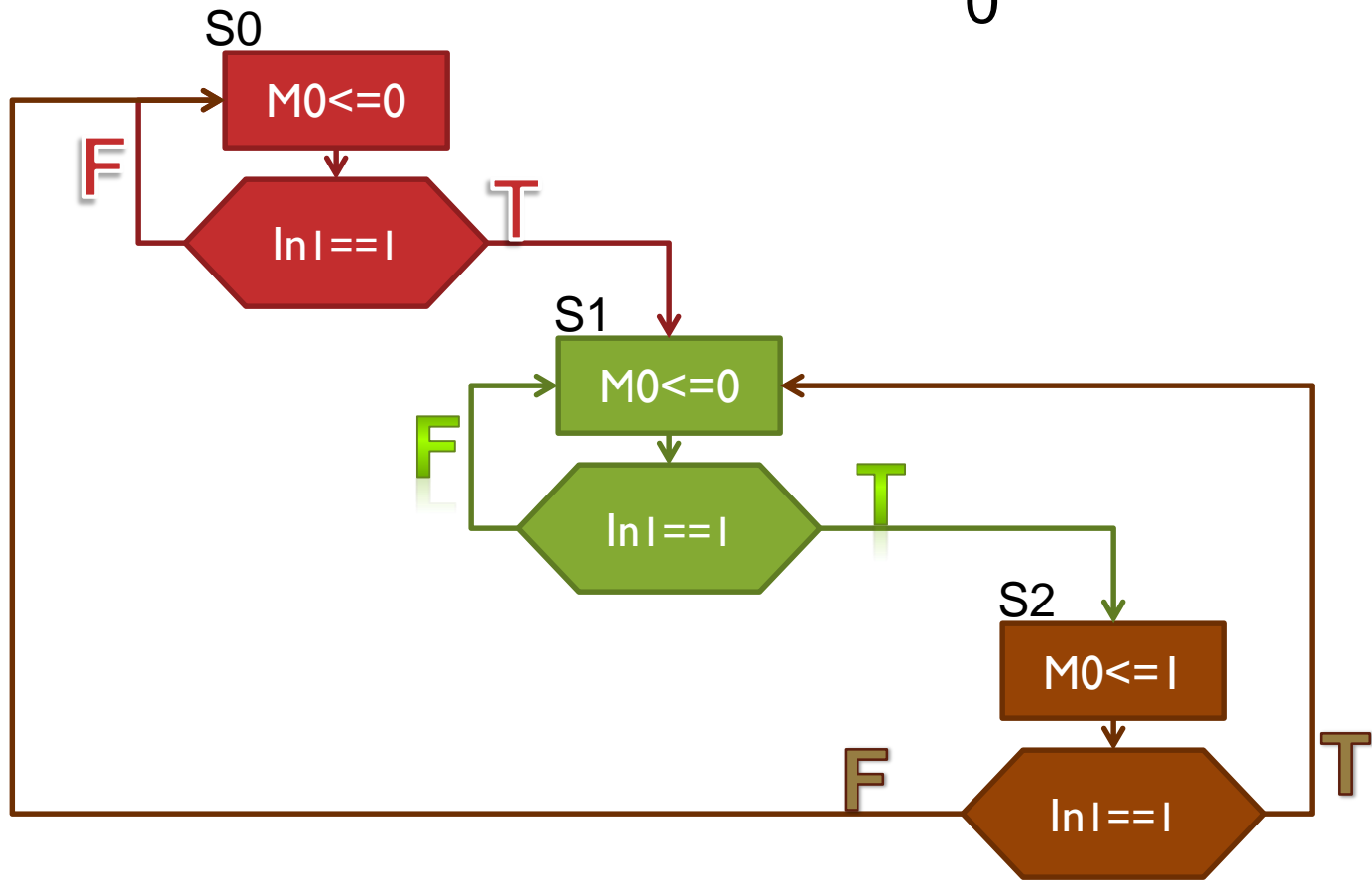 



Moore ASM

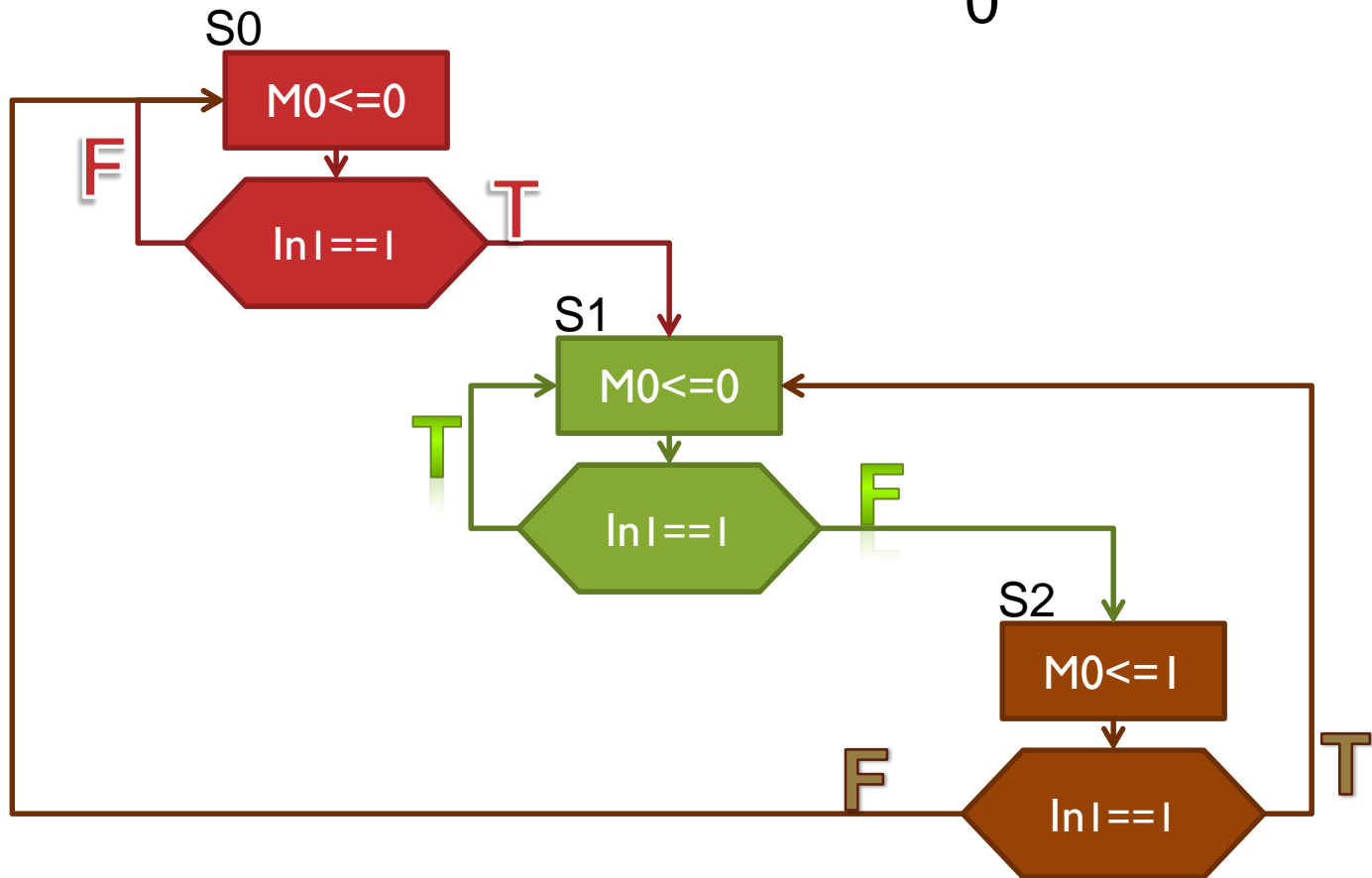 


Mealy ASM

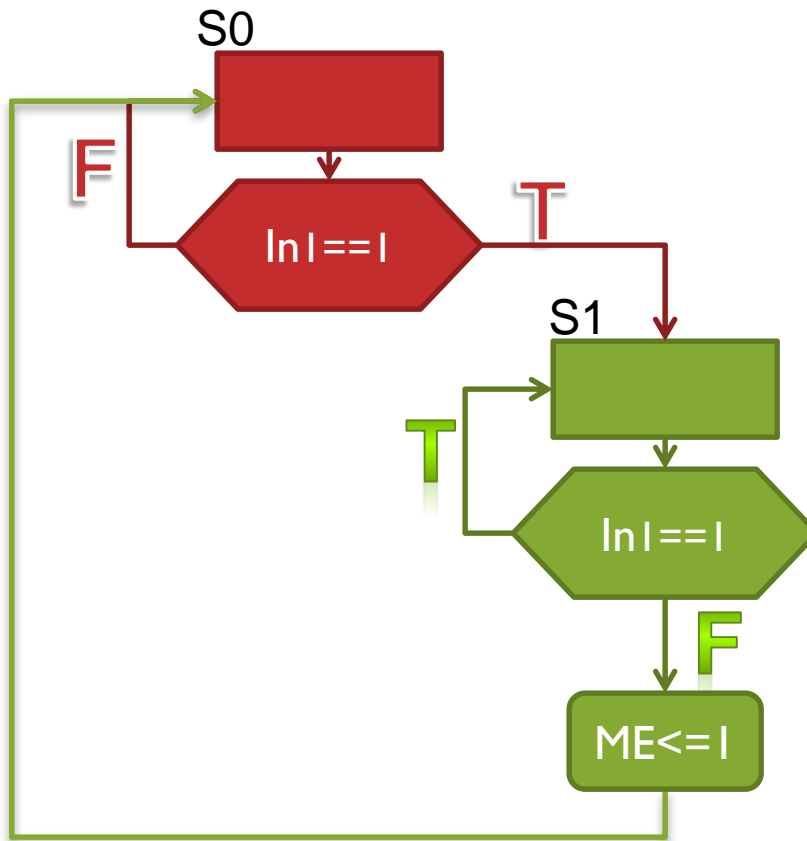 


Moore vs. Mealy

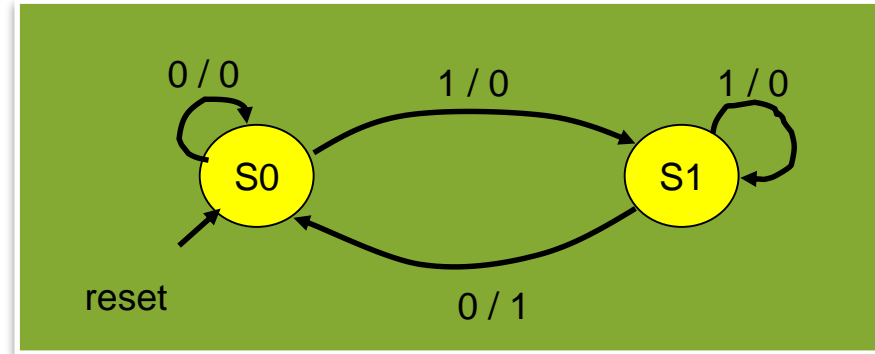 

Mo

 


Me

 


Moore FSM - Example 1

- VHDL of Moore: Again

 

Moore FSM in VHDL (I)

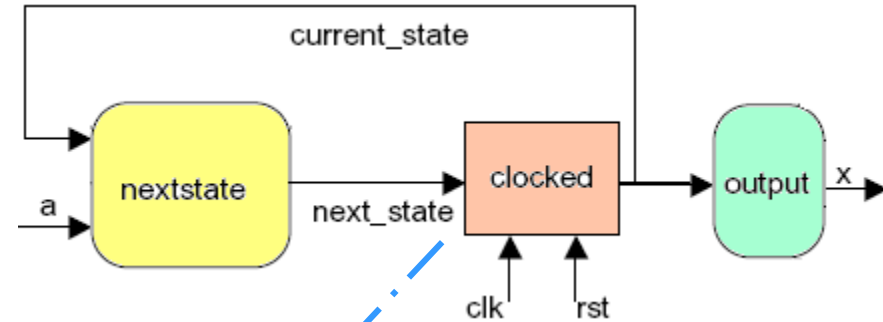

```
clocked : PROCESS ( clk, rst )
```

```
BEGIN
```

```
  IF (rst = '1') THEN
```

```
    current_state <= s0;
```

```
    -- Reset Values
```

```
  ELSIF (clk'EVENT AND clk = '1') THEN
```

```
    current_state <= next_state;
```

```
    -- Default Assignment To Internals
```

```
  END IF;
```

```
END PROCESS clocked;
```


rst	i/p	Crt st	Nxt st	o/p
1	-	-	S0	0
0	0	S0	S0	0
0	1	S0	S1	0
0	0	S1	S2	1
0	1	S1	S1	0
0	0	S2	S0	0
0	1	S2	S1	0

Moore FSM in VHDL (I)

nextstate : PROCESS (a, b, current_state)

```

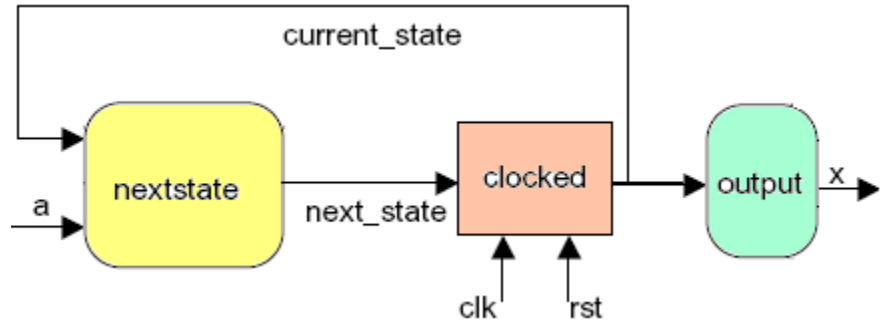-----
BEGIN
CASE current_state IS
WHEN S0 =>IF input = '1' THEN
    Next_state <= S1;
ELSE
    Next_state <= S0;
END IF;
WHEN S1 =>IF input = '0' THEN
    Next_state <= S2;
ELSE
    Next_state <= S1;
END IF;
WHEN S2 =>IF input = '0' THEN
    Next_state <= S0;
ELSE
    Next_state <= S1;
END IF;
END CASE;
END PROCESS nextstate
    
```



rst	i/p	Crt st	Nxt st	o/p
1	-	-	S0	0
0	0	S0	S0	0
0	1	S0	S1	0
0	0	S1	S2	1
0	1	S1	S1	0
0	0	S2	S0	0
0	1	S2	S1	0

Moore FSM in VHDL (2)

Output <= '1' WHEN current_state = S2 ELSE '0';

output : **PROCESS** (current_state)

BEGIN

-- Default Assignment

o/p <= '0';

-- Default Assignment To Internals

-- State Actions

CASE current_state **IS**


WHEN s2 => o/p <= '1';

WHEN OTHERS => NULL;

END CASE;

END PROCESS output;

rst	i/p	Crt st	Nxt st	o/p
1	-	-	S0	0
0	0	S0	S0	0
0	1	S0	S1	0
0	0	S1	S2	1
0	1	S1	S1	0
0	0	S2	S0	0
0	1	S2	S1	0






FSM Implementation

Moore paradigm

Enumerate Data type

rst	i/p	Crt st	Nxt st	o/p
1	-	-	S0	0
0	0	S0	S0	0
0	1	S0	S1	0
0	0	S1	S2	1
0	1	S1	S1	0
0	0	S2	S0	0
0	1	S2	S1	0

 

rst	w	y_1y_2	y_1y_2	o/p
1	-	-	00	0
0	0	00	00	0
0	1	00	01	0
0	0	01	10	1
0	1	01	01	0
0	0	10	00	0
0	1	10	01	0

Enumerate Data type

rst	w	y_1y_2	Y_1Y_2	o/p
1	-	-	00	0
0	0	00	00	0
0	1	00	01	0
0	0	01	10	1
0	1	01	01	0
0	0	10	00	0
0	1	10	01	0

$Y_1 = \bar{w} \quad y_2 = \text{o/p}$

w	y_2y_1	00	01	11	10
0	0	0	0	d	1
1	0	0	0	d	0


$Y_2 = w$

w	y_2y_1	00	01	11	10
0	0	0	0	d	0
1	0	1	1	d	1

Realization


$$Y_2 = w$$

$$Y_1 = \bar{w} \quad y_2 = \text{o/p}$$

 

Mealy FSM - Example 1

 - Mealy FSM that Recognizes Sequence “10”



Mealy FSM in VHDL (1)

```
-----
clocked : PROCESS ( clk, rst )
-----
```

```
BEGIN
```

```
IF (rst = '1') THEN
```

```
    current_state <= s0;
```

```
    -- Reset Values
```

```
    x <= '0';
```

```
ELSIF (clk'EVENT AND clk = '1') THEN
```

```
    current_state <= next_state;
```


```
    -- Registered output assignments
```

```
    x <= x_int;
```

```
    -- Default Assignment To Internals
```

```
END IF;
```

```
END PROCESS clocked;
```

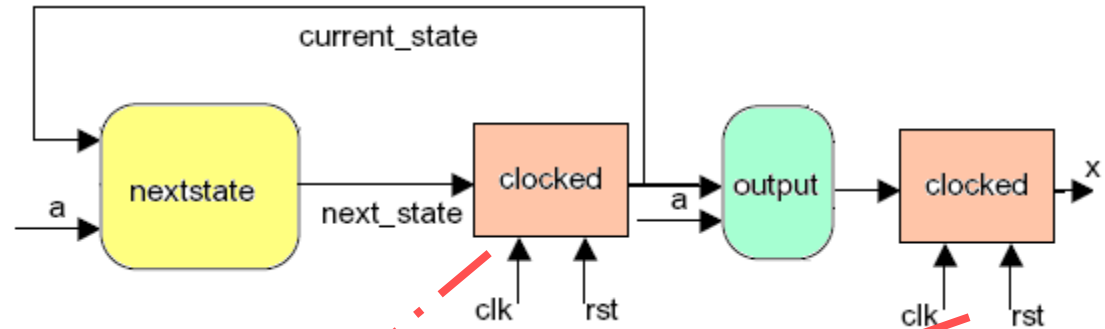

rst	i/p	Crt st	Nxt st	o/p
1	-	-	S0	0
0	0	S0	S0	0
0	1	S0	S1	0
0	0	S1	S0	1
0	1	S1	S1	0

Mealy FSM in VHDL (2)

```
nextstate : PROCESS ( a, b, current_state )
```

```
BEGIN
```

```
CASE current_state IS
```

```
  WHEN S0 =>
```

```
    IF input = '1' THEN
```

```
      next_state <= S1;
```

```
    ELSE
```

```
      next_state <= S0;
```

```
    END IF;
```

```
  WHEN S1 =>
```

```
    IF input = '0' THEN
```

```
      next_state <= S0;
```

```
    ELSE
```


```
      next_state <= S1;
```

```
    END if;
```

```
  WHEN OTHERS => next_state <= s0;
```


```
END CASE;
```

```
END PROCESS;
```

 

rst	i/p	Crt st	Nxt st	o/p
1	-	-	S0	0
0	0	S0	S0	0
0	1	S0	S1	0
0	0	S1	S0	1
0	1	S1	S1	0

Mealy FSM in VHDL (3)

 

```
output : PROCESS ( a, b, current_state )
```

```
BEGIN
```

```
x_int <= '0';
```

```
CASE current_state IS
```

```
  WHEN s0 => IF (a = '1') THEN
```

```
    x_int <= '0';
```

```
  END IF;
```

```
  WHEN s1 => IF (a = '1') THEN
```


```
    x_int <= '1';
```

```
  END IF;
```

```
  WHEN OTHERS => NULL;
```

```
END CASE;
```


```
END PROCESS output;
```

 

Challenge your mind

Moore or Mealy? **Function?**

State the table of the next diagram?

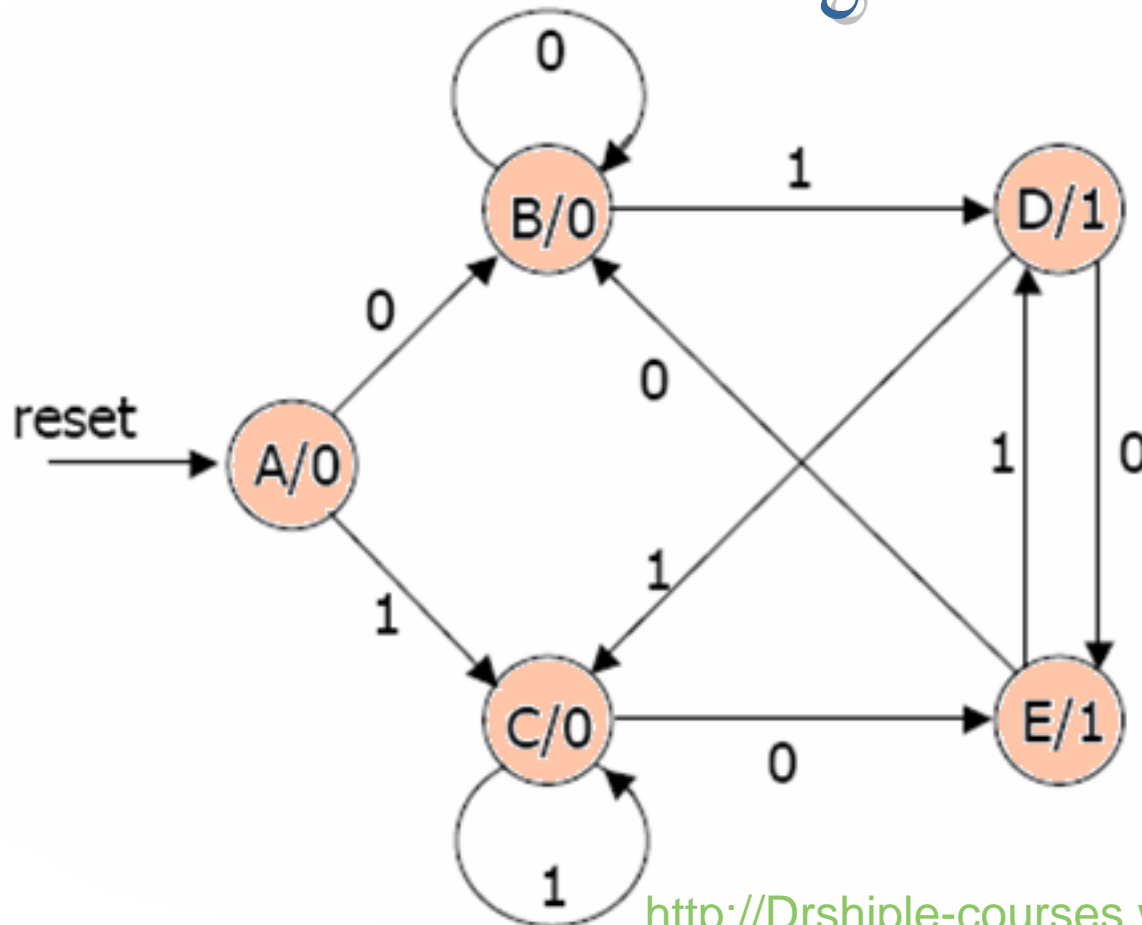


The answer is : Moore

Function : sequence detector for 01 or 10


Switch the diagram to be Mealy?

reset	input	current state	next state	output
1	-	-	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1

 


Function : sequence detector for 01 or 10

State FSM table?

 



Function : sequence detector for 01 or 10

reset	input	current state	next state	output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0


 


Comparison of Mealy and Moore Machines

- **Moore Machines are safer to use**
 - Outputs change at clock edge (always one cycle later)
 - In Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback
- **Mealy Machines react faster to inputs**
 - React in same cycle – don't need to wait for clock
 - In Moore machines, more logic may be necessary to decode state into outputs – more gate delays after

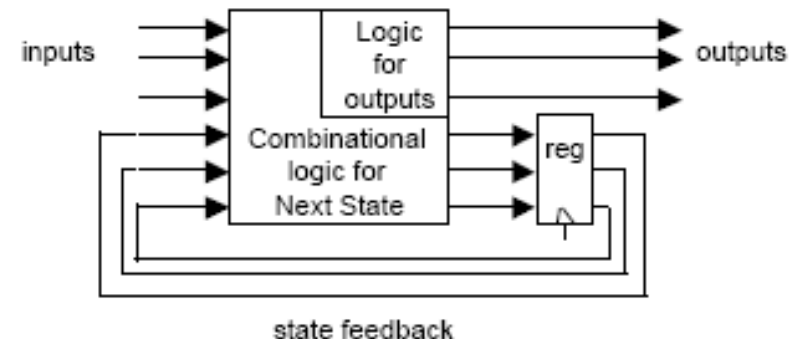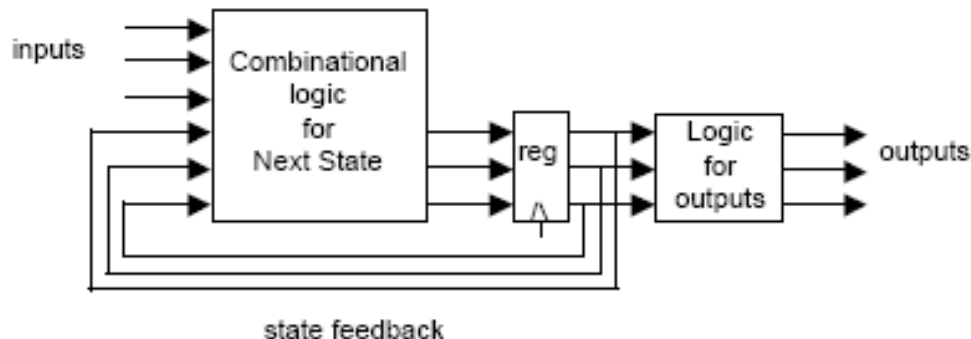

Serial Adder (Mealy)

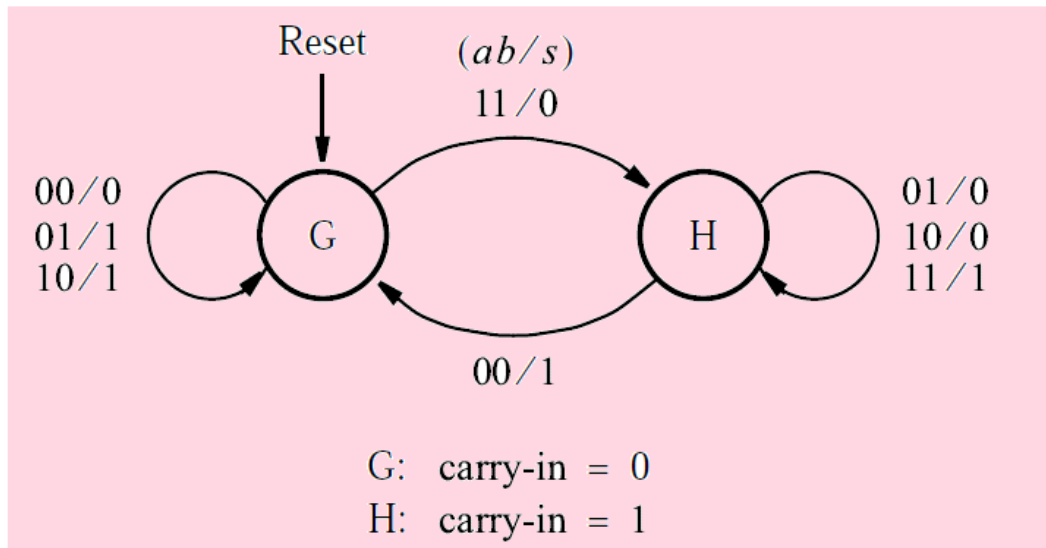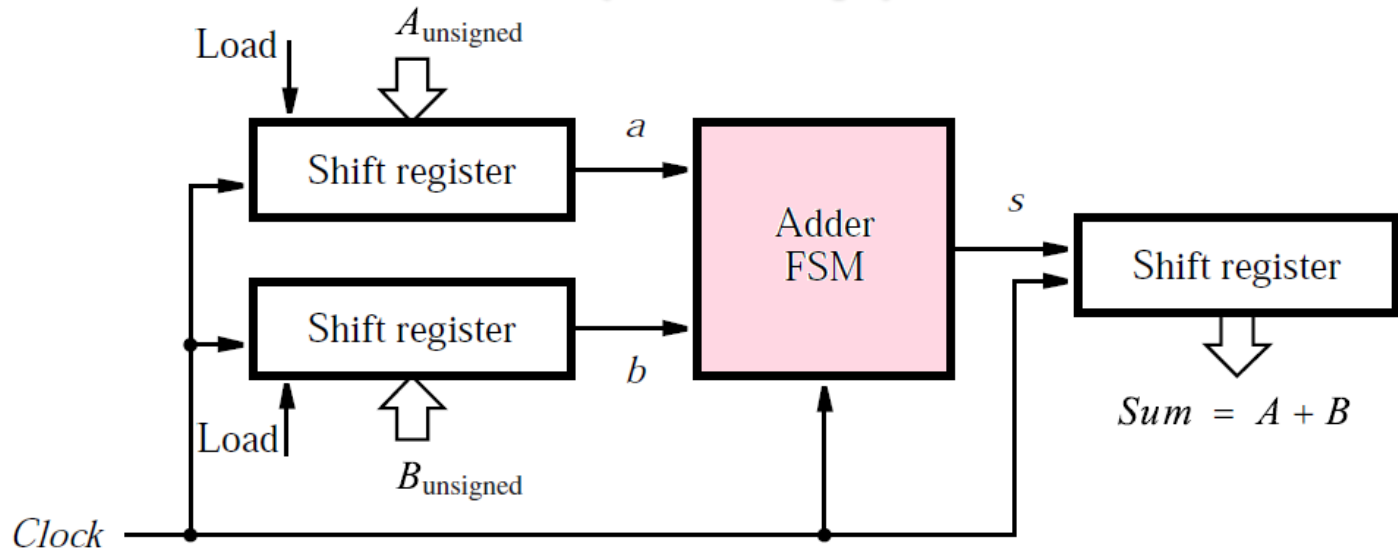


Truth Table



Present state	Next state				Output s			
	$ab = 00$	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1

Present state	Next state				Output			
	$ab = 00$	01	10	11	00	01	10	11
y	Y				s			
0	0	0	0	1	0	1	1	0
1	0	1	1	1	1	0	0	1

Realization

 

Serial Adder (Moore)

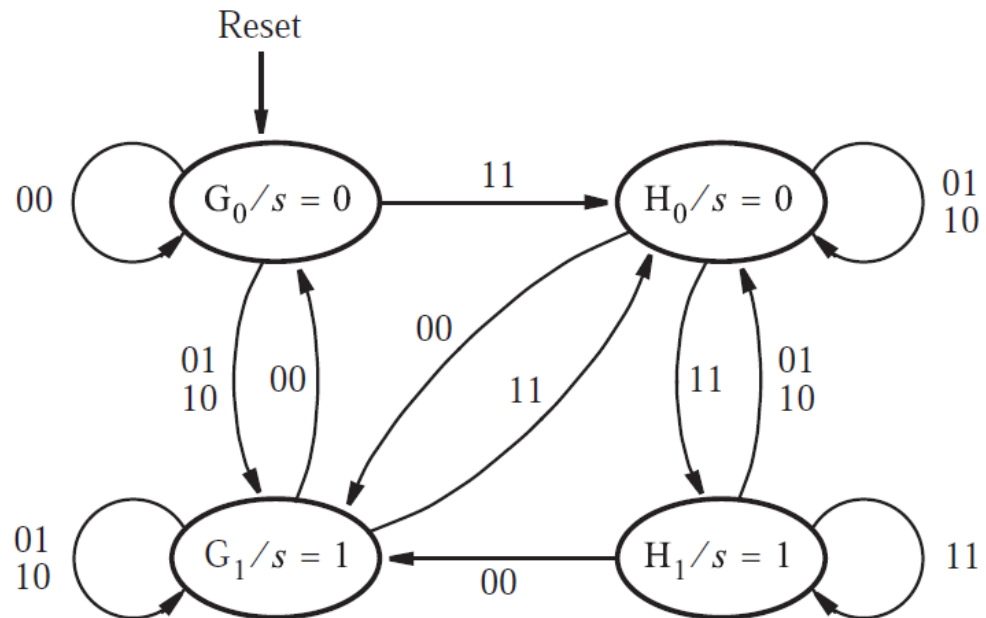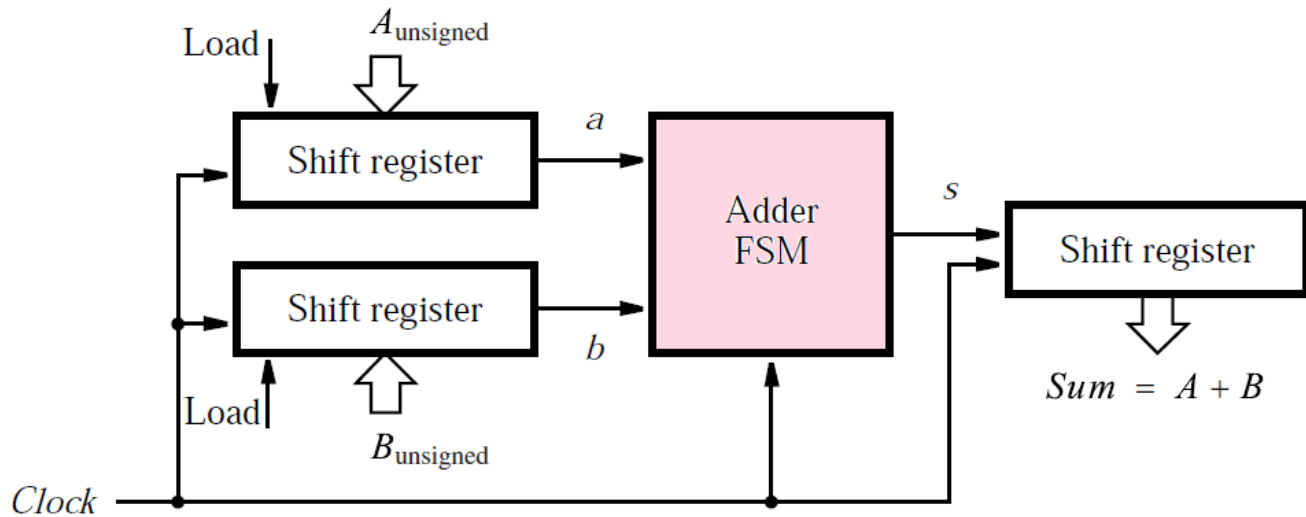


Truth Table


Present state	Next state				Output s
	$ab = 00$	01	10	11	
G_0	G_0	G_1	G_1	H_0	0
G_1	G_0	G_1	G_1	H_0	1
H_0	G_1	H_0	H_0	H_1	0
H_1	G_1	H_0	H_0	H_1	1

Present state y_2y_1	Next state				Output s
	$ab = 00$	01	10	11	
	Y_2Y_1				
00	00	01	01	10	0
01	00	01	01	10	1
10	01	10	10	11	0
11	01	10	10	11	1

Realization

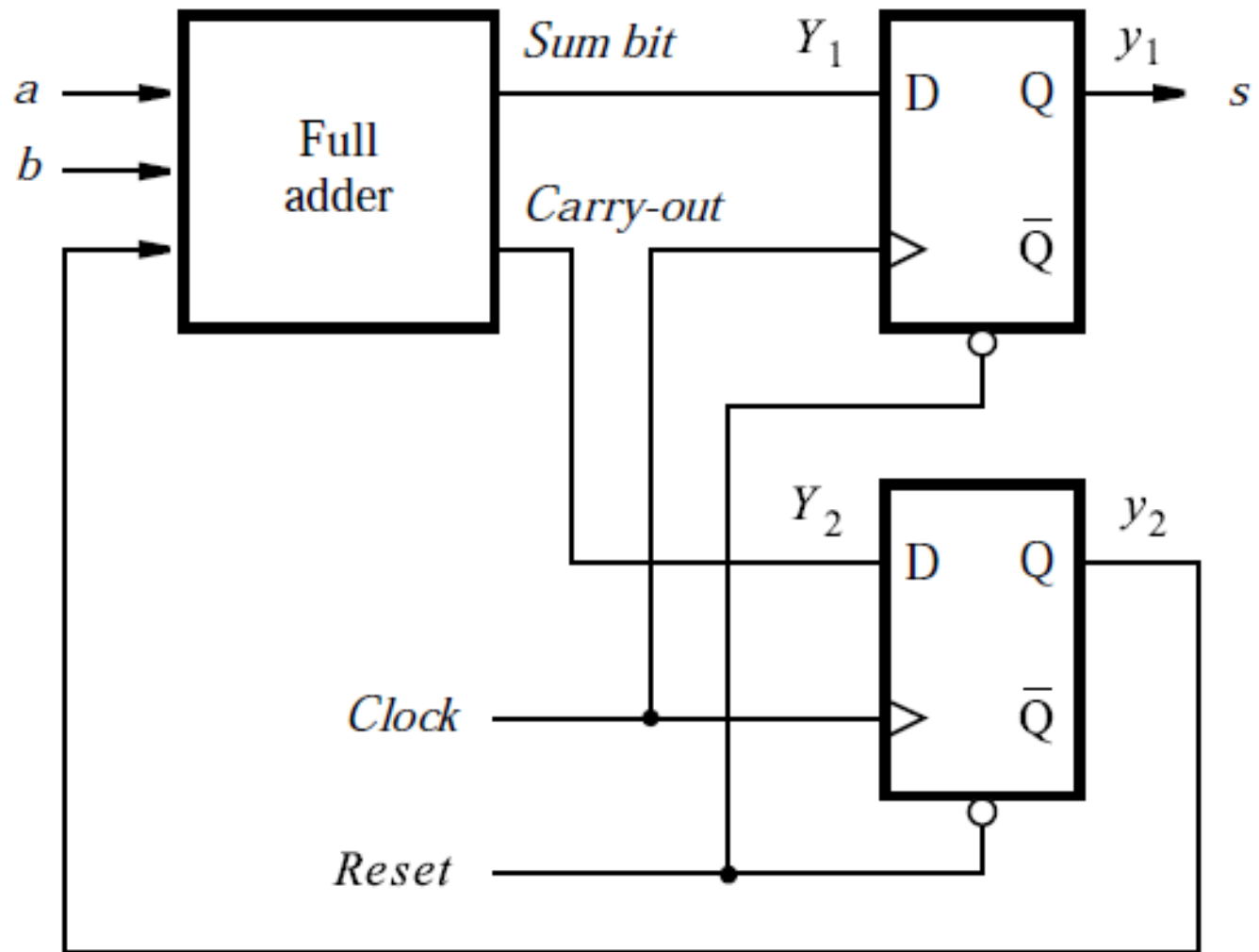

State Encoding

 

High Performance

CoolClock

Low Power

PowerPac



State Encoding Problem

- State Encoding Can Have a Big Influence on Optimality of the FSM Implementation
 - No methods other than checking all possible encodings are known to produce optimal circuit
 - Feasible for small circuits only
- Using Enumerated Types for States in VHDL Leaves Encoding Problem for Synthesis Tool

Types of State Encodings

State	Binary Code	Gray Code	One-Hot Code
S0	000	000	10000000
S1	001	001	01000000
S2	010	011	00100000
S3	011	010	00010000
S4	100	110	00001000
S5	101	111	00000100
S6	110	101	00000010
S7	111	100	00000001
# states=n FF	2^n	2^n	n

Types of State Encodings (I)

- One-Hot – Only One Bit Is Active
 - Number of used flip-flops as big as number of states (n)
 - Simple and fast transition functions
 - Preferable coding technique in FPGAs

Types of State Encodings (I)

- Binary (Sequential) – States Encoded as Consecutive Binary Numbers
 - Small number of used flip-flops ($\log_2 n$)
 - Potentially complex transition functions leading to slow implementations.
 - High Power Consumption .
 - Preferable coding technique in CPLD
 - Could generate Hazard circuits

Types of State Encodings (I)


- Grey Code
 - Small number of used flip-flops ($\log_2 n$)
 - Potentially complex transition functions leading to slow implementations (more than Binary).
 - **Low** Power Consumption .
 - Preferable coding technique in CPLD
 - Could generate Hazard circuits

The Stream Cipher




MICKEY-128


Cipher System

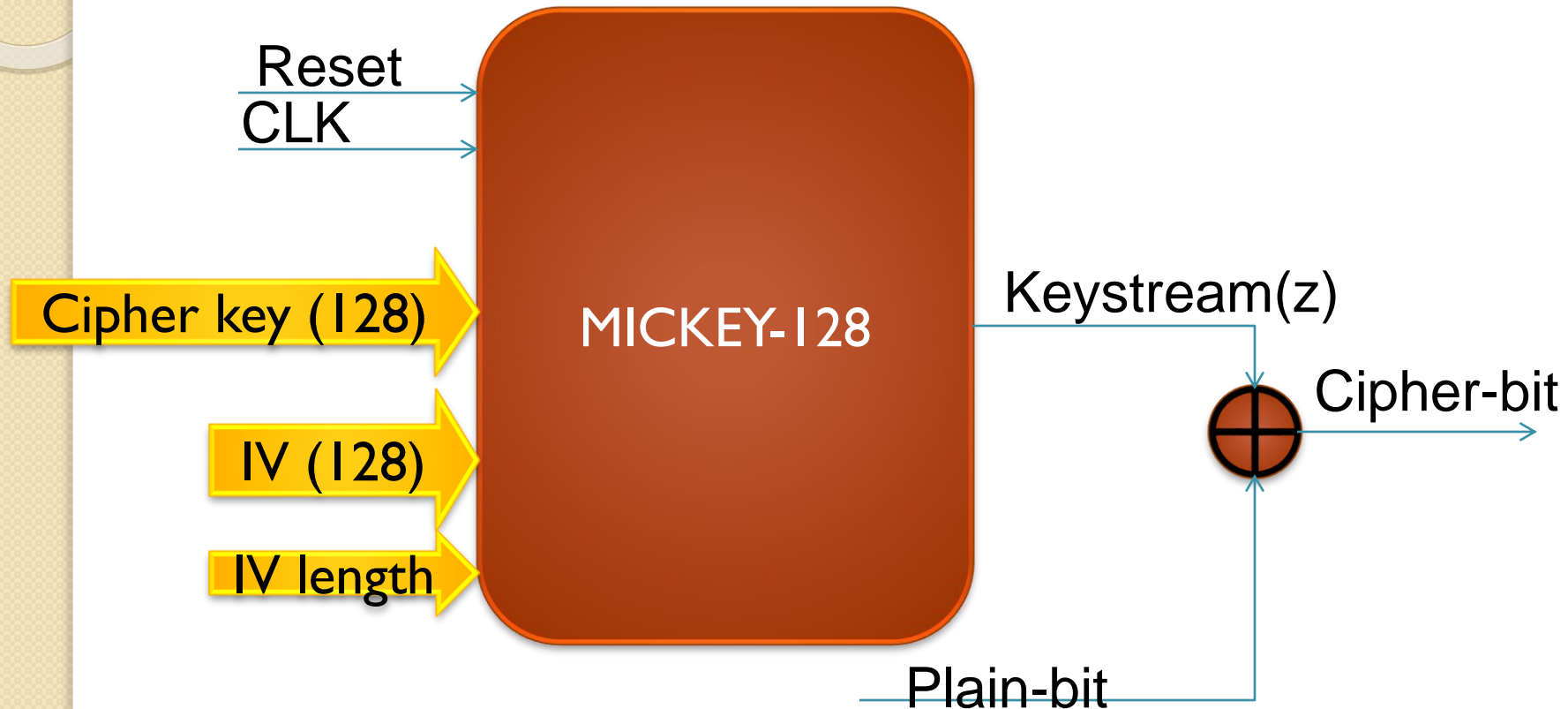

Mickey 128

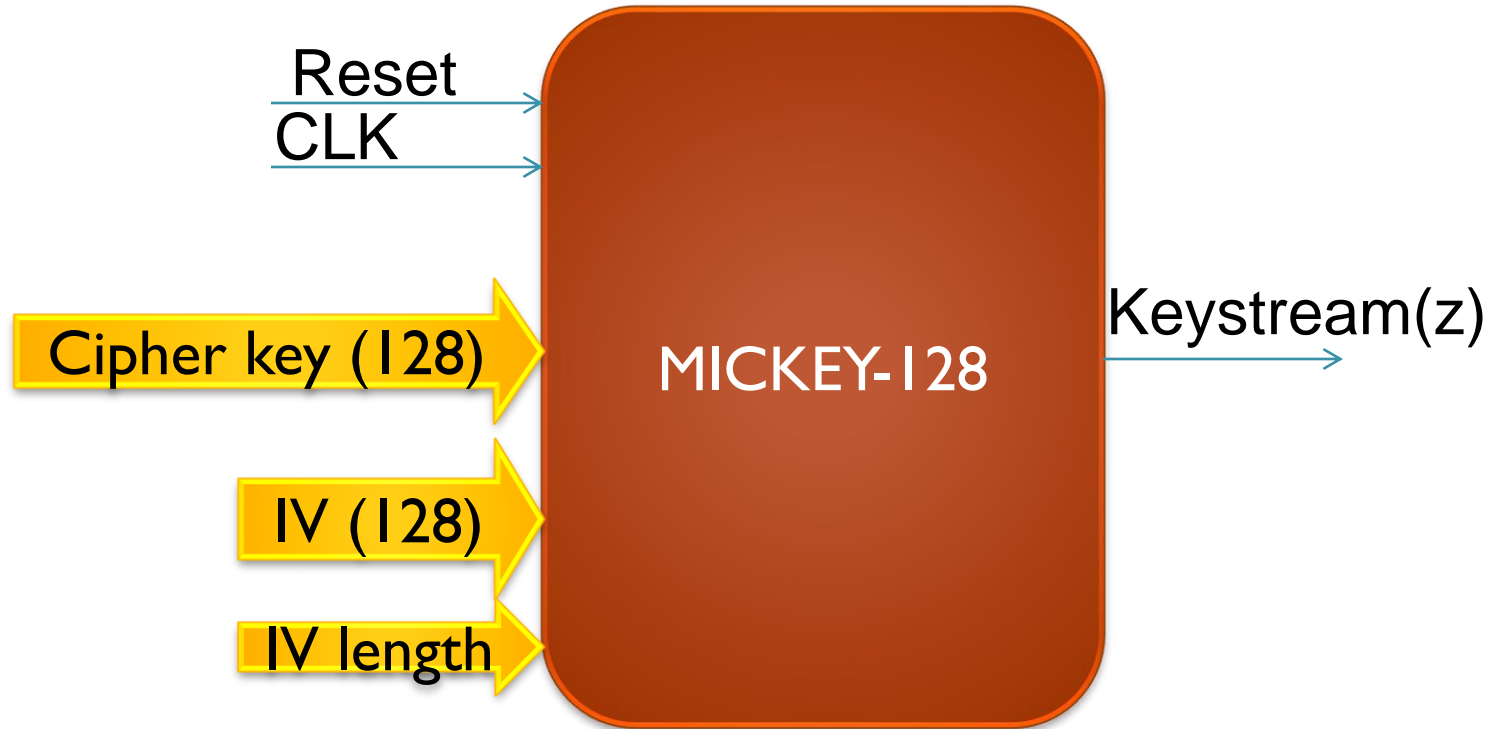


Clocking and overall generator

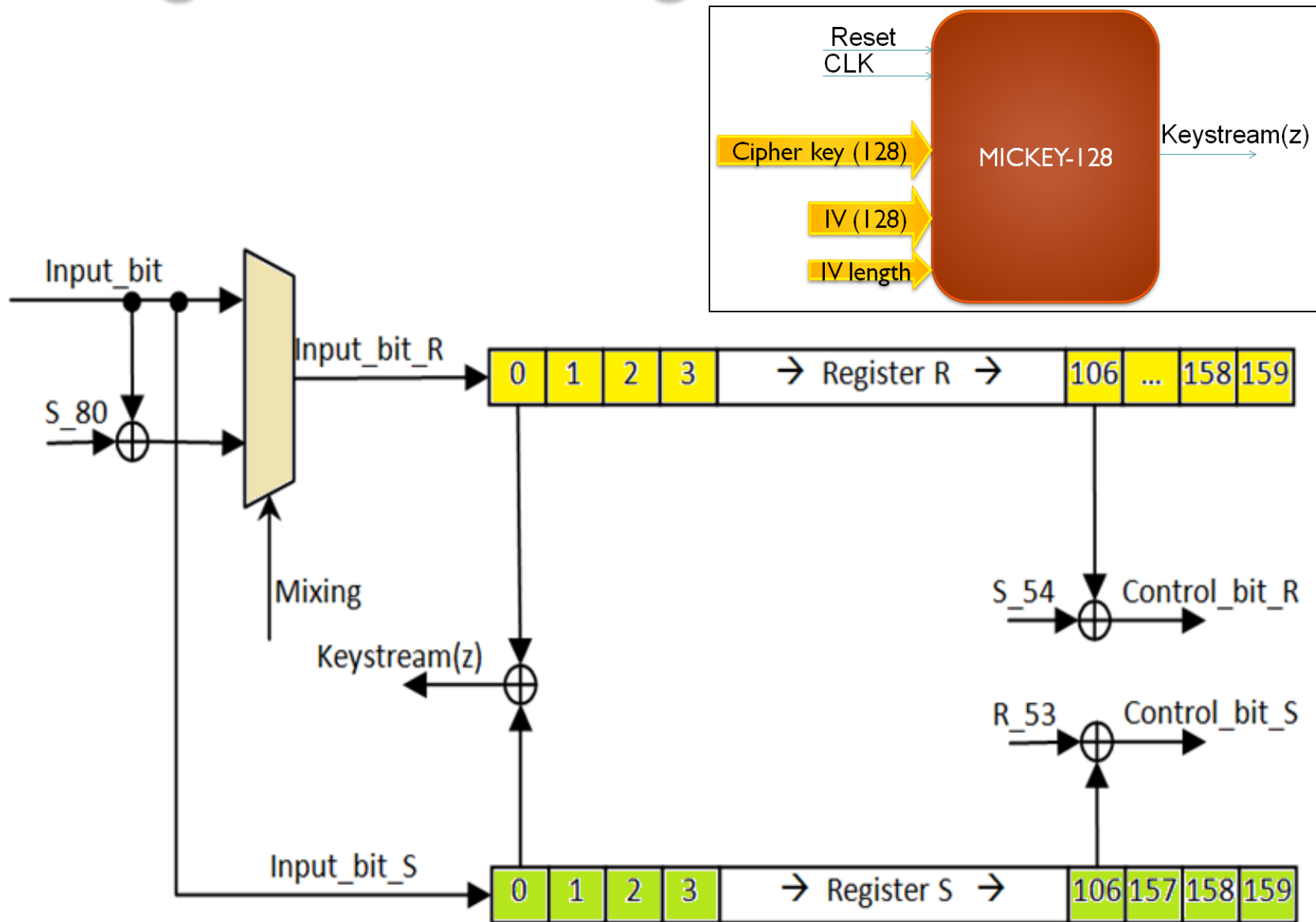

Register R Entity




Register R

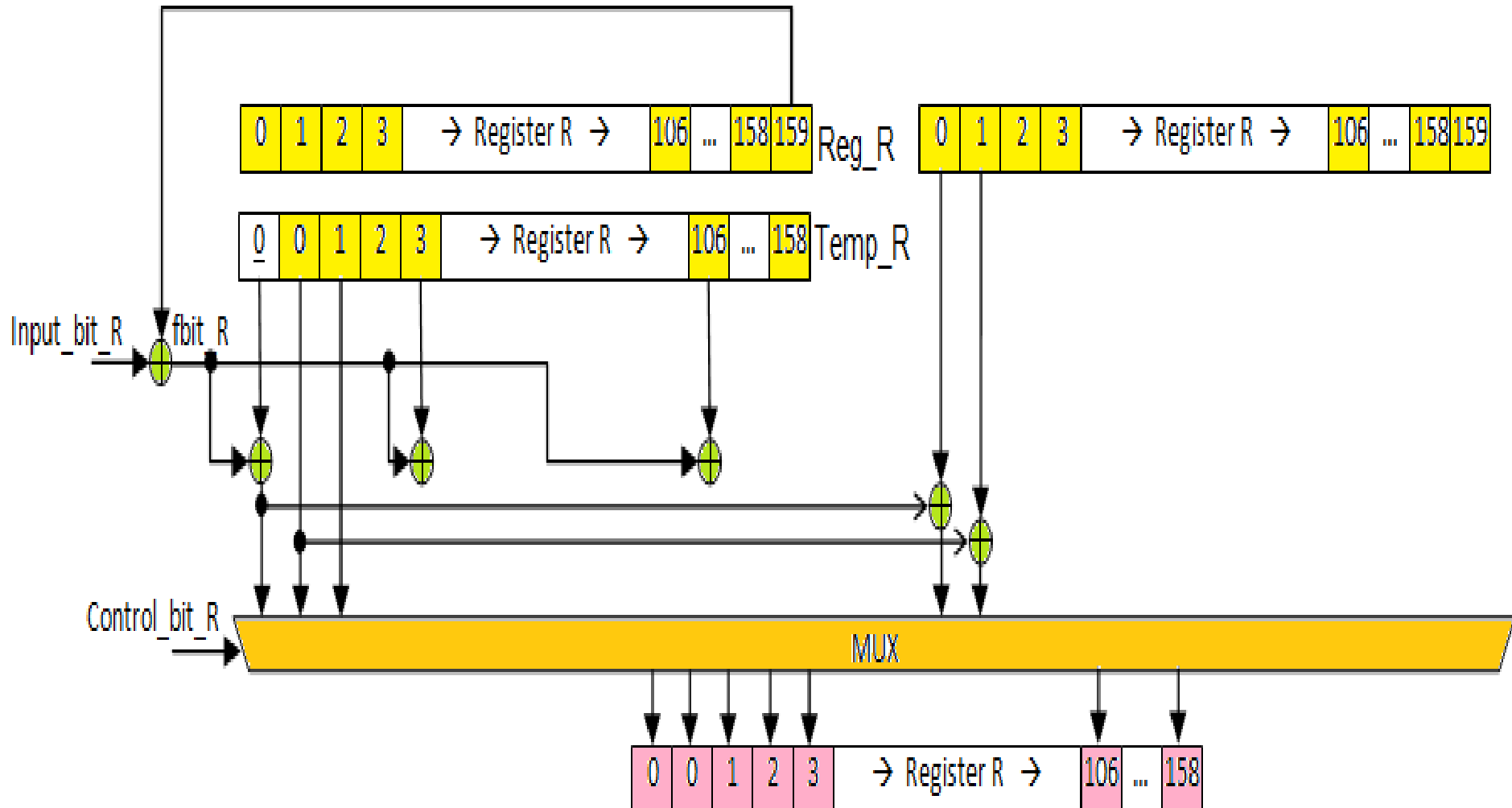

Register S Entity



Register S

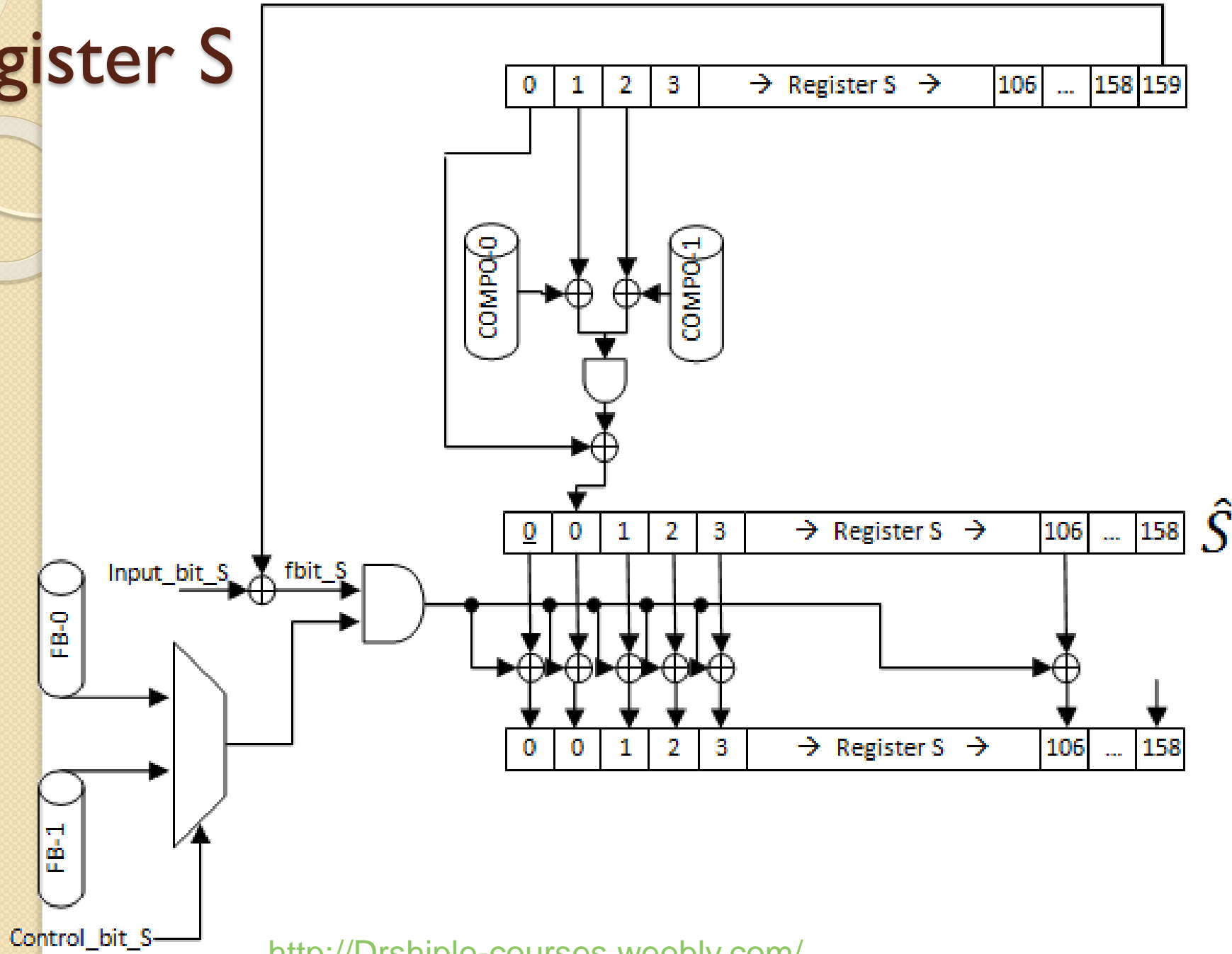



End of Presentation