

Synthesizers and VHDL Interpreting




By:


Mustafa M. Shiple


<http://Drshiple-courses.weebly.com/>

Xilinx Flow

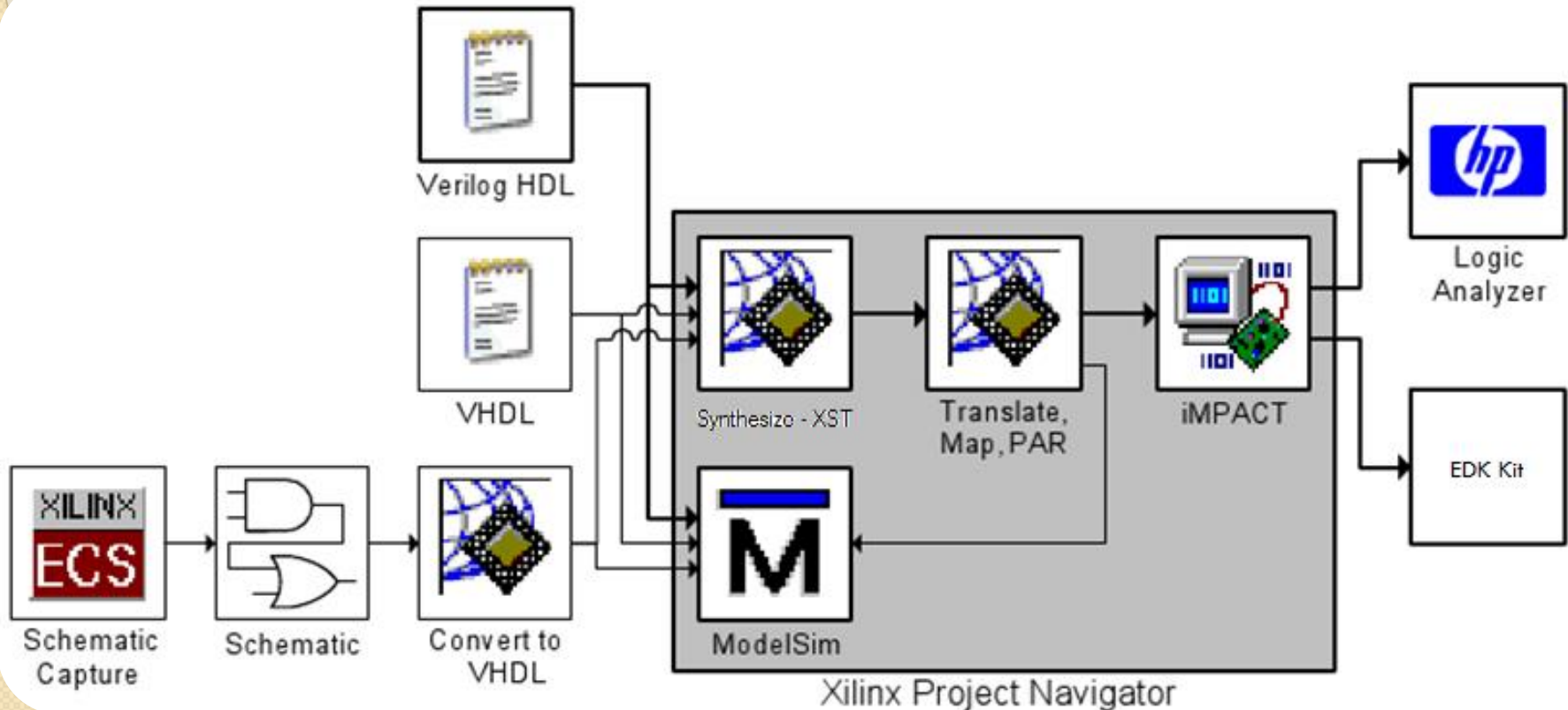


ISE Synthesizer

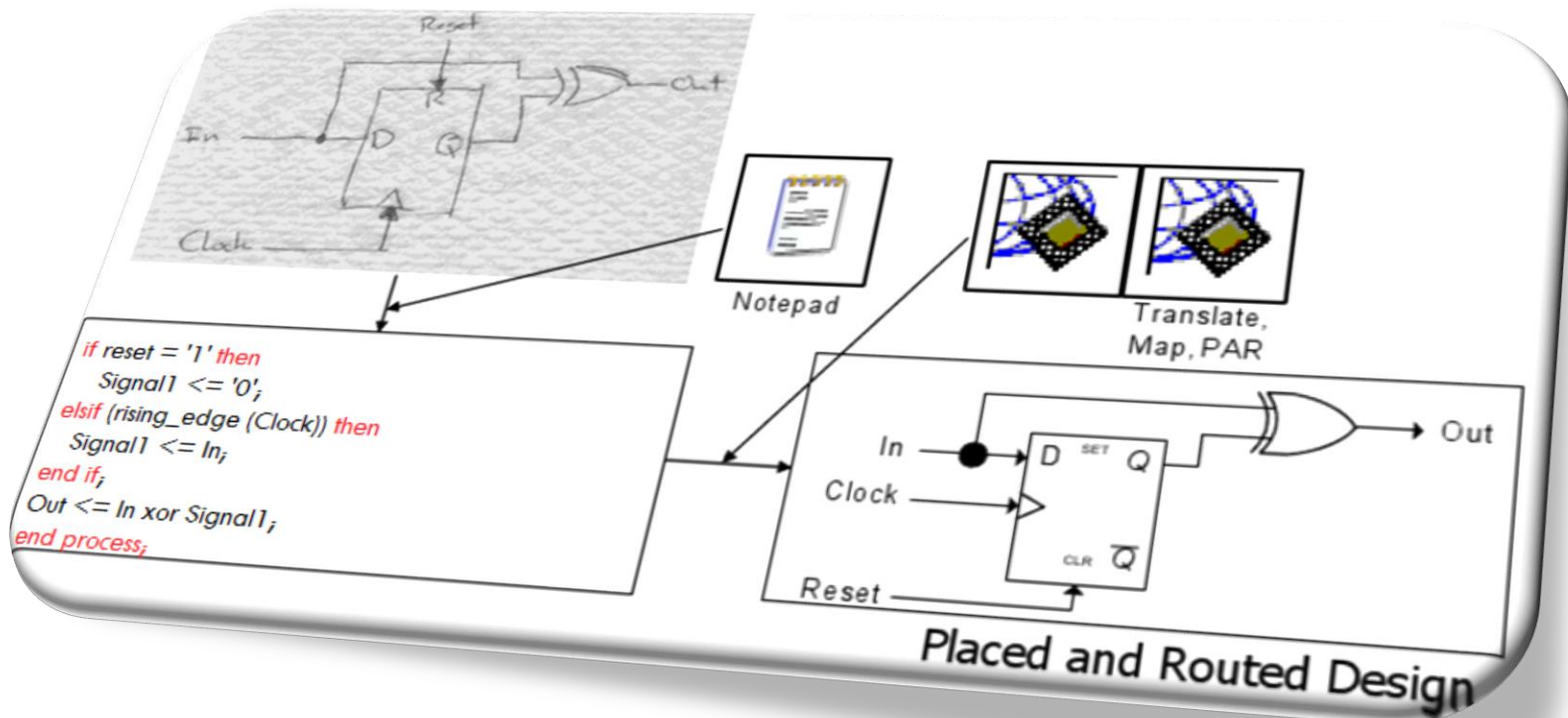

 

Programming Combinational Logic

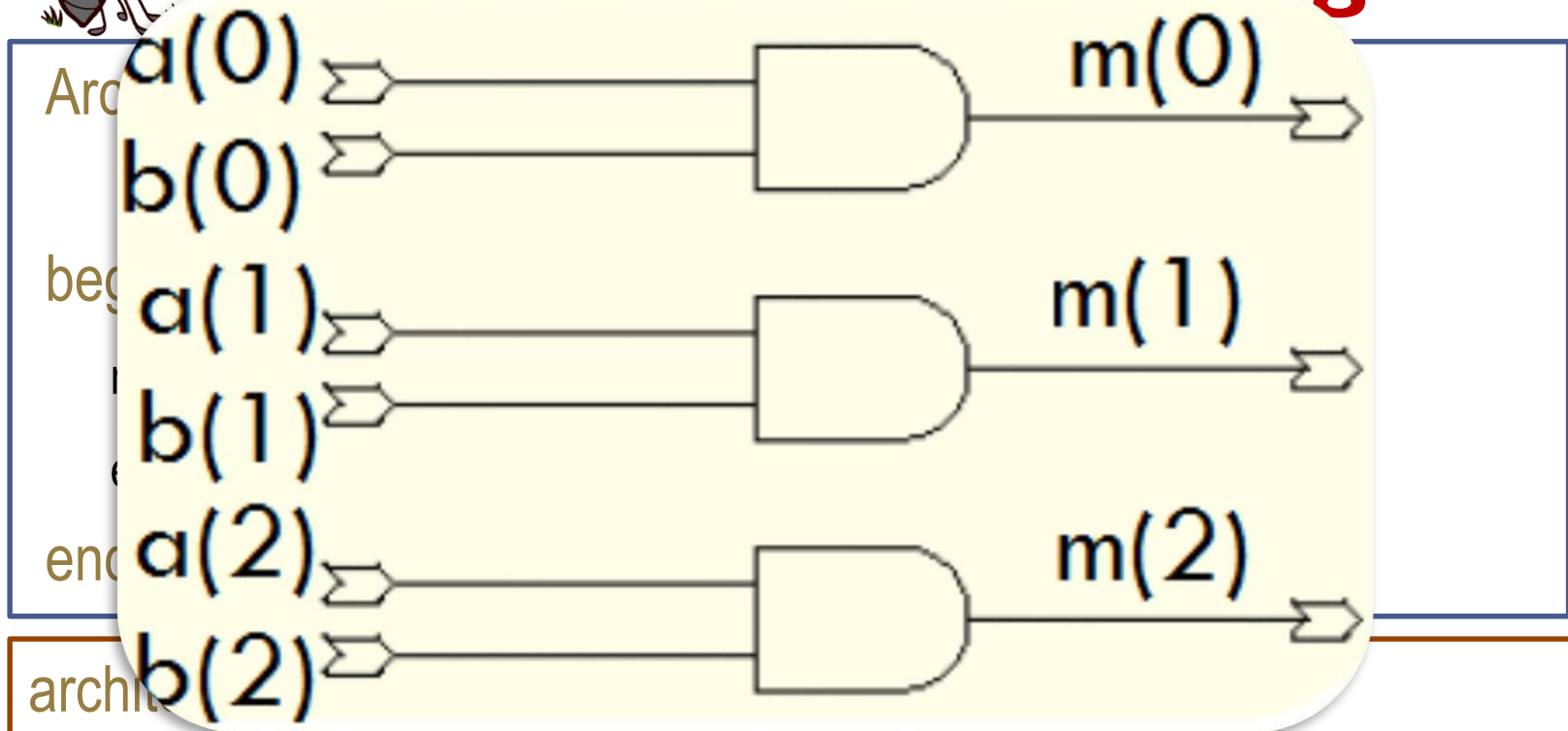

archi

begin


```
m <= a and b; -- a, b: in std_logic_vector (0 to 2);
```

```
end example;
```



Relational Operators

Equality : $M_out \leq A_{in} = B_{in}$;

 



Greater than or equal to : $M_out \leq A_{in} \geq B_{in}$;

A _{in}	B _{in}	M _{out}
0	0	1
0	1	0
1	0	1
1	1	1





If Statement
  
```
process (a, b, c)
  variable n: std_logic;
Begin
  if a = '1' then
    n := b;
  else
    n := c;
  end if;
  m <= n;
end process;
```



Incomplete *assignment*
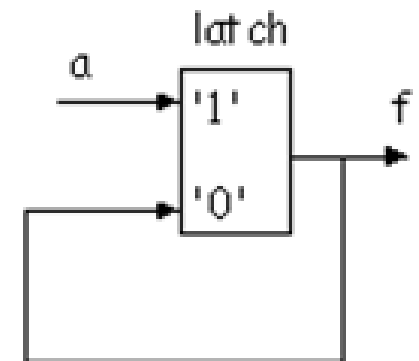 
```
process (a, b, c)
  variable n: std_logic;
begin
  if a = '1' then
    n := b;
  end if;
  m <= n;
end process;
```




HDL Synthesis

Synthesizing Unit <testgats>.
Related source file is D:/PHD/FINAL-VHDL/RIJNDEAL/CSbox_simulation/testgats.vhd

WARNING:Xst:647 - Input <c> is never used.
WARNING:Xst:736 - Found 1-bit latch for signal <\$n0000> created at line 23.

Case statement

 

```
process (sel, a, b, c, d)
begin
    case sel is
        when b"00" => m <= c;
        when b"01" => m <= d;
        when b"10" => m <= a;
        when others => m <= b;
    end case ;
end process;
```




ERROR:HDLParser:812 - D:\testgats.vhd Line 27. A value is missing in case.



Tri-states

```
process (b, a)
begin
  if b = '1' then
    m <= a;
  else
    m <= 'Z';
  end if;
end process;
```

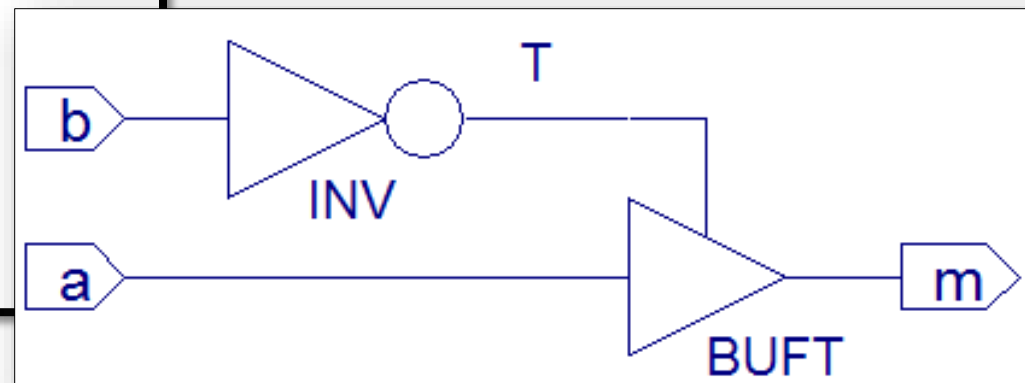


Found 1-bit tristate buffer for signal <m>.

Summary:


inferred 1 Tristate(s).

Latches or FF
 
```
process (a, b, c)
    variable n: std_logic;
begin
    if a = '1' then
        n := b;
    end if;
    m <= n;
end process;
```


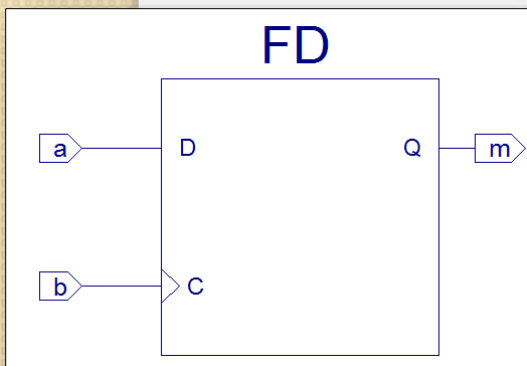
```
process (b, a)
begin
    if rising_edge (b ) then
        n <= a;
    end if;
    m<=n;
end process;
```




Exercise

```
● if rising_edge (b ) then
  if d = '1' then
    m<= a;
  else
    m<= c;
  end if;
end if;
```





Solution
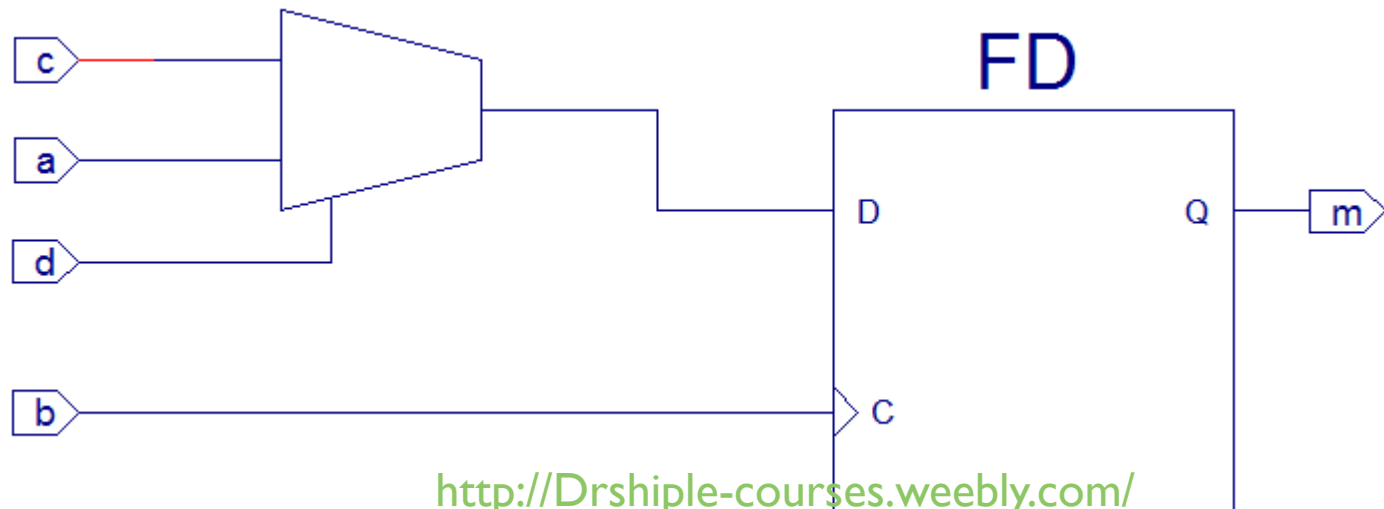
```
if rising_edge (b ) then
  if d = '1' then
    m<= a;
  else
    m<= c;
  end if;
end if;
```




Gate Enable
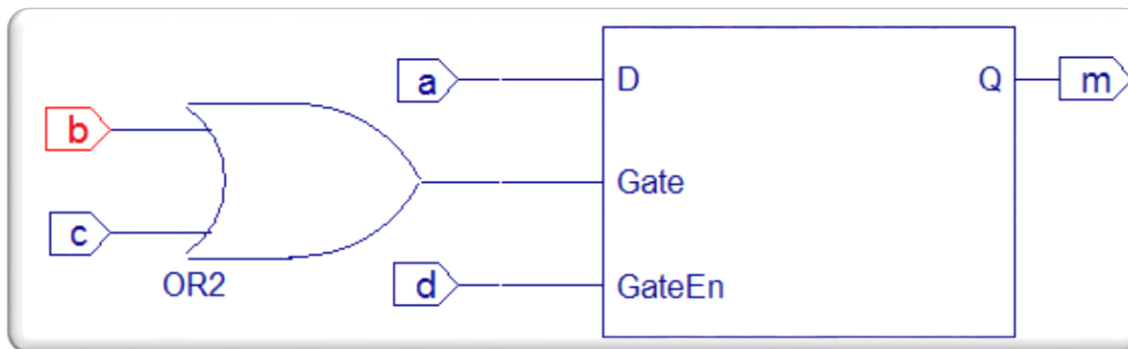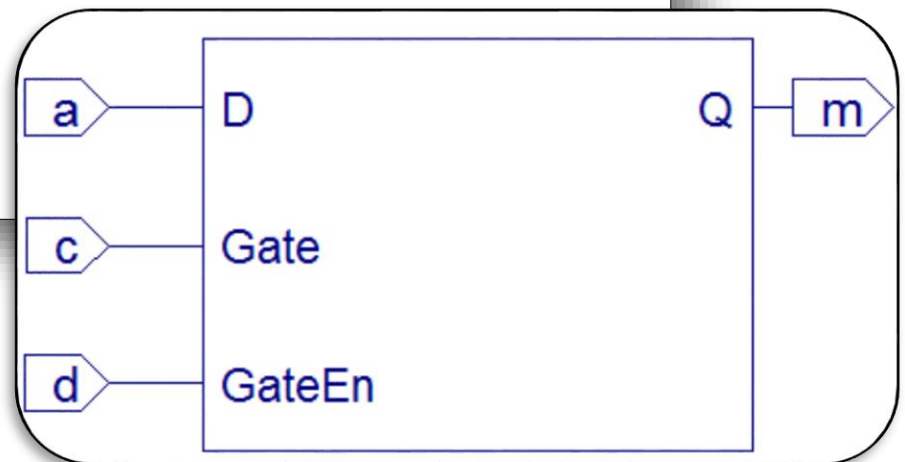
```
if d = '1' and c = '1' then  
  m <= a;  
end if;
```



Solution

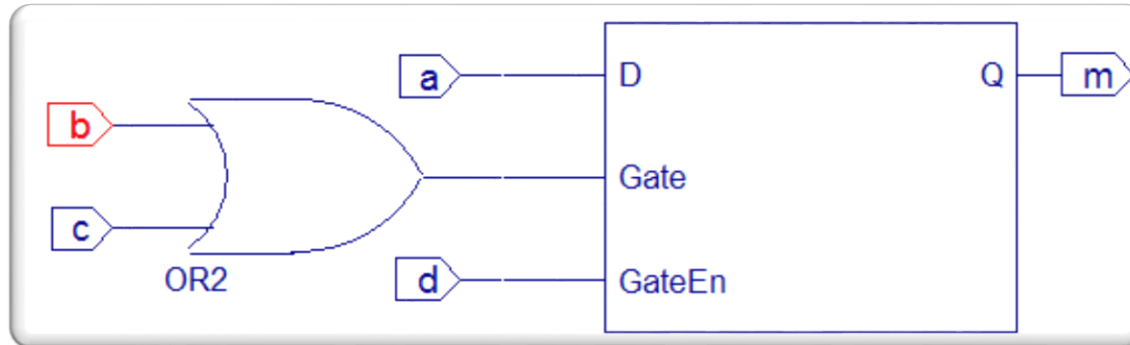


```
if d = '1' and (c = '1' or b = '1') then
  m<= a;

end if;
```

Synchronous Set or Reset

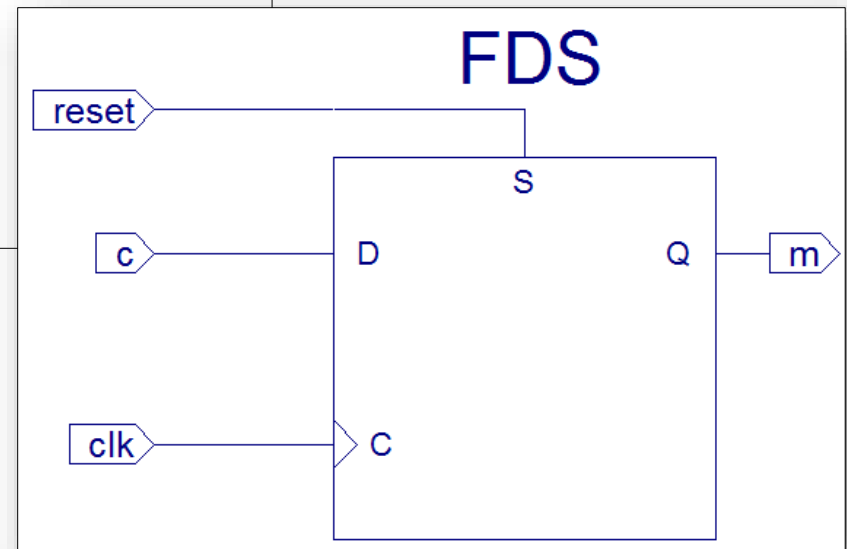
```
if rising_edge (clk) then
  if reset = '1' then
    m <= '1';
  else
    m <= c;
  end if;
end if;
```



Test when $m \leq '0'$

Asynchronous Set or Reset

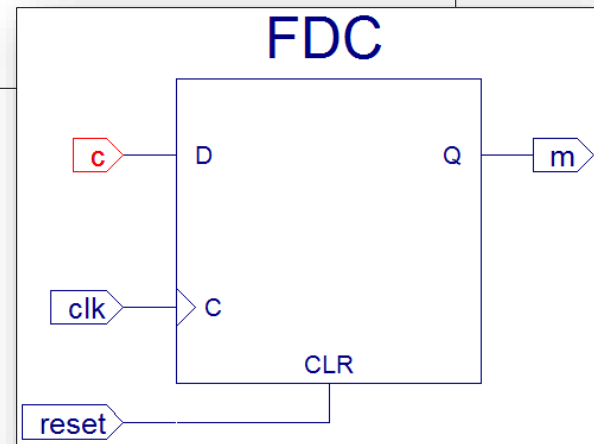
```
if reset = '1' then
  m <= '0';
elsif rising_edge (clk) then
  m <= c;
end if;
```



Test when $m \leq '1'$

Double process
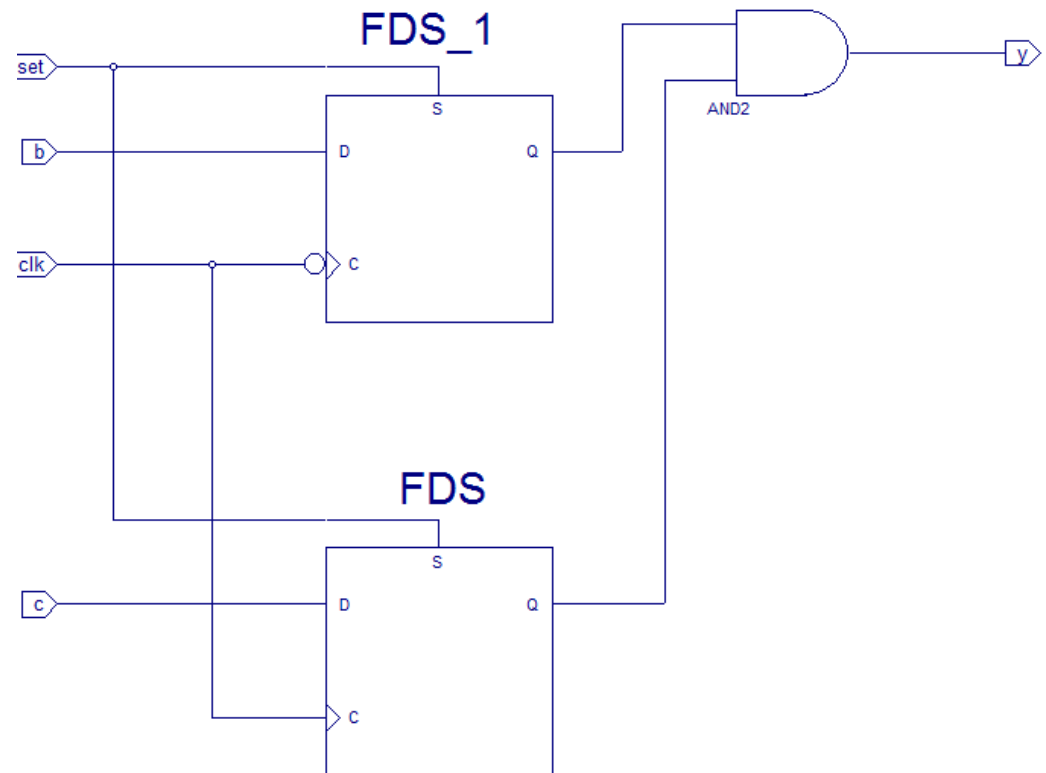
```
process (b, a,c)
begin
  if rising_edge (clk) then
    if reset = '1' then
      m<= '1';
    else
      m<= c;
    end if;
  end if;
end process;
y <= m and n;
process (b, a,c)
begin
  if falling_edge (clk) then
    if reset = '1' then
      n<= '1';
    else
      n<= b;
    end if;
  end if;
end process;
```



Errors

```
if rising_edge (b ) then
  m<= a;
else
  m<= c;
end if;
```


Signal m cannot be synthesized, bad synchronous description.

Flip Flops inferred by Variables

```
architecture EG of FLIPFLOP is
begin
  process (clk)
    variable a,b : std_logic;
  begin
    if (clk'event and clk='1') then
      Q <= b;
      b := a;
      a := D;
    end if;
  end process;
end EG;
```

This assignment of signal needs to have a FF with output a

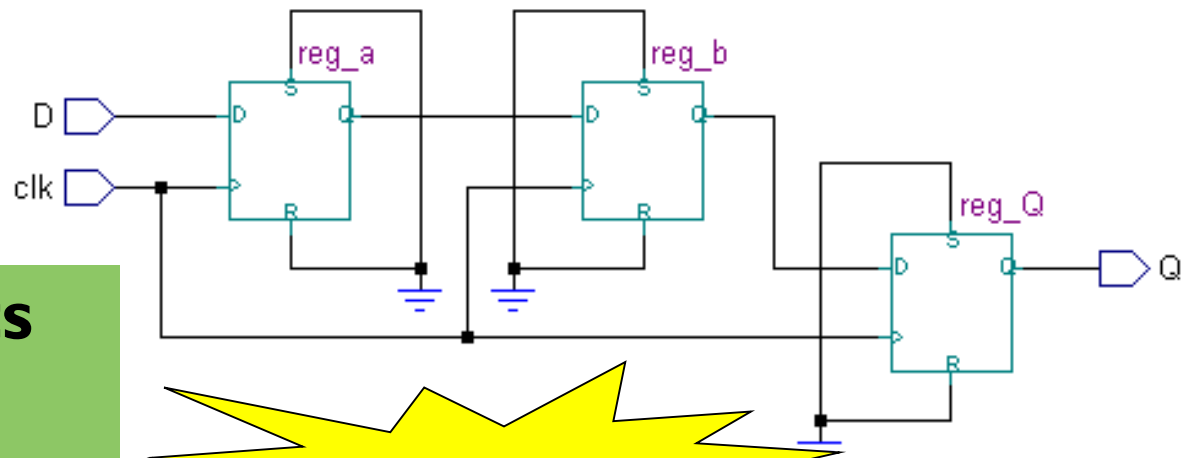Here variable b has no value, it is created only after a has value and a only after D has value



This is strange

For every variable we have a ff.


- We obtain a 3 bits shift register
- Explain why it is so

Flip Flops inferred by Variables

```
architecture EG of FLIPFLOP is
begin
  process (clk)
    variable a,b : std_logic;
  begin
    if (clk'event and clk='1') then
      a := D;
      b := a;
      Q <= b;
    end if;
  end process;
end EG;
```

Remember that variables are assigned immediately

 The only difference here is order of assignments in process, here we have variable assignments first.




- Variable assignment order – FF created when assigned before use.

Order of variables again!!!!

```
signal A,B,C,D: bit
...
NO_MEMORY: process (A,B,C)
variable TMP: bit;
begin
    TMP := A and B;
    D <= TMP or C;
end process;
```
 
```
signal A,B,C: bit
...
IS_IT_LATCH: process (A,B,C)
variable TMP: bit;
begin
    C <= TMP and B;
    TMP := A or C;
end process;
```




Implementation of TMP : wire

Implementation of TMP : **latch**. Do you real want it?


Incomplete Sensitivity list

```
process (en)
--variable tmp:std_logic;
begin
  Q<= clk and en;
end process;
```

complete

 

Simulation incomplete

 

Synthesize incomplete

One or more signals are missing in the process sensitivity list. To enable synthesis of FPGA/CPLD hardware, **XST will assume that all necessary signals are present in the sensitivity list.** Please note that the result of the synthesis may differ from the initial design specification. The missing signals are:

<clk>